opular Electronics®

9

WORLD'S LARGEST-SELLING ELECTRONICS MAGAZINE

JUNE 1981 $1.25

Dolby's New Noise Killer

Multiband Shortwave Antenna

1802 EPROM Programmer

For Special-Effect Photos:

BUILD THE POOR MAN'S STROBE

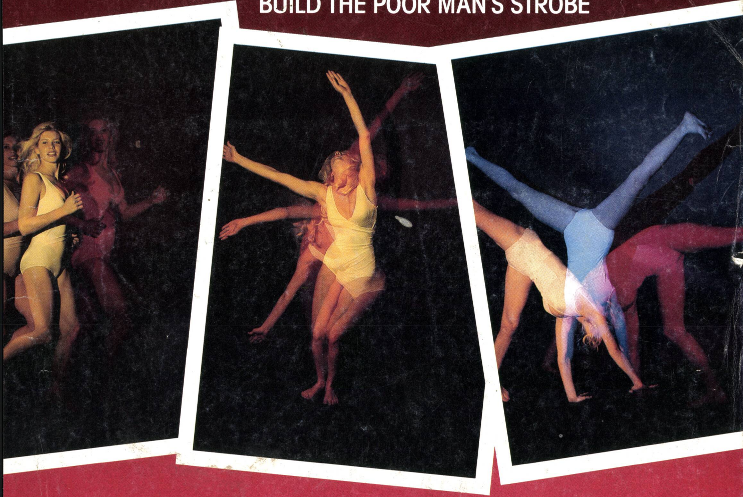

Tested in this issue:

Atari 800 Microcomputer
Sansui AU-D11 Amplifier
GE 13AC1542W TV Receiver

06

14024 14278

oneer
isc player
ggested
ice of
ptional
ntrol
more.)
ing,
h movie on
an even cost less than taking
out to the movies. And about
d of the price of that
same movie on video tape.

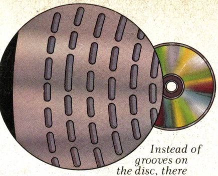

Instead of grooves on the disc, there are microscopic pits.

YOU WON'T BELIEVE IT UNTIL YOU SEE IT.

Irrespective of how much we say here, the true magic of LaserDisc can only be appreciated in person. So we've arranged for a personal demonstration in your area. Just call us at **800-621-5199**,** and we'll give you the names of the stores nearest you. Go by all means. You won't believe your eyes. Or your ears.

*Suggested retail price. Actual price set by dealer. **(In Illinois 800-972-5855).

CIRCLE NO. 58 ON FREE INFORMATION CARD

Simulated TV picture from The Blues Brothers.

© 1981 U.S. Pioneer Electronics Corp.

LaserDisc

PIONEER
We bring it back alive.

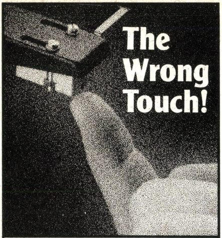

The Right Touch Is a Discwasher SC-2 Stylus Care System.

The SC-2 is a three-function system which safely removes microscopic stylus contaminations that cause record abrasion.

SC-2 Fluid enhances and speeds cleaning and yet protects diamond adhesives, cartridge mounting polymers and fine-metal cantilevers against the corrosive effects of many other "cleaners".

The Discwasher SC-2 System. Stylus care with which your cartridge and records can live.

discwasher®
PRODUCTS TO CARE FOR YOUR MUSIC

Discwasher, Inc.
1407 N. Providence Rd.
Columbia, MO 65201

CIRCLE NO. 13 ON FREE INFORMATION CARD

JUNE 1981

Popular Ele

WORLD'S LARG

The Pi
LaserD
has a su
retail pr
$749.*(O
remote co
just $50*
As surpris
a full lengt
LaserDisc c
your family
half or a thir

Feature Articles

A MULTIBAND SHORTWAVE ANTENNA FOR SWLs
Multiple trap dipole for the major SW br

SHHH! DOLBY DOES IT AGAIN/*Martin Forrest*
Dolby C noise-reduction system is twice as effective as its

USING THE 4060 AS A TIMER/*T.A.O. Gross*
CMOS device offers advantages over the 555 in some applications.

ENGLISH BROADCASTS AUDIBLE IN NORTH AMERICA/*Glenn Hauser*

Construction Articles

BUILD THE POOR MAN'S STROBE/*Imre Gorgenyi*
Capture a moving subject on film with timed flashes.

COMMERCIAL KILLER FOR A CLOCK RADIO/*Herbert L. Bresnick*
System cuts off the audio on cue.

AN 1802-BASED EPROM PROGRAMMER/*Larry Bregoli*
Program, copy, and verify data in a 2708.

BUILD A HEADLIGHT MODULATOR FOR CYCLE SAFETY/*Stan Jones*
Circuit pulses high beam to enhance visibility.

AN APPLIANCE "OFF" REMINDER/*M.T. Valescu*
When indicator light goes off, audible alert goes on.

Equipment Reviews

SANSUI MODEL AU-D11 INTEGRATED STEREO AMPLIFIER

GENERAL ELECTRIC 13AC1542W 13" COLOR TV RECEIVER

HICKOK MODEL MX-333 UNIVERSAL DIGITAL MULTIMETER

ATARI MODEL 800 PERSONAL COMPUTER

Columns

ENTERTAINMENT ELECTRONICS/*Harold A. Rodgers*
Digital Sturm und Drang.

COMPUTER BITS/*Leslie Solomon*
Free Computer Networks.

COMPUTER SOURCES/*Leslie Solomon*

SOLID-STATE DEVELOPMENTS/*Forrest M. Mims*
Jellybean Op Amps.

HOBBY SCENE/*John McVeigh*

EXPERIMENTER'S CORNER/*Forrest M. Mims*
Do-It-Yourself Batteries.

PROJECT OF THE MONTH/*Forrest M. Mims*
Steam Engine and Whistle Sound Synthesizer.

Departments

EDITORIAL/*Harold A. Rodgers*
By their fruit. . . .

LETTERS

NEW PRODUCTS

TIPS AND TECHNIQUES

ELECTRONICS LIBRARY

OPERATION ASSIST

NEW LITERATURE 1

ADVERTISERS INDEX 1

PERSONAL ELECTRONICS NEWS 1

COVER PHOTOS BY IMRE GORGENYI

COPYRIGHT © 1981 BY ZIFF-DAVIS PUBLISHING COMPANY. All rights reserved.

Popular Electronics (ISSN 0032-4485) 1981, Volume 19, Number 6. Published monthly by Ziff-Davis Publishing Co., at One Park Ave., New York, NY 10016. Phi Korsant, President; Selwyn Taubman, Treasurer; Bertram A. Abrams, Secretary. One year subscription rate for U.S. and Pos sions, $14.00; Canada, $17.00; all other countries, $19.00 (cash orders only, payable in U.S. currency). Second Class Pos Paid at New York, N.Y. 10016 and at additional mailing offices. Authorized as second class mail by the Post Office Dept., Ott Canada, and for payment of postage in cash. POPULAR ELECTRONICS including ELECTRONICS WORLD, Trade Mark Regist Indexed in the Reader's Guide to Periodical Literature. Ziff-Davis also publishes Boating, Car and Driver, Cycle, Flying, Po Photography, Skiing, Stereo Review, Electronic Experimenter's Handbook, and Tape Recording & Buying Guide. **Forms 3579 all Subscription Correspondence:** POPULAR ELECTRONICS. Circulation Dept. P.O. Box 2774, Boulder, CO 80302. Please at least eight weeks for change of address, enclosing, if possible, an address label from a recent issue. **Permissions.** Mate this publication may not be reproduced in any form without permission. Requests for permission should be directed to John cock, Rights and Permissions, Ziff-Davis Publishing Co., One Park Ave., New York, NY 10016.

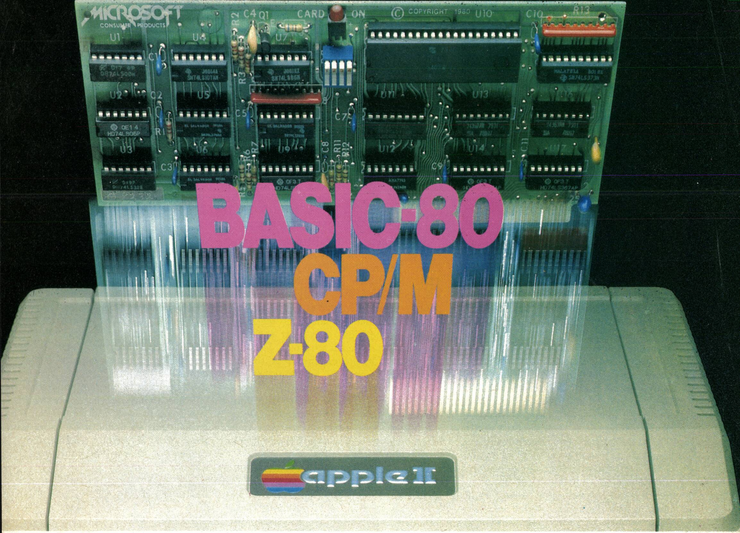

Turn your Apple into the world's most versatile personal computer.

The SoftCard™ Solution. SoftCard turns your Apple into two computers. A Z-80 and a 6502. By adding a Z-80 microprocessor and CP/M to your Apple, SoftCard turns your Apple into a CP/M based machine. That means you can access the single largest body of microcomputer software in existence. Two computers in one. And, the advantages of both.

Plug and go. The SoftCard system starts with a Z-80 based circuit card. Just plug it into any slot (except 0) of your Apple. No modifications required. SoftCard supports most of your Apple peripherals, and, in 6502-mode, your Apple is still your Apple.

CP/M for your Apple. You get CP/M on disk with the SoftCard package. It's a powerful and simple-to-use operating system. It supports more software than any other microcomputer operating system. And that's the key to the versatility of the SoftCard/Apple.

BASIC included. A powerful tool, BASIC-80 is included in the SoftCard package. Running under CP/M, ANSI Standard BASIC-80 is the most powerful microcomputer BASIC available. It includes extensive disk I/O statements, error trapping, integer variables, 16-digit precision, extensive EDIT commands and string functions, high and low-res Apple graphics, PRINT USING, CHAIN and COMMON, plus many additional commands. And, it's a BASIC you can compile with Microsoft's BASIC Compiler.

More languages. With SoftCard and CP/M, you can add Microsoft's ANSI Standard COBOL, and FORTRAN, or Basic Compiler and Assembly Language Development System. All, more powerful tools for your Apple.

Seeing is believing. See the SoftCard in operation at your Microsoft or Apple dealer. We think you'll agree that the SoftCard turns your Apple into the world's most versatile personal computer.

Complete information? It's at your dealer's now. Or, we'll send it to you and include a dealer list. Write us. Call us. Or, circle the reader service card number below.

SoftCard is a trademark of Microsoft. Apple II and Apple II Plus are registered trademarks of Apple Computer. Z-80 is a registered trademark of Zilog, Inc. CP/M is a registered trademark of Digital Research, Inc.

MICROSOFT
CONSUMER PRODUCTS

Microsoft Consumer Products, 400 108th Ave. N.E.,
Bellevue, WA 98004. (206) 454-1315

CIRCLE 37 ON READER SERVICE CARD

EDITORIAL

By their fruit. . . .

Wolves have been known, at least figuratively, to wear sheep's clothing and while so disguised work considerable mischief. The same ploy has been used by manufacturers who, unwilling to have their products compete on their own merits, dress them in trade styles established by others.

One of the latest victims of this deceptive practice is Pioneer of America, whose car audio speakers are currently being "knocked off" by several sources reportedly based in Taiwan. A knock-off operation consists of manufacturing a product designed to look almost exactly like an established one, except that the name of the manufacturer being copied is not overtly used. Such copies usually imitate not only the styling of the product itself but its packaging as well, right down to details like type style. Needless to say, knock offs are virtually always inferior to the original.

Such practices are distressingly common in the field of consumer electronics. Pioneer is only one of the later victims. TDK and Maxell, in the audio tape market, and Shure Bros. with replacement phonograph styli, have suffered as well (although Shure has made no claim of unfair competition, only that the second-source product is inferior). What is dangerous for the consumer is that a particular instance of knocking off becomes generally known only after it has become fairly widespread. In addition, the pirates have the advantage of taking the initiative. (Are you sure that that balky disk drive is what you thought you were buying?)

Obviously, since the target manufacturers lose sales and profits as a result of these sleazy operators, they take whatever steps are available to suppress these patently unfair business practices. But because of the flexibility with which the perpetrators can operate, changing fro product to product and introducing bo gus brand after bogus brand, a mor flexible line of defense is necessar That line of defense is you.

If consumers scrutinize what they ar buying carefully and make sure that it what it is said to be, knock-off operato will be out of business. After all, there no point in their producing what the cannot sell. And, of course, considerin the second-rate merchandise that yo will not be buying, there is a reward fo you here as well. So beware of "bar gains" that seem too good to be true— they probably aren't. Remember, th money you save will be your own.

Hal Rodgers

JOE MESICS
Publisher

ARTHUR P. SALSBERG
Editorial Director

HAROLD A. RODGERS
Executive Editor

LESLIE SOLOMON
Senior Technical Editor

JOHN R. RIGGS
Managing Editor

EDWARD I. BUXBAUM
Art Director

ALEXANDER W. BURAWA
Features Editor

JOHN J. McVEIGH
Technical Editor

ANDRE DUZANT
Technical Illustrator

CARMEN ROBLES
Production Editor

JEFF NEWMAN
Editorial Assistant

Contributing Editors
Carl Warren, Stan Prentiss
Glenn Hauser, Julian Hirsch, Forrest Mims

MARIE MAESTRI
Executive Assistant

OLIVIA WILSON
Promotion Coordinator

PEARL HARRINGTON
Assistant to the Publishing Director

SIDNEY HOLTZ
Publishing Director

Popular Electronics

Editorial and Executive Offices
One Park Avenue
New York, New York 10016
212 725-3500

Publisher
Joe Mesics
212 725-3568

New York Office
Advertising Manager:
Richard Govatski (725-7460)

Eastern Advertising Manager
Bonnie B. Kaiser (725-3580)
Richard B. Eicher (725-3578)

Midwestern Office
Suite 1400, 180 N. Michigan Ave.,
Chicago, IL 60601 (312 346-2600)
Sales: Ted Welch

Western Representative
Norman S. Schindler & Associates, Inc.
7050 Owensmouth Ave., #209
Canoga Park, CA 91303 (213 999-1414)
Sales: Norm Schindler, Jon Marshall

Representation In Japan
James Yagi
Oji Palace Aoyama
6-25, Minami Aoyama, 6 Chome, Minato-Ku
Tokyo, Japan (407-1930/6821, 582-2851)

Ziff-Davis Publishing Company

Philip B. Korsant	Preside
Richard Friese	Senior Vice Preside
Phillip T. Heffernan	Senior Vice Preside
Sidney Holtz	Senior Vice Preside
Edward D. Muhlfeld	Senior Vice Preside
Philip Sine	Senior Vice Preside
Albert S. Traina	Senior Vice Preside
Robert Bavier	Vice Preside
Paul Chook (Research)	Vice Preside
Baird Davis (Production)	Vice Preside
Edgar W. Hopper (Marketing)	Vice Preside
George Morrissey	Vice Preside
Selwyn Taubman	Treasu
Bertram A. Abrams	Secreta
W. Bradford Briggs	Vice Chairm

Ziff Corporation

William Ziff	Chairm
I. Martin Pompadur	Preside
Hershel B. Sarbin	Executive Vice Preside
Furman Hebb	Vice Preside
Bruce Maggin	Vice Preside
Lawrence Sporn	Vice Preside

Editorial correspondence: POPULAR ELECTRONICS, 1 Pa Ave., New York, NY 10016. Editorial contributions must be acco panied by return postage and will be handled with reasonable ca however, publisher assumes no responsibility for return or safety manuscripts, art work, or models submitted.

The publisher has no knowledge of any proprietary rights wh will be violated by the making or using of any items disclosed in t issue.

Member Audit Bureau of Circulations

Radio Shack's TRS-80™ Model III is Your Best Buy in Desktop Computers.

$2495

(Because the "Extras" are Built In!)

With the TRS-80 Model III, you don't pay extra for the features you want. For $2495, you get a *complete,* ready-to-run desktop computer. Go ahead — judge their extras by our standards:

32K RAM. Expandable to 48K.

Two Double-Density Disk Drives. You get two *built-in* 175K disk drives, and can add up to two more externally.

BASIC in 14K ROM. Our powerful Model III BASIC provides a program line editor, machine language programming, real time clock, and more. Compatible with most Model I Level II BASIC programs, too.

Upper and Lower Case Characters. *With* a special graphics character set, and 64 characters-per-line format.

Built-In Monitor. 12," high-resolution.

12-Key Datapad. As well as repeating keys and keyboard-controlled screen print.

Parallel Printer Port. Add one of our printers anytime.

RS-232 Serial Interface. For data communications, just add a modem.

Nationwide Support. Backed by 6100 Radio Shack stores and dealers, 130 Computer Centers and 135 service centers throughout the USA.

Available Now. Why pay more? Get a demonstration of our 32K, two-disk TRS-80 Model III computer today. For less demanding applications (or if you want a personal "starter" system), check out our 16K Model III — only $999.

Retail prices may vary at individual stores and dealers. Special order may be required.

Radio Shack®

The biggest name in little computers™

A DIVISION OF TANDY CORPORATION

Read about your best buy in computers. Send for a TRS-80 catalog.

Radio Shack, Dept. 81-A-297
1300 One Tandy Center
Fort Worth, Texas 76102

NAME ____________________

STREET ____________________

CITY ____________ STATE ________

ZIP ________ PHONE ____________

LETTERS

Preamplifier Performance Specs

Regarding the "High-Performance Phono Preamplifier," described in your March 1981 issue, before I build the unit, I would like to know what I can expect as far as noise and distortion goes.—*Philip A. Wilson, San Jose, CA.*

The author gives the following figures for the moving-magnet preamp: input impedance, 47 kΩ and 100 pF; input overload, 150 mV at 1 kHz; playback equalization, RIAA or IEC ± ¼ dB; frequency response (AUX), 16 to 100,000 Hz, +0/−3 dB; input sensitivity, 1.5 to 10 mV at 1 kHz; S/N (re 5 mV) 85 dB IHF A wtd.; distortion, less than 0.01%; output clipping, 8 V rms (into 2.2 kΩ); slew rate, ±13 V/μs (AUX), ±2 V/μs (PHONO) (limited by RIAA Eq). For the moving coil preamp: input impedance, 100 Ω; input overload, 5 mV at 1 kHz; input sensitivity, 50 μV to 300 μV at 1 kHz (re 500 mV output); S/N, (re 0.5 mV), 88 dB IHF A wtd.—Ed.

Encouragement from an Author

The "Project of the Month" by Forrest Mims on the Transistorized Light Flasher (March 1981) was most interesting to me because it provided additional insight into the prolific workings of Mr. Mims. I first met Forrest a few years ago and it was he who encouraged me to write my first book (*Listen to Radio Energy, Light, and Sound*, Howard W. Sams). I had had a number of technical articles published but had never ventured into the field of books. With his encouragement and comments, my first effort hit pay dirt. By continuing to publish his articles, which are very innovative and inventive, you are doing a service by providing easy, workable projects for electronics experimenters—the backbone of the electronics community of the future.—*Calvin R. Graf, San Antonio, TX.*

Re Speech-Synthesis ICs

Telesensory Systems, Inc. has been building, since 1975, a talking calculator for the blind with a proprietary speech-synthesis integrated circuit using Dr. Forrest Mozer's waveform encoding technique. National Semiconductor has, as you mentioned in your editorial, recently introduced a chip based on the same techique. In the meantime, our device was selected by Fidelity Electronics for use in their highly successful Voice Chess Challenger, which is now available in four languages. We also introduced an industrial speech board based on this chip, which is used in talking voltmeters, depth sounders, etc.—*David Gilblom, Telesensory Systems, Inc., Palo Alto, CA.*

THE FUTURE OF TELEVISION IS TODAY WITH DOWNLINK.

Why wait until 1985 just to get three channels of satellite reception when Downlink's D-2X receiver can give you sixty channels of brilliantly clear unedited movies, sporting events, world news and special programming from the many satellites over the North American continent...Now.
The D-2X's modular format and state-of-the-art circuitry allow for sharp, colorful reception of the entire satellite bandwidth (from 3.7-4.2 gHz). So you can get all sixty channels *plus* the new channels that will be available in the future.
Made from the finest microwave components, the Downlink D-2X receiver features dual-conversion design, permitting multiple receiver installations and phase-lock loop processing which brings living color to your TV.
So live the future of television now...with Downlink.
For the name of the Downlink dealer nearest you call toll-free 800-641-4645, ext. 214. In Missouri, call 800-492-4892.

For more information, contact:
Downlink, Inc.
30 Park Street
Putnam, Connecticut 06260
(203) 928-7731

DOWNLINK™

CIRCLE NO. 14 ON FREE INFORMATION CARD

OUT OF TUNE

In "Power Supplies for Op Amps" (April, p 57), on page 59, column 1, line 14 should read "*C1, C2*, and *D1*" instead of "*C1* and *D1*". On page 60, column 3, line 2 should read "*R5* and *R6*" instead of "*R5* and *R7*" and line 3 should read "*R1* and *R7*" instead of "*R1* and *R6*." In Fig. 7, *R4* should be moved so that it is in series with the V+ supply, between the supply and *C1*, *R2*, *C4*, and the V+ terminal of *IC1*.

In "Build a High-Performance Phono Preamplifier" (March 1981), there are two *R23*s on the schematic and component layout. The 100-kΩ fixed resistor for *R23* is not included on the Parts List. In the Parts List, *Q1* and *Q2* should be listed as 2SB7375 not 25B7375.

How to master tape.

Eventually, you reach a point with your tape recording system where you realize you just can't make the kind of quality recordings you want.

Even though your equipment may be the very finest.

Because despite Dolby,®* the tape still has too much noise. It doesn't give you enough headroom. And its dynamic range – the range of volume that makes music sound alive and real – is just too restricted.

If you've reached that point, you're ready for the dbx Recording Technology Series. Noise reduction systems that eliminate tape hiss and allow you to record with a quality equal to studio master tapes.

With a dbx Recording Technology Series Model 224 or 222, noise is reduced by 30 dB across the *entire* frequency range. You get 10 dB more headroom. You can even make live recordings with 80 dB or more of dynamic range. Remarkably close to a live performance.

And there's one final touch. The dbx Recording Technology Series includes a built-in dbx Disc Decoder that lets you play the revolutionary dbx Discs and Digital dbx Discs, the world's first Full Dynamic Range Recordings.

See your authorized dbx retailer for a demonstration of the dbx Model 224 and 222 and learn which is best suited for your system.

Short of buying your own recording studio, it's the only way to master tape.

dbx, Inc., 71 Chapel St., Newton, Mass. 02195 U.S.A. Tel. (617) 964-3210. Telex 92-2522. Distributed throughout Canada by BSR (Canada) Ltd., Rexdale, Ontario.

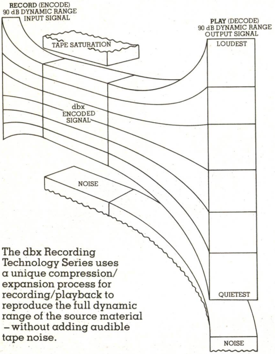

The dbx Recording Technology Series uses a unique compression/expansion process for recording/playback to reproduce the full dynamic range of the source material – without adding audible tape noise.

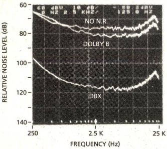

Dolby B reduces noise by only 10 dB in the high frequency range. dbx reduces noise by more than 30 dB across the entire frequency range. (Unretouched laboratory photograph. Data for cassette recorder from "The Importance of Dynamic Range," Audio Magazine, January, 1980. For a copy of the article, write dbx.)

*Dolby is a registered trademark of Dolby Laboratories, Inc.

Making good sound better dbx®

CIRCLE NO. 10 ON FREE INFORMATION CARD

dbx
POWER
Recording Technology Series
MODEL 224
TAPE
BYPASS
dbx DISC
SIMULTANEOUS ENCODE/DECODE
TYPE II TAPE NOISE REDUCTION SYSTEM

Learning electronics is no picnic.

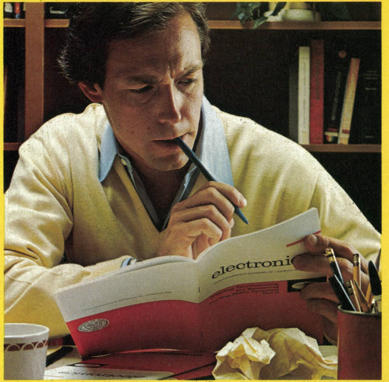

At any level it takes work and a few sacrifices. But with CIE, it's worth it.

Whoever said, "The best things in life are free," was writing a song, not living a life. Life is not just a bowl of cherries, and we all know it.

You fight for what you get. You get what you fight for. If you want a thorough, practical, working knowledge of electronics, come to CIE.

You can learn electronics at home by spending just 12 hard-working hours a week, two hours a day. Or, would you rather go bowling? Your success is up to you.

At CIE, you *earn* your diploma. It is not handed to you simply for putting in hours. But the hours you do put in will be on your schedule, not ours. You don't have to go to a classroom. The classroom comes to you.

Why electronics training?

Today the world depends on technology. And the "brain" of technology is electronics. Every year, companies the world over are finding new ways to apply the wonders of electronics to control and program manufacturing, processing...even to create new leisure-time products and services. And the more electronics applications there are, the greater the need will be for trained technicians to keep sophisticated equipment finely tuned and operating efficiently. That means career opportunities in the eighties and beyond.

Which CIE training fits you?

Beginner? Intermediate? Advanced? CIE home study courses are designed for ambitious people at all entry levels. People who may have:

1. No previous electronics knowledge, but do have an interest in it;
2. Some basic knowledge or experience in electronics;
3. In-depth working experience or prior training in electronics.

You can start where you fit and fit where you start, then go on from there to your Diploma, FCC License and career.

Many people can be taught electronics.

There is no mystery to learning electronics. At CIE you simply start with what you know and build on it to develop the knowledge and techniques that make you a specialist. Thousands of CIE graduates have learned to master the simple principles of electronics and operate or maintain even the most sophisticated electronics equipment.

CIE specializes exclusively in electronics.

Why CIE? CIE is the largest independent home study school that specializes exclusively in electronics. Nothing else. CIE has the electronics course that's right for you.

Learning electronics is a lot more than memorizing a laundry list of facts about circuits and transistors. Electronics is interesting! It is based on recent developments in the industry. It's built on ideas. So, look for a program that starts with ideas and builds on them. Look to CIE.

Programmed learning.

That's exactly what happens with CIE's Auto-Programmed® Lessons. Each lesson uses famous "programmed learning" methods to teach you important principles. You explore them, master them completely, before you start to apply them. You thoroughly understand each step before you go on to the next. You learn at your own pace.

And, beyond theory, some courses come fully equipped with electronics gear (the things you see in technical magazines) to actually let you perform hundreds of checking, testing, and analyzing projects.

Experienced specialists work closely with you.

Even though you study at home, you are not alone! Each time you return a completed lesson, you can be sure it will be reviewed, graded and returned with appropriate instructional help. When you need additional individual help, you get it fast and in writing from the faculty technical specialist best qualified to answer your question in terms you can understand.

CIE prepares you for your FCC License.

For some jobs in electronics, you must have a Federal Communications Commission (FCC) License. For others, some employers tend to consider your license a mark in your favor. Either way, your license is government-certified proof of your knowledge and skills. It sets you apart from the crowd.

More than half of CIE's courses prepare you to pass the government-administered exam. In continuing surveys, nearly 4 out of 5 graduates who take the exam get their licenses! You can be among the winners.

Associate Degree

Now, CIE offers an Associate in Applied Science Degree in Electronics Engineering Technology. In fact, all or most of every CIE Career Course is directly creditable towards the Associate Degree.

Today is the day. Send now.

Fill in and return the postage-free card attached. If some other ambitious person has removed it, cut out and mail the coupon. You'll get a FREE school catalog plus complete information on independent home study. For your convenience, we'll try to have a CIE representative contact you to answer any questions you may have.

Mail the card or the coupon or write CIE (mentioning name and date of this magazine) at: 1776 East 17th Street, Cleveland, Ohio 44114.

Pattern shown on oscilloscope screen is simulated.

CIE **Cleveland Institute of Electronics, Inc.**
1776 East 17th Street, Cleveland, Ohio 44114

PE-40

☐ **YES...** I want to learn from the specialists in electronics — CIE. Send me my FREE CIE school catalog...including details about the Associate Degree program...plus my FREE package of home study information.

Print Name ____________________

Address ____________________ Apt. ______

City ____________________

State ____________________ Zip ______

Age ________ Phone (area code) ____________________

Check box for G.I. Bill bulletin on Educational Benefits: ☐ Veteran ☐ Active Duty

MAIL TODAY!

NEW PRODUCTS

Additional information on new products covered in this section is available from the manufacturers. Either circle the item's code number on the Free Information Card or write to the manufacturer at the address given.

Kenwood Audio Purist AM/FM Tuner

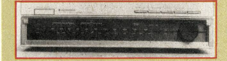

Kenwood's Model KT-1000 AM/FM-stereo tuner features a touch-activated servo-locked tuning system and exclusive pulse-counting detector and sample-and-hold MPX circuits. The tuning system automatically adjusts FM tuning to the center of the i-f bandpass, while the pulse-counting detector digitally recreates the FM signal. Direct r-f conversion prevents interference from strong stations, while normal conversion can be used when greater sensitivity is needed. Other features include: wide/narrow i-f bandpass selector, recording calibration switch, stereo pilot canceller, automatic muting, preselector bypass switch, fixed and variable outputs, and AM i-f output jack (for AM-stereo decoder). Specifications: FM section—usable sensitivity, 10.3 dBf; stereo S/N, 85 dB; stereo THD (1 kHz), 0.04%; alternate-channel selectivity, 45 dB; separation (1 kHz), 60 dB. AM section—usable sensitivity, 10 μV; S/N, 52 dB, image rejection, 70 dB; selectivity, 30 dB (wide i-f). $450.

CIRCLE NO. 89 ON FREE INFORMATION CARD

Magnavox Deluxe Video Cassette Recorder

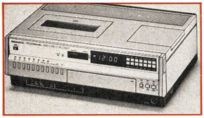

Magnavox's Model 8340 is a VHS-format videocassette recorder that permits unattended recording for up to 6 hours. It has a built-in digital clock/controller and a remote pause control that makes armchair editing possible. Features include search forward and reverse at nine times normal speed, fast motion at two times normal speed, variable slow motion, frame-by-frame advance, and freeze-frame operations, all through the special-effects remote controller. In addition, there is 14-day/seven-event programmability, unattended recording of one additional event at the same time each week, feather-touch controls, automatic rewind, and transitional editing.

CIRCLE NO. 87 ON FREE INFORMATION CARD

Micro Electronic Systems Mini PC Board Holder

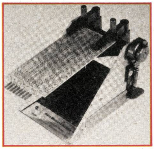

Micro Electronic Systems has a new holder that serves as a "third hand" for work on small printed-circuit boards and collapses for easy storage. A pc board is held by two small vise-like grippers that can rotate to provide access to the reverse side. The steel-and-plastic holder (Part No. 1521) sells for $41.40. Address: Mini Electronic Systems, Inc., 159 Main St., Danbury, CT 06810.

Alphacom Printer/Plotter

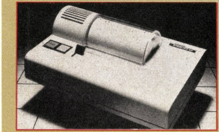

The Alphacom Sprinter 40 from Olivetti is a high-speed thermal dot-matrix printer with plotting capability. It prints up to 240 40-character lines per minute on standard thermographic paper, using a 5 x 7 dot matrix to produce 96 upper- and lower-case characters. It requires only 14 seconds to produce a 280-line CRT display in hard copy within a 280 by n-dot matrix. Among the functions available are: automatic carriage return and line feed, reset, right justification, form feed, graphics control, and multiple-line feed. Interface with a computer is user selectable and can be either 7-bit ASCII parallel with STROBE, BUSY, and ACK (Centronics standard) or RS-232 serial with choice of 110, 150, 300, 600, 1200, 2400, 4800, or 9600 baud. The Sprinter 40 is designed to be connected to any computer that uses a standard interface. $390.

CIRCLE NO. 88 ON FREE INFORMATION CARD

Bogen Wireless Intercoms

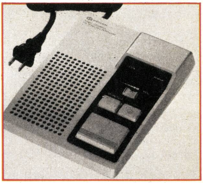

The new Models WI-1 and WI-3 wireless intercom systems from Bogen require no station-to-station wiring, relying instead on carrier current transmission over the power mains. The WI-1 offers one-channel capability and the WI-3, three-channel capability, both using FM for interference immunity and automatic squelch for minimum noise. A phase-locked loop (PLL) maintains frequency stability. Calls can be announced by tone or voice. A locking button permits continuous transmission for monitoring nurseries, sickrooms, etc. Each system is packaged with one pair of stations, and can be expanded to accommodate more.

CIRCLE NO. 91 ON FREE INFORMATION CARD

Numark Equalizer/Analyzer

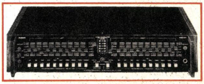

According to Numark, the 10-band Model EQ-2700 computerized equalizer/analyzer permits accurate fine tuning of a hi-

"My computer helped me write The Final Encyclopedia. I wouldn't trust anything less than Scotch® Brand Diskettes to make a long story short."

Cover art by Michael Whealen, courtesy of Ace Publishing Co.

Gordon R. Dickson,
Science Fiction Author,
Minneapolis, Minnesota

Gordon Dickson: a small businessman whose product is his own imagination. He's written more than 40 novels and 150 short stories; his newest work is *The Final Encyclopedia*. He uses his personal computer and word processing software to maximize his production. All his words—his product—are stored on diskettes. He calls up sentences and paragraphs on demand, and gets more rewrite out of the time available. So he depends on Scotch diskettes to save himself production time.

Dependable Scotch media can work just as hard for you. Each Scotch diskette is tested before it leaves our factory, and certified error-free. So you can expect it to perform exactly right.

Scotch 8" and 5¼" diskettes are compatible with computer/diskette systems like TRS-80, Apple, PET, Wang and many others. Get them from your local 3M distributor. For the one nearest you, call toll-free: 800/328-1300. (In Minnesota, call collect: 612/736-9625.) Ask for the Data Recording Products Division. In Canada, contact 3M Canada, Inc., Ontario.

If it's worth remembering, it's worth Scotch Data Recording Products.

3M Hears You...

3M

fi system to match the sonic conditions of a listening area. A built-in pink-noise generator permits adjustment in octave bands. An optional measurement microphone (Model STD272) is available. Specifications: frequency response 10 to 100,000 Hz ±1 dB; center frequencies, 60, 120, 240, 480, 960, 1920, 3840, 7680, and 15,360 Hz with a ±15-dB adjustment in each band; IM and THD, 0.02% (0.01% at 1-V output); hum and noise, −102 dB (2-V output, input shorted). Analyzer measurement frequencies are the same as tone-control center frequencies but are selected by pushbutton switch. Price is $450, which includes an optional microphone.

CIRCLE NO. 92 ON FREE INFORMATION CARD

IC Insertion Tool

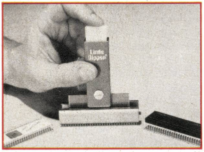

The new "Little Dipper" tools from Techni-Tool permit safe, easy insertion of 64-pin dual in-line package (DIP) ICs with 0.9″ pin-row spacing into sockets of printed-circuit boards. One model is for ICs with "radiators" bonded to their surfaces, while a relief-cut model offers protection to delicate hybrid-circuit device top seals. All tools in the Little Dipper line are claimed to be safe for use with MOS and CMOS devices and are adjustable for direct board or socket insertion. Each is made from aluminum and stainless steel. Address: Techni-Tool, Inc., 5 Apollo Rd., Plymouth Meeting, PA 19462.

Orion Emulator/Programmer For TRS-80

Orion Instrument's "Developmate 81" allows a TRS-80 microcomputer to be used as a full development system. It adds both in-circuit Z80 emulation and EPROM/EEPROM programming capability. Developmate 81 plugs into the TRS-80's expansion connector. The PROM programmer has a personality module that defines voltages and connections to the PROM so that devices with up to 28 pins can be accommodated. Software for programming 2758, 2508, 2716, and 2532 EPROMs and 2816 and 48016 EEPROMs is included. Clock speed during emulation is 1.8 MHz. The system comes with power supply, emulation and TRS-80 cables, and a "universal" personality. It's designed to work with any TRS-80 Model I, with or without expansion interface. $329.

CIRCLE NO. 94 ON FREE INFORMATION CARD

Acoustic Research Bookshelf Speaker System

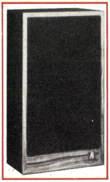

The Model AR28 bookshelf/floor-standing speaker system from Acoustic Research is a two-way design said to deliver 50 to 24,000 Hz, +0, −3 dB frequency response. Crossover from its 8″ woofer to 1″ dome tweeter is at a nominal 2 kHz. The system requires a minimum input of 15 watts and can accommodate amplifiers rated at 100 watts continuous power per channel, driven to clipping no more than 10% of the time. Sensitivity is rated at 87 dB SPL at 1 meter on-axis for 1 watt input. Nominal impedance is 6.5 ohms, 4.5 ohms minimum. Size is 21$\frac{7}{16}$″H x 11$\frac{3}{4}$″W x 7$\frac{3}{4}$″D and weight is 24 lb. Sold only in pairs, AR28s carry a suggested retail price of $125 each.

CIRCLE NO. 95 ON FREE INFORMATION CARD

Bearcat Synthesizer Scanner

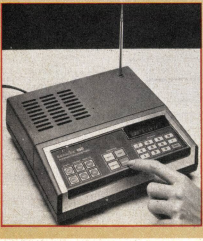

The "Bearcat 150" from Electra is a new low-cost 10-channel synthesized scanning receiver that covers 30 to 512 MHz, including low- and high-band vhf, uhf, and uhf-T land-mobile and public-safety bands and the entire 2-meter and 440-to-450-MHz portion of the 70-cm amateur bands. Among its features are a received-frequency fluorescent display and a "flat-plane" panel that controls all functions including volume via UP and DOWN buttons. Ten memory channels provide automatic scanning of those frequencies of most interest. In addition, direct channel access permits quick recall of individual channels. Also included is an automatic lockout function to suppress any given channel in the scan mode.

CIRCLE NO. 93 ON FREE INFORMATION CARD

Tascam Cassette Recorder

The Tascam Model 122 stereo cassette deck by Teac contains a 1$\frac{7}{8}$- and 3$\frac{3}{4}$-ips, two-motor transport and three-head record/play capability. A built-in Dolby HX (Headroom Extension) circuit is said to add up to 10 dB of headroom beyond 10 kHz, without sacrificing audible performance. Tapes made with HX can be played on any deck with a Dolby B noise-reduction system. An optional dbx noise-reduction system is also available. All transport functions are LSI logic circuitry controlled and can be operated through an optional remote-control unit (Model RC-90). Three-position switches and screwdriver-adjustable controls permit bias and equalization for any premium tape formulation, including metal. $700.

CIRCLE NO. 96 ON FREE INFORMATION CARD

(Continued on page 16)

Here's great news for electronics enthusiasts on small budgets.

Now you can take home a Fluke DMM for $125*."

Whether you're just starting out in electronics or moving up from an analog VOM to a digital multimeter, you'll be smart to make sure that you're getting your money's worth.

In your search for a basic-performance DMM, be sure to consider the new D 800 from Fluke. Priced at only $125,* this dependable six-function handheld DMM is available now at select electronics supply stores throughout the U.S.

The D 800 offers 0.5% basic dc accuracy (five times better than analog voltmeters), a razor-sharp 3½-digit LCD readout, unsurpassed overload protection, and true, one-hand operation.

This hard-working basic measurement multimeter is designed from the inside out for long life and reliability. All D 800 specifications are traceable to the National Bureau of Standards.

As part of Fluke's new Series D line of low-cost digital multimeters, the D 800 carries a limited one-year parts and labor warranty and comes complete with the battery, and safety-designed test leads.

Ask your supplier about the D 800, then compare it feature-for-feature with any other low-cost DMM. You'll find that for only $125,* there's never been more multimeter than the new D 800 from Fluke.

From the world leader in DMM's. Now we've designed one for you.

World leader in DMM's. Now we've designed one for you.
Pliers
12.34
FLUKE

Suggested U.S. list price

For technical data circle no.
20 ON FREE INFORMATION CARD

If your dealer doesn't carry Series D Multimeters yet, call this number. We'll be happy to tell you who does. **1-800-426-9182**

FLUKE®

WANT AUTO-RANGING?

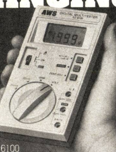

AWS EZ 6100

AND...

- **An unprecedented five-year warranty**
- Pricing as low as $105
- 3 1/2 digit display
- Autoranging on Volts and Ohms
- Continuity buzzer (Model EZ 6100)
- Range hold (Model EZ 6100)
- Autopolarity
- Automatic indication, unit and signs
- Feather touch button to select AC/DC - Lo Ω/Ω function
- Low battery warning sign
- Safety fused

EZ 6100	
DCV 0-1000	5-Autoranges
ACV 0-600	4-Autoranges
DCMA 0-200	2-Ranges
ACMA 0-200	2-Ranges
Ω 0-2000KΩ	5-Autoranges
Low Power Ω	0-2000KΩ
4-Autoranges	Plus Continuity Buzzer
EZ 6200	
DCV 0-1000	5-Autoranges
ACV 0-600	4-Autoranges
DCMA 0-200	1-Range
ACMA 0-200	1-Range
Ω 0-2000KΩ	5-Autoranges
Low Power Ω	0-2000KΩ
4-Autoranges	

- Order AWS EZ 6200 . . . **$105**
- Order AWS EZ 6100 with continuity buzzer and range hold **$142**
- Order AWS C-30 Ever-Ready carrying case **$20**

☐ For ordering information call toll-free: **800-645-5398** (N.Y., Hawaii, Alaska call collect 516-231-7050).

A.W. SPERRY INSTRUMENTS INC.
The Measurable Advantage.
245 Marcus Blvd., Hauppauge, N.Y. 11787

CIRCLE NO. 53 ON FREE INFORMATION CARD

(Continued from page 14)

Avanti Autosound Telescoping Antenna

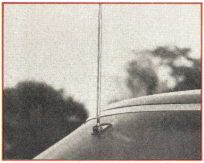

Spirit II is a new autosound antenna from Avanti, designed to be mounted on glass surfaces and telescope to only 18" from its fully extended 48". Spirit I is said to reduce noise, static, and "picket fence" fading and to have gain superior to similar antennas. The exclusive on-glass mounting scheme eliminates the need to drill holes in a vehicle's body, and the coupling unit mounts inside the vehicle, where it's protected from the elements. The antenna can be mounted at any angle.

CIRCLE NO. 97 ON FREE INFORMATION CARD

Fisher Direct-Drive Turntable

Model MT6420C is a semiautomatic dc servo-controlled direct-drive turntable. The controls for this 33⅓- and 45-rpm turntable are located on a front panel, where they can be operated with the dust-cover closed. Among the unit's features are an integral tonearm equipped with magnetic cartridge, adjustable calibrated antiskate control, automatic arm return/shutoff system, viscous-damped cueing lever, stylus force adjustment control, strobe light and separate fine speed trim controls, and detachable headshell. $169.95.

CIRCLE NO. 98 ON FREE INFORMATION CARD

Autotek Premium In-Dash Car Stereo

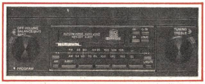

Autotek's top-of-the-line Model CSR-3300 AM/FM-stereo receiver/cassette car-stereo system is designed for in-dash installation. It has an adjustable voltage at its high-impedance output that is said to assure compatibility with virtually any car-stereo power amplifier. Its auto-reverse cassette deck features a sendust head, Dolby B noise reduction, 31-to-15,000-Hz range with metal tape, and 0.015% wrms wow and flutter. The tuner has a FET front end, LOCAL/DX switch, and FM muting. Amplifier output power is rated at 2.2 watts continuous per channel ±3 dB from 30 to 15,000 Hz with no more than 1% THD. Size is 7"W x 5¼"D x 2"H. $299.95.

CIRCLE NO. 99 ON FREE INFORMATION CARD

Page Alert Vehicle Security & Pocket Pager System

Page Alert Systems recently introduced a deluxe vehicle security system with pocket pager communication facilities. Installed in a vehicle, the Page Alert 4444's 4-watt transmitter sends out an individually coded radio signal to a small pocket pager if a break-in is attempted. Range is said to be 2 miles or more. A switch on the transmitter can be set to PAGE to send a signal to the pager and light its PAGE indicator. Setting the switch to SECURITY causes the pager to beep, but lights the SECURITY indicator. The two-tone sequential coding system used for the 4444 has over 10,000 individual combinations. Address: Page Alert Systems, Inc., 23842 Hawthorne Blvd., Torrance, CA 90505.

Cybernet Wireless Stereo Headphone System

Cybernet's new Model TM-301 "Freedom Stereo" wireless headphone system connects to any line-level (preamp, tape, tuner, headphone output) source and feeds a wire-loop "antenna." Signals radiated from the antenna are said to be receivable anywhere in a home, even on other floors, via the wireless headset. A TALK button and built-in microphone in the transmitter permit paging as well. The phones feature left and right volume controls, frequency range of 50 to 14,000 Hz, and channel separation of 40 dB (frequency not specified). The transmitter measures 7⅞"W x 7¼"D x 2⅝"H and weighs 3 lb. Phones weigh 11 oz and are powered by two AA cells. Price of $199.95 includes 100 feet of antenna wire and one stereo audio cable.

CIRCLE NO. 100 ON FREE INFORMATION CARD

Computers for people.™

"Atari graphics and sound stand in a class by themselves."

David D. Thornburg
Compute Magazine, November/December 1980

"Its superiority lies in three areas: drawing fancy pictures (in color), playing music, and printing English characters onto the screen. Though the Apple can do all these things, Atari does them better."

Russell Walter
"Underground Guide to Buying a Computer"
Published 1980,
SCELBI Publications

"The Atari machine is the most extraordinary computer graphics box ever made..."

Ted Nelson
Creative Computing Magazine, June 1980

"...so well packaged that it is the first personal computer I've used that I'm willing to set up in the living room."

Ken Skier, OnComputing, Inc. Summer 1980

"...well constructed, sleekly designed and user-friendly—expect reliable equipment, and strong maintenance and software support."

Videoplay
December, 1980

What computer people are saying about Computers for people.™

To find out about the ATARI® 800™ Computer
first hand, ask your local computer dealer
for a hands-on demonstration.
Or call, 800-538-8547 (In California 800-672-1404)

ATARI®
Computers for people.™

©1981, ATARI, Inc.
A Warner Communications Company

For further information write: Atari Inc., Computer Division, 1196 Borregas Avenue, Sunnyvale, CA 94086 Dept. C-51

CIRCLE NO. 6 ON FREE INFORMATION CARD

ENTERTAINMENT ELECTRONICS

By Harold A. Rodgers
Executive Editor

Digital Sturm und Drang

NO SOONER has digital audio begun to mature and come into its own than it has fallen under heavy attack from various critics, some apparently well meaning, some (I suspect) defending their vested interests in older technology, and some just plain ignorant. Naturally, this creates confusion among audio fans, who begin to wonder, "Is this technology all it is said to be?" This is unfortunate, for I have heard samples of digital recording that I would nominate for "best ever," if such a determination could really be made.

The Criticisms. Let's dispose of an ignorant objection first. Consider the notion that "chopping the music into 50,000 or so samples per second irretrievably loses a part of it." On the face of things, this is obviously true—whatever happens between sampling times is not recorded. Yet, it is not too difficult to show that what is lost, if it was there in the first place, is so high in frequency as to be of absolutely no significance to human ears. The problem is that the argument establishing this point is mathematical and a bit subtle. Apparently unable to comprehend it, certain "subjectivists," as they like to call themselves, give their fantasies free rein and decide that they hear what simply isn't there (or hear the lack of what isn't missing). Claiming to have golden ears, they display what might be better called brazen imagination.

Are we to believe that information theory, whose technological fruit are as diverse and extraordinary as high-resolution images of Saturn gleaned via space probe and the packing of literally thousands of simultaneous telephone messages into a single optical fiber is suddenly inadequate for the relatively straightforward task of analyzing a signal whose bandwidth extends only to 20 kHz or so? I think not.

Yet, it is not too hard to see how digital master recordings might well contain objectionable sounds. Such sounds may very well have been in the input signal to the recorder. Though it may come as a surprise to some, including a digital recorder in the signal path is no guarantee of a superior recording. If anything, the greater transparency of the digital recording may well render errors of miking or signal degradation that occurs in the console *more* noticeable than they would be with an analog recorder. Clearly, to blame the digital recorder for this makes about as much sense as chopping off the head of a messenger who brings bad news.

Another point to consider, since few of us are fortunate enough to be listening to actual digital tapes, is that no matter how good the mastering, poor production of the analog disc can render the overall result substandard. All digitally mastered discs are not the same, and finding one or two that are poor does not necessarily reflect on the entire technology.

Much has been made, too, of the idea that, once the parameters of a digital system are set, the level of performance it can deliver is fixed and cannot be improved. This is not entirely true, as it might well be possible at a later time to introduce improved error-correcting systems or slightly more linear analog-to-digital and digital-to-analog conversion. More to the point, however, there are theoretical limits on every recording system—vinyl disc, magnetic tape, or whatever. The difference is that the digital system lets us get close to the limit right away, whereas the vinyl disc, for example, has latent capabilities that we still cannot practically realize.

The Stress Controversy. In the January 1981 installment of this column, I mentioned the findings of Dr. John Diamond concerning the idea that digital recordings produce physiological stress in those who listen to them. At that time I reported the work of Nelson Morgan, who, using methods more conventional than those of Dr. Diamond, came up with sharply conflicting results, namely that digital recordings are biologically innocuous.

Since that time we have received several communications from supporters of Dr. Diamond to the effect that my acceptance of Morgan's findings was premature and might be serving to hinder a legitimate area of scientific inquiry. One of these communications, from Don and Carolyn Davis of Syn Aud Con in California, contained substantial documentation in support of Dr. Diamond's position. Lacking professional expertise in these matters, I referred this material to Dr. Laurence Greenhill, a practicing psychiatrist and sometime contributor to this column. Dr. Greenhill's comments are as follows:

> The definition and concept of stress, as promoted by Dr. Diamond, requires clarification. Contemporary research on stress depends on independent validation using physiological measures with high interest reliability. Such measures have evolved from a sound, published experimental foundation. Changes in blood pressure, heart rate, cortisol and testosterone secretion, and in galvanic skin response are but a few of the respectable documented stress measures. These tests also have validity in linking stress to such consequence as heart disease. The Behavioral Kinesiology (BK) deltoid reflex test, regardless of Dr. Diamond's assertions, has not yet received wide acceptance among respected researchers who publish data in refereed journals. The link between the BK test and stress in human subjects has not been proven experimentally.
>
> The "BK" test, done openly, can be totally explained on the basis of expectation and suggestion effects. Hypnotists routinely demonstrate feats of muscle weakness or strength in naive subjects by manipulating them through prior suggestion. Only double-blind techniques, described below, can remove such biases.
>
> The methodology involved in the BK-deltoid muscle test at present has grave weaknesses; Dr. Diamond's demonstration before the AES was open and uncontrolled and was plainly subject to the researcher's biases. Did Dr. Diamond press down harder on his subject's arms when the digital music was being played? Scientific methodology places the burden of proof on those who made the observation of digital stress. Digitally mastered records will remain innocent until proven guilty.
>
> Double-blind conditions must be used, where neither the tester or testee knows what type of record is being used. A reliable standardized mechanical "arm-displacer" and polygraphic recorder of the displacement and reflex must be used. Multiple baseline runs to establish strength and muscle fatigue decay under no-music conditions must precede the actual experimental run. Time of day and time of month (if the subject is female) must be controlled. Even if these procedures produce positive results, the findings have to be replicated in other laboratories. Such is the tedium of science.

(Continued on page 22)

When you're responsible for millions of miles of sky, you don't fly it alone.

This is no drill. This is the Air National Guard. The professionals who keep watch on the skies over America. All day. Every day.

It's serious business, because it's for real. And everyone from the jet engine mechanic to the weather technician knows it.

That's why they're here.

They know every time a pilot leaves the ground, they're riding with him. Their communications network, his ears. Their radar scopes, his eyes. Their aircraft maintenance, his life.

And whether it's a ground check on an electronic circuit. Or a steady hand on a refueling boom nine miles high, everything they do brings a special satisfaction. Because it counts.

If you're looking for the chance to do something meaningful. If you've got what it takes to take on a real job. If you get that tingle down your spine when a jet engine fires up. Then maybe you should help us do what we do. We Guard America's Skies.

See your local Air National Guard recruiter. Or call us toll-free 800-638-0936 (except in Alaska, Hawaii and Puerto Rico); in Maryland call 301-981-3610.

We Guard America's Skies.

AIR NATIONAL GUARD
The Guard belongs.

CIRCLE NO. 40 ON FREE INFORMATION CARD

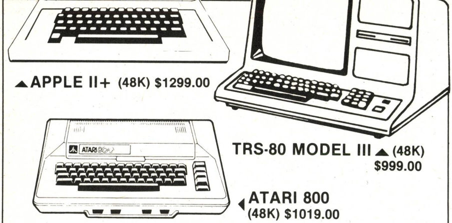

▲APPLE II+ (48K) $1299.00

TRS-80 MODEL III▲ (48K)
$999.00

◀ATARI 800
(48K) $1019.00

PRINTERS

MICROLINE-80	$489.00
MICROLINE-82	$669.00
MICROLINE-83	$999.00
EPSON MX-70	$419.00
EPSON MX-80	$519.00
EPSON MX-80FT	$619.00
CENTRONICS 737	call for price

TERMS: Prices and specifications are subject to change. HARDSIDE accepts VISA & MASTERCARD. Certified checks and Money Orders; Personal checks accepted (takes 3 weeks to clear). HARDSIDE pays all shipping charges (within 48 states) on all PREPAID Orders OVER $100.00. On all orders under $100 a $2.50 handling charge must be added. COD orders accepted (orders over $250 require 25% deposit) there is a $5.00 handling charge. UPS Blue Label. Air Freight available at extra cost. TRS-80, APPLE and ATARI are trademarks of Tandy, Apple Computer Co. and Warner Communications, respectively.

TSE-HARDSIDE
6 South St., Milford, NH 03055 (603) 673-5144
TOLL FREE OUT-OF-STATE 1-800-258-1790

CIRCLE NO. 25 ON FREE INFORMATION CARD

FREE McIntosh
STEREO CATALOG
and FM DIRECTORY

Get all the newest and latest information on the new McIntosh catalog. In addition you will receive an FM station directory that covers all of North America.

SEND TODAY!

McIntosh Laboratory, Inc. PE
East Side Station P.O. Box 96
Binghamton, N.Y. 13904

NAME ____________________
ADDRESS ____________________
CITY __________ STATE ____ ZIP ______

If you are in a hurry for your catalog please send the coupon to McIntosh.
For non rush service send the **Reader Service Card** to the magazine.

CIRCLE NO. 39 ON FREE INFORMATION CARD

(Continued from page 18)

Finally, there is the basic scientific issue. Dr. Diamond has made an observation that fatigue and stress result from listening to digitally encoded analog recordings. Doug Sax and Mark Levinson, among others, have reported similar digital-induced listener fatigue in print. But no one has done the appropriate work to prove or to disprove it. What is required is old-fashioned laboratory stress-research involving time, thought, subjects—and money.

Even if we grant Dr. Diamond his hypothesis, a strong case can be made that it is irrelevant. His control, after all, was not live music, but analog recordings. One could feel justified, therefore, in concluding that music that has not been passed through the analog recording process is stressful. In other words, it may be that *live music* is stressful and digital recording simply *preserves that quality while analog recording does not*.

Moreover, Dr. Diamond discovered the alleged stressfulness of digitally recorded music while using it as a therapeutic agent, something that seems doubtful as the primary purpose of a major composer or, indeed, any of the other artists involved. In fact, if we accept the well-circulated story of why Haydn inserted the sudden, loud chords into the second movement of his "Surprise" Symphony, here is a case in which a composer *deliberately* sought to induce stress in listeners. And does it seem credible that Tchaikovsky included cannons and bells in the score of the 1812 Overture for their restful, soothing quality? Or that Beethoven piled the entire d minor scale into a single chord to produce euphonious harmony, free of conflict? To me it does not, and to the extent analog recording reduces this heavy emotional impact and substitutes restfulness, its own displacement by a more accurate process cannot come too soon.

Doubtless there is some legitimacy to the use of music in therapy, but this must give way to the primary purpose of esthetic expression. (Music I have heard that was written expressly for therapeutic purposes has been pleasing in a bland way, but tends to be supremely boring compared to what I think of as real music.) Nevertheless, it would seem that there is abundant room to live and let live. The vast library of existing analog recordings should prove sufficient for Dr. Diamond and his patients, while those of us who are foolish enough to want all the emotional qualities that great composers put into their music to come through in recordings are free to listen to digital, stress and all. Even if digital recordings were to be imprinted with a health warning similar to that on cigarette packages, I don't think I could give them up. ◇

Audio Product of the Month

CHOSEN BY THE EDITORS OF POPULAR ELECTRONICS

Sansui AU-D11 Integrated Stereo Amplifier

"SUPER feedforward" rather than conventional negative feedback is used to cancel distortion in the Sansui AU-D11 integrated stereo amplifier. The unit is rated to deliver 120 watts per channel to 8-ohm loads between 10 and 20,000 Hz with no more than 0.005% total harmonic distortion. Direct coupled, the amplifier has a specified slew rate of 250 V/μs, and a rise time of 0.8 μs. The amplifier is 17 9/16" W × 17½"D × 6 7/16"H, and weighs 38.5 lb. A black panel and knobs contrast with the rosewood veneer cabinet. The suggested retail price is $1000.

General Description. The control knobs of the Sansui AU-D11 (which incorporate the minimum number of detented positions) include tone and balance controls and a large VOLUME control with a 70-dB calibrated range. The tone controls have selectable turnover frequencies (150 or 300 Hz for the BASS and 3 or 6 Hz for the TREBLE) selected by pushbuttons. The switch labelled SPEAKERS at the upper left of the panel can connect either, both, or neither of two sets of speakers to the power-amplifier outputs.

The pushbutton controls of the AU-D11 are elongated flat bars. One bypasses the tone-control circuits, two others engage 6-dB-per-octave filters with turnover frequencies of 16 Hz and 20 kHz, and a fourth (MUTE) reduces the gain by 20 dB.

On the INPUT SELECTOR, there are positions for two magnetic PHONO cartridges, TUNER, and AUX sources. A separate REC SELECTOR directs signals to the tape output jacks, which can handle two tape decks. With the control in its OFF setting, the tape outputs are completely isolated from the amplifier circuits. The SOURCE position feeds the

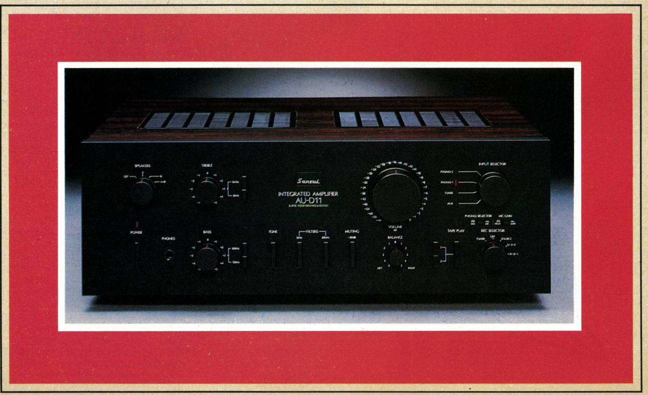

source selected by the INPUT SELECTOR to the tape output jacks. A position marked TUNER allows recording from a tuner while listening to another source. There are two DUBBING positions that can be used to record the selected SOURCE on one deck, or for dubbing from either deck to the other.

To hear the playback from either tape deck, or to monitor a program being recorded on a three-head machine, a TAPE PLAY pushbutton next to the REC SELECTOR is engaged. Two smaller buttons select the playback from either machine (playback is independent of the setting of the REC SELECTOR).

The phono section of the AU-D11 includes a built-in head amplifier for moving-coil cartridges. A small button between the INPUT SELECTOR and the REC SELECTOR converts the phono input from MM (moving magnet) to MC (moving coil), simultaneously changing the phono input impedance from 47,000 ohms to 100 ohms. A second button provides a choice of HI or LO gain settings for different moving-coil cartridges.

Activation of the individual pushbuttons, as well as the setting of the INPUT SELECTOR, is indicated by adjoining red LEDs. On initial power-up, the light above the pushbutton blinks for several seconds, until the amplifier's operating voltages have stabilized. Then a relay connects the speaker outputs and the light glows steadily. If the amplifier's overload protection circuit is tripped at any time, the outputs are disconnected immediately, and the POWER pilot light begins to blink. After the fault has been cleared, power must be shut off for a few seconds and then reapplied to restore normal operation.

Phono jacks for all the signal inputs and the tape recorder connections, along with insulated binding posts for the speaker leads, are located on the amplifier's rear apron. Of the three ac convenience outlets in that same general area, one is switched.

Removing the wooden cabinet from the AU-D11 reveals an unusually rugged and well-finished interior, with the metalwork completely copper plated. The massive power supply has more than 65,000 μF of filter capacitance, and the internal connections between the capacitors and from them to the rectifiers use heavy metal bus bars instead of wire. This is apparently meant to reduce the output impedance of the power supply to a minimum.

The output transistors, four in all, are mounted on a metal plate that transfers their heat to an internal sealed convection cooling system. Refrigerant vaporized by the heat circulates through a finned heat exchanger and is cooled by air moving through the chassis by convection. The entire cooling system is contained in the cabinet.

The Sansui "Super Feedforward" circuit is a combination of feedback and feedforward techniques. Negative feedback alone, if used in large amounts, requires careful control of the phase and gain in order to preserve stability. In the large amounts used in most transistorized amplifiers, it has been blamed for transient intermodulation distortion (TIM) when the open-loop bandwidth of the amplifier is too small.

In a typical feedforward system, the error signal sensed by comparing the input and output waveforms is fed to a very-low-distortion error amplifier that inverts it and sums it with the signal at the output, thereby cancelling the distortion at that point.

Negative feedback is applied conventionally, except that less of it is used than would normally be the case. Signal is tapped before the output stage but after the point where the fedback signal has been combined with the input signal and fed forward through a very-low-distortion error amplifier. With appropriate phase corrections, it is summed with the amplifier output.

Also incorporated in the AU-D11 are such refinements as symmetrical balanced amplifier stages throughout the unit and direct-coupled signal path. One benefit claimed for this design approach is reduced envelope distortion of low-frequency signals.

Laboratory Measurements. As a rule, we consider distortion of 0.01% or less negligible, and categorize amplifiers having that quality as "nondistorting." The Sansui AU-D11 easily meets that standard; the highest distortion we measured from it was 0.006% at 20,000 Hz. Over much of the audio range, the distortion was well under 0.001% for power outputs from a fraction of a watt to well above rated power.

Even when we drove 4- and 2-ohm loads (operation into 2 ohms is specifically *not* recommended by Sansui) the distortion was negligible until clipping occurred. This happened at 153 watts per channel into 8 ohms (IHF Clipping Headroom = 1.06 dB) and at 210 watts when driving 4-ohm loads. The maximum power into 2 ohms was set by the amplifier's protective circuit, which shut it off at 200 watts—before any waveform distortion was visible.

When we used the 20 millisecond tone-burst signal of the IHF Dynamic Headroom test, the 8-ohm maximum output was actually slightly *less* than its continuous output, measuring 135 watts for a clipping headroom rating of 0.5 dB. However, into a lower load impedance the short-term output was impressively high, 257 watts at 4 ohms and 304 watts at 2 ohms (again, the protective relay intervened before distortion).

Although we do not attempt to measure TIM by any of the several methods that have been proposed for that purpose (there are no current standards for TIM measurements), its absence can be inferred from several of the tests we did make. The two-tone IM distortion with equal amplitude output signals at 19 and 20 kHz having a peak amplitude equal to that of a 120-watt sine-wave signal, was a barely detectable −92 dB for the third-order product at 18 kHz, and the second-order distortion at 1 kHz was our measurement residual of −96 dB. The IHF Slew Factor exceeded our measurement limit of 25, and measured

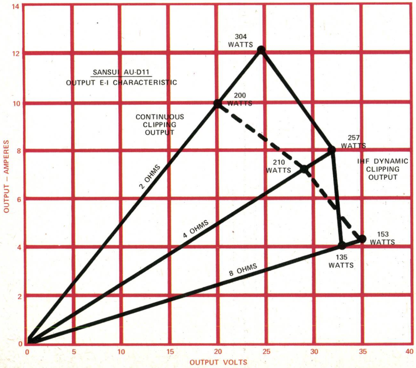

Power output characteristic of the Sansui AU-D11 with loads of 2,4 and 8 ohms.

Here's the easy way to join the microprocessor revolution.

Heathkit/Zenith Self-Study Courses give you a thorough understanding of microprocessor theory and applications. They put you in command of your electronics future.

From TV's and toys to cars and computers, the microprocessor finds its way into our lives. Your future in electronics requires a working knowledge of microprocessors and now there's an easy, low-cost way to get it.

Heathkit/Zenith step-by-step home-study. You learn at your own pace with an illustrated, easy-to-follow text, reinforced by color visuals and audio cassettes. The easy step-by-step format organizes the material into bite-size units. Test questions at the end of each step assure a thorough understanding before proceeding to the next step. Learning has never been easier.

Hands-on programming exercises. You learn by doing, not just reading. Special exercises performed on the Heathkit/Zenith Microprocessor Trainer give you hands-on experience in programming and interfacing. You come away with a complete working command of the microprocessor and how it's used in a growing number of devices today.

Recommended for college credit. Many Heathkit/Zenith Courses are now recommended for college credit by the American Council on Education. If you can't go back to college, now you can bring college home to you.

Free Heathkit Catalog. Details and prices on the complete line of Heathkit/Zenith Self-Study Courses are in the new, free Heathkit Catalog. Send for yours today or pick one up at your nearby Heathkit Electronic Center.

DON'T LET CHANGING TECHNOLOGY PASS YOU BY.
Heathkit/Zenith offers a complete line of home-study courses on the latest in electronic specialties:

Operational Amplifiers
Phase-Locked Loops
I.C. Timers
Active Filters
Digital Techniques
Electronic Test Equipment
Electronic Circuits
Semiconductor Devices
AC & DC Electronics
Electronics for Hobbyists
Communications

Send for free catalog.
Write to Heath Co., Dept. 010-784,
Benton Harbor,
MI 49022.
In Canada, write Heath Co.,
1478 Dundas Street East,
Mississauga, Ontario, L4X 2R7.

Visit your Heathkit Store.
Heathkit products are displayed, sold and serviced at 62 Heathkit Electronic Centers in the U.S. and Canada. See your telephone white pages for locations.
In the U.S., Heathkit Electronic Centers are units of Veritechnology Electronics Corporation.

CIRCLE NO. 26 ON FREE INFORMATION CARD

Heathkit
ZENITH Educational Systems

ED-161

J&R MUSIC WORLD

"RATED NO. 1 FOR SERVICE & RELIABILITY"

THIS MONTH'S SUPER SPECIALS!

VIDEO SPECTACULAR!

VIDEO RECORDERS	
AKAI VPS-7350 Port VHS	$1295
JVC HR-6700 VHS Recorder	$795
JVC HR-2200 Port. VHS Rec	$945
MAGNAVOX 8340 VHS Rec.	$990
MAGNAVOX 8310 VHS Rec.	$625
MAGNAVOX 8372 Port. VHS	$995
MAGNAVOX 8371 Port. VHS	$895
MAGNAVOX 8370 Port. VHS	$825
PANASONIC PV-1210 VHS Rec.	$625
PANASONIC PV-1300 VHS Rec.	$795
PANASONIC PV-1400 VHS Rec.	$875
PANASONIC PV-1750 VHS	$1040
PANASONIC PV-3100 Port. VHS	$795
PANASONIC PV-A35P Tun. Tim	$295
PANASONIC PV-3200 Port. VHS	$945
RCA VET 250 VHS Recorder	$750
RCA VET 450 VHS Recorder	$845
RCA VET 650 VHS Recorder	$1050
RCA VET 170 Portable VHS	$1050
SONY SL-5400 Beta Recorder	$775
SONY SL-5600 Beta Recorder	$875
SONY SL-5800 Beta Recorder	$1045
SONY SL-3000 Portable Beta	$950
SONY TT-3000 Tuner/Timer	$395
TECHNICOLOR 212 Port ¼"	$850
ZENITH VR-9000 Beta Rec	$695
ZENITH VR-9750 Beta Rec	$945

VIDEO CAMERAS	
AKAI VC-X1 Auto Focus	$875
JVC GX-88 Camera	$699
MAGNAVOX 8244 Camera	$699
PANASONIC PK-700 Camera	$675
PANASONIC PK-750 Camera	$675
PANASONIC PK-800 Camera	$875
RCA CC-007 Camera	$750
RCA CC-010 Camera	$799
SONY HVC-2010 Camera	$595
SONY HVC-2200 Camera	$985
SONY HVM-100 B/W Camera	$225
TOSHIBA IK-1850 Auto Focus	$849

SONY COLOR TV	
KV-4000 (4" Screen)	$429
KV-5200 (5" Screen)	$409
KV-8100 (8" Screen)	$429
KV-9400 (9" Screen)	$389
KV-1217 12" Screen)	$369
KV-1221R (12" Remote)	$429
KV-1543R (15" Remote)	$479
*KV-1715R (17" Remote)	$499
*KV-1913 (19" Screen)	$449
*KV-1943R (19" Remote)	$569
*KV-2601 (26" Screen)	$799
*KV-2643R (26" Remote)	$899

*Shipped Freight Collect

VIDEO DISC PLAYERS	
MAGNAVOX VH-8000 Laser	$599
PIONEER VP-1000 Laserdisc	$649
ROA SFT-100 CED Disc Player	$425

CAR STEREO

PIONEER CASSETTE IN-DASH W/RADIO	
KP-5500	124.90
KP-8500	141.90
KE-2100	174.90
KEX-20	214.90
KP-4502 (foreign cars)	144.90
KP-8000	139.90
KPX-9000-(reg. amp)	154.90
KPX9500-(reg. amp)	176.90
KE-5100	209.90
CASSETTE UNDER DASH	
KP-373	84.90
KP-575	94.90
KP-500	134.90
KP-77G-(reg. amp)	104.90
KPX600	118.90
KP707G	144.90
POWER AMPS/EQUALIZER	
BP-320	54.90
AD-30	94.90
AD-50	141.90
GM-120	106.90
CD-5	89.90
GM-2	34.90
GM-4	54.90
CAR SPEAKERS	
TS-M2	34.90/PAIR
TS-T3	34.90/PAIR
TS107	39.90/PAIR
TS167	54.90/PAIR
TS168	84.90/PAIR
TS695	99.90/PAIR
TS-X6	74.90/PAIR
TX-X9	134.90/PAIR

CLARION	
PE-683A (With Fast Forward)	79.95
PE-550A (Auto Rev. w/Dolby	169.95
PE751C (P/B Auto. Rev.)	229.95
PE-958A (Electronic Tuning)	289.95
PE-768A (P/B Auto Rev.)	179.95
PE-956B (Electronic Tuning)	319.95
PE-959A (Elec. Top Of Line):	569.95

JENSEN CASSETTE IN-DASH W/RADIO	
R-402 receiver	174.90
R-406 receiver	199.90
R-410 receiver	219.90
R-420 receiver	259.90
RE-512 (Auto-Reverse)	259.90
SPEAKERS	
J-1001 6x9 separates	98.90/PAIR
J-1065 6x9 triax	64.90/PAIR
J-1033 6x9 triax II	83.90/PAIR
J-1201 6x9 coax II thin	62.90/PAIR
J-1101 4x10 triax	66.90/PAIR
J-1130 4x10 triax II	88.90/PAIR
J-1174 5¼ triax	66.90/PAIR
J-1124 5¼ triax II	88.90/PAIR
J-1188 6½ coax thin	43.90/PAIR
J-1069 6x9 coax	43.90/PAIR
J-1037 6x9 coax II	64.90/PAIR
J-1041 5¼ coax II	53.90/PAIR

SANYO IN-DASH CASSETTE	
FT-C2 (Mini-Cassette)	59.90
FT-C8 (Hor./Vert. Mount.)	99.90
FT-C12 (Digital Display)	114.90
FT-C13 (Pushbutton)	119.90
FT-C15 (Auto. Pushbutton)	134.90
FT-C16 Dolby & Metal Tape)	147.90
FT-C18 (Pushbutton Dolby)	169.90
FT-2200 (Digital Tuning)	229.90

BLAUPUNKT	
CR-2001	249.90
CR-3001	429.90
CR-4000	259.90
CR-5001	339.90
BEA-100	107.90
BEA-200	159.90

WE ALSO CARRY THE FULL LINE OF CAR STEREOS BY PANASONIC, GRUNDIG, MITSUBISHI, CONCORD, SONY, AUDIOVOX AND CRAIG.

BLANK CASSETTES

AUDIO	
AMPEX GRAND MASTER I OR II C90	2.99
BASF PRO I, II OR III C90	2.99
FUJI FX I OR II C90	2.99
SCOTCH Highlander C-90 3Pk	3.99
MEMOREX HI BIAS C90	2.99
SCOTCH MASTER I OR III C90	3.25
SONY FECR C90	3.25
SONY LNX C90	1.64
TDK HD-01 DEMAGNETIZER	16.95
TDK DC90	1.68
TDK ADC90	2.45
TDK SAC90	2.99
TDK MA C90 (METAL)	6.29
TDK MA C90 (METAL)	7.99
MAXELL UDXL I or UDXL II C-90	3.47

MAXELL PRICES ARE TOO LOW TO ADVERTISE. CALL OR WRITE FOR PRICES.

VIDEO

WE CARRY VIDEO TAPES BY AMPEX, BASF, FUJI, JVC, MAXELL, PANASONIC, MEMOREX, TDK, SCOTCH, SONY, RCA.

ALL BETA L500	10.95
ALL BETA L750	13.95
ALL VHS T-120 (Except HG)	14.95
MATTEL INTELLIVISION	229.50
ATARI VIDEO GAME CX2600	148.95
SPECIAL	
MEMOREX VHS T-120	13.95

WE STOCK ALL VIDEO DISCS.

WE STOCK B&W AND COLOR TV'S. VHS AND BETA VIDEO RECORDERS, AND HOME MOVIES FROMALL MAJOR HOLLYWOOD STUDIOS. SEND FOR CATALOGUE.

MINIMUM ORDER 12 TAPES 100% GUARANTEED

RECORDS & TAPES

ALL ROCK, JAZZ & CLASSICAL

All 7.98 List 4.99 All 8.98 List 5.99 All 9.98 List 6.99

Cassette & 8-Track Same Price as LP; Minimum Order . . . 5 Records or Tapes We Stock all Major Labels.

HOW TO ORDER BY MAIL: For prompt and courteous shipment send money order, certified check, cashier's check, Master Charge or Visa (include card number, expiration date and signature) Shipping/Insurance charge is 5% of total order on VIDEO items and $3.95 on CAR STEREO or TAPES. (Please double these charges for orders outside continental U.S. or Canada) New York residents add tax. All merchandise 100% guaranteed brand new and factory fresh. 3 weeks delay on personal or business checks. No C.O.D.'s.

ORDER TOLL FREE (800) 221-8180
Customer Service Hot Line (212) 233-0857

IN NEW YORK, CANADA, ALASKA AND HAWAII. CALL: (212) 732-8600

SEND FOR OUR 260 PAGE FREE CATALOG
23 PARK ROW, NEW YORK, N.Y. 10038

DEPT. PE

CIRCLE NO. 33 ON FREE INFORMATION CARD

rise time was about 1 microsecond.

All the preceding tests suggest that the AU-D11 cannot be overloaded at high frequencies any more easily than at low frequencies, and that its exceptional linearity, even at full power, is maintained over the full audio band and well beyond its upper limits. In other words, we would not expect any TIM, no matter how defined or measured, to be induced in this amplifier under any practical conditions. It should be noted, also, that we measured the AU-D11 through its AUX inputs so its preamplifier stages were included in our measurements.

Stability of the amplifier was not impaired when we drove a highly reactive simulated speaker load; and in the IHF overload recovery test, it recovered fully from a 10-dB overload in about 10 microseconds, an inaudibly short interval.

Tone control characteristics were good, with considerable adjustment range available at the frequency extremes with no effect over most of the midrange, especially when using the 150-Hz and 6-kHz turnover frequencies. RIAA phono equalization varied only 0.5 dB overall from 20 to 20,000 Hz. Phono input impedance (MM) could not be modeled as a single parallel R-C combination, but it measured 55,000 ohms at low and middle frequencies. There was some interaction with a high inductance phono cartridge that caused the response to roll off slightly above 15,000 Hz when the equalization was measured with the cartridge coil in series with the input signal. However, this effect was insignificant with most magnetic cartridges. Although we made no measurements through the MC head amplifier, we used it for listening tests and found it to be quite satisfactory in gain and noise characteristics.

Both filters, high and low, were relatively ineffective for attenuating noise. The "16 Hz" filter began to roll off the output slightly below 50 Hz and was down 2 dB at 20 Hz. The "20 kHz" filter effect began at about 4 kHz, and its response was down about 5 dB at 20 kHz. Since the AU-D11 is direct-coupled from its high-level inputs to the speakers, and can be rendered inoperative by even a small dc component in its input signal, some means of blocking dc is clearly desirable. That should have been a capacitor large enough not to affect the audio range. Similarly, since the amplifier's bandwidth extends beyond 300 kHz, exclusion of ultrasonic "garbage" might well be in order. The filter cut-off frequency should have been above the audio band, or a steeper slope should have been used. Sansui chose the mild filter slopes, a company spokesman says, because steeper ones were judged to impair sound quality.

Input sensitivity for a 1-watt reference output was 26 millivolts (AUX) and 0.21 millivolts (PHONO-MM). The respective A-weighted signal-to-noise ratios were 84 and 81 dB referred to 1 watt output, both excellent. The phono input overloaded at 200 millivolts at middle and low frequencies, and at 178 millivolts at 20 kHz (referred to the equivalent 1-kHz level).

User Comment. Although we have made some criticisms of the AU-D11, they apply only to its design features, not to its electrical performance. It is surely one of the most advanced amplifiers we have seen in respect to low distortion and noise, wide bandwidth, and overall stability. Trying to measure its performance limitations was a challenge that made us highly appreciative of our test instruments.

The amplifier can deliver more than ample power for just about any home music installation. Construction is superb, and the protection is impressively effective. Especially noteworthy is the ability of the AU-D11 to drive low-impedance loads with ease (a very unusual characteristic in integrated amplifiers we have seen), yet with no loss of protection.

One oversight that surprised us is the omission of a MONO switch. When playing mono records, it is usually desirable to parallel the signal channels to reduce noise and vertical rumble. We also noted the absence of separate PRE OUT/MAIN IN jacks in the rears of the amplifier. The only rationale we can find for this is that the AU-D11 can be used as a power amplifier without the need to by-pass its preamplifier section, since its performance is so good. Again, Sansui indicates that the additional wiring needed to provide this feature tends to degrade sound quality.

In our listening tests, we did not notice any consistent difference between the sound from the AU-D11 and other high-quality amplifiers and, indeed, Sansui concedes that any difference that might be detectable would be extremely subtle. This is consistent with our past experience—good amplifiers tend to sound very much alike, except for occasional subtle differences that are difficult to prove or classify.

In its electrical performance, the AU-D11 is about as close to ideal as any amplifier we know. As a power amplifier, we would expect it to behave impeccably, especially with highly reactive speakers that many amplifiers find "difficult." Used with premium-grade components having clean outputs, the AU-D11 should give no trouble at all.

Whether the few small omissions in the design of the control section will prove problematic will vary from user to user. Mono records, after all, are virtually antiques, and external signal-processing equipment can easily be patched into a tape monitor loop. As it is, the control section should satisfy the overwhelming majority of listeners, and it would hardly surprise us if a substantial number of audiophiles find the Sansui AU-D11 worth its price for the power-amp section alone. —*Julian D. Hirsch*

CIRCLE NO. 101 ON FREE INFORMATION CARD

Popular Electronics Tests

General Electric 13AC1542W 13" Color TV Receiver

GENERAL ELECTRIC's Model 13AC1542W differs considerably from the deluxe 19" and 25" EC and EM color-TV chassis in the company's 1981 lineup (see review of 19ECO77OW, PE, September 1980). This 13" set has no removable modules and lacks vertical-interval color reference VIR II circuitry. There are also fewer integrated circuits (four total, all in sockets). Even so, the 1542W approaches the performance of a much more expensive color-TV receiver.

A programmable infrared remote-control system is standard in this set. It's a simplified version of the one used in GE's higher-priced sets, offering up/down tuning and volume-control setting but no direct channel addressing. However, all stations are user programmable, and scanning (via either the remote controller or the front-panel keyboard) is very fast. Also provided are the usual CATV midband channels, although there is no manual fine-tuning or extended-range automatic fine tuning (aft) arrangement for capturing nonstandard CATV carriers.

The set measures 20½"W x 15¼"D x 14"H and weighs 35¼ lb. Price is about $450, depending on area.

General Description. The LMP-91 four-frequency remote-control transmitter's volume-control and channel-selector buttons generate 41-to-54-kHz signals that modulate the continuous-wave infrared carrier. Channels between 2 and 92 can be initially set numerically or out of sequence, depending on user programming. Buttons for ADD, CLEAR, and PROGRAM are located behind a small door on the front panel. These are used to set up the various channels. A phase-locked-loop (PLL) frequency-synthesizer system automatically locks the frequency and phase of the video and sound for each channel chosen.

Composite video and audio enter the chassis through a network of capacitors and tunable inductors that matches tuner and i-f impedances. One LC network is set to 43.8 MHz for maximum video response, while another tailors the overall response curve so that video and chroma carriers occupy their assigned places (usually 50% on the swept response curve).

Three additional parallel-tuned traps attenuate the 39.75-MHz upper adjacent video, 47.25-MHz lower adjacent sound, and 41.25-MHz sound carriers but permit passage of the audio carrier to its takeoff point in the video i-f IC. Another inductor across the i-f chip input tunes for both maximum bandpass and balanced input.

The complex video chip performs the following functions: i-f amplification; synchronous video demodulation; automatic fine tuning (aft) detection; video amplification; and 4.5-MHz sound take-

Now NRI takes you inside the new TRS-80 Model III microcomputer to train you at home as the new breed of computer specialist!

NRI teams up with Radio Shack advanced technology to teach you how to use, program, and service state-of-the-art microcomputers.

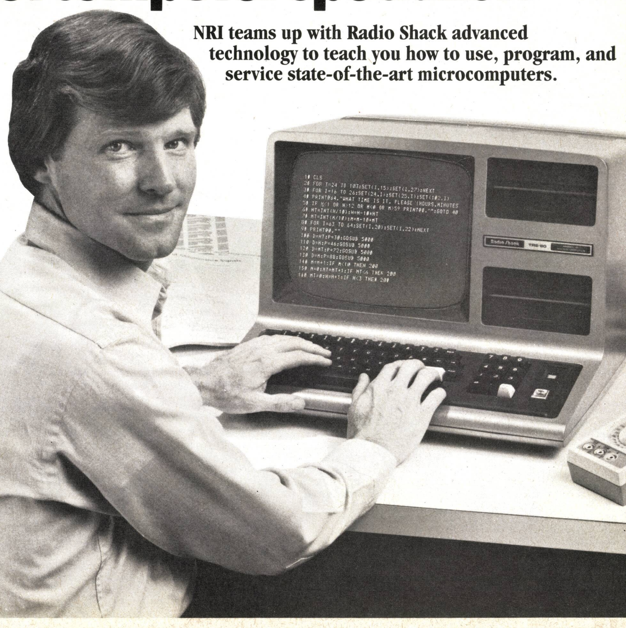

```
10 CLS
20 FOR I=24 TO 103:SET(I,15):SET(I,27):NEXT
30 FOR I=16 TO 26:SET(24,I):SET(25,I):SET(102,I)
40 PRINT@64,"WHAT TIME IS IT. PLEASE (HOURS,MINUTES
50 IF H<1 OR H>12 OR M<0 OR M>59 PRINT@0,"":GOTO 40
60 HT=INT(H/10):H=H-10*HT
70 MT=INT(M/10):M=M-10*MT
80 FOR I=63 TO 64:SET(I,20):SET(I,22):NEXT
90 PRINT@0,""
100 D=HT:P=30:GOSUB 5000
110 D=H:P=46:GOSUB 5000
120 D=MT:P=72:GOSUB 5000
130 D=M:P=88:GOSUB 5000
140 M=M+1:IF M<10 THEN 200
150 M=0:MT=MT+1:IF MT<6 THEN 200
160 MT=0:H=H+1:IF H<3 THEN 200
```

It's no longer enough to be just a programmer or a technician. With microcomputers moving into the fabric of our lives (over 250,000 of the TRS-80™ alone have been sold), interdisciplinary skills are demanded. And NRI can prepare you with the first course of its kind, covering the complete world of the microcomputer.

Learn At Home in Your Spare Time

With NRI training, the programmer gains practical knowledge of hardware, enabling him to design simpler, more effective programs. And, with advanced programming skills, the technician can test and debug systems quickly and easily.

Only NRI gives you both kinds of training with the convenience of home study. No classroom pressures, no night school, no gasoline wasted. You learn at your convenience, at your own pace. Yet you're always backed by the NRI staff and your instructor, answering questions, giving you guidance, and available for special help if you need it.

You Explore the New TRS-80 Model III Inside and Out

NRI training is hands-on training, with practical experiments and demonstrations as the very foundation of your knowledge. You don't just program your computer, you go inside it...watch how circuits interact...interface with other systems...gain a real insight into its nature.

Training includes the new TRS-80 Model III microcomputer, 6-function LCD Beckman multi meter, and the NRI Discovery Lab with hundreds of tests and experiments.

You also work with a precision 26-scale, 6-function LCD Beckman multimeter featuring full portability and a 3½ digit display. Using it along with the exclusive NRI Discovery Lab and your TRS-80, you perform over 60 separate experiments in all. You learn how to troubleshoot and gain greater understanding of the information your tests give you.

Advanced Technology Microcomputer Is Yours to Keep

As part of your training, NRI sends you the new, state-of-the-art TRS-80 Model III microcomputer. This functional unit is complete with 65-key keyboard and 12" display in one desk-top unit. It features high-speed cassette loading, built-in interface for parallel printer, and provisions for optional disk drive. Its 4K RAM is internally expandable to 16K or 48K and its BASIC language is compatible with most Model I software.

Along with your multimeter and the NRI Discovery Lab, this latest concept in advanced microcomputers is yours to learn with, yours to keep and use for your own personal programs, business use, and other applications.

Send for Free Catalog...No Salesman Will Call

Get all the details on this exciting course in NRI's free, 100-page catalog. It shows all equipment, lesson outlines, and facts on other electronics courses such as Complete Communications with CB, TV and Audio Servicing, Digital Electronics, eleven different interest areas in all.

Send today, no salesman will ever bother you. Keep up with the latest technology as you learn on the world's most popular computer. If postcard has

been used, write to NRI Schools, 3939 Wisconsin Ave., Washington, D.C. 20016.

NRI Schools
McGraw-Hill Continuing Education Center
3939 Wisconsin Ave.
Washington, D.C. 20016

We'll train you for the good jobs.

(TRS-80 is a trademark of the Radio Shack division of Tandy Corp.)

off. There are only three inductors in this circuit, two used for setting the 45.75-MHz synchronous video detector and aft frequency variables. Interstage i-f tuning is nonexistent.

Lacking a comb filter, this receiver has both a conventional delay line and a 3.58-MHz chroma trap in the second (discrete) video amplifier stage. It also has a beam-current limiter and five stages of video amplification that provide more than adequate gain for the final video driver. In addition, it delivers luminance information to the emitters of the red, blue, and green mixer power amplifiers that drive the picture tube.

A very interesting and significant circuit in this set is the color monitor (Fig. 1), which contains only three transistor stages and a few diodes. Dc restorer *Q295* processes horizontal pulses of varying amplitudes from a winding on the primary of the flyback transformer (not illustrated). The R − Y and B − Y sensors *Q282* and *Q284* receive color information from the outputs of chroma demodulators in the chroma processor via pins 7, 8, and 9 of connector *PG5*. With switch *S300* set to AUTO, combined G − Y and B − Y feedback reaches the base of *Q284* through *C284*, while R − Y supplies feedback through *C281* to the base of *Q282*.

As the flyback transformer's current increases and decreases, *Q295* does two things. First, it passes positive spikes of voltage through its emitter to diodes *Y282* and *Y284*, which become bias and dc restorers for the R − Y and B − Y sensors. Secondly, it delivers an inverted pulse that charges *C298*. This pulse is then rectified by *Y295* and becomes a negative clamp for the collectors of *Q282* and *Q284* during retrace. By this means, the average levels of R − Y and B − Y are sensed, G − Y becomes a tint phase shifter, all sensors are brightness and high-voltage controlled, and the common R − Y/B − Y collectors produce a matrixed output. This output then either adds to or subtracts from the chroma signals, ultimately maintaining a relatively constant output under varying color tracking conditions. The heavily filtered outputs from these parallel-connected transistors then supply a control voltage for the color-control portion of the chroma-processor IC. Output from the chroma processor goes to the final RGB amplifiers and cathodes of the picture tube. Color and tint levels are further preset and limited through a resistor that is bypassed during manual chroma control.

Like many other modern table-model color sets, this one has both a bridge rectifier and start-up circuit composed of four diodes and a silicon controlled rectifier (SCR). When power is applied, and after the degaussing coils cut out, the power supply develops an unregulated 145-volt dc source for selected vertical circuits. This 145 volts is also divided and sent to the start-up SCR. When triggered, the SCR's output goes to the scan power source, vertical and horizontal countdown circuits, and horizontal driver. Meanwhile, the +145-volt source furnishes current and voltage to the primary of the flyback transformer to drive the horizontal output. Other operating voltages are derived from various half-wave diodes and a special circuit connected to windings on the flyback transformer.

This circuit is interesting because it operates from the flyback transformer at the 15,734-Hz horizontal rate, through a ferroresonant saturable reactor that regulates the CRT filament voltages and the 35-, 22-, and 12-volt sources. Fully isolated secondaries supply 90% regulation for ICs and various other bias and operating functions.

In addition to a side pincushion trans-

GENERAL ELECTRIC MODEL 13AC1542W RECEIVER LABORATORY DATA

Parameter	Measurement
Tuner/receiver sensitivity (min. signal for snow-free picture):	vhf (Ch. 3): −10 dBmV uhf (Chs. 30, 50): −5 dBmV
Voltage regulation (line varied from 105 to 130 V):	Low voltage: 145-V supply—81% 22-V supply—89% High voltage: 25-kV supply—83%
Luminance bandpass at CRT:	3 MHz
Luminance bandpass at video detector:	4 MHz
S/N at CRT:	41.9 dB
Horizontal overscan:	8%
Agc signal swing (after r-f agc adjust):	51 dB
Audio bandpass (3 dB down):	80 Hz to 6 kHz (usable past 12 kHz)
Dc restoration:	80%
Power requirement (signal applied):	100 W (including remote)

Note: Instruments used in these measurements are: Tektronix/Telequipment D66, D67A oscilloscopes; Sadelco FS-3D VU f/s meter; Data Precision 258, 1350, 1750 multimeters; B&K-Precision 1248, 1250, 3020 color and function generators; Sencore VA48 (modified), CG169, and PR57 video analyst, color and power sources.

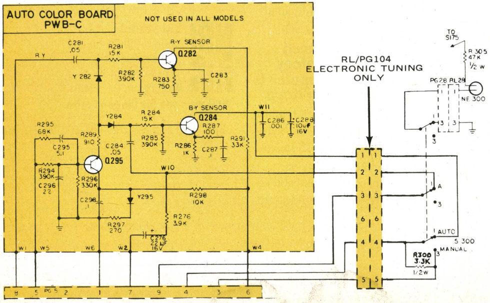

Fig. 1. The color monitor contains only three transistor stages to provide a signal that eventually controls the chroma-processor IC.

ADVERTISEMENT

Gas Saver Tested & Patented

DENVER—The Copley News Service reported that United States Patents have now been issued to Wm. Trevaskis, California veteran electrical engineer, for his Vapor-Jet® brand water vapor injector (Pat. #4,119,062).

Trevaskis has developed what amounts to a 20 cents per gallon "rebate" on gasoline, by designing a low-cost injector for automobiles, ight trucks, vans and recreational vehicles.

The Vapor-Jet® system has test results showing miles per gallon improvement of 17.3 per cent on Trevaskis' 1971 Ford Galaxy and 13.3 per cent on a 1973 Olds Starfire.

Water injectors were developed to a highly refined state during World War II, to give combat planes increased speed and extended range. However, up to now, the low price of gas and the high cost and extremely difficult nstallation required for earlier injectors combined to make them unattractive for automobiles and light trucks.

The design of Trevaskis' new Vapor-Jet® is, on the other hand, very inexpensive ($29.95 + $3.00 shipping) and can be easily nstalled in ten to fifteen minutes.

The Vapor-Jet® has an unconditional 60 day guarantee. If for any reason you are not atisfied you may return it within 60 days of he day you installed it for a $29.95 refund. Following are some questions most frequently asked about Vapor-Jet® :

How does the Vapor-Jet® system work?

Vapor-Jet® operates very simply with no moving parts to wear out. It uses engine vacuum to pull outside air through a reservoir containing a water/methanol mixture which is ttached to the car under the hood. This causes the fluid to bubble and splash forming a mist of water droplets and vapor in the upper part of the reservoir. This mist is then drawn by vacuum through a hose which is connected to any intake manifold suction hose. This connection is made very simply by our exclusive hypodermic-like injector nozzle which contains a regulator to allow just the ight amount of mist to pass into the combusion chamber.

The introduction of this mist into the fuel air mixture has a cooling effect that increases he mixture density, extends the burning rate, and improves combustion efficiency. This eliminates ping (predetonation) and dieseling (after running of motor). Since steam is a good cleaner it also helps dissolve carbon deposits on the spark plugs and cylinder walls of older vehicles and helps prevent carbon buildup in new ones. Tests prove engine horsepower and octane ratings are increased with Vapor-Jet® because more fuel is converted into power producing energy. Vapor-Jet® combined with regular gas gives "premium" results.

How much mileage increase can be expected?

This varies from car to car. Independent testing on Trevaskis' car obtained improvements from 13.3% to 17.3%.

Will Vapor-Jet® fit all cars and is it easy to install?

Yes. Vapor-Jet® is easily installed on all domestic and foreign cars, vans, light trucks, R.V.s, campers, motor homes, and small boats. It will work on fuel injection, lean burn cars and cars with turbo chargers and super chargers and rotary engines. It will also work with unleaded gas, gasohol, or propane burning cars. The same kit fits all cars and contains everything needed. Simple installation instructions with a diagram are included and even a novice should be able to install it in less than 10 minutes. Simply take an ice pick or drill and make a small hole through any intake manifold suction hose (i.e.; PCV hose, brake assist hose, vacuum advance hose, etc.). Screw the injector nozzle into the hole, mount the reservoir by means of the bracket and screw supplied and connect the reservoir to the injector nozzle by means of the hose supplied. If you don't want to install it yourself most service stations will for a few bucks.

Can Vapor-Jet® damage my engine or cause rust?

Absolutely not! Vapor-Jet® cools down the fuel air mixture giving a better burn and supresses ping thus aiding your engine. The mist that enters into the engine turns immediately into vapor and exits out the exhaust similar to driving on a rainy day.

What is the purpose of the methanol V.I.M. (Vapor Injector Mix) and how long does it last?

The reservoir measures 3½" × 5½" × 7½" and holds just under ½ gal. A full reservoir should last 1,000 to 1,500 miles. Methanol (wood) alcohol is mixed with water mainly to prevent freezing and lesser amounts used to keep the injector nozzle clean in non-freezing weather. The cost of the methanol is minimal because in all but the very coldest climates one gallon will last about 8,000 miles in below 18°F weather and 16,000 miles or more in all weather above 18°F. Sources of methanol are drug stores, paint supply stores, service stations, chemical supply houses and bottled gas companies. Substitutions are ethanol (grain) alcohol or other gas line antifreezes that contain methanol.

For purchase, or further information write or call Ft. Morgan Vapor-Jet® , 15160 Hwy 144, #7, Ft. Morgan, CO 80701, (303) 867-9320. Dealerships available. (offer void in Ca.)

I, enclose $29.95 + $3.00 postage and handling:

☐ Check ☐ Cash ☐ Mastercard

☐ VISA ☐ C.O.D. Total ________

Card # ________

Exp. Date ________

Name ________

Address ________

City ________

State ________ Zip ________

60 day money back guarantee

former and a bridge or ring modulator type of dynamic convergence, this set features dual-diode scan rectification. This involves +13- and −13-volt sources from the secondary of the flyback transformer, developed by oppositely polarized diodes for the collector and emitter of the two vertical-output transistors. Operating during line time forward scan, they supply operating voltages based on conduction time of the horizontal output transformer to the vertical-output stages. This compensates for any changes in the usual 4:3 rectangular aspect raster ratio that might occur due to large beam-current drains or changes in ac supply voltages.

The convergence modulator receives vertical, horizontal, and pincushion inputs and mixes them in a diode bridge. This circuit shapes yoke currents so that red, blue, and green phosphors on the CRT are energized symmetrically and linearly. Dynamic adjustments for left, right, top, and bottom are made by one series inductor and four rheostats connected to the various inputs of the bridge. All are mounted on a separate plug-connected module.

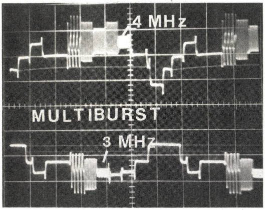

Fig. 2. Multiburst test patterns at video detector and CRT cathodes show 4 MHz and 3 MHz respectively.

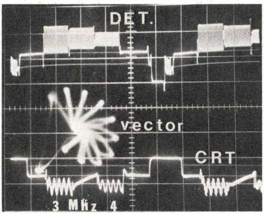

Fig. 3. Swept chroma at video detector and CRT. Normal vector has only slight distortion.

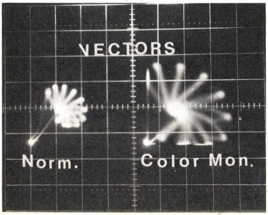

Fig. 4. Normal vector pattern on left, color monitor vector on right.

Test Results. The tuner exhibited better-than-average sensitivity and signal-to-noise ratio (S/N). A full 4 MHz of multiburst was measured at the video detector, while luminance bandpass at the CRT was 3 MHz (Fig. 2.). Swept chroma response was good, as shown in Fig. 3. Agc swing between saturation and cutoff measured 51 dB, which is adequate if the r-f agc potentiometer has been carefully adjusted. With this receiver, you can easily set the r-f agc for greater tuner sensitivity but less agc swing, making the 1542W excellent for long-distance reception. Using only 40 dB of agc swing, we measured vhf and uhf tuner sensitivities before snow of −12 and −20 dBmV, respectively.

Vector differences between manual and color-monitor control are illustrated in Fig. 4. Additional R − Y drive forces enlargement of the vector on the right and produces extra expansion and clipping in the eighth through tenth petals, although not nearly as much as fixed or static circuits that jam oranges and reds together and expand blues, distorting R − Y and B − Y angles of demodulation to 110° or 120°. There is no spreading of fleshtones from their normal hues.

Antiflutter time constants were adequate to prevent or minimize most low-frequency disturbances from aircraft. There was also only slight CB interference on channel 2 at a distance of 60 feet from the transceiver.

Despite somewhat loose voltage regulation, the picture remained stable from 110 to 130 volts ac on the power line. Audio from the 4″ Dynapower PM speaker was passable, and light, bright, colorful, pictures with strong contrast reflect the 21-to-26-kV high voltage generated, as well as plenty of video drive from the five luminance amplifiers and 24-pin chroma IC.

User Comment. While some of this set's measurements are a little off target, its color pictures, stylish appointments, and fast responses are pure pleasure. Its hot front end, excellent S/N, and other merits place it a good cut above its competition.

A combination of good luminance/chroma/brightness seems to compensate well for only 3 MHz of bandpass at the CRT. The way this set performs, one could easily be fooled into thinking it had a comb filter. All in all, we'd rate the 13AC1542W the best of the 13″ sets available at the time we performed our tests.—*Stan Prentiss.*

CIRCLE NO. 102 ON FREE INFORMATION CARD

Why use their flexible discs:

Ampex, Athana, BASF, Caelus, Control Data, Dysan, IBM, Inmac, K-Line, Maxell, Nashua, Scotch, Shugart, Syncom, 3M, Verbatim or Wabash

when you could be using

MEMOREX

for as low as $1.99 each?

Find the flexible disc you're now using on our cross reference list...
then write down the equivalent Memorex part number you should be ordering.

Product Family	Product Description	Memorex Part Number (3201-)	CE quant. 100 price per disc ($)	Ampex	Athana	BASF	Caelus	Dysan	IBM	K-Line	Maxell	Nashua	Scotch 3M	Shugart	Syncom	Verbatim	Wabash	Inmac	Control Data
Flexible Disc 1s Single-Headed Drives Single-Density Media	IBM Compatible (128 B/S, 26 sectors)	3060	2.19	5FD-111110	473071	53428	CM-F11	800506	2305830	40013	FD1-128	FD-1	740-0	S/A 100	15002	FD34-1000	F111111X	7870-K	421602
	IBM Compatible (128 B/S, 26 sectors) w/ W.P.N.	3062	2.24	–	–	–	–	–	–	–	–	–	740-0	–	–	–	–	–	–
	IBM Compatible (128 B/S, 26 sectors) w/ W.P.N. & Hub ring	3064	2.55	–	–	–	–	–	–	–	–	–	–	–	–	–	–	–	–
	IBM Compatible (128 B/S, 26 sectors) REVERSIBLE	1729	3.35	5FD-113110	473072	54431	–	–	–	40015	–	FD-2	740/2-0	–	15150	FF34-2000	F171111X	7860-K	–
	IBM System 6 Compatible	3066	2.19	–	473077	54561	–	800509	1669959	40014	–	–	740-0 0S6	–	15003	FD60-1000	F116111X	–	–
	IBM Compatible (256 B/S, 15 sectors)	3109	2.19	5FD-111210	473073	–	–	800584	2305845	40040	–	–	740-3600	–	15005	FD36-1000	F112111X	7861-K	–
	IBM Compatible (512 B/S, 8 sectors)	3110	2.19	–	473074	–	–	800585	1669954	40044	–	–	–	–	15004	FD60-1000	F113111X	7889-K	–
	Shugart Compatible, 32 hard sector	3015	2.19	5FD-211010	470901	53802	CM-F21	101/1	–	40016	FH1-32	FD-132	740-32	S/A-101	15025	FD32-1000	–	7890-K	421322
	Shugart Compatible, 32 hard sector REVERSIBLE	3025	3.35	5FD-213010	–	–	–	–	–	40017	–	–	740/2-32	–	15151	FF32-2000	–	7880-K	–
	Wang Compatible, 32 hard sector w/Hub ring	3087	2.50	–	–	54491	–	–	–	–	–	–	740-32RM	–	–	–	F37A411X	–	–
	CPT 8000 Compatible	3045	2.79	–	–	–	–	–	–	–	–	–	–	–	15226	–	–	–	–
Flexible Disc 1d Single-Headed Drives Double-Density Media	IBM Compatible (128 B/S, 26 sectors)	3090	2.95	5FD-121010	474071	54568	–	3740/1D	–	40047	FD1-128/M2100	FD-1D	741-0	–	–	FD34-8000	F131111X	7857-K	423002
	Soft Sector (128 B/S, 26 sectors) REVERSIBLE	3093	3.99	–	–	–	–	–	–	–	–	–	–	–	–	–	–	–	–
	Shugart Compatible, 32 hard sector	3091	2.95	5FD-221010	470801	54596	–	101/1D	–	40024	FH1-32D	–	741-32	S/A-103	15075	FD32-8000	F33A410X	7887-K	423322
	Shugart Compatible, 32 hard sector REVERSIBLE	3094	3.99	–	–	–	–	–	–	–	–	–	–	–	–	–	–	–	–
	Wang Compatible, 32 hard sector w/Hub ring	3088	3.20	–	–	–	–	–	–	–	–	–	–	–	–	–	F22A411X	–	–
Flexible Disc 2s Double-Headed Drives Single-Density Media	Soft Sector (Unformatted)	3101	3.84	–	–	–	–	–	–	–	–	–	–	–	–	–	–	–	–
	Soft Sector (128 B/S, 26 sectors)	3113	3.84	–	–	54428	–	800814	1766870	–	–	–	–	S/A-150	15153	FD10-4026	F121111X	–	–
	Soft Sector (256 B/S, 15 sectors)	3106	3.84	–	473477	54226	–	800815	2736700	40043	FD2-256D	–	742-0	–	15154	FD10-4015	F122111X	7856-K	424612
	32 Hard Sector	3108	3.84	–	–	–	–	–	–	–	FH2-32	–	–	–	–	–	–	–	–
Flexible Disc 2d Double-Headed Drives Double-Density Media	Soft Sector (Unformatted)	3102	3.49	–	473485	–	–	DY150	–	40028	FD2-XDM	FD-2D	743-0	–	15103	DD34-4001	–	–	425002
	Soft Sector (128 B/S, 26 sectors)	3115	3.49	–	–	–	–	–	–	–	–	–	–	S/A-150	–	–	–	–	–
	Soft Sector (256 B/S, 26 sectors)	3103	3.49	–	473471	54325	–	800817	1766872	40019	FD2-2560	–	743-0/256	–	15101	DD34-4026	F144111X	7858-K	425602
	Soft Sector (512 B/S, 15 sectors)	3114	3.49	–	473472	54479	–	800818	1669044	40039	–	–	743-0/512	–	15100	DD34-4015	F145111X	–	425612
	Soft Sector (1024 B/S, 8 sectors)	3104	3.49	–	473473	54485	–	800819	1669045	40020	–	–	743-0/1024	–	15102	DD34-4008	F147111X	7859-K	425622
	32 Hard Sector	3105	3.49	5FD-321010	470851	–	–	101/2D	–	40021	FH2-32D	–	743-32	S/A-151	15125	DD32-4000	F34A411X	7881-K	425322
	Burroughs B-80 Compatible 32 Hard Sector	3092	3.49	–	–	–	–	–	–	–	–	–	–	–	–	–	F34A611X	–	–
	Soft Sector (1024 B/S, 8 sectors) w/ Hub Ring	3116	3.75	–	–	–	–	–	–	–	–	–	–	–	–	–	–	–	–
Flexible Disc FD Memorex 651 or Equiv. Drive Compatible	FD VI (Vinyl Jacket)	30712003	2.95	–	470651	–	CM-F31	FDIV	–	40002	–	FD-165	511-0	–	15026	FD65-1000	F61A111X	7910	–
Mini Flexible Disc 1s 5¼" Single-Headed Drives Single-Density Media	Soft Sector (Unformatted)	3401	1.99	–	475001	54256	–	104/1	–	40500	MD1	MD 1	744-0	S/A-104	15300	MD525-01	M11A211X	7897	441002
	10 Hard Sector	3403	1.99	–	475010	54257	–	107/1	–	40501	–	MD 110	744-10	S/A-107	15325	MD525-10	M41A211X	7898	441102
	16 Hard Sector	3405	1.99	–	475016	54258	–	105/1	–	40502	MH1	MD 116	744-16	S/A-105	15326	MD525-16	M51A211X	7899	441162
	Soft Sector (Unformatted) W/Hub Ring	3431	2.19	–	–	–	–	–	–	–	–	–	–	–	–	MD525-01	–	–	–
	10 Hard Sector, w/Hub Ring	3433	2.19	–	–	–	–	–	–	–	–	–	–	–	–	MD525-10	–	–	–
	16 Hard Sector, w/Hub Ring	3435	2.19	–	–	–	–	–	–	–	–	–	–	–	–	MD525-16	–	–	–
Mini Flexible Disc 1d 5¼" Single-Headed Drives Double-Density Media	Soft Sector	3417	2.24	–	–	54646	–	104/1D	–	–	–	–	–	–	–	MD540-01	–	–	–
	10 Hard Sector	3418	2.24	–	–	54649	–	107/1D	–	–	–	–	–	–	–	MD540-10	–	–	–
	16 Hard Sector	3419	2.24	–	–	54652	–	105/1D	–	–	–	–	–	–	–	MD540-16	–	–	–
Mini Flexible Disc 2d 5¼" Double-Headed Drives Double Density Media	Soft Sector	3421	2.74	–	–	54624	–	104/2D	–	–	MD2-D	–	745-0	S/A-154	–	MD550-01	–	–	–
	10 Hard Sector	3423	2.74	–	–	54627	–	107/2D	–	–	–	–	745-10	S/A-157	–	MD550-10	–	–	–
	16 Hard Sector	3425	2.74	–	–	54630	–	105/2D	–	–	MH2-D	–	745-16	S/A-155	–	MD550-16	–	–	–

Memorex Flexible Discs...The Ultimate in Memory Excellence

Quality

Memorex means quality products that you can depend on. Quality control at Memorex means starting with the best materials available. Continual surveillance throughout the entire manufacturing process. The benefit of Memorex's years of experience in magnetic media production, resulting, for instance, in proprietary coating formulations. The most sophisticated testing procedures you'll find anywhere in the business.

100 Percent Error Free

Each and every Memorex Flexible Disc is certified to be 100 percent error free. *Each* track of *each* flexible disc is tested, individually, to Memorex's stringent standards of excellence. They test signal amplitude, resolution, low-pass modulation, overwrite, missing pulse error and extra pulse error. They are torque-tested, and competitively tested on drives available from almost every major drive manufacturer in the industry including drives that Memorex manufacturers. Rigid quality audits are built into every step of the manufacturing process and stringent testing result in a standard of excellence that assures you, our customer, of a quality product designed for increased data reliability and consistent top performance.

Customer-Oriented Packaging

Memorex's commitment to excellence does not stop with a quality product. They are proud of their flexible discs and they package them with pride. Both their packaging and their labeling have been designed with your ease of identification and use in mind. The desk-top box containing ten discs is convenient for filing and storage. Both box labels and jacket labels provide full information on compatibility, density, sectoring, and record length. Envelopes with multi-language care and handling instructions and color-coded removable labels are included. A write-protect feature is available to provide data security.

Full One Year Warranty — Your Assurance of Quality

Memorex Flexible Discs will be replaced free of charge by Memorex if they are found to be defective in materials or workmanship within one year of the date of purchase. Other than replacement, Memorex will not be responsible for any damages or losses (including consequential damages) caused by the use of Memorex Flexible Discs.

Quantity Discounts Available

Memorex Flexible Discs are packed 10 discs to a carton and 10 cartons to a case. Please order only in increments of 100 units for quantity 100 pricing. We are also willing to accommodate your smaller orders. Quantities less than 100 units are available in increments of 10 units at a 10% surcharge. **Quantity discounts** are also available. Order 500 or more discs at the same time and deduct 1%; 1,000 or more saves you 2%; 2,000 or more saves you 3%; 5,000 or more saves you 5%; 10,000 or more saves you 7%; 25,000 or more saves you 8%; 50,000 or more saves you 9% and 100,000 or more discs earns you a 10% discount off our super low quantity 100 price. Almost all Memorex Flexible Discs are immediately available from **CE**. Our warehouse facilities are equipped to help us get you the quality product you need, when you need it. If you need further assistance to find the flexible disc that's right for you, call the Memorex compatibility hotline. Dial 800-538-8080 and ask for the *flexible disc hotline* extension 0997. In California dial 800-672-3525 extension 0997.

Buy with Confidence

To get the fastest delivery from **CE** of your Memorex Flexible Discs, send or phone your order directly to our Computer Products Division. Be sure to calculate your price using the **CE** prices in this ad. Michigan residents please add 4% sales tax. Written purchase orders are accepted from approved government agencies and most well rated firms at a 10% surcharge for net 10 billing. All sales are subject to availability. All sales are final. Prices, terms and specifications are subject to change without notice. Out of stock items will be placed on backorder automatically unless **CE** is instructed differently. International orders are invited with a $20.00 surcharge for special handling in addition to shipping charges. All shipments are F.O.B. Ann Arbor, Michigan. No COD's please. Non-certified and foreign checks require bank clearance.

Mail orders to: **Communications Electronics**, Box 1002, Ann Arbor, Michigan 48106 U.S.A. Add $8.00 per case or partial-case of 100 8-inch discs or $6.00 per case of 100 5¼-inch mini-discs for U.P.S. *ground* shipping and handling in the continental U.S.A. If you have a Master Charge or Visa card, you may call anytime and place a credit card order. **Order toll-free** in the United States. Call anytime 800-521-4414. If you are outside the U.S. or in Michigan, dial 313-994-4444. **Dealer inquiries invited**. All order lines at **Communications Electronics** are staffed 24 hours.

Copyright ©1981 Communications Electronics™

CIRCLE NO. 1 ON FREE INFORMATION CARD

MEMBER
DIRECT MAIL MARKETING ASSOCIATION

CODE OF ETHICS

VISA

master charge
THE INTERBANK CARD

Order Toll-Free!
(800) 521-4414

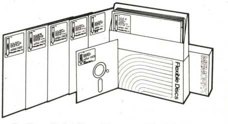

For Data Reliability—Memorex Flexible Discs

COMMUNICATIONS
ELECTRONICS™

Computer Products Division

854 Phoenix □ Box 1002 □ Ann Arbor, Michigan 48106 U.S.A.
Call TOLL-FREE (800) 521-4414 or outside U.S.A. (313) 994-4444

ALL NEW!

ALBIA ELECTRONICS

DM-10 LOW OHM METER MODULE

Measures resistance from 10 milliOhms to 20 Ohms. Now you can measure resistance down to 10 milliOhms with this low cost, easy to use DVM module. Check coil resistance, transformers, relays, chokes, printed circuit board copper paths and ground cables. Special zero balance control nulls out input cable resistance to insure accurate readings. Your DVM has to be set to 2V range during operation.

- Resistance range 10 milliOhms to 20 Ohms
- Zero Calibration control
- Battery powered (push to read battery saver circuit). Requires 1 9 Volt Battery (not included).
- Size 6.25" x 3.75" x 2" (Input cables not included or available)

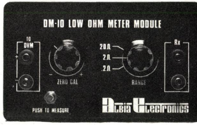

Completely assembled and tested! Ready to use!

FREQUENCY METER MODULE LOW COST DM-11, "5Hz to 100MHz"

Measure frequencies from 5Hz to 100MHz on your digital voltmeter with a resolution of 3½ digits — easy to use — perfect for field service — lab testing — home hobbyist! Connect the DM-11 to your DVM, set the DVM to the 2VDC range, connect a signal to the DM-11 via a BNC cable (not included) and measure the frequency of any source. Hi Lo Range LED's insure fast accurate readings.

- Frequency Range 5Hz to 100MHz
- Input Impedance 1 MegOhm

Completely assembled and tested! Ready to use!

- Input Sensitivity: < 100Hz < 80MV
  100Hz – 60MHz < 30MV
  > 60MHz < 70MV
- Size 6.25" x 3.75" x 2"
- External 9V DC power supply included. (Model MMAC-2)
- BNC Input Cable Accessory (Model PSA-2 add $14.95)

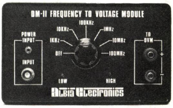

YOUR CHOICE $69.95 EACH

Any 2 For **$124.99**

All 4 For **$239.99**

8 CHANNEL SCOPE MULTIPLEXER, DM-12

Convert your single channel scope into a 4 or 8 channel instrument; just connect the DM-12, 8 channel scope multiplexer to your scope, clip the 8 input probes to the signals you want to view. Simple, easy, fast — can handle logic level TTL signals from DC to 3MHz. Features separate spacing and trace amplitude controls and selectable sampling rate — all to insure easy clear scope display.

- 8 TTL compatible input channels (1 TTL load per channel) can drive 50 Ohm scope cable.
- Maximum full screen amplitute 1.6 Volts adjustable.
- Trace amplitude and spacing controls.
- 4 or 8 channel selector switch.
- 8 color coded input cable, 24" long with insulated alligator clips.
- External 9 VDC power supply included (Model MMAC-2).
- Size 6.25" x 3.75" x 2"
- BNC Output Cable Accessory (Model PSA-2 add $14.95).

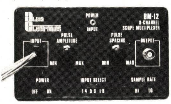

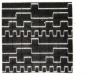

Completely assembled and tested! Ready to use!

LOW COST DM-8 CAPACITANCE METER MODULE

Connect this high quality low cost Capacitance Meter Module, DM-8 to your digital Volt Meter and turn it into a Digital Capacitance Meter — the Low Cost Way!

(When placing order specify the make and model DVM you're using so that factory modifications, if required, may be made before shipment is made.)

- Push to read range (button) from 1pF to 20,000µF
- Zero calibration control
- In one easy to use, self-contained package.
- Battery powered, with "push to read" battery saver circuit (9V batteries not included).
- Size 6.25" x 3.75" x 2"

Completely assembled and tested! Ready to use!

INSTANT ORDER INFORMATION BELOW!

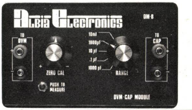

LOW COST HIGH FREQUENCY COUNTER – NOW IN STOCK!!

The Albia Model DM-7, 8 Digit High Frequency Counter is easy to use, switch selectable time base input by a single BNC, nothing to build — nothing more to buy!

- 5 Hz to 550 MHz
- 8 big easy-to-read .43" high intensity LED display
- Crystal (±3 ppm @ 25 C) controlled 0.1 or 1.0 sec. gate times
- Convenient benchtop size (7"x10"x3") durable attractive case

NEVER BEFORE AT THIS LOW PRICE .... $149.95 Includes Warranty

COMPLETELY ASSEMBLED • PRE-CALIBRATED • PRE-TESTED

REGULATED TRIPLE POWER SUPPLY
BARGAIN PRICED ALBIA MODEL DM-6

A fully assembled and tested power supply that provides a solid, fully wired triple power supply including fixed 5V @ 1 Amp, 5V to 15V @ 0.5 Amp, and −5V to −15V @ 0.5 Amp — all supplies regulated, short proof. Each supply has short indicator LED. Complete and ready for use in a durable (8"x6"x3½") metal case.

$99.95 Includes Warranty

FREE!!
NEW 1981 SPRING/ SUMMER CATALOG

Exciting new products! Send today!!

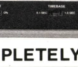

ALBIA SATISFACTION WARRANTY: If for any reason, whatsoever, you are not completely satisfied with your purchase, return it within 30 days of purchase date for a full refund — it's as simple as that!

POSTAGE & HANDLING	
ORDERS	ADD
UP TO $10.00	$1.95
$10.01 - $25.00	3.75
$25.01 - $50.00	4.65
$50.01 - $100.00	6.45
ORDERS OVER $100.00 WITHIN UNITED STATES	7.55

FOR FAST AND DEPENDABLE DELIVERY SERVICE
CALL TOLL FREE: 1-800-243-6953 9 A.M. to 5 P.M. E.S.T.
WE ACCEPT MASTER CHARGE, VISA AND AMEX CREDIT CARDS
Connecticut Residents add 7½% Sales Tax • Prices shown in U.S. currency only. Foreign orders add 15%.

ALBIA ELECTRONICS INC

24 Albia St. • New Haven, CT 06512

FREE ALBIA "TEMPLATE" WITH EVERY ORDER RECEIVED by June 25, 1981

CIRCLE NO. 2 ON FREE INFORMATION CARD

Popular Electronics Tests

The Hickok Model MX-333 Digital Multimeter

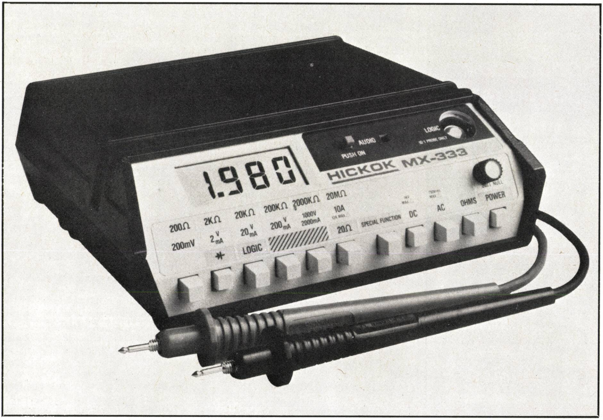

THE Hickok MX-333 Universal Digital Multimeter is designed for both bench and field use. It has a 3½-digit, 0.5″ high LCD display and features autodecimal point positioning, autopolarity, and overrange indication. A LOBAT annunciator on the LCD display turns on when the battery is down to the last 15-20% of its life expectancy. The high-impact plastic case is 2.2″ high, 6.7″ wide, and 6″ deep and weighs 22 ounces. The LCD display is mounted in a 45°-tilted front panel to allow the user to see the display clearly when the instrument is on a flat workbench or suspended from the user's belt (via a belt-clip). This also allows the light-reflecting LCD display to use the maximum ambient light. Up to 6-kV transient protection is provided on the ac and dc functions, 500 volts on resistance, and a fuse protects the current functions. Suggested retail price is $249.

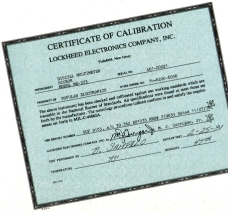

CERTIFICATE OF CALIBRATION
LOCKHEED ELECTRONICS COMPANY, INC.
Plainfield, New Jersey

INSTRUMENT DIGITAL MULTIMETER HICKOK MODEL MX-333
SERIAL NO. 661-00221
PROPERTY OF POPULAR ELECTRONICS
WORK ORDER NO. 74-6200-6956

The above instrument has been checked and calibrated against our working standards which are traceable to the National Bureau of Standards. All specifications were found to meet those set forth by the manufacturer. The metrology procedures utilized conform to and satisfy the requirements set forth in MIL-C-45662A.

NBS REPORT NUMBER GUF 9155, s/n 39.362 ES1035 NBS# 219833 Dated 11/27/78
LOCKHEED ELECTRONICS COMPANY, INC. by M J Corrigan Jr. M. J. Corrigan, Jr.
DATE OF TEST 2-25-81
TEST PERFORMED BY B. SAMPALO
HUMIDITY 47%
TEMPERATURE 73°

LEC 1314

General Description. The MX-333 is equipped with four recessed test-lead connectors—COM, V/Ω, 10A, and mA/20Ω. On the straight portion of the front panel are 10 function and range

FREE

The newest in home computers, fine stereo components, color TV, HAM radio, precision test equipment, innovative electronics for the home—all in easy-to-build, money-saving kits.

Send today for your FREE Heathkit® Catalog

If coupon is missing, write
Heath Co., Dept. 010-782
Benton Harbor, MI 49022

Send to: Heath Co., Dept. 010-782
Benton Harbor, MI 49022.

Send my free Heathkit Catalog now. I am not currently receiving your catalog.

Name ______________________

Address ____________________

City ______________ State ______

CL-724A Zip ______

CIRCLE NO. 27 ON FREE INFORMATION CARD

pushbuttons, the power on/off pushbutton, and a control used to null test-lead resistance when using the 20-ohm resistance range. Besides the LCD display, the sloping portion of the front panel also supports an audio tone on/off pushbutton (with associated small speaker hole), and a BNC connector for use with an optional 10:1 probe in what Hickok calls the LOGI-TRAK function. The internal 9-volt battery is accessed via a finger-screw locked sliding panel on the rear.

The audio portion of the MX-333, called VARI-PITCH, is used for "eyes-off" operation. When it is on, an audio tone with a frequency proportional to the LCD display indication is produced.

VARI-PITCH operates on all ranges and functions. In the resistance function, the tone is off at open circuit and increases in frequency with diminishing resistance. On other functions, the tone begins at a display of 40 or less and extends to four times full scale. Response time is less than 100 ms.

The LOGI-TRAK function, which works in conjunction with VARI-PITCH, uses any 10:1 scope-type probe and has an input impedance of 10 megohms/10 pF. It operates when the LOGIC pushbutton is depressed. The minimum pulse width detected is typically 5 ns; pulse indication is a colon on the display and an audio signal. Maximum frequency is 80 MHz. Overload protection extends to 300 V dc or rms continuous.

The *dc voltage* function provides five ranges from 200 mV to 1 kV full scale with an accuracy of ±0.1% reading plus 1 digit. Overload protection extends to 1 kV dc/peak ac, and up to 6-kV for transients. Input resistance is 10 megohms on all ranges. Normal-mode rejection ratio is 50 dB at 60 Hz; common-mode rejection ratio is 100 dB.

The *ac voltage* function provides five ranges from 200 mV to 1 kV full scale with an accuracy of ±1% reading plus 2 digits between 45 and 1 kHz, and ±5% reading plus 5 digits between 1 kHz and 5 kHz on the 200-mV to 20-V ranges. Overloads up to 1 kV dc or 750 V rms are protected on all except the 200-mV range, which must not be exposed to anything over 200 V rms for more than 15 seconds. Input impedance is 10 megohms on all ranges. Dc blocking voltage is 1 kV dc plus peak ac.

The *resistance* function has seven decade-spaced ranges from 20 ohms to 20 megohms. Accuracy is ±3% on the 20-ohm range; 0.2% on 200 ohms; 0.1% on 2k, 20k, 200k, and 2 megohms; and 1% plus 1 digit on the 20-megohm range. There is overload protection to 500 V dc/rms on all ranges, with a 2-ampere fuse in the 20-ohm range. Voltage dropped across the component under test is 0.25 volt for full scale indication and 3.2 V maximum (open circuit).

The *diode test* range measures the forward drop of a semiconductor junction between 0 and 2 volts dc. The test levels are 2 mA nominal and 2.5 volts open circuit. Overload protection covers 500 V dc or rms.

Both *ac and dc current* functions provide five ranges from 2 mA to 10 amperes. Resolution ranges from 1 μA on the 2-mA range to 10 mA on the 10-ampere range. Dc accuracy is ±1% on the 2-mA, 20-mA, and 200-mA ranges; ±1.5% on the 2-ampere range; and ±1.2% on the 10-ampere range. All are plus 1 digit. The ac current accuracy is ±2.5% on the 2-mA range and ±1.5% on the 20-mA range, both measured between 45 and 65 Hz; and ±1.5% on the upper three ranges, measured between 45 and 400 Hz. All are plus 2 digits. The voltage burden is 0.25 volt on the lower three ranges and 0.5 volt on the 10-ampere range. Overload protection is good for 250 V at 2 amperes except on the 10-ampere range, where it is 15 amperes for one minute maximum.

Packaged with the instrument is a 9-volt battery, a set of safety test leads (red and black), alligator clips, a belt clip and four extra skidproof feet.

Comments. The MX-333 was checked by the Lockheed Electronics Company Instrumentation Measurements Laboratory, against standards traceable to the National Bureau of Standards. After the tests, the IML issued a certificate testifying that the MX-333 met its published specifications in all respects.

The instrument was used on a test bench for several weeks performing conventional functions. The DMM was very easy to use because of the unambiguous pushbuttons for function and range. The positive detenting of the pushbuttons made selection easy. Having the LCD display angled at 45° not only makes the instrument easy to read when placed on a flat surface, but also keeps the display well illuminated when overhead lighting is used. One slight problem was the reflection of overhead fluorescent lights on the front surface of the display.

The VARI-PITCH function takes a little getting used to, but once you do, it is quite handy—especially for making continuity checks. Similarly, LOGI-TRAK is excellent for measurements on high-impedance CMOS circuitry.

If you do much servicing of console equipment, the belt-clip operation of the MX-333 can be very handy. Since the test-lead connectors are mounted on the side of the instrument, the leads do not get in the way. The slope of the display panel, which we found too acute for bench-top operation because of glare, also creates a problem when the instrument is clipped to the belt. The user must bend over slightly in order to see the display.

In conclusion, we find the MX-333 an excellent instrument, quite at home both on the bench and in the field. Although it may cost a little more than other portable DMMs, its versatility provides compensation.—*Leslie Solomon*

CIRCLE NO. 104 ON FREE INFORMATION CARD

Start learning and computing for only ***$129.95*** *with a Netronics 8085-based computer kit. Then expand it in low-cost steps to a business/development system with 64k or more RAM, 8" floppy disk drives, hard disks and multi-terminal I/O.*

THE NEW EXPLORER/85 SYSTEM

Special! *Full 8" floppy, 64k system for less than the price of a mini! Only* **$1499.95!**

(Also available wired & tested, $1799.95)

Imagine — for only $129.95 you can own the starting level of Explorer/85, a computer that's expandable into full business/development capabilities — a computer that can be your beginner system, an OEM controller, or an IBM-formatted 8" disk small business system. From the first day you own Explorer/85, you begin computing on a significant level, and applying principles discussed in leading computer magazines. Explorer/85 features the advanced Intel 8085 cpu, which is 100% compatible with the older 8080A. It offers onboard S-100 bus expansion, Microsoft BASIC in ROM, plus instant conversion to mass storage disk memory with standard IBM-formatted 8" disks. All for only $129.95, plus the cost of power supply, keyboard/terminal and RF modulator if you don't have them (see our remarkable prices below for these and other accessories). With a Hex Keypad/display front panel, Level "A" can be programmed with no need for a terminal, ideal for a controller, OEM, or a real low-cost start.

Level "A" is a complete operating system, perfect for beginners, hobbyists, industrial controller use. $129.95

Full 8" disk system for less than the price of a mini (shown with Netronics Explorer/85 computer and new terminal). System features floppy drive from Control Data Corp., world's largest maker of memory storage systems (not a hobby brand!)

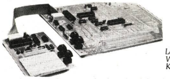

Level "A" With Hex Keypad/Display.

LEVEL "A" SPECIFICATIONS

Explorer/85's Level "A" system features the advanced Intel 8085 cpu, an 8355 ROM with 2k deluxe monitor/operating system, and an advanced 8155 RAM I/O . . . all on a single motherboard with room for RAM/ROM/PROM/EPROM and S-100 expansion, plus generous prototyping space.

PC Board: Glass epoxy, plated through holes with solder mask. • **I/O:** Provisions for 25-pin (DB25) connector for terminal serial I/O, which can also support a paper tape reader . . . cassette tape recorder input and output . . . cassette tape control output . . . LED output indicator on SOD (serial output) line . . . printer interface (less drivers) . . . total of four 8-bit plus one 6-bit I/O ports. • **Crystal Frequency:** 6.144 MHz. • **Control Switches:** Reset and user (RST 7.5) interrupt . . . additional provisions for RST 5.5, 6.5 and TRAP interrupts onboard. • **Counter/Timer:** Programmable, 14-bit binary. • **System RAM:** 256 bytes located at F800, ideal for smaller systems and for use as an isolated stack area in expanded systems . . . RAM expandable to 64K via S-100 bus or 4k on motherboard.

System Monitor (Terminal Version): 2k bytes of deluxe system monitor ROM located at F000, leaving 0000 free for user RAM/ROM. Features include tape load with labeling . . . examine/change contents of memory . . . insert data . . . warm start . . . examine and change all registers . . . single step with register display at each break point, a debugging/training feature . . . go to execution address . . . move blocks of memory from one location to another . . . fill blocks of memory with a constant . . . display blocks of memory . . . automatic baud rate selection to 9600 baud . . . variable display line length control (1-255 characters/line) . . . channelized I/O monitor routine with 8-bit parallel output for high-speed printer . . . serial console in and console out channel so that monitor can communicate with I/O ports.

System Monitor (Hex Keypad/Display Version): Tape load with labeling . . . tape dump with labeling . . . examine/change contents of memory . . . insert data . . . warm start . . . examine and change all registers . . . single step with register display at each break point . . . go to execution address. Level "A" in this version makes a perfect controller for industrial applications, and is programmed using the Netronics Hex Keypad/Display. It is low cost, perfect for beginners.

HEX KEYPAD/DISPLAY SPECIFICATIONS

Calculator type keypad with 24 system-defined and 16 user-defined keys. Six digit calculator-type display, that displays full address plus data as well as register and status information.

LEVEL "B" SPECIFICATIONS

Level "B" provides the S-100 signals plus buffers/drivers to support up to six S-100 bus boards, and includes: address decoding for onboard 4k RAM expansion selectable in 4k blocks . . . address decoding for onboard 8k EPROM expansion selectable in 8k blocks . . . address and data bus drivers for onboard expansion . . . wait state generator (jumper selectable), to allow the use of slower memories . . . two separate 5 volt regulators.

LEVEL "C" SPECIFICATIONS

Level "C" expands Explorer/85's motherboard with a card cage, allowing you to plug up to six S-100 cards directly into the motherboard. Both cage and card are neatly contained inside Explorer's deluxe steel cabinet. Level "C" includes a sheet metal superstructure, a 5-card, gold plated S-100 extension PC board that plugs into the motherboard. Just add required number of S-100 connectors.

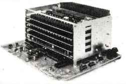

Explorer/85 With Level "C" Card Cage.

LEVEL "D" SPECIFICATIONS

Level "D" provides 4k of RAM, power supply regulation, filtering decoupling components and sockets to expand your Explorer/85 memory to 4k (plus the original 256 bytes located in the 8155A). The static RAM can be located anywhere from 0000 to EFFF in 4k blocks.

LEVEL "E" SPECIFICATIONS

Level "E" adds sockets for 8k of EPROM to use the popular Intel 2716 or the TI 2516. It includes all sockets, power supply regulator, heat sink, filtering and decoupling components. Sockets may also be used for 2k x 8 RAM IC's (allowing for up to 12k of onboard RAM).

DISK DRIVE SPECIFICATIONS

- 8" CONTROL DATA CORP. professional drive.
- LSI controller.
- Write protect.
- Single or double density.
- Data capacity: 401,016 bytes (SD), 802,032 bytes (DD), unformatted.
- Access time: 25ms (one track).

DISK CONTROLLER/ I/O BOARD SPECIFICATIONS

- Controls up to four 8" drives.
- 1771A LSI (SD) floppy disk controller.
- Onboard data separator (IBM compatible).
- 2 Serial I/O ports
- Autoboot to disk system when system reset.
- 2716 PROM socket included for use in custom applications.
- Onboard crystal controlled.
- Onboard I/O baud rate generators to 9600 baud.
- Double-sided PC board (glass epoxy.)

DISK DRIVE CABINET/POWER SUPPLY

- Deluxe steel cabinet with individual power supply for maximum reliability and stability.

ORDER A COORDINATED EXPLORER/85 APPLICATIONS PAK!

Beginner's Pak (Save $26.00!) — Buy Level "A" (Terminal Version) with Monitor Source Listing and AP-1 5-amp Power Supply: (regular price $199.95), now at SPECIAL PRICE: **$169.95** plus post. & insur.

Experimenter's Pak II (Save $53.40!) — Buy Level "A" (Hex Keypad/Display Version) with Hex Keypad/Display, Intel 8085 User Manual, Level "A" Hex Monitor Source Listing, and AP-1 5-amp Power Supply: (regular price $279.35), all at SPECIAL PRICE: **$219.95** plus post. & insur.

Special Microsoft BASIC Pak (Save $103.00!) — Includes Level "A" (Terminal Version), Level "B", Level "D" (4k RAM), Level "E", 8k Microsoft in ROM, Intel 8085 User Manual, Level "A" Monitor Source Listing, and AP-1 5-amp Power Supply: (regular price $439.70), now yours at SPECIAL PRICE: **$329.95** plus post. & insur.

ADD A TERMINAL WITH CABINET, GET A FREE RF MODULATOR: Save over $114 at this SPECIAL PRICE: **$499.95** plus post. & insur.

Special 8" Disk Edition Explorer/85 (Save over $104!) — Includes disk-version Level "A", Level "B", two S-100 connectors and brackets, disk controller, 64k RAM, AP-1 5-amp power supply, Explorer/85 deluxe steel cabinet, cabinet fan, 8" SD/DD disk drive from famous CONTROL DATA CORP. (not a hobby brand!), drive cabinet with power supply, and drive cable set-up for two drives. This package includes everything but terminal and printers (see coupon for them). Regular price $1630.30, all yours in kit at SPECIAL PRICE: **$1499.95** plus post. & insur. Wired and tested, only **$1799.95.**

Special! Complete Business Software Pak (Save $625.00!) — Includes CP/M 2.0, Microsoft BASIC, General Ledger, Accounts Receivable, Accounts Payable, Payroll Package: (regular price $1325), yours now at SPECIAL PRICE: **$699.95.**

Please send the items checked below:

☐ **Explorer/85 Level "A" kit** (Terminal Version) . . . **$129.95** plus $3 post. & insur.
☐ **Explorer/85 Level "A" kit** (Hex Keypad/Display Version) . . . **$129.95** plus $3 post. & insur.
☐ **8k Microsoft BASIC** on cassette tape, **$64.95** postpaid.
☐ **8k Microsoft BASIC in ROM kit** (requires Levels "B", "D" and "E") . . . **$99.95** plus $2 post. & insur.
☐ **Level "B" (S-100) kit** . . . **$49.95** plus $2 post. & insur.
☐ **Level "C" (S-100 6-card expander) kit** . . . **$39.95** plus $2 post. & insur.
☐ **Level "D" (4k RAM) kit** . . . **$69.95** plus $2 post. & insur.
☐ **Level "E" (EPROM/ROM) kit** . . . **$5.95** plus 50¢ p&h.
☐ **Deluxe Steel Cabinet** for Explorer/85 . . . **$49.95** plus $3 post. & insur.
  ☐ Fan For Cabinet . . . **$15.00** plus $1.50 post. & insur.
☐ **ASCII Keyboard/Computer Terminal kit:** features a full 128 character set, u&l case; full cursor control; 75 ohm video output; convertible to baudot output; selectable baud rate, RS232-C or 20 ma. I/O, 32 or 64 character by 16 line formats, and can be used with either a CRT monitor or a TV set (if you have an RF modulator) . . . **$149.95** plus $3.00 post. & insur.
  ☐ **DeLuxe Steel Cabinet** for ASCII keyboard/terminal . . . **$19.95** plus $2.50 post. & insur.
☐ **New! Terminal/Monitor:** (See photo) Same features as above, except 12" monitor with keyboard and terminal is in deluxe single cabinet; kit . . . **$399.95** plus $7 post. & insur.
☐ **Hazeltine terminals:** Our prices too low to quote — **CALL US**
☐ **Lear-Sigler terminals/printers:** Our prices too low to quote: **CALL US**
☐ **Hex Keypad/Display kit** . . . **$69.95** plus $2 post. & insur.
☐ **AP-1 Power Supply Kit** ±8V @ 5 amps) in deluxe steel cabinet . . . **$39.95** plus $2 post. & insur.
☐ **Gold Plated S-100 Bus Connectors** . . . **$4.85** each, postpaid.
☐ **RF Modulator kit** (allows you to use your TV set as a monitor) . . . $8.95 **postpaid.**
☐ **16k RAM kit** (S-100 board expands to 64k) . . . **$199.95** plus $2 post. & insur.
☐ **32k RAM kit** . . . **$299.95** plus $2 post. & insur.
☐ **48k RAM kit** . . . **$399.95** plus $2 post. & insur.
☐ **64k RAM kit** . . . **$499.95** plus $2 post. & insur.
☐ **16k RAM Expansion kit** (to expand any of the above in 16k blocks up to 64k) . . . **$99.95** plus $2 post. & insur. each.
☐ **Intel 8085 cpu Users' Manual** . . . **$7.50** postpaid.
☐ **12" Video Monitor** (10MHz bandwidth) . . . **$139.95** plus $5 post. & insur.
☐ **Beginner's Pak** (see above) **$169.95** plus $4 post. & insur.
☐ **Experimenter's Pak** (see above) . . . **$219.95** plus $6 post. & insur.
☐ **Special Microsoft BASIC Pak Without Terminal** (see above) . . . **$329.95** plus $7 post. & insur.
☐ Same as above, plus **ASCII Keyboard Terminal With Cabinet, Get Free RF Modulator** (see above) . . . **$499.95** plus $10 post. & insur.
☐ **Special 8" Disk Edition Explorer/85** (see above) . . . **$1499.95** plus $26 post. & insur.
  ☐ **Wired & Tested** . . . **$1799.95** plus $26 post. & insur.
☐ **Extra 8" CDC Floppy Drives** . . . **$499.95** plus $12 post. & insur.
  ☐ **Cabinet & Power Supply For Drive** . . . **$69.95** plus $3 post. & insur.
☐ **Drive Cable Set-up For Two Drives** . . . **$25** plus $1.50 post. & insur.
☐ **Disk Controller Board With I/O Ports** . . . **$199.95** plus $2 post. & insur.
☐ **Special: Complete Business Software Pak** (see above) . . . **$699.96** postpaid.
  SOLD SEPARATELY:
  ☐ **CP/M 1.4** . . . **$100** postpaid.
  ☐ **CP/M 2.0** . . . **$150** postpaid.
  ☐ **Microsoft BASIC** . . . **$325** postpaid.
☐ **Intel 8085 cpu User Manual** . . . $7.50 **postpaid.**
☐ **Level "A" Monitor Source Listing** . . . **$25** postpaid.

Continental U.S.A. Credit Card Buyers Outside Connecticut

CALL TOLL FREE: 800-243-7428

To Order From Connecticut Or For Technical Assistance, call (203) 354-9375

Total Enclosed (Conn res. add sales tax) $ ________
Paid By:
☐ Personal Check ☐ Cashier's Check/Money Order
☐ **VISA** ☐ **Master Charge** (Bank No. __ __ __ __)
Acct. No. ____________________ Exp. Date ______
Signature ______________________________
Print
Name ______________________________
Address ______________________________
City______________________________
State ______________ Zip______________

NETRONICS Research & Development Ltd.
333 Litchfield Road, New Milford, CT 06776

COMPUTER BITS

By Leslie Solomon
Senior Technical Editor

Free Computer Networks

A VIRTUALLY limitless information resource lies almost at your fingertips in the form of some 250 computerized bulletin boards that can be accessed by any microcomputer having a 300-baud, Bell-103 compatible modem. Most use the carriage return as the speed-recognition character and become self-prompting thereafter.

Some systems offer specialized information (medicine, astronomy, photography, ham radio, etc.), while others are more generalized. Most are available evenings or weekends when phone rates are low, while others operate 24 hours a day, 7 days a week. The listing of a telephone number offers no assurance that the system is in operation, as many shut down periodically for maintenance, and others may stop without notice.

Novation, Inc., Tarzana, CA, a modem manufacturers, offers a free dial-up directory with up-to-date listings. Operating 24 hours a day, it can be reached by calling 213-881-6880 and when the message LOGON PLEASE appears, type CAT, then carriage return (or ENTER). An 18-item menu consisting of Novation product information, a glossary of computer terms, and a modem/printer test will appear. Item 18 is the directory of dial-up systems that is updated each month.

As a service to our readers, we would like to be kept up to date on all free bulletin boards, times of operation, and what services are offered. Send all information to this column care of POPULAR ELECTRONICS, 1 Park Ave., New York, NY 10016.

201
283-2724
457-0893
528-6623
688-7117
753-1225
753-8152
764-4974
835-7228
843-4563
874-6833
891-7441
968-1074

202
281-2125
337-4694
635-5730

203
348-6353
357-1920
746-4644

205
272-5069
945-1489

206
244-5438
246-8983
334-7394
482-5134
482-5590
524-0203
546-6239
723-3282
937-0444

209
638-6392

212
245-4363
448-6576
787-5520
933-9459
997-2186

213
276-4276
291-9314
316-5706
329-3715
340-0135
346-1849
349-5728
360-6332
394-1505
395-1592
396-3905
424-3506
428-4718
459-3177
459-6400
566-8035
631-3186
657-8803
673-2206
675-8803
709-5423
787-4004
795-3788
799-1632
799-6514
826-0325
828-3400
843-5390
881-6880
921-2111

214
288-4859
634-2668
634-2775
641-8759

215
563-0674

216
486-4176
644-1965
745-7855

217
429-5505

301
344-9156

303
759-2625
771-3826
789-0936

305
261-3639
566-0805
689-3234
772-4444
821-7401
862-6917
989-9647

309
688-0470
694-6531

312
236-7522
255-6489
269-8083
296-7486
337-6631
359-9450
420-7995
528-7141
545-8086
622-8802
622-9609
726-8263
767-0202
782-8180
782-9751
941-9009
964-7768

313
288-0335
357-1422
465-9531
477-4471
484-0732
569-2063
588-7054

314
227-8495
781-1308
838-7784

316
746-2078

319
353-6528
557-9618

404
394-4220
733-3461
790-8614
793-1045
939-1520
939-8429
953-0723

405
353-2554
528-8009

408
227-5416
241-1956
296-5799
263-0248
263-9650

414
241-5406
241-8364
282-8118

415
348-2139
348-2396
493-7691
527-0400
573-8768
593-1200
647-9524
661-0705
683-4703
792-8406
851-3453
948-1474
968-5140

417
862-7852

419
351-3845
865-1594

502
245-8288
896-9624

503
641-5510
641-8555
641-9029
646-5510

512
657-0779

513
671-2753
874-2283

515
279-8863

523
223-3672

602
866-0258
956-5612
957-4428
957-9282

604
687-2640

607
754-5571
797-6416

609
983-5970

612
561-6311
929-8966

Educator, Entertainer, Accountant.

Your Challenger Personal Computer.

Through the miracle of modern technology, a complete computer as powerful as the multimillion dollar room-sized computers of a few years ago can be put in a package the size of a typewriter and sells for as little as a color television set!

Through its years of microcomputer experience, Ohio Scientific has effectively channeled this tremendous computer power into a "friendly" computer with hundreds of personal uses, via a huge software library of programs for a broad range of personal, home, educational and business use.

This available software allows you to use and enjoy your computer without becoming an expert. The Challenger, however, is a powerful, general purpose computer which can be programmed in several languages by those who choose to.

Here are just a few of the popular uses of an Ohio Scientific Challenger Computer:

Education

The personal computer is the ultimate educational aid because it can entertain while it educates. Software available ranges from enhancing your children's basic math, reading and spelling ability, through tutoring high school and college subjects, to teaching the fundamentals of computers and computer programming.

Entertainment

Many of the Challenger's games educate while they entertain, from cartoons for preschoolers to games which sharpen mathematical and logical abilities. But, entertainment doesn't stop here. The Challenger's graphics capabilities and fast operation allow it to display action games with much more detail than the best video games, providing spectacular action in games such as Invaders, Space Wars, Tiger Tank and more! All popular sports such as golf, baseball and bowling are available as simulated computer games as well as many conventional games such as chess where the computer plays the role of a formidable opponent.

Accounting

Your Challenger computer can keep track of your checkbook, savings account, loans, expenses, monitor your calorie intake and your biorythms.

If you are involved in a business, you can use it to do word processing; accounting, inventory control, order processing, customer lists, client records, mailing labels and planning.

And more:

This may seem like a lot of uses, but it's only the tip of the iceberg for a general purpose computer. For example, your Challenger can be expanded to control lights and appliances, manage your energy usage and monitor for fire and break-ins. Furthermore, it can communicate with you, with other computers and the new personal computer information services over the telephone.

In fact, the uses of general purpose, personalized computers are expanding daily as more and more people discover the tremendous capabilities of these new technological wonders.

Ohio Scientific offers you four personalized computer systems starting at just $479.

For a free catalog and the name of the dealer nearest you, call 1-800-321-6850 toll free.

OHIO SCIENTIFIC
a M/A-COM Company
1333 SOUTH CHILLICOTHE ROAD
AURORA, OH 44202 • (216) 831-5600

CIRCLE NO. 46 ON FREE INFORMATION CARD

New, Unique, Hard-To-Find Products

Alternate Energy, Biofeedback, Telescopes, Optics, Tools, Weather, Motors, Magnets, Microscopes, Lab Equipment, & More!

In One Giant FREE Catalog

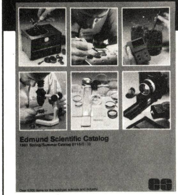

No. 247 1981 Edmund Scientific Co.

Best Quality! Best Selection! Biggest Catalog! For over 40 years, thousands of engineers, craftsmen, hobbyists, and do-it-yourselfers nationwide, have been going directly to the Edmund Scientific Catalog. They find top quality products for every need. . .fully guaranteed!

FREE! You can have a copy of this unique catalog now, just for the asking. Simply fill in below, mail today, and your Edmund Scientific Catalog will be on its way to you.

☐ Send **FREE** Catalog

NAME ______________________________

ADDRESS ______________________________

CITY______________ STATE______________ ZIP__________

Edmund Scientific Dept. 3240 AV12 Edscorp Bldg. Barrington, N.J. 08007

computique computique computique

TEXAS INSTRUMENTS
INCORPORATED
electronic calculators

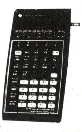

TI–35 STU MATH		22.50
BUS ANAL I		21.95
BA II EXEC		44.95
BUS CARD		39.95
INVEST ANAL		48.95
TI–55 SCI		34.95
TI–57 SCI PROG		49.95
TI–5100 PRINTER		39.95
TI–5015 PRINTER		54.95
TI–5040 PRINTER	NEW	69.95
TI–5135 PRINTER		69.95
TI–5142 PRINTER	NEW	99.95
TI–58C		99.95
TI–59		209.95
PC–100C		169.95
SPEAK & SPELL		59.95
SPEAK & READ		74.95
SPEAK & MATH		67.95
99/4 HOME COMPUTER		CALL

THE HP-85!

Complete Enhancements, Peripherals and Accessories

Your HEWLETT PACKARD *Headquarters*

HP–67	299.95
HP–97	599.95
HP–33C SCI	79.95
HP–34C SCI	114.95
HP–38C BUS/RE	119.95
HP–32E SCI	44.95
HP–37E BUS	59.95
HP–41, 41CV, SYS I, II	CALL
HP–85	CALL
HP–83	CALL

(714) 549-7373
INFORMATION LINE

(800) 432-7066
TOLL FREE (Within CA)

(800) 854-0523
TOLL FREE (Outside CA)

apple computer MEANS BUSINESS

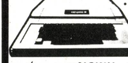

- Personal Computers Designed for Analysis and Business Word Processing
- Immediate Delivery
- Ask about Peripherals and Software
- All at Great Prices!!

apple /// NOW!!
AUTHORIZED DEALER
AND LEVEL 1 SERVICE CENTER

CHESS CHALLENGER "7"	99.95
SENSORY CHESS CHALLENGER "8" NEW	129.95

TOUCH THE FUTURE
ATARI
800 (16K) STARTER SYSTEM 899.95
VISICALC AVAILABLE ......CALL

CODE-A-PHONE
1000 .... 99.95
1750 NEW 269.95

ALSO: CANON, TOSHIBA, NSC, SEIKO, MATTEL, PEARLCORDER, ITT, GTE, CASIO, SHARP, AND MANY OTHERS. ALL AT GREAT PRICES!!

WE WILL MEET OR BEAT ANY COMPETITOR'S ADVERTISED PRICE ON MOST ITEMS IF HE HAS THE MDSE. ON HAND. VISA, MASTERCARD, MONEY ORDER, PERS. CK. (14 WRKG. DAYS TO CLR.), COD ACCEPTED; MIN. $4.95 SHIPPING U.S.A.; AIR ON REQST.; CAL. RES. ADD 6% SALES TX.; ALL MDSE. SUBJ. TO AVAIL.; PRICES SUBJ. TO CHANGE;

MAIL & PHONE ORDERS ONLY

Send orders to:
3211 SO. HARBOR BLVD.
SANTA ANA, CA 92704

computique

WRITE OR CALL FOR
FREE CATALOG
POPEL-JU 81

NEWPORT
(714) 549-7373

WEST LOS ANGELES
(213) 820-0423

TARZANA
(213) 705-7507

MID-WILSHIRE
(213) 385-7777

LAWNDALE
(213) 370-5795

PASADENA
(213) 795-3007

BREA
(714) 990-6600

PROFESSIONAL DISCOUNTS

CIRCLE NO. 8 ON FREE INFORMATION CARD

613
725-2243

614
272-2759
649-7097

615
254-9193

617
354-4682
388-5125
431-1699
649-7097
692-3973
864-3819
897-0346
963-8310

702
826-7234
873-9491
454-3417

703
281-2125
281-2222
379-0303
620-4990
734-1387
750-0930
893-9474
978-7561

707
448-9055

713
233-7943
654-0759
693-8080
977-7019

714
287-9379
449-5689
463-0461
495-6458
526-3687
537-7913
565-0961
571-5550
582-9557
730-1206
739-0711
751-1422
772-8868
898-1984
952-2110
962-7979
963-7222

801
375-7000
466-1737
753-6800

802
748-9089
879-4981

803
270-5372
270-5392
279-5392
771-0922
772-1592

804
340-5246
543-7194

805
484-9904
527-9321
682-7876
964-4115

806
355-5612

813
223-7688

816
523-9121
531-1050
861-7040
931-3135
931-9316

817
776-1325
855-3916
855-3918
923-0009

901
276-8196
362-2222
761-4743

902
794-8198

904
243-1257
243-8565

913
362-6398
651-3744
764-1520
782-5115

915
584-5393

916
393-4459

918
224-5347

◇

THIS MAY BE THE MOST IMPORTANT BOOK YOU READ THIS YEAR

COMPUTER
REFERENCE
GUIDE

135 South Harper Avenue,
Los Angeles, CA 90048.

Phone: (213) 852-4886

MICROCOMPUTER REFERENCE HANDBOOK

The **MICROCOMPUTER REFERENCE HANDBOOK** reviews in detail more than 130 microcomputer systems from over 50 major microcomputer suppliers, including some of the latest Japanese manufacturers. It is designed to aid both first time and experienced computer users in choosing a single-board microcomputer or microcomputer system to suit their application. It is presented in four parts.

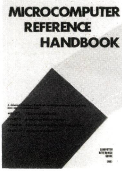

PART I. Chapters 1 to 3 include a wealth of useful information on microcomputer theory including peripheral and software capability. Succeeding Chapters provide additional microcomputer information under the following headings: ***BASIC Language Summary; Guidelines for the Selection of Microcomputers in Commercial Applications; Microcomputers and Word Processing, Big Future for Desktop/Personal Computers*** (containing comments by IDC, a leading industry information resource); ***Future Trends in Microprocessing and Microcomputing; Communications and Networking with Microcomputers; Microcomputers in Education; and Microcomputing For The Home Hobbyist.***

PART II. Covers a range of microcomputer software from independent vendors. Products discussed are broken down into the five major system types: CP/M-based; Apple Systems; Commodore Systems; Radio Shack TRS-80 Systems; and the 6800-based models. The different programs described include operating systems, high-level languages, utilities and a wide variety of application packages.

PART III. Provides a 2 to 5 page summary on more than 130 different microcomputers and microcomputer systems from over 50 suppliers. These summaries describe hardware, software, peripherals, pricing and head office location. The different microcomputer suppliers covered include, in manufacturer order:

• APF • AI Electronics Corp. • Archives • Alpha Microsystems • Altos • Apple • Atari • CADO • California Computer Systems • Commodore • Compucolor • Compucorp • Cromemco • Data General • Datapoint • Diablo Systems • Digilog • Digital Equipment • Durango • Exidy • Findex • Hewlett-Packard • IBM • IMS • Intel • Intelligent Systems • Intertec • MicroDasys Millie • Micro V Corp. • Micromation • Mitsubishi • Motorola • Panasonic • QASAR • National Semiconductor • North Star • Ohio Scientific • Onyx • Pertec • Radio Shack • Sinclair ZX80 • Smoke Signal • SORD • SWTPC • Tektronix • Texas Instruments • Vector Graphic • Wang • Zenith • Zilog ... plus others.

PART IV. Includes a summary on a selection of terminals and printers for microcomputers. Both visual display and keyboard printing terminals are discussed as well as a number of low and high-speed character printers.

If you are interested in keeping abreast of this very important segment of the market or are planning to purchase a microcomputer for home, office or factory use then this Handbook is of vital interest to you. For just $25 (or $20 with introductory offer) it can save you up to six months of your own research, time and effort. The publication is printed 10.75" x 8.2" and contains over 250 pages. This publication will be available in May.

I would like to order the **MICROCOMPUTER REFERENCE HANDBOOK**. The cost of the HANDBOOK is normally $25, plus $2 postage and handling.

Special Introductory Offer (now extended to June 30th) is $20, plus $2 postage and handling.

Name .... Company ....
Address ....
....
Zip Code .... Telephone (   ) ....

☐ Check enclosed ($22) OR you may use your credit card
☐ Master Charge Card No. ....
☐ Visa Expiration ....

Californian purchases please add 6% sales tax.
Signature
(for Credit Card) ....

Mail this coupon or a copy to:
Computer Reference Guide, 135 South Harper Avenue, Los Angeles, CA 90048. (213) 852-4886

PE 6/81

COMPUTER SOURCES

By Leslie Solomon
Senior Technical Editor

Software

The Last One. The majority of computer users need some "canned" programs to get along because most of them are not too proficient in creating and developing relatively complex programs. Of course, some can (and do) modify existing programs to add or delete certain items if the changes are not complicated. They can also create relatively simple programs in one of the high-level languages. Most shy away from creating large machine-language programs however, simply because they don't fully understand what is really happening at the bit level. In any case, we have had enough of seemingly endless debugging.

A computer, even a simple one, is a marvelous device that can be made to speak, listen, play music, perform all manner of external control tricks, and interact marvelously with the human operator. There are many programs, especially some of the more advanced word processors and statistical packages (WordStar and Visicalc for example) that appear to have some "intelligence"

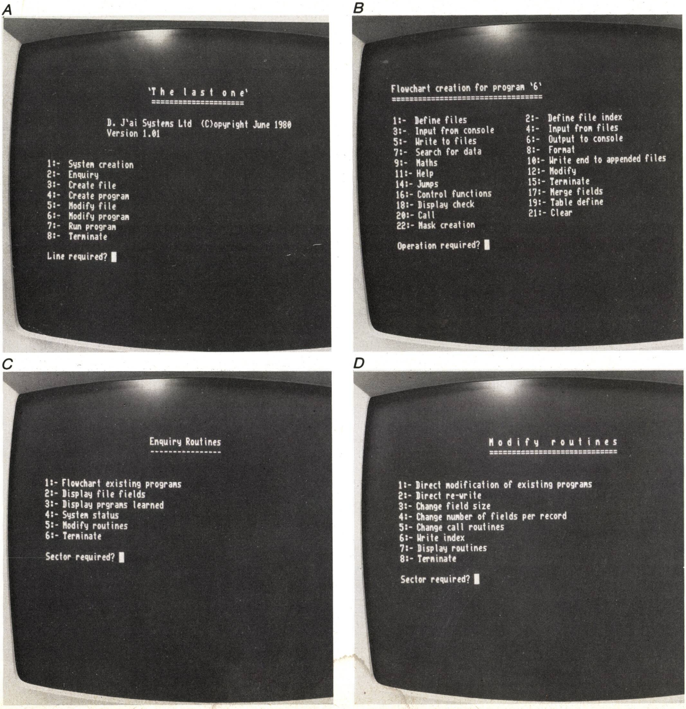

At (A) is the entry menu into The Last One; (B) creates a flow chart; (C) is enquiry mode; and (D) is modify menu. Once a file has been modified, any program calling that file is also modified.

A

```
                    'T h e   l a s t   o n e'
                    =====================

              D. J'ai Systems Ltd  (C)opyright June 1980
              Version 1.01


       1:-  System creation
       2:-  Enquiry
       3:-  Create file
       4:-  Create program
       5:-  Modify file
       6:-  Modify program
       7:-  Run program
       8:-  Terminate

       Line required? █
```

B

```
Flowchart creation for program '6'
==================================

 1:-  Define files                2:-  Define file index
 3:-  Input from console          4:-  Input from files
 5:-  Write to files              6:-  Output to console
 7:-  Search for data             8:-  Format
 9:-  Maths                      10:-  Write end to appended files
11:-  Help                       12:-  Modify
14:-  Jumps                      15:-  Terminate
16:-  Control functions          17:-  Merge fields
18:-  Display check              19:-  Table define
20:-  Call                       21:-  Clear
22:-  Mask creation

Operation required? █
```

C

```
                    Enquiry Routines
                    ----------------


      1:- Flowchart existing programs
      2:- Display file fields
      3:- Display prgrams learned
      4:- System status
      5:- Modify routines
      6:- Terminate

      Sector required? █
```

D

```
                    M o d i f y   r o u t i n e s
                    =============================


   1:- Direct modification of existing programs
   2:- Direct re-write
   3:- Change field size
   4:- Change number of fields per record
   5:- Change call routines
   6:- Write index
   7:- Display routines
   8:- Terminate

   Sector required? █
```

and the industry seems to have made some strides in "artificial intelligence." So, why can't a computer be made to create its own programs if the human operator defines just what the program is supposed to do?

This is exactly what has happened in England. Two computer experts, Scotty Bambury and David James, have come up with what they call "The Last One"—a program that interacts with the human operator via a set of menus. The operator need have no knowledge of either the computer or the high-level language being used. He need only have the capability of understanding what the menus are "looking for," and what his program should do. The program originated in connection with work in artificial intelligence.

In use, once the program of interest has been defined by answering the menu questions, the system will produce bug-free(!) code in BASIC (or any other high-level language, and even in machine code). Actual program generation takes very little time—with a couple of hundred BASIC statements requiring only five or six minutes. Since The Last One is presently written in BASIC, once it gets converted to machine code, the generation speed will increase.

The Last One generates two versions of each program, one following the precise structure laid down by the program designer and the other using optimized coding. The system then tests each program, compares the results, and uses the best one. Work is presently being done to allow the user to choose between running speed and memory efficiency.

File design is such that if any file is changed, all programs using that file are also modified and regenerated. If a program is modified, The Last One asks the necessary questions to create its new design and then generates fresh code.

The Last One was designed on an Ohio Scientific system using a hard disk, but is being modified for use with almost any other system.

Marketing decisions for The Last One have not yet been firmed up, but it is hoped that this program will soon be available in the U.S.A.

Atari Screen Print. The Screen Printer Package enables almost anything displayed by the Atari 400 or 800 to be printed on a Trendcom 200 or IDS 440G "Paper Tiger" printer. The image can be printed in gray scale, black-and-white, or reversed (white on black). It also allows LPRINT and LIST P commands. The software is a 3K auto-booting machine-language program supplied on disk or cassette. Examples are provided. $139. Address: Macrotronics, Inc., 1125 N. Golden State Blvd., Turlock, CA 95380 (Tel: 209-667-2888).

BASIC Coding Form. The Pocket BASIC Coding Form can be used to display the computer fixed memories side-by-side with space for program title, programmer's name, date, page number, special notes, and comments. The reverse of the 8½ x 11 inch form contains 30 horizontal program lines divided into 80 columns. Forms can be used with any BASIC programming. 50-sheet pads are $3.95, 100 sheets are $4.95. Address: ARCsoft Publishers, Box 132, Woodsboro, MD 21798 (Tel: 301-845-8856).

Catalog Available. The Winter/Spring Software Catalog for the Apple II, Apple II Plus, TRS-80, and TI-99/4 computers is now available. The catalog features a wide selection of professional, educational, and business software at up to 30% discount. Address: Creative Discount Software, 256 South Robertson Blvd., Suite 2156, Beverly Hills, CA 90211 (Tel: 800-824-7888; in Alaska and Hawaii 800-824-7919; California 800-852-7777. Ask for Operator 831 and catalog 47B).

Accounts Receivable System. Written for TRSDOS 1.2 on a Model II machine, AR is a complete invoicing

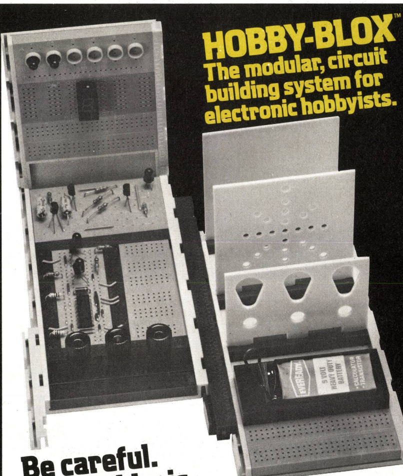

HOBBY-BLOX™
The modular, circuit building system for electronic hobbyists.

Be careful.
Your hobby is about to become an obsession.

The 14 modular units in the solderless, Hobby-Blox™ system are color-coded and cross-indexed. Projects go faster, easier.

For the beginner, there are two starter packs. One for integrated circuits, one for discrete components. Each has its own 10 project booklet.

Once you get into Hobby-Blox, look out. You're going to get hooked.

For a free catalog and the name of your nearest Hobby-Blox dealer, call Toll Free 800 321-9668. In Ohio call collect (216) 354-2101.

Patents Pending.
©AP PRODUCTS INCORPORATED 1980

A P PRODUCTS INCORPORATED
9450 Pineneedle Drive
P.O. Box 603
Mentor, Ohio 44060
(216) 354-2101
TWX: 810-425-2250

In Europe, contact A P PRODUCTS GmbH
Baeumlesweg 21 • D-7031 Weil 1 • W. Germany

Free Project-of-the-Month to Hobby-Blox purchasers!

CIRCLE NO. 5 ON FREE INFORMATION CARD

and monthly statement generating system that keeps track of current and old accounts receivable. It maintains a complete file for each customer consisting of name, address, phone number, type of account, current balance, tax rate, and other account status information. It uses an 80-column screen and requires 64K memory and dual-disk. It is interactive, menu-driven, self-instructing and integrated with the ISAM general ledger system. $129. Address: Micro Architect Inc., 96 Dothan St., Arlington, MA 02174 (Tel: 617-643-4713).

Apple APL. APL/V80 requires an Apple, Z80 Softcard, CP/M, and a 24 x 80 video card. This version uses mnemonic symbols to represent the APL characters. Features include 11 APL arithmetic functions, 11 Boolean and relationship functions, 11 selectional and structural functions, and 9 general functions. It also features canonical representation, function fix, share offer, and share retract. Copy and erase can be executed from functions. It also has disk-based workspace and copy-object libraries, supports arrays to 8 dimensions, and allows booting directly into an application program. $500. Address: Vanguard Systems Corp., 6901 Blanco, San Antonio, TX 78216 (Tel: 512-340-1978).

Small Business Software. Written for the TRS-80, Level II, 16K machine, this four-program package is for the small entrepreneur with no employees, who operates as a home-based business: (1) The 12-Column Ledger prints a ledger of income or expense with page, month, and grand totals; (2) Speed Letter allows formating letters, notes, or forms and is menu oriented; (3) 3-Across Mailing Labels handles up to 220 names and addresses with data sorted on entry by zip code, name, city, etc.; (4) Auto Dialer holds 500 names and phone numbers and requires a phone interface relay. Elapsed timer calculates call costs and redials the last number. $10 each or all four for $25. Address: Blechman Enterprises, Suite H, 7217 Bernadine Ave., Canoga Park, CA 91307 (Tel: 213-346-7024).

Atari Graphics Editor. PLOT & DRAW for the Atari computer allows the user to generate graphics in three colors plus a background. Single keystroke commands and ability to draw pictures allow the user to produce complex drawings. A crosshair coordinate system is used for precision and flexibility. $18. Address: Mosiac Electronics, Box 748, Oregon City, OR 97045.

Debugging Program. RAID is a new software debugging tool for 8080/8085 systems using CP/M. It requires 13K of space and uses no overlays. Features multiple breakpoints, with pass count and "snapshot" dumps of memory and registers, symbolic input of arguments, symbolic display and alteration of registers, and a built-in assembler/disassembler. Single-step and multiple-step tracing can be performed. There is also a mixed mode execution, so that some parts of the program can be run in real time, while others are emulated. It has eight input and display formats, memory search, and direct disk access. $250. Address: Lifeboat Associates, 1651 Third Ave., New York, NY 10028 (Tel: 212-860-0300).

Software Library. Contains a number of programs for the Pet and Atari computers. Categories include games, graphics, music, ham radio, astronomy, home use, and utility programs. For more information contact Kinetic Designs, 401 Monument Rd., #171, Jacksonville, FL 32211.

Hardware

5M Byte Disks. The 5M byte series of Winchester disk systems are available for the TRS-80 Models I and II, Apple II, Altos, Alpha Micro, Intertec Superbrain, NEC PC-8001, Ontel, and S-100 bus systems running under CP/M or OASIS. In the near future, TRS-80 Model III, PET, H-89, Atari, and HP-85 machines will be added. The system contains a drive, a Z80-based controller, an interface with firmware and software for the system in use, and a power supply for world-wide power-line standards. Unformatted capacity is 6.9M bytes (5.8M bytes formatted), seek time of 10 ms, average seek and latency times of 50 and 8.3 ms. Power consumption is 120 watts. About $3750. Address: Corvus Systems, 2029 O'Toole Ave., San Jose, CA 95131 (Tel: 408-946-7700).

New Printer. The MX-70 prints unidirectionally at 80 cps with a user-defined choice of 40 (double-width characters), or 80-column printing. It features top-of-form recognition, programmable line feed and form length, self test, and adjustable tractor feed. It uses a 5 x 7 matrix. It also has GRAFTRAX II, a high-resolution (60 dots per inch) function. This provides bit images free from jitter, wander, and walk. The replaceable print head has a life expectancy between 50 and 100 million characters. $450. Address: Epson America, Inc., 23844 Hawthorne Blvd., Torrance, CA. 90505 (Tel: 213-378-2220).

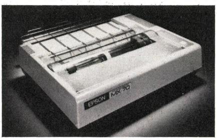

Speech Kits. The TMSK101, using the TMS5100 speech-synthesis chip, and the TMSK201 using the TMS5200 chip use linear-predictive coding (LPC). The TMSK101 provides speech synthesis based on 4-bit processors or single-chip computers and includes a ROM having 204 words. The TMSK201 kit can be used with 8- and 16-bit machines. Its EPROM contains 32 words, 2 phrases, and one tone, each individually encoded. LPC provides natural sounding speech and requires 900-1600 bits/second of speech (450-1000 bits per word). $140. Available from Texas Instruments distributers.

Apple Time. TIME II is a real-time clock/calendar for the Apple II. It provides date with year, month, day of week, and leap year. It also provides 24- or 12-hour format with AM/PM indication. Latched I/O enables programming in BASIC. An on-board battery provides 4 months of power when the system is turned off. Selectable interrupt permits foreground/background operation of two simultaneous programs so you can call up schedules, time events, or date listings. $150. Address: Applied Engineering, Box 470301, Dallas, TX 75247.

Dynamic Static RAM. The Z6132 is an NMOS chip organized as 4K x 8. Having the capability of *on-chip* refresh, it combines the convenience of static RAM with the high density and low power consumption of dynamic RAM. The power requirement is 1/16th that of 2114 types, and one Z6132 does the work of eight 2114s. The 28-pin chip operates from a single 5-volt line and has access times of 250, 300, and 350 nanoseconds. Address: Zilog, 10340 Bubb Rd., Cupertino, CA 95014 (Tel: 408-446-4666).

6502 Handbook. The 6502 Instruction Handbook is a 44-page reference containing a synopsis of each instruction for the 6502. Mnemonics and machine codes in hex format are provided. The instruction set is listed alphabetically, by assembler mnemonics, and machine code. It also includes hex-to-decimal conversion chart, chip pin-out, basic timing, and chip architecture. $4.95. Address: Scelbi Publications, 20 Hurlbut St., Elmwood, CT 06110.

Speech Board. The LPC Speech Board has a vocabulary up to 458K bits, typically 200 to 300 seconds of speech. It interfaces with the Multibus, parallel I/O, or RS232 serial I/O. It includes a 40-word vocabulary for time, calculator, frequency counter, and voltmeter applications, an 8085 processor, and a 1.5-watt audio amplifier. The user can enter his own phrases and words to form his own sentences. Words can be randomly accessed to create messages. Linear predictive coding is used. Several other synthetic speech modules are available. Address: Telesensory Speech Systems, 3408 Hillview Ave., Palo Alto, CA 94304 (Tel: 415-493-2626). ◇

POPULAR ELECTRONICS
$1600 SWEEPSTAKES

Popular Electronics
APRIL 1981
An Oscilloscope Buyer's Guide
Expanding Microcomputer Memories
Build a Rumble-Canceling Circuit
Speed Control for Synchronous Motors
PMC-80
Personal Micro Computers, Inc.

Save up to 41% on *Popular Electronics* too!

The Popular Electronics Sweepstakes is open to all our readers. No purchase is required—and you'll receive a fantastic home computer system worth $1600 if you're the lucky winner!

Here's how the Sweepstakes works: Just mail the attached card or the coupon below after filling in your name and address. Be sure to indicate whether you're also subscribing to *Popular Electronics* at the special rates shown—you can save as much as 41%.

Then, if you win, all this top-quality equipment will be yours! First, a $645 PMC-80 microcomputer, distributed by Simutek. The PMC-80 has 16,000 characters of in-computer memory, and uses the same easy Level II Basic Language that the TRS-80 uses—which means you can run the thousands of TRS-80 programs on your PMC-80. Next comes the Leedex 100 black-and-white video monitor, a $160 value. Then the superb $695 Epson MX printer, the leader in its field with its rugged construction, disposable print head and outstanding software. Plus $100 worth of connecting cables and accessories, including 25 great Simutek programs ranging from loan payment and depreciation to a series of fantastic animated games. In all, a computer system valued at a cool $1600!

You're sure to win with *Popular Electronics!*

Whether or not you win our Sweepstakes, your electronics projects are certain to be winners when you subscribe to *Popular Electronics*. It's the Number One magazine in its field—your best source for news about computers, audio and video equipment, communications and intriguing build-it-yourself projects.

Why not enjoy a year or more of *Popular Electronics* at our low introductory prices? You'll save 29% on a one-year subscription...or as much as 41% on a three-year subscription if you order at the same time you enter our Sweepstakes!

OFFICIAL RULES
NO PURCHASE REQUIRED

1. On an official entry form or a 3" x 5" piece of paper, hand-print your name, address and zip code. Enter as often as you wish, but mail each entry separately to Popular Electronics Sweepstakes, P.O. Box 2782, Boulder, Colorado 80322. Entries must be received no later than July 31, 1981, and the drawing will be held by August 24, 1981.

2. Winner will be selected in a random drawing from among all entries received, under the supervision of the publishers of Popular Electronics, whose decision is final. Only one prize will be awarded in this Sweepstakes. Winner will be notified by mail and may be required to execute affidavit of eligibility and release. Odds of winning will depend on the number of entries received. Ziff-Davis will arrange delivery of prize. Taxes are the responsibility of the winner. Any manufacturers' claims and warranties will apply, but Ziff-Davis makes no claims or warranties with regard to any prize. Prize is not transferable. No substitutions or exchanges for prizes.

3. Sweepstakes open to all U.S. residents except employees of Ziff-Davis Publishing Co., its affiliates, advertising and promotion agencies. Void wherever prohibited or restricted by law.

4. For the winner's name, send a stamped, self-addressed envelope to Popular Electronics Sweepstakes, Circulation Dept., Ziff-Davis Publishing Co., One Park Avenue, New York, N.Y. 10016.

OFFICIAL ENTRY FORM

MAIL TO: **Popular Electronics Sweepstakes**
P.O. Box 2782, Boulder, Colorado 80322

☐ **YES!** Enter my name in the Popular Electronics Sweepstakes and start my subscription to *Popular Electronics* for the term checked:

- ☐ One year only $9.97—29% off!
- ☐ Two years only $17.97—36% off!
- ☐ Three years only $24.97—41% off!

Savings based on full one-year subscription price of $14.

CHECK ONE: ☐ Payment enclosed. ☐ Bill me.

☐ **NO** I don't wish to subscribe now, but tell me if I've won the Popular Electronic Sweepstakes.

8H104

Mr.
Mrs.
Ms. ____________________
(please print full name)
Address____________________ Apt.______
City____________________ State__________ Zip__________

Offer valid only in the U.S. Please allow 30 to 60 days for delivery of first issue if you subscribe.

Popular Electronics Tests

Atari Model 800 Personal Computer

THE Atari Model 800 is a personal computer based on a 6502 microprocessor with color graphics and sound capability. It comes with a TV/GAME isolation switch that allows its use with any TV receiver. Preferably, the 800 can be connected to a high-quality color monitor, using the RGB (*not* composite) video output on the computer's rear panel.

Housed in an attractive plastic case covering an RFI-shielded enclosure, Model 800 features a full-size keyboard with 57 full-stroke and four function typewriter-like keys, four interface connectors for using joystick or paddle controls, an eight-bit parallel interface port, TV channel 2/3 switch, a video monitor connector, 16K bytes of RAM (that can be expanded to 48K), 10K bytes of system ROM (that can be expanded by cartridges), and an Atari BASIC interpreter cartridge. The highest graphics resolution is 320 x 192, and three text modes are provided.

Base price is $1080. Optional items include: Model CX8101 Master Diskette with disk operating system and file manager ($25); Models CX852 and CX853 8K and 16K byte RAM modules ($124.95 and $199.95, respectively); Model 410 cassette program recorder ($89.95); Model 810 5.25-inch single-sided, single-density floppy-disk drive and controller ($599.95); Model 815 double-density, dual-disk drive ($1,499.95); Models 820 and 825 40- and 80-column dot-matrix printers ($449.95 and $999.95, respectively); Model 830 modem ($199.95); Model 850 interface module ($219.95); Model CX40-04 joystick controller package ($19.95); and the CX-70 Light Pen ($74.95). Atari also has a long list of additional useful peripherals, ranging from cables to printer accessories. Software available from Atari includes games, educational courses, and financial programs on cassette tapes ($14.95 to $29.95) and in plug-in ROM cartridges ($24.95 to $39.95). Besides BASIC (CXL4002) included with the machine, there is an assembly editor (CXL4003 at $59.95). Soon to be announced are cartridges for PILOT (CX405 at an as yet unknown price) and PASCAL.

General Description. The Atari 800 doesn't have a user-oriented bus structure. Instead, it uses an r-f system that minimizes radio-frequency (RFI) and electromechanical interference (EMI) with an electrically tight cartridge-slot system for RAM and ROM cartridges. A similar system is used for the BASIC interpreter and game cartridges that slip into one or both of the "game" slots in the console. When the cartridge door is opened, the computer automatically switches off.

The 6502 microprocessor operates with a 0.56-μs cycle at 1.8 MHz. Since the computer is designed to operate with home TV receivers on channel 2 (54 to 60 MHz) or 3 (60 to 66 MHz), the on-screen display is limited to 24 lines of 40 characters because of the available bandwidth in most sets. The TV/GAME isolation switch mounts directly on the TV receiver and connects to the console via a 15-ft cable terminated with a phono plug. Power for the console is supplied by an ac power adapter.

Before turning on the system, you must set the switch on the console and the receiver's tuner to either channel 2 or channel 3, depending on the channel not in use in your viewing area. About 6 seconds after power-up, "ATARI COMPUTER MEMO PAD" will be displayed on the screen in white on a blue background.

Atari's keyboard is designed to generate upper- and lower-case alphabetics, numerals, and graphics and has screen-editing functions. Under software control, each key can also be redefined for special functions. You can move the cursor to any desired location on the screen with the up-, down-, left-, and right-arrow keys. Automatic repeat is possible simply by holding down any desired key for about 5 seconds. The repeat function remains enabled for as long as the key is held down thereafter.

A special key, identified with the Atari symbol, allows entry to and escape from the inverse-video mode. Automatic wraparound immediately drops the cursor to the beginning of the next line once the 38th character is typed in any given line, obviating the need to press RETURN and LINE FEED at the end of each line.

Peripherals can be added to the 800 in two ways. If you have the cassette recorder but no disk drive, you can use the port located on the side of the console. For larger system configurations, however, you'll need the Model 850 interface module, which provides four RS232C serial ports (including one with 20-mA capability), and an 8-bit parallel output port. Serial ports have baud rates to 9600, and Baudot rates to 100 wpm.

Software for the 800 is broken down into two distinct groups—system and applications. The latter is further divided into games, educational, and business programs. Many of the games are in ROM cartridges that plug directly into the console and come up instantly. Other games are on cassette tapes that usually load in about a minute. The game programs let you choose speed, number of players, and how you wish to play, all by pushing one of the function keys.

To use many of the educational cassettes, an Education System Master ROM cartridge ($24.95) is required. This "control" cartridge allows you to carry on a dialogue with the computer. Other educational cassettes are used with BASIC.

The Atari Telelink-1 program is used with the Model 830 modem and can support a printer when connected to the console via the interface module. This ROM-cartridge program slips into the left slot in the console. The software in it is fairly flexible and takes into account the select and option keys that permit setting up a buffer and dumping to the printer. Moreover, it can be configured to allow for automatic dumping to the printer, signalling the host computer to shut off, or sending an X OFF or X ON to control transmission. Since Telelink doesn't support use of a disk drive, you can't save transmit files.

Atari's disk operating system (DOS) is designed to extend the capabilities of the BASIC cartridge. To boot up the system, you turn on the disk drive, insert the diskette, and then turn on the console. Boot-up is then automatic.

The DOS and file manager let you run programs mounted in cartridge

LISTING 1
GRAPHICS TEST PROGRAM FOR DRAWING A TRIANGLE

```
4 GOTO 100
100 CLR
110 GRAPHICS 0
120 PRINT "ENTER NUMBER OF SIDES";
130 INPUT A
140 PRINT "ENTER NUMBER OF FRAMES ";
150 INPUT B
160 DIM C(A,2),D(A,2)
170 REM GENERATE INITIAL COORDINATE ARAY
180 FOR I=1 TO A
190 C(I,1)=RND(-1)*130
200 C(I,2)=RND(-1)*100
210 NEXT I
220 REM GENERATE INCREMENT ARRAY
230 FOR I=1 TO A
240 D(I,1)=(RND(-1)*130-C(I,1))/B
250 D(I,2)=(RND(-1)*100-C(I,2))/B
260 NEXT I
270 GRAPHICS 0
275 GRAPHICS 7
280 FOR J=1 TO B
290 POSITION C(A,1),C(A,2)
300 REM DRAW POLYGON
310 FOR I=1 TO A
320 DRAWTO C(I,1),C(I,2)
330 NEXT I
340 REM ADD INCREMENT ARRAY TO COORDINATE ARRAY
350 C=C+D
360 NEXT J
370 END
```

slots, direct files to either the printer or the screen, and create backup and data diskettes. This is a user-oriented, menu-driven operating system that requires no special setups. Both sequential and random files are supported, and such standard commands as OPEN, CLOSE, READ, and INPUT are employed for ease of developing programs in BASIC. Operating under the Atari DOS, each disk can store up to 73K bytes of data on a system diskette or 84K bytes on a data diskette.

The BASIC interpreter supplied by Atari is designed to support the color graphics and sound functions built into the 800. While it may appear at first glance to be minimal in nature, this BASIC includes such important primitive graphics commands as DRAWTO, POSITION, and PLOT, which are usually found only in more extensive BASICs. The string operators MID$, LEFT$, and RIGHT$ are missing, but string splitting information is provided.

This BASIC is a graphics- and input-oriented language. Consequently, it contains such operators as SOUND, SETCOLOR, and functions that integrate the joystick and paddle controllers for movement on-screen and depression of a firing button.

This computer has facilities for generating 16 colors, each with 8 intensities, that can be called from BASIC using the SETCOLOR command. There are four independent sound synthesizers, in addition to the TV audio, each covering four octaves with variable volume and tone. An internal speaker is provided. The SOUND command permits setting a note on the full musical scale, as well as pitch, volume, and amount of distortion for creating sound effects.

There are nine different graphics modes possible in the 800. The first mode, GRAPHICS 0 permits a 40 x 24 display with two colors without split-screen features. When GRAPHICS 0 is invoked, it clears the screen and places the entire system in its default settings. This mode requires 993 bytes of RAM.

GRAPHICS 1 and 2 are also character/text display modes. In GRAPHICS 1, characters appear on-screen twice normal width but normal height, while in GRAPHICS 2, characters appear double width and double height. Therefore, the displays generated can be either 20 x 24 or 20 x 12, respectively. These two modes permit the use of five colors and provide a split-screen format for mixed graphics and text. Graphics 1 and Graphics 2 require 513 and 261 bytes of RAM respectively.

GRAPHICS 3 through 8 set up additional graphics and screen formats. High-resolution mode GRAPHICS 8, for example, permits creation of a full-screen display consisting of 320 x 192 (61,440) dots. It requires 7.9K bytes of RAM. Graphics 3,4,5,6, and 7 require 273, 537, 1017, 2025, and 3945 bytes of RAM, respectively.

Everything you do in the graphics modes is I/O related. Therefore, all commands result in an output to a text or graphics window or to the basic text screen. Once you've mastered the handling of the graphics functions, you'll find it relatively easy to develop your own on-screen displays in color, including three-dimensional effects.

Evaluation. We tested a fully configured system, including the Model 800 console, interface module, both printer models, two joystick controllers, acoustic modem, program cassette recorder, 5.25-inch floppy-disk drive, and two 16K- and one 8K-byte RAM cartridges. An additional 10K-byte ROM cartridge was used for system control.

LISTING 2
GRAPHICS
TEST PROGRAM
FOR A POLYGON

```
10 GRAPHICS 0
20 GRAPHICS 7
30 PLOT 80,10
40 DRAWTO 40,40
50 DRAWTO 120,40
60 DRAWTO 80,10
70 END
```

Setting up the system is a simple, straightforward procedure. We encountered a minor problem with the TV/GAME switch, which is supposed to mount on the back of the TV set with a self-stick pad. The weight of the switch box and cable appear to be too much for the adhesive. As a result, the switch box can work loose and pull the interconnecting 300-ohm twinlead from the TV set's antenna terminals. Instead of mounting the box on the rear of the set, we recommend that you place it on top and make interconnection by way of a quick clip.

We observed little or no TV interference (TVI) when the console was operating. All in all, this is a very "quiet" console/cable system. The same can't be said about the Model 825 80-column printer, however. With the printer powered and located within 10 feet of the TV set, we observed RFI noise in the display.

While we very much like the "feel" and flexibility of the console's keyboard, we don't care much for the location of CAPS LOCK (just below the RETURN key). This makes it too easy to accidentally switch between upper- and lower-case.

We also have reservations about the use of separate ac adapters for the console and each peripheral instead of a single hefty power supply and bus to feed the peripherals. A fully configured system ties up a multitude of ac outlets. Worse still, you end up with a tangle of trailing wires that can be tripped over or accidentally dislodged.

The floppy-disk drive sample supplied to us proved prone to head misalignment and medium warping, and the controller wasn't exactly bug-free either. Testing the drive with multiple reads and writes produced an error on every fourth entry. When we checked several other samples, we found similar problems, albeit on a random basis. Atari is aware of the difficulty, and the necessary redesign is underway. System hardware operated smoothly in all other respects.

Software supplied by Atari is generally excellent, especially in the area of educational software. While Atari's games software creditably exercises the color-graphics capabilities of the system, two games that give a really rigorous demonstration are "Checker King" and "Microchess" from Personal Software on cassette tape for $19.95 each. The programs are written in machine language to take full advantage of the 6502's speed, displaying a lifelike board and extremely well-defined playing pieces. When a move is made, you actually see motion on the screen.

Since the BASIC interpreter in the Model 800 is unique to this computer, we developed two benchmarks to demonstrate the capabilities of the machine. Listing 1 draws a triangle. Line 10 clears the screen, line 20 sets up a 160-column by 80-row display, line 30 establishes the apex of the triangle, and lines 40 through 60 draw the triangle's sides. The program runs in less than a second and draws fairly smooth lines.

Listing 2 demonstrates the ability of the 800 to draw a multisided polygon by setting up an array using randomly defined points. Although this program readily creates a single-view polygon, expanded views, defined by the frame input, weren't possible. In operation, a 30-sided figure took 11 seconds to format and less than a second to draw. The increment array coordinates remained set at zero, allowing only one view, which demonstrates the inadequacy of the random (RND) statement to correctly generate random numbers that are greater than 1.

Comment. Generally speaking, the Atari Model 800 is a top-notch computer that far surpasses its immediate competition. In addition to its fine assortment of peripherals and software, it incorporates various extra features, such as the music synthesizers and built-in speaker. Its capabilities with respect to graphics seem especially comprehensive. Despite our few minor reservations, the overall system deserves high marks.—*Carl Warren*

CIRCLE NO. 103 ON FREE INFORMATION CARD

YOU HAVE 10 DAYS TO DISCOVER THE COMPUTER AGE.

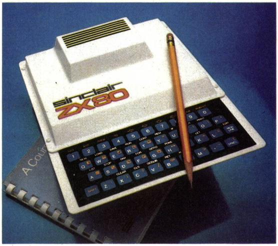

EVERYTHING YOU NEED. For just $199.95, you get everything you need to operate your ZX80. You just hook it up to your TV (either black & white or color). Then to store your programs, you can use any ordinary cassette tape recorder. We'll also send you a 128-page guide to computing that's yours to keep as a free gift.

$199⁹⁵

If you've never used a computer, you're missing something.

Programming your own computer is more fun than playing backgammon. More challenging than crossword puzzles.

And more practical than about anything else you could do.

Because the fact is, you're living in the age of computers. And now you can discover what it's all about. For 10 days, at no risk and no obligation, you can have your very own Sinclair ZX80 computer. To play with, experiment with, learn with.

ANYONE CAN USE IT.

You'll discover the ZX80 is incredibly easy to use for anyone 10 years or older. You don't have to know anything about computers when you start out. We'll send you a complete 128-page guide that takes you step-by-step into the world of computing. In one day, you'll be writing your own programs!

The ZX80 will absorb you for hours as you find new ways to use it. You can create games. Home budgets. Math lessons for your children. Almost anything, in fact.

THE ZX80 IS YOURS FOR 10 DAYS. THE COMPUTER GUIDE IS YOURS FOREVER.

For your 10-day home trial, just call our toll-free number and order with your Master Charge or VISA. Or send the coupon along with a check or money order for the remarkably low price of $199.95, plus shipping. (Other personal computers cost two or three times as much!)

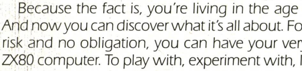

For an extra $49.95, you can also have the Sinclair Computer Learning Lab – a set of 100 experiments and lessons on cassette tapes that make the ZX80 itself your teacher.

And we'll send you the Sinclair ZX80 personal computer. It's yours for 10 days. If you decide you don't want to keep it, then send it back. We'll give you a full refund. Either way, the 128-page guide to computing – a $5.95 value – is yours to keep as a free gift.

But we have to be honest with you. After you've discovered the fun of owning a ZX80 computer, we don't think you'll send it back.

10-DAY MONEY-BACK HOME TRIAL CALL TOLL FREE 800-543-3000.

Ask for operator #508. In Ohio call 800-582-1364. Phones open 24 hours a day, 7 days a week.

Mail to: Sinclair Research Ltd.
One Sinclair Plaza, Nashua, N.H. 03061

Check one:

☐ ZX80 Personal Computer	$199.95
Shipping	$ 4.00
Total	$203.95*

☐ ZX80 Personal Computer	$199.95
Computer Learning Lab	$ 49.95
Shipping	$ 4.00
Total	$253.90*

If I'm not fully satisfied with my purchase I can return it in 10 days for a full refund. The 128-page guide is mine to keep.

Name____________________

Address____________________

City, State, Zip____________________

*U.S. dollars.

O6PE

sinclair

SINCLAIR RESEARCH LTD., ONE SINCLAIR PLAZA, NASHUA, N.H. 03061

A fascinating new range of micro electronic Hobby Kits – designed to bring the silicon chip into play!
Using all the carefully selected electronic components with our easy to follow – step by step instructions, each kit builds into a different and absorbing game that fits into the original case.

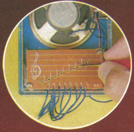

Electronic Organ EK–2 $11.89*
Maestro of the keyboard – with this kit you really do make the music. A full scale to compose on.

Quick Reaction EK–1 $9.90*
It's the fastest draw in the West –
Move at the speed of light!
Cheats are shown up!

Digital Roulette EK–3 $14.90*
Monssieur et Madame –
place your bets –
your numbers up.

Morse Code EK–5 $6.51*
Got the message?
Build this kit and you can send them!
Full morse alphabet enclosed.

Electronic Dice EK–4 $13.80*
Flashing Dice – a game of nerves
Throw a switch to win!

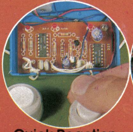

Quick Reaction

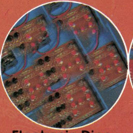

Electronic Dice

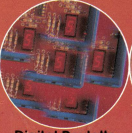

Digital Roulette

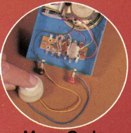

Morse Code

OK Hobby Products
3455 Conner St., Bronx, N.Y. 10475 U.S.A. Tel. (212) 994-6600 Telex 125091
*Minimum billings $25.00, add shipping charge $2.00 New York State residents add applicable tax

CIRCLE NO. 42 ON FREE INFORMATION CARD

Popular Electronics
June 1981

A MULTIBAND SHORTWAVE ANTENNA FOR SWLs

Transmission-line traps of novel construction allow this antenna to resonate on the 49-, 31-, 25-, 19-, 16-, 13-, and 11-meter shortwave bands

BY ROBERT H. JOHNS

TODAY'S shortwave receivers are so sensitive that simple random-length wire antennas are all that's needed for casual listening. However, serious DXing—picking up signals from distant, low-power stations, for example—calls for a resonant antenna. The classic method of resonating an antenna is cutting it to the appropriate length, but that implies the use of several antennas for multiband reception. A much more convenient approach is possible. The Multiband Shortwave Antenna employs *traps* that automatically adjust its effective length to resonate with the received signal. It can be constructed from

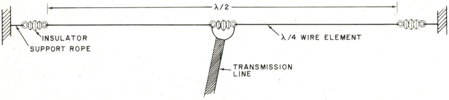

Fig. 1. The basic half-wave dipole antenna.

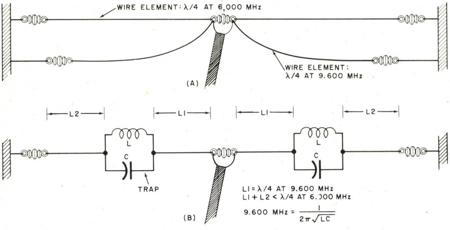
WIRE ELEMENT: λ/4 AT 6.000 MHz
WIRE ELEMENT: λ/4 AT 9.600 MHz
(A)
L2
L1
L1
L2
L
C
L
C
TRAP
L1 = λ/4 AT 9.600 MHz
L1 + L2 < λ/4 AT 6.000 MHz
9.600 MHz = 1/(2π√LC)
(B)

Fig. 2. (A) Two or more half-wave dipoles can be connected in parallel to a single transmission line for dual- or multi-band coverage. (B) A dipole antenna with a single pair of traps can resonate on two different bands.

PARTS LIST

Hard-drawn copper antenna wire; 7/8-inch diameter plastic tubing or PVC pipe; ceramic end insulators; 300-ohm twinlead, ceramic center insulator and silicone weatherproofing compound or 50- or 75-ohm coaxial cable and combination center insulator/4:1 balun transformer (see text); nylon rope; suitable supporting structures; two 35-foot spools of Radio Shack two-conductor Rainbow Wire (Catalog No. 278-755) or equivalent; solder, suitable hardware, in-line lightning arrestor, etc.

Note: A trap antenna for the 11-, 13-, 16-, 19-, 25-, 31-, and 49-meter bands with 50 feet of 72-ohm twinlead transmission line is available for $29.50 from Scientific Instruments, 3379 Papermill Rd., Huntingdon Valley, PA 19006.

readily available, inexpensive materials and can perform well on the major international broadcast bands.

About the Antenna. The basic antenna from which the multiband trap design is derived is the half-wave dipole. As shown in Fig. 1, the dipole consists of two elements and has an effective length of one-half wavelength at the frequency of resonance. Effective length is not necessarily equal to the actual physical length. An antenna can be made to exhibit an effective length greater than its physical length by the introduction of inductive reactance. Similarly, an antenna's effective length can be made less than its physical length by the introduction of capacitive reactance.

An antenna that resonates at 6.000 MHz in the 49-meter international shortwave broadcast band is 77 feet long, and one that resonates at 9.600 MHz in the 31-meter band is 48 feet long. The classic way to construct an antenna that resonates at these two frequencies involves connecting two dipoles, each cut for one of the frequencies of interest, to a common transmission line that feeds signals to the receiver (see Fig. 2A). Each dipole is active at and near its resonant frequency. Its effect on the performance of the other, whose resonant frequency is far removed, is minimal.

The trap approach to the problem of providing a resonant antenna at these two different frequencies is shown in Fig. 2B. It comprises a transmission line, four lengths of wire, and two traps or parallel LC networks that resonate at 9.600 MHz. At resonance, the impedance of the traps is very high and purely resistive. Above resonance, the trap impedance is lower and capacitive. Similarly, below the resonant frequency, the trap impedance is lower and inductive.

The inner wire sections of the antenna comprise a half-wavelength at 9.600 MHz. When the antenna is excited by r-f energy at that frequency, the high resistance of the traps (practically open circuits) decouples the outer wire sections from the inner sections. The antenna thus acts as a half-wave dipole cut for resonance at 9.600 MHz.

At the second, lower frequency of interest (6.000 MHz), the traps are not resonant. Rather, they behave like inductive reactances. When the antenna is excited by a 6.000-MHz r-f signal, the outer wire sections of the antenna are effectively connected to the inner sections through these inductive reactances. The total physical length of the antenna is shorter than would normally be required for resonance at 6.000 MHz. However, the antenna's effective or electrical length is a half-wavelength. The reason for this is that the inductive reactance of the traps supplies the needed electrical length. The traps function as loading coils at this lower frequency and the antenna resonates. This physical shortening of the antenna can be of particular advantage where space is limited.

There is no reason why more than one set of traps cannot be installed in an antenna for operation on more than two bands. That's exactly what's done in the Multiband Shortwave Antenna shown in Fig. 3. Each leg of the antenna contains six traps, allowing the antenna to exhibit resonance on the 49-, 31-, 25-, 19-, 16-, 13- and 11-meter bands. Although it resonates only on those bands, it will offer good performance in other

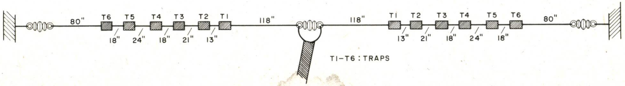

Fig. 3. The Multiband Shortwave Antenna employs six pairs of traps.

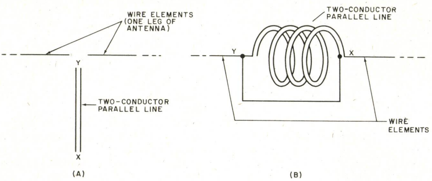
WIRE ELEMENTS (ONE LEG OF ANTENNA)
Y
TWO-CONDUCTOR PARALLEL LINE
X
(A)
TWO-CONDUCTOR PARALLEL LINE
Y
X
WIRE ELEMENTS
(B)

Fig. 4. How a two-conductor parallel transmission line (A) can be made into a trap by coiling it and using its distributed capacitance (B).

portions of the hf spectrum. The traps also shorten the antenna considerably compared to a full-size dipole cut for the 49-meter band.

Construction. The traps used in the Multiband Shortwave Antenna are assembled from inexpensive, lightweight, and readily available materials. Two-conductor parallel transmission line—actually, Radio Shack two-conductor Rainbow Wire, Catalog No. 278-755—is employed. It has an interconductor capacitance of approximately 15 pF per foot. Refer to Figs. 4, 5, and 6 for trap details.

To simplify construction, one wire of the pair is employed as the trap's inductor, and the distributed capacitance between it and the other conductor forms the trap's capacitor. A suitable length of two-conductor line with ends *X* and *Y*, as shown in Fig. 4A, is selected. The line is wound into a helix and its conductors connected to two of the wire elements of one leg of the antenna as in Fig. 4B.

One conductor has its *X* and *Y* ends connected to each of the two wire elements. The *Y* end of the other conductor is left floating; the *X* end is connected back to the *Y* end of the other. The result is an LC parallel network whose inductance and capacitance are determined by the pitch of the line's helix, the number of turns comprising the helix, and the length of the line. For mechanical support, the line is wound on an electrically inert, plastic cylindrical form.

The prototype antenna was made using lengths of ⅞-inch outer-diameter polypropylene tubing. This tough, light material was salvaged from a hula hoop that had steel balls inside the tubing. Some other electrically inert material such as PVC pipe can be used as the trap forms, but the coil-winding data in the box, "Details of Trap Construction," is valid only for cylindrical forms with outside diameters of ⅞ inch.

DETAILS OF TRAP CONSTRUCTION

Trap Number	Band (meters)	Resonant Frequency (MHz)	Number of Turns	Length of Trap Form (inches)
T6	31	9.6	18	2.75
T5	25	11.7	15	2.50
T4	19	15.3	11.5	2.00
T3	16	17.7	9.5	1.75
T2	13	21.8	8.5	1.50
T1	11	25.8	7.5	1.50

Begin construction by cutting 12 suitable lengths of tubing (two of each length listed in the box for traps *T1* through *T6*). Drill four holes approximately ½ inch from the ends of each length of tubing, using Fig. 5 as a guide. Then take one of the 2¾-inch forms and slip one end of two suitable lengths of antenna wire through two of the holes at each end of the form. The form will support trap *T6* of the left leg of the antenna (see Fig. 3) and the two wire elements will be the "80-inch" and the outer "18-inch" components of that leg.

Note that the wire lengths given in Fig. 3 are those between end insulators and traps, between traps, and between traps and the center insulator. Several extra inches of wire will be needed at each end to form loops and wraps, so make allowances before cutting. The wire can be insulated or bare, stranded or solid, but it should be hard-drawn copper. Soft-drawn copper has a tendency to stretch under load. An antenna made from it will deform and sag, thus detuning itself.

The other end of the "80-inch" wire should be fed through one end of a ceramic antenna end insulator (*not* an "egg" type guy-wire insulator) and wrapped back upon itself for mechanical support. For additional strength, the end of the antenna wire should be soldered where it is wrapped. Feed the other end of the "80-inch" wire through two of the holes at the left end of the 2¾-inch form and wrap it back upon itself, adjusting its length so that the distance between the end of the ceramic insulator and the left end of the trap form is exactly 80 inches. This wrap should not be soldered yet—it will be soldered later, when the assembly of trap *T6* is completed.

Next, slip one end of the "18-inch" wire through two of the holes at the right end of the trap form and wrap it back upon itself. Then separate the conductors at one end of a length of Radio Shack Rainbow Wire for several inches and cut the white wire short by five inches. Remove ¾ inch of insulation from each of the wires. Slip the shortened end of the white wire through one of the two remaining holes on the right side of the trap form and wrap it around the antenna wire. Then slip the end of the black wire through the remaining hole and pass it through the interior of the trap form so that it exits at the left

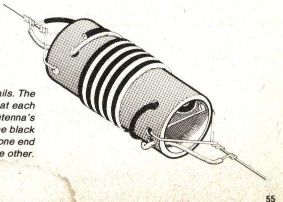

Fig. 5. Trap wiring details. The white wire is connected at each end to one of the antenna's wire elements. The black wire is left floating at one end and cross-connected at the other.

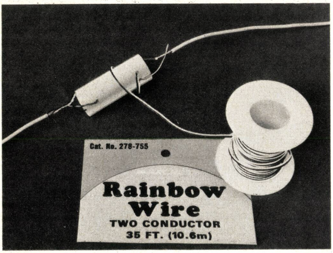

Fig. 6. Two of the antenna's wire elements have been connected to the plastic form and the Rainbow Wire attached.

side. Wrap the exposed conductor of the black wire around the end of the antenna wire.

Next, closely wind 18 turns of the Rainbow Wire around the form from right to left. Cut the wire after the 18th turn, leaving several inches for connection. The black wire should be separated from the white and cut at the completion of the 18th turn. Strip the insulation from the end of the white wire and wrap it over the antenna wire and the black wire that runs from the other end of the trap form. Solder the wires at ends of the form, but do not apply too much heat or the plastic tubing will melt. Trap *T6* of the left leg is now complete, and should resemble the trap that is shown in Fig. 7.

Following the same procedure, assemble the remaining traps and wire elements of the left leg, working in toward the center point of the antenna. The lengths of the trap forms and the number of turns comprising each of the remaining traps are specified in the box. Inter-trap distances that are related to the lengths of the remaining wire elements of the left leg appear in Fig. 3.

When assembly of the left leg of the antenna has been completed, the right leg can be constructed. Follow the same procedure. As before, assembly should begin at the outer extremity and finish with the 118-inch inner section.

If you have access to a grid-dip meter, you can check the resonant frequencies of the traps. They should be close to those listed in the box. If a trap's frequency of resonance is incorrect, it can be adjusted by spacing the turns out somewhat (to raise the frequency) or by squeezing them closer together (to lower the frequency). Larger changes should not be necessary, but can be accomplished by adding or removing turns. When the desired resonant frequencies have been obtained, the trap windings can be secured in place with coil dope or epoxy cement.

When both legs of the antenna have been assembled, they should be connected to a transmission line and a center insulator. To prevent deterioration of the transmission line, a weatherproof center insulator should be used. Alternatively, a ceramic end insulator can be employed, and silicone weatherproofing compound applied after the connections between the inner wire elements of the antenna and the transmission-line conductors have been soldered. Similarly, weatherproofing of the traps is recommended to prevent moisture buildup from detuning the traps. This can be accomplished by enclosing each trap in a cylindrical Plexiglas or PVC form.

Two factors influence the choice of transmission line: the impedance of the antenna and its electrically balanced nature. A dipole fed at its center and mounted in free space has an impedance of 72 ohms, but a dipole mounted close to the ground in terms of wavelength will have a different impedance. The impedance plot of the prototype Multiband Shortwave Antenna, which was mounted approximately 20 feet above ground, appears in Fig. 8. It is readily apparent that the impedance of the antenna as measured by the author varies considerably across the hf region of the radio spectrum. At resonance in the 49- and 11-meter bands, the feedpoint impedance is approximately 70 ohms, but it is higher in the other shortwave broadcast bands for which it is designed, even at resonance.

The prototype was fed with 300-ohm twinlead for three reasons. First, its impedance is a good compromise, considering the wide variation in the feedpoint impedance of the antenna. Second, twinlead is a balanced line, making it appropriate for use with the dipole, an electrically balanced antenna, and for use with shortwave receivers that have balanced-input antenna terminals. Finally, twinlead is relatively inexpensive and easy to work with.

If you decide to use 300-ohm twinlead, select a high-quality line. It should be foam-filled to keep signal losses low and to minimize the deleterious effects of dirt and moisture that build up on the line's outer jacket. The best balanced line to use is shielded twinlead. It is the most expensive and is somewhat more difficult to work with than thinner, flatter varieties. However, shielded twinlead has a considerably greater useful lifetime (ordinary twinlead deteriorates rather rapidly outdoors) and its impedance is not disturbed by nearby metallic objects.

Coaxial cable can also be used as the lead-in for the Multiband Shortwave Antenna. A 75-ohm coaxial line such as RG-59/U weathers well and has relatively low losses. The fact that it is shielded means that it can be passed near metallic objects or even buried underground without adverse electrical effects. If 75-ohm coax is to be used, it should be teamed up with a 75-ohm-to-300-ohm balun transformer. The balun will step up the impedance of the line at the antenna's feedpoint and make for a better match between the unbalanced transmission line and the balanced dipole antenna. As a bonus, most baluns

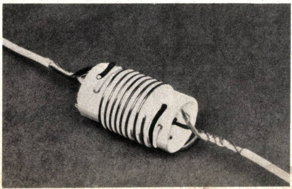

Fig. 7. A completed trap ready to be soldered. Note that the Rainbow Wire has been closely wound around the form.

Licenced by Sinclair Research Ltd.

A Microcomputer for everyone at a Micro Price

The MicroAce - a new generation of miniature computers

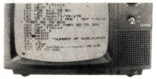

A COMPLETE COMPUTER for $149.00 for 1K Kit

Post and Packing FREE

(Add 6% Tax for Shipments inside California)

The unique and valuable components of the MicroAce

The MicroAce is not just another personal computer. Quite apart from its exceptionally low price, the MicroAce has two uniquely advanced components: the powerful BASIC interpreter, and the simple teach yourself BASIC manual.

The unique versatile BASIC interpreter offers remarkable programming advantages:

- **Unique 'one-touch' key word entry: the MicroAce eliminates a great deal of tiresome typing. Key words (RUN, PRINT, LIST, etc.) have their own single-key entry.**
- Unique syntax check. Only lines with correct syntax are accepted into programs. A cursor identifies errors immediately. This prevents entry of long and complicated programs with faults only discovered when you try to run them.
- Excellent string-handling capability — takes up to 26 string variables of any length. All strings can undergo all relational tests (e.g. comparison). The MicroAce also has string input — to request a line of text when necessary. Strings do not need to be dimensioned.
- Up to 26 single dimension arrays.
- FOR/NEXT loops nested up 26.
- Variable names of any length.
- BASIC language also handles full Boolean arithmetic, conditional expressions, etc.
- Exceptionally powerful edit facilities, allows modification of existing program lines.
- Randomise function, useful for games and secret codes, as well as more serious applications
- Timer under program control.
- PEEK and POKE enable entry of machine code instructions, USR causes jump to a user's machine language sub-routine.
- High-resolution graphics with 22 standard graphic symbols.
- All characters printable in reverse under program control.
- Lines of unlimited length.

'Excellent value' indeed!

For just $149.00 (excluding handling charge) you get everything you need to build a personal computer at home... PCB, with IC sockets for all ICs; case; leads for direct connection to a cassette recorder and television (black and white or color); everything!

Yet the MicroAce really is a complete, powerful, full-facility computer, matching or surpassing other personal computers at several times the price.

The MicroAce is programmed in BASIC, and you can use it to do quite literally anything, from playing chess to managing a business.

The MicroAce is pleasantly straightforward to assemble, using a fine-tipped soldering iron. It immediately proves what a good job you've done: connect it to your TV ... link it to the mains adaptor ... and you're ready to go.

Fewer chips, compact design, volume production-more power per Dollar!

The MicroAce owes its remarkable low price to its remarkable design: the whole system is packed on to fewer, newer, more powerful and advanced LSI chips. A single SUPER ROM, for instance, contains the BASIC interpreter, the character set, operating system, and monitor. And the MicroAce 1K byte RAM (expandable to 2K on board) is roughly equivalent to 4K bytes in a conventional computer — typically storing 100 lines of BASIC. (Key words occupy only a single byte.)

The display shows 32 characters by 24 lines.

And Benchmark tests show that the MicroAce is faster than all other personal computers.

No other personal computer offers this unique combination of high capability and low price.

The MicroAce teach-yourself BASIC manual.

If the features of the BASIC interpreter mean little to you-don't worry. They're all explained in the specially-written book *free* with every kit! The book makes learning easy, exciting and enjoyable, and represents a complete course in BASIC programming-from first principles to complex programs. (Available separately-purchase price refunded if you buy a MicroAce later.)

A hardware manual is also included with every kit.

The MicroAce Kit: $149.00 with IK COMPLETE $169.00 with 2K

Demand for the MicroAce is very high: use the coupon to order today for the earliest possible delivery. All orders will be despatched in strict rotation. If you are unsuccessful in constructing your kit, we will repair it for a fee of $20.00, post and packing FREE. Of course, you may return your MicroAce as received within 14 days for a full refund. We want you to be satisfied beyond all doubt — and we have no doubt that you will be.

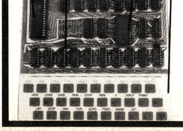
Z80 A microprocessor chip, widely recognised as the best ever made.
Sockets for TV, cassette recorder, power supply.
Expansion Connector
UHF TV modulator
SUPER ROM.
Clock.
RAM chips
Rugged, flush, Keyboard

Your MicroAce kit contains...

- Printed circuit board, with IC sockets for all ICs.
- Complete components set, including all ICs-all manufactured by selected world-leading suppliers.
- New rugged keyboard, touch-sensitive, wipe-clean.
- Ready-moulded case.
- Leads and plugs for connection to domestic TV and cassette recorder. (Programs can be SAVEd and LOADed on to a portable cassette recorder.)
- Mains adaptor of 600 mA at 9VDC nominal unregulated.
- FREE course in BASIC programming and user manual.

JOIN THE REVOLUTION - DON'T GET LEFT BEHIND - ORDER YOUR MICRO ACE NOW!!

Send Check, Money Order or quote your Credit Card No. to:
MicroAce 1348 East Edinger, Santa Ana, California, Zip Code 92705.
or phone (714) 547 2526 quoting your Credit Card Number.

Quantity	Description	Unit Price	TOTAL
	MicroAce Kit 1K	$149.00	
	MicroAce Kit 2K	$169.00	
	Manual	$10.00	
	1K Upgrade Kit	$29.00	
Shipments inside California add 6% TAX		TOTAL	

☐ Amex.
☐ Diners
☐ Check
☐ Money Order
☐ Master Charge
☐ Visa

Card No.________________

Exp. Date________________

Name________________

Address________________

City________________ State________________ Zip________________

CIRCLE NO. 35 ON FREE INFORMATION CARD

designed for amateur-radio use double as weatherproof center insulators. If you decide to employ coaxial line and a balun, make sure that the balun is of the 4:1, as opposed to the 1:1, variety. Many contemporary shortwave communications receivers have unbalanced, low-impedance antenna inputs, so in most cases a second balun transformer won't be needed at the receiver end of the transmission line.

Installing the Antenna. There are two basic ways that the Multiband Shortwave Antenna can be set up at the receiving site—either as a flattop dipole or as an inverted vee (see Fig. 9). The flattop dipole has a higher feedpoint impedance than an inverted vee and is somewhat directional—it responds best to signals striking it at right angles. It requires two high supports (Fig. 9A), one at each end of the antenna. In most cases, the dipole does not require a center support.

The inverted vee (Fig. 9B) is more omnidirectional and has the advantage of requiring only one high support at the center. This also lessens the stress on the antenna structure. Although the feedpoint impedance of the inverted vee is somewhat lower than that of a flattop dipole, it is still a good match for 300-ohm twinlead or a coax/balun combination, but slightly better results will be obtained with 50-ohm coax than with 75-ohm line.

Nylon rope should be used between the insulators and the antenna supporting structures. In the case of a flattop dipole whose ends are supported by trees, the ropes should pass through halyards attached to the trees and their ends secured to weights. This will allow the antenna to remain stationary even when the supporting structures sway in the wind. If the metallic mast is used to support the center of an inverted vee, tension should be placed on the antenna wires and the feedline to keep them at least several inches away from the mast. In any event, try to keep the feedline at right angles to the antenna for as long a run as possible. The use of an in-line lightning arrestor is also highly recommended for safety's sake.

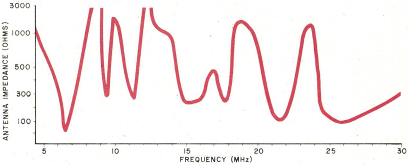

Fig. 8. A impedance plot of the author's prototype installed at a height of 20 feet.

If only a limited space is available for installation, the ends of the antenna can be bent at right angles. The straight, central portion of the antenna should be as long as possible. The antenna can be installed in an attic, but best results will be obtained if the antenna is mounted straight, in the clear, outdoors, and as high as possible.

For really tight quarters, an excellent performer on the 11-, 13-, 16- and 19-meter bands can be built by eliminating traps *T4*, *T5*, and *T6* and the three outer wire sections of each leg of the antenna. This shortened version has an overall length of approximately 28 feet and will also do a good job, though not as good as a full-size antenna, on the lower-frequency bands. ◇

Note—*Readers are encouraged to build the traps described in this article for their own use, but are cautioned that a patent application has been filed on this and other types of transmission-line traps.*

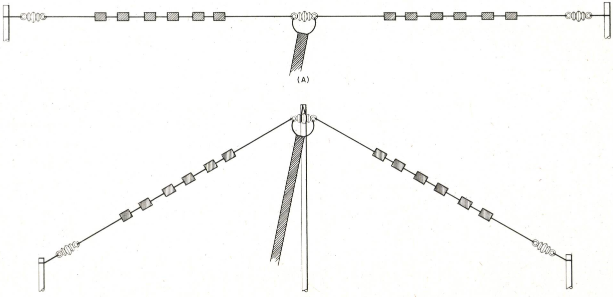

Fig. 9. Two ways to install the Multiband Shortwave Antenna—as a flattop dipole (A) and as an inverted vee (B).

Shhh!

DOLBY DOES IT AGAIN

A new noise-reduction system that works twice as well as the ubiquitous Dolby B

BY MARTIN FORREST

IF you ask any audio authority what development of the last 15 years influenced home high-fidelity recording the most, the answer you are likely to hear is: "Dolby B noise reduction." To be sure, the success—not to say dominance—of the stereo cassette recorder is in large measure due to the incorporation of Dolby B encoding and decoding circuitry in all but the very least expensive models.

The Challenges of Noise Reduction. It is generally agreed that in a high-quality sound system, residual noise (in cassette tapes that means largely tape hiss) should be at least 50 dB lower than the peak levels of the program material. But in the late 1960s and early 1970s the best signal-to-noise ratio that could be had from existing cassette tapes and decks was about 42 to 45 dB. The solution to this problem, as almost everyone knows by now, was Dolby B, a compander system that, when properly used, offered as much as 10 dB of tape hiss reduction. Adding this 10 dB to the 42 to 45 dB S/N available from cassette tape systems in 1970 gave 52 to 55 dB. This was hardly total absence of noise, but it could be fairly easily tolerated by those who sought to make high-fidelity music recordings at home.

Over the years, cassette tapes and recorders have improved in small increments, so that now, using premium-quality hardware, it is possible to achieve signal-to-noise ratios in excess of 60 dB. However minute they may seem, such noise levels are nevertheless still audible. Furthermore, program source material has improved too, so that what is available to the home recordist for transcription onto cassettes, (favorite discs, once-in-a-lifetime FM concerts, etc.) is apt to have more dynamic range than when Dolby B was introduced.

Today's direct-to-disc and digitally mastered records can, in some cases, deliver S/N ratios as high as 75 or even 80 dB (measured with an appropriate form of weighting curve). If you tried to transfer such a disc to cassette tape, even with Dolby B, you would either saturate the tape in the loudest passages or "bury" the softest passages below the tape hiss.

Largely for these reasons, several companies other than Dolby have recently developed and marketed compander noise-reduction systems that suppress noise by substantially more than does Dolby B. The dbx linear companding system, for example, can provide up to 30 or 35 dB of noise reduction. Telefunken, of West Germany, developed a noise reduction system, known as High-Com II that is sold in the U.S. in its consumer version by Nakamichi. Sanyo has a system called Super-D (which, like High-Com II provides about 20 dB of noise reduction), while Toshiba markets (in Japan only, thus far) a noise-reduction system known as ADRES, that is similar in concept to the dbx system.

One obvious common characteristic of these new noise-reduction systems is that all can improve S/N by 20 dB or more, compared with the 10-dB maximum of Dolby B. Despite the widespread acceptance that had been achieved, pressure on Dolby began to mount, even to the point where competing noise reducers were finding their way into consumer cassette decks right beside the familiar B system. It began to seem that the sun was setting on the mountain of which Dolby B had been king for so long.

But the limitation to 10 dB of noise reduction for Dolby B had been neither capricious nor abritrary. It is generally conceded that the more compression/expansion there is applied to an audio signal, the more likely it is that modulation of the noise accompanying the signal by the compander will become audible. (This is the source of the much dreaded "breathing" or "pumping" heard in some systems at times.) Furthermore, precisely because Dolby B had been so widely accepted, it was necessary that any new Dolby system be at least reasonably compatible with its predecessor. Finally, it would be desirable that, as is the case with B, a tape encoded in the new system be tolerable to listen to undecoded. At last, early this year, Dolby felt that it had sufficiently met these challenges and introduced a consumer noise-reduction system that offered a 20-dB improvement in S/N for any given recorder or tape. That system, logically enough, was called Dolby C noise reduction.

How Dolby C Works. Dolby C noise reduction lowers the noise inherent in low-speed tape recordings by about 20 dB above 1 kHz. Figure 1 is a multiple plot of noise spectra measured with a constant-bandwidth wave analyzer and weighted using the CCIR/ARM curve to reflect the ear's sensitivity to low-level noise. While Dolby B reaches its greatest effectiveness above approximately 4 kHz and from there upward reduces noise by about 10 dB compared with unprocessed tape recordings, Dolby C reaches full effectiveness at about 1 kHz and offers as much as 20 dB of noise reduction above that frequency. Like the two other Dolby systems (in addition to Dolby B, there is the professional Dolby A system) Dolby C is double-ended. The signal is processed during recording and "deprocessed" in

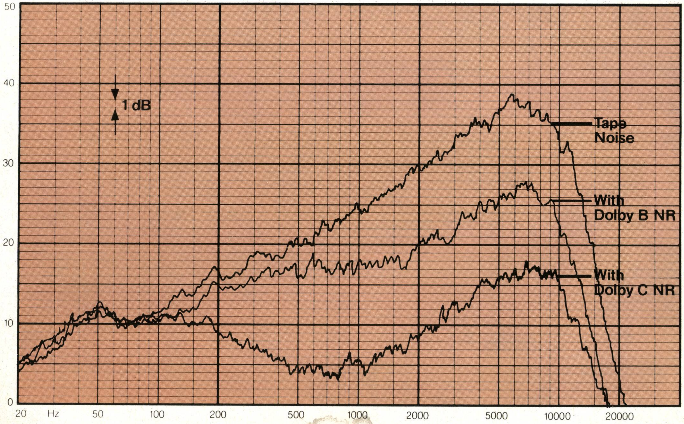

Fig. 1. Comparison of noise (CCIR/ARM weighted) from cassette tapes without noise reduction, with Dolby B, and with Dolby C noise reduction.

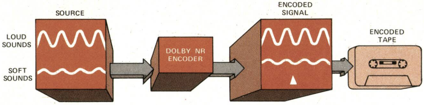

Fig. 2. In encoding, low-level mid- and high-frequency signals are boosted, high-level signals are not altered.

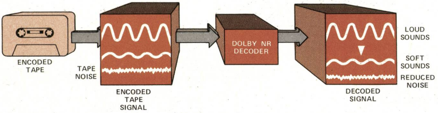

Fig. 3. In Dolby C decoding, low-level signals previously boosted are restored to correct relative amplitudes.

playback. This is illustrated in Figs. 2 and 3. Like Dolby A and B, Dolby C operates only at low program levels, where noise is audible, leaving unaltered high-level sounds that normally can mask tape hiss. Also, like Dolby B, Dolby C is a "sliding band" system. Full noise reduction occurs only in that part of the spectrum where it is most needed.

The chief difference between Dolby C and Dolby B is the *amount* by which signals are boosted during the recording half of the process and attenuated during playback. Dolby C also operates over a greater range of frequencies than did Dolby B, extending noise reduction downward to midrange frequencies, as plotted in Fig. 4. Achieving these new capabilities while satisfying all necessary constraints required several new developments.

A simplified block diagram of the Dolby C encode/decode circuitry is shown in Fig. 5. Each circuit incorporates two sliding-band stages that operate much as does a Dolby B processor. The two operate at different levels, however. Each stage provides 10 dB of compression during recording and the complementary expansion during playback. The high-level stage of Fig. 5 is sensitive to signals at about the same levels as the B-type. Since the two stages operate in tandem, their effect is to successively multiply the signal (or its equivalent, to add or subtract the corresponding number of dB) so that a total of 20 dB of compression/expansion takes place during encode/decode. This, in turn, results in a net reduction in noise of 20 dB. At no time is the program signal subjected to 20 dB of compression or expansion by a *single circuit*. Figure 6 illustrates the principle involved. According to Dolby, the tandem two-stage configuration is much more accurate than a single compander circuit would be.

In addition to the tandem processing, Dolby C incorporates two further developments worth mentioning. One of these, called spectral skewing, reduces the likelihood of encode/decode errors by reducing the sensitivity of the processing circuitry to frequency-response errors above 10 kHz. This allows for the usual variations in high-frequency response often encountered in casual use of a cassette recorder (such as by using a tape for which the deck has not been optimally adjusted). In Fig. 4, the plot shows that the maximum amount of compression in the C-type system diminishes above 10 kHz and crosses the B-type curve at around 20 kHz. This reduction in high-frequency compression results from the spectral-skewing and anti-saturation networks in the C system (Fig. 5). The anti-saturation network, as its name implies, operates at high signal levels to prevent tape saturation. Nakamichi, one of the first manufacturers to introduce Dolby C (albeit as a separate add-on unit), has demonstrated that Dolby C, used with the Model 1000ZXL Cassette Recorder and metal tape, provided a record/play frequency response at 0 dB recording level that was down only 1.0 dB at 20 kHz. Without the anti-saturation networks, record/play response for the same conditions was down some 11 dB at the same frequency.

Recordings made with C-type noise reduction, while not perfectly reproduced, will be listenable when played back on cassette decks equipped with Dolby B decoding. They will even be tolerable with no noise reduction, though purists would say that to call this compatibility is stretching a point.

How Expensive Will It Be? Dolby C-type noise-reduction circuitry is more complex than the B system, and will cost more to incorporate into consumer cassette decks. For the moment, two Dolby-B IC circuits can be configured to carry out C-type noise reduction. Further-

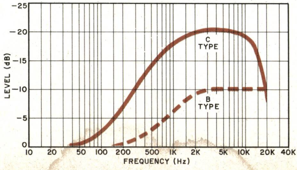

Fig. 4. Comparison of low-level encoding frequency response for Dolby B and Dolby C noise reduction systems.

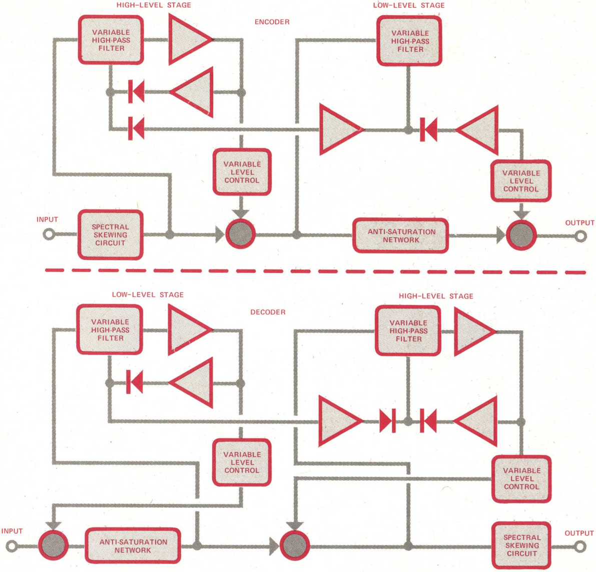

Fig. 5. Simplified block diagram of the encoding and decoding circuitry for a Dolby C noise reduction system.

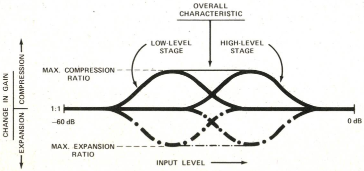

Fig. 6. In the two-level, two-stage Dolby C configuration, effects of the two stages multiply (add in dB) to achieve the full 20 dB of processing required.

more, one of the two stages can be conveniently reconfigured through switching to provide the B-type characteristic as well. It is expected that upcoming development of an IC chip for the C system will reduce costs further yet, but they will always be somewhat higher than those of Dolby B.

On the positive side, Dolby C should not represent a substantially larger fraction of the cost of the cassette decks in which it appears than does Dolby B now. This is because it takes a high-performance recorder to realize the benefits of the new system. Naturally, such machines are expensive to begin with, so it seems reasonable to suppose that the extra cost of Dolby C will not be much more than proportionate, if that. ◇

BUILD THE POOR MAN'S STROBE

Inexpensive circuitry allows timed, sequential flashes for multiple photographic exposures of moving subjects

BY IMRE GORGENYI*

STROBOSCOPIC photography, which exposes a single frame with light from a sequence of timed flashes, is an interesting way to capture a moving subject on film. The result is a series of still images that catch the subject in successive positions along its path, clearly suggesting motion. Stroboscopic photographs of a gymnast working out appear on the cover of this issue.

Unfortunately for shutterbugs, commercial equipment for stroboscopic photography is high in price. There are, however, circuits designed around readily available, inexpensive components that are easily built and will enable amateur photographers to experiment with the technique.

The Basic Poor Man's Strobe. The circuit (Fig. 1) triggers a flash unit at a predetermined time after the receipt of a light pulse from another flash unit actuated by the camera's flash-sync output. A portion of the light from the camera-triggered flash falls on the window of phototransistor *Q1*, which briefly conducts. The resulting negative voltage pulse at the collector of *Q1* triggers the timing circuit comprising *C1*, *R2* through *R6*, and *Q2*.

At the end of the timing interval, whose duration is adjustable by means of potentiometer *R3*, *Q3* and its associated passive components generate a positive voltage pulse and couple it to the gate of *SCR1*. The SCR breaks into conduction and triggers the flash unit whose sync contacts are connected to jack *J1*. Simultaneously, the timing circuit resets itself by means of *R6* to prepare for the next triggering light pulse. Power for the circuit is provided by a 9-volt alkaline battery via switch *S1*. Quiescent current drain is approximately 1 mA, so long battery life can be expected.

The delay between the arrival of the triggering light pulse and the actuation of the secondary flash can be varied from approximately 0.1 to 1 second. For shorter delays, the value of *C1* can be reduced to 0.1 μF. If this is done and *R3* is set for minimum resistance, the delay is so short that the attached flash unit can be used as a simple slave. Light from the slave will reinforce that from the camera-triggered unit and will yield brighter or more diffuse lighting of the subject. Of course, a number of basic Poor Man's Strobes can be built and each one adjusted for a different delay time to produce multiple images on a single emulsion.

Other Circuits. The slave-trigger circuit in Fig. 2 has practically no delay at all. It is therefore suitable for situations in which the slight delay introduced by the timing circuit of the PMS would cause an undesirable second image or smearing. This circuit has two unusual characteristics—it is not triggered by steady-state ambient light, and it derives its modest operating power from the flash to which it is connected.

Although ambient light would tend to cause phototransistor *Q1* to conduct, inductor *L1* prevents this from happening. Upon receipt of a light pulse, however, a voltage is set up across the inductor and the base-emitter junction of the phototransistor, and the device briefly conducts. This in turn forward-biases the base-emitter junction of switching transistor *Q2*, and a positive voltage appears across *R12*. The SCR breaks into conduction and triggers the flash unit whose sync contacts are connected to jack *J1*. A manual trigger switch (*S1*) is wired in parallel with *SCR1*. Power for *Q1* and *Q2* is derived from the flash unit by means of voltage divider *R3R4* and storage capacitor *C1*, which is wired in parallel with the *R3* leg of the voltage divider. The circuit's power requirements are so modest that almost any flash unit can easily satisfy them.

The circuit shown in Fig. 3 is a sequential flash trigger that can ac-

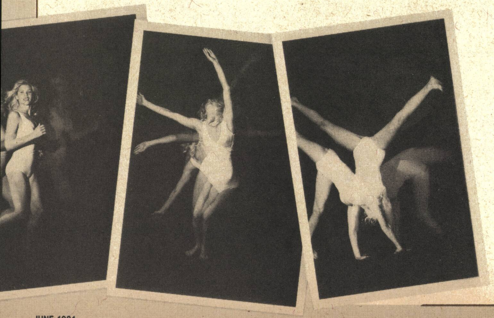

---

*Motorola Semiconductor Group

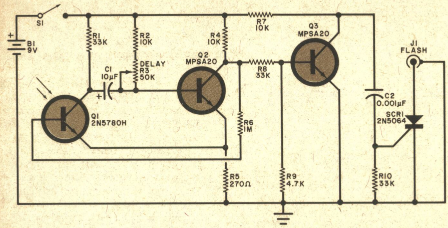

Fig. 1. Schematic diagram (above) of the basic Poor Man's Strobe. Below, a photograph of the author's prototype. The large control knob determines delay between trigger pulse and actuation of flash.

PARTS LIST

B1—9-volt alkaline battery
C1—10-µF, 16-V tantalum capacitor
C2—0.001-µF, 50-V disc ceramic capacitor
J1—Suitable jack (chosen to match the plug of the flash unit's sync extension cord)
Q1—2N5780H npn silicon phototransistor
Q2,Q3—MPSA20 npn silicon transistor
R1,R8,R10—33-kΩ, ¼-W, 10% resistor
R2,R4,R7—10-kΩ, ¼-W, 10% resistor
R3—50-kΩ, linear-taper potentiometer
S1—Spst switch
SCR1—2N5064 or similar silicon controlled rectifier (minimum voltage rating, 200 volts)
Misc.—Perforated board, battery holder, battery clips, sync extension cord, control knob, suitable enclosure, hookup wire, solder, hardware, etc.

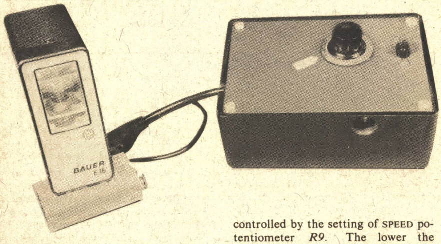

tuate as many as five flash units. These units will be triggered at equal intervals after the camera's sync contacts close. The circuit functions as follows: when the sync contacts close, transistor *Q3* cuts off and capacitor *C2* begins to receive charging current from the constant-current source comprising *Q4*, *Q5*, and their associated passive components. The ramp voltage that appears across the capacitor is coupled to position 1 of switch *S2* by Darlington emitter follower *Q6*. If *S2* is in position 1, the ramp voltage is applied to the gates of *SCR2*, *SCR3*, *SCR4*, and *SCR5* through a series of voltage dividers. The gate of *SCR1* receives a separate voltage pulse via a different circuit path almost immediately after the camera's sync contacts close.

As the ramp voltage at the pole of *S2* increases in amplitude, *SCR2*, *SCR3*, *SCR4*, and *SCR5* successively break into conduction and trigger the flash units to whose sync contacts they are connected. The rate at which the SCRs fire is determined by the slope of the ramp, which is ultimately controlled by the setting of SPEED potentiometer *R9*. The lower the resistance of *R9*, the greater the output of the constant-current source. Thus, more current will flow through *LED1*, and the LED will glow more brightly to indicate that the slope of the ramp will be steep and the flash sequence rapid. The total duration of the flash sequence can be adjusted from approximately 50 milliseconds to 3 seconds.

The monostable multivibrator comprising *Q1*, *Q2* and associated passive components performs two functions. First, it triggers *SCR1* when the camera's sync contacts close. Then, after three seconds, it resets the rest of the circuit to prepare for the next flash sequence. When switch *S2* is in position 2, the initial pulse across *R1* is simultaneously applied to the gates of *SCR1* through *SCR5*, triggering all the flash units simultaneously. Power

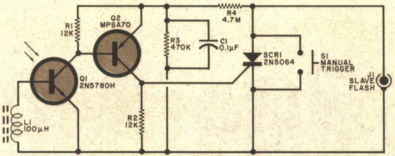

Fig. 2. Circuit for a slave-flash trigger that is not affected by steady-state ambient light.

PARTS LIST

C1—0.1-µF, 250-V Mylar capacitor
J1—Suitable jack (chosen to match the plug of the slave flash unit's sync extension cord)
L1—100-µH choke
Q1—2N5780H npn silicon phototransistor
Q2—MPSA70 pnp silicon transistor
R1,R2—12-kΩ, ¼-W, 10% resistor
R3—470-kΩ, ¼-W, 10% resistor
R4—4.7-MΩ, ¼-W, 10% resistor
S1—Normally open, momentary-contact pushbutton switch
SCR1—2N5064 or similar silicon controlled rectifier (minimum 200-volt rating)
Misc.—Perforated board, sync extension cord, suitable enclosure, hookup wire, solder, hardware, etc.

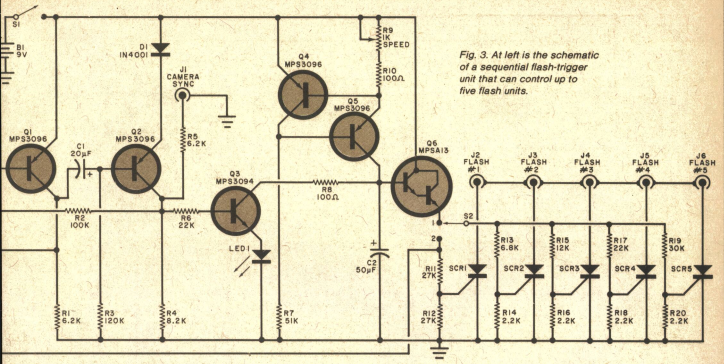

Fig. 3. At left is the schematic of a sequential flash-trigger unit that can control up to five flash units.

PARTS LIST

B1—9-volt akaline battery
C1—20-µF, 25-V aluminum electrolytic
C2—50-µF, 25-V aluminum electrolytic
D1—1N4001 rectifier
J1—Suitable jack (to match the plug of the camera's sync extension cord)
J2 through J6—Suitable jacks to match the plugs of the sync extension cords for Flash #1 through Flash #5)
LED1—Light-emitting diode
Q1,Q2,Q4,Q5—MPS3096 pnp silicon switching transistor
Q3—MPS3094 npn silicon transistor
Q6—MPSA13 npn silicon transistor

The following, unless otherwise specified, are 1/4-W, 10% tolerance, carbon-composition fixed resistors

R1,R5—6.2 kΩ
R2—100 kΩ
R3—120 kΩ
R4—8.2 kΩ
R6,R17—22 kΩ
R7—51 kΩ
R8,R10—100 Ω, 1/2-watt
R9—1-kΩ, linear-taper potentiometer
R11,R12—27 kΩ
R13—6.8 kΩ
R14,R16,R18,R20—2.2 kΩ
R15—12 kΩ
R19—30 kΩ
S1—Spst switch
S2—Spdt switch
SCR1 through SCR5—2N5064 or similar silicon controlled rectifier (minimum voltage rating, 200 volts)
Misc.—Perforated board, sync extension cords, suitable enclosure, battery holder, battery clips, control knob, hookup wire, LED mounting collar, solder, hardware, etc.

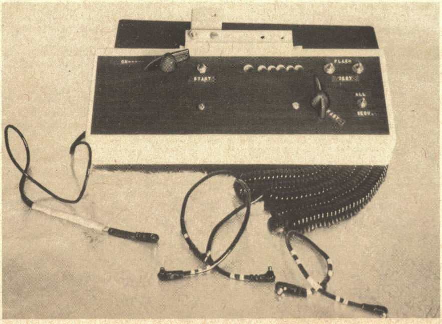

Photo of the prototype sequential flash-trigger unit.

for the circuit is supplied by 9-volt alkaline battery *B1* via switch *S1*.

Another sequential flash trigger circuit is shown schematically in Fig. 4. Here, the trigger pulse from the camera's sync contacts enables unijunction transistor *Q1* to generate clock pulses that drive CMOS decade counter/decoder *IC1*. The rate at which clock pulses are generated is determined by the position of rotary switch *S3*, which selects one of five RC timing networks (*R22C3* through *R26C7*). The gate of *SCR1* is driven by the output pulses of the UJT, but the gates of the other SCRs are driven by various of the counter's decoded output lines. Switch *S1* allows the user to determine whether the gate of *SCR5* will be driven by the Q_4 or Q_6 output line of the counter—that is, whether the flash unit connected to

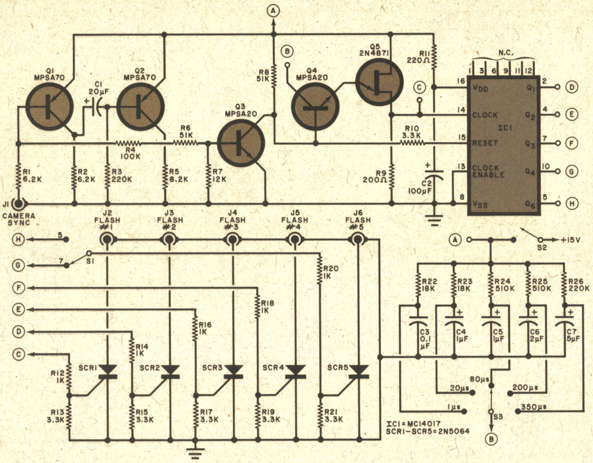

Fig. 4. Another sequential flash-trigger unit. This circuit employs a UJT clock and a CMOS decade counter/decoder.

PARTS LIST

C1—20-μF, 25-V aluminum electrolytic
C2—100-μF, 25-V aluminum electrolytic
C3—0.1-μF, 50-V Mylar capacitor
C4,C5—1-μF, 25-V tantalum capacitor
C6—2-μF, 25-V tantalum capacitor
C7—5-μF, 25-V tantalum capacitor
IC1—MC14017 decade counter/decoder
J1—Suitable jack (to match the plug of the camera's sync extension cord)
J2 through J6—Suitable jacks (to match the plugs of the sync extension cords for Flash #1 through Flash #5)
Q1,Q2—MPSA70 pnp silicon transistor
Q3,Q4—MPSA20 npn silicon transistor
Q5—2N4871 unijunction transistor
The following, unless otherwise specified, are 1/4-W, 10% tolerance, carbon-composition fixed resistors.
R1,R2—6.2 kΩ
R3,R26—220 kΩ
R4—100 kΩ
R5—8.2 kΩ
R6,R8—51 kΩ
R7—12 kΩ
R9—200 Ω
R10,R13,R15,R17,R19,R21—3.3 kΩ
R11—220 Ω
R12,R14,R16,R18,R20—1 kΩ
R22,R23—18 kΩ
R24,R25—510 kΩ
R26—220 kΩ
S1—Spdt switch
S2—Spst switch
S3—Single pole, 5-position nonshorting rotary switch
SCR1 through SCR5—2N5064 or similar silicon controlled rectifier (minimum 200-volt rating)
Misc.—+15-volt power supply or battery, perforated board, sync extension cords, suitable enclosure, IC socket, control knob, hookup wire, solder, hardware, etc.

jack *J6* will fire at the fifth or seventh clock pulse. As in the circuit of Fig.3, a monostable multivibrator built around *Q1* and *Q2* resets the circuit to prepare for the next flash sequence. Power for the circuit is provided by a +15-volt supply (not shown) via switch *S2*.

Construction. The prototype Poor Man's Strobes were assembled using perforated board and point-to-point wiring. However, printed-circuit construction can also be used. Type 2N5064 silicon controlled rectifiers are specified for each of the circuits that have been described. These devices have TO-92 plastic packages and are rated at 200 volts peak blocking voltage, 200 μA gate trigger current, and 6 amperes peak forward surge current. They are compatible with most flash units on the market. However, if you intend to use a flash unit that impresses more than 150 volts or so across its sync terminals, an SCR with a greater peak blocking voltage rating will have to be used.

Circuit layout is not critical, and the projects can be housed in any convenient enclosures. The various input and output jacks should be selected to match the plugs of the sync extension cords that your photographic gear employs. Photographs of the prototypes whose circuits are shown in Figs. 1 and 3 appear with the respective diagrams. In the circuits of Figs. 1, 3 and 4, the use of alkaline cells will extend battery life. Be sure to observe standard CMOS handling procedures for *IC1* of Fig. 4 and to use an IC socket to mount it.

Using the Poor Man's Strobes. As with any photographic hardware, a good deal of experimentation is required to learn how to use the Poor Man's Strobes for the best results.

Start with two flash units in an unlit room with dark walls or wall coverings. If you are using the circuit shown in Fig. 1, connect one flash to the camera's sync contacts and the other to jack *J1*. If you are using one of the circuits shown in Figs. 3 and 4, connect one flash unit to *J2* and the other to *J3*. Run a sync extension cord from the camera to input jack *J1*. Place your camera in its "B" (bulb) exposure mode and either set the object to be photographed in motion or direct your model to move around the room. Trip the shutter and hold it open. One flash will fire immediately, and the other will be triggered after a delay. Release the shutter after the second flash has fired.

This first trial should be a "dry run" with no film in the camera. Your eyes will register the strobed images. Repeat the experiment several times, varying the delay between the triggering of the two flash units and the rate at which the object or model is moving. If you have built several of the basic Poor Man's Strobes or one of the sequential trigger circuits shown in Figs. 3 and 4, add more flash units to see how multiple-flash stroboscopic photographs will look.

Next, determine a sequence of connecting the flash units to the output jacks and applying power that does not result in inadvertent triggering of the units. The proper procedure might be as follows: apply power to the Poor Man's Strobe; connect the flash units to it; and finally apply power to the flash units.

Once you have acquired a feel for the Poor Man's Strobe, you can take real pictures. Here again experimentation is needed. Vary the positions of the flash units, use different levels of light output, and for color work place different color filters on each flash unit. With a bit of experience, you'll be able to turn out interesting and unusual photographs that are as much fun to display as they are to take. ◇

COMMERCIAL KILLER FOR A CLOCK RADIO

Low-cost system cuts off the audio on cue from the listener and restores it after one minute

BY HERBERT L. BRESNICK

DID you ever wish you could eliminate radio commercials and TV commercial sound? My clock radio, tuned to the local news station, is set for 6:00 a.m. This means 5 minutes of news interspersed with 5 minutes of commercials, and I find few things worse than listening to soap or laxative jingles at that hour! Fortunately, most commercials are exactly one minute long—which makes them not too hard to silence.

Basically, the system cuts off the audio on cue from the listener and uses a one-minute delay circuit to restore it—presumably after the commercial is over. Figure 1 shows the schematic diagram of the system, which uses about $3.00 worth of parts, depending upon the size and condition of your parts junkbox. Here's how it works: As soon as the commercial starts, push switch *S1* momentarily. This triggers *IC1*, a 555 IC timer chip, wired as a monostable. Triggering forces pin 3 of the IC high, operating relay *K1*, which pulls in, opening its normally closed contacts. These contacts, in series with the loudspeaker, squelch the audio. After one minute (as set by *C1* and *R1*), pin 3 goes low releasing the relay and restoring the audio—just in time for resumption of the broadcast.

The circuit is easily wired, point-to-point on a 2" x 2" piece of perf board. Supply voltage (9 to 12 volts) is tapped from the radio or TV at any convenient point, and one speaker lead is placed in series with the relay contacts. It is recommended that a resistor be placed across the two leads that normally feed the speaker, as most power circuits do not like to be left unloaded. A 10- or 20-ohm resistor will do fine. Wrap the board with tape to protect the wiring and position it in a convenient space inside the receiver. The trigger wires can be brought out through the rear of the set, and connected to a pushbutton switch that can be placed at any convenient location.

Adding the "commercial killer" to my radio, has restored my sanity, and I'm able to face the morning shower, my wife, and the world with a smile. It may do as well for you. ◇

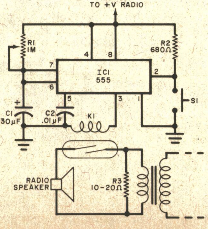

Fig. 1. Duration of silencer period is set by R1 and C1.

PARTS LIST

C1—30-μF, 15-V capacitor
C2—0.01-μF, disc capacitor
IC1—555 timer
K1—9-to-12-V, reed relay
R1—1-MΩ trimpot
R2—680 Ω, ½-W resistor
R3—10-to-20 Ω, ½-W resistor
S1—Momentary-contact pushbutton switch
Misc.—Perf board, wire, solder, etc.

AN 1802-BASED EPROM PROGRAMMER

Hardware and software to program, copy, and verify data in a 2708 EPROM, using an 1802 microprocessor

BY LARRY BREGOLI

MOST computer fans have a few favorite programs such as monitors, machine-language utilities, and even high-level languages that are used so often that storing them in ROM would be beneficial. When in this permanent memory, these programs can be accessed at any time, without the often tedious loading procedure. The ROM can even work from a power-up state.

There are numerous ROM programmers available for most systems, but few for those based on the 1802 processor. The programmer described here will help to alleviate this shortage. Although designed for 2708 devices, it can be user modified to accept 2716 devices. This permits doubling the ROM size with no increase in board space.

Circuit Operation. A simplified block diagram of the EPROM programmer is shown in Fig. 1. When the I/O Select Line calls for the programmer, three events occur. In conjunction with the arrival of the $\overline{\text{MWR}}$ (memory write) signal, the Program-Cycle-Latch causes the Address-Latches to: (1) hold the address currently on the address bus; (2) remove the data latches from their three-state mode to allow them to latch and hold the data currently on the data bus; and (3) via the Program-Pulse-Circuit place the 2708 in the write-enable mode so that timing pulses from the CPU will allow a programming pulse to be applied.

The eight Three-State Switches remain in their high-impedance state until the 2708 is read. At this time the $\overline{\text{MRD}}$ (memory read) pulse allows data from the 2708 to be placed on the system data bus. The read function is handled in this manner because it is easier than using the 2708's $\overline{\text{CS}}$ (chip select) circuit that requires three voltage levels. The 2708 data lines go three-state when the $\overline{\text{CS}}$ voltage is at +5 volts, and when the data is read from the 2708, the $\overline{\text{CS}}$ line must be low (the same as ordinary RAM). The 2708 is placed in the write mode by bringing the $\overline{\text{CS}}$ line to +12 volts.

The complete schematic is shown in Fig. 2. Some of the IC grounds shown are functionally necessary while others are required because all unused CMOS inputs must be terminated with either a ground or +5 volts to avoid noise problems. The reset (pin 4) of *IC1*, the program cycle latch, is connected to the system reset line, while the clock input (pin 3) is connected to one of the N lines from the 1802. The Q signal at pin 1 of *IC7A*, is the serial-output line of the 1802 and is set high or low by the system software. Note that the Q pulses cannot get to the pulse circuit unless *IC7A* is enabled by the pin 1 output of *IC1*. The only TTL device used is *IC9*.

The 2708 both sinks and sources current at its programming input (pin 18) during programming and this must be included in the circuitry or the voltage at this pin will be pulled up by the sink current during the low-voltage level of the program pulse. Pin 4 of *IC9* provides this function. Data latches *IC2* and *IC3* may be replaced with 4076's if you want to stick with all 4000-series IC's. The $\overline{\text{MWR}}$ and $\overline{\text{MRD}}$ pulses are both gated by the $\overline{\text{CE}}$ (chip enable) signal from the addressing system. The $\overline{\text{CE}}$ does not have to select the 2708 directly since the EPROM is always in the read mode when not being programmed. There's an additional advantage in this approach, since in the read mode the 2708 uses the minimum standby power without a special power-down circuit. The data-latching-strobe to *IC2* and *IC3* is a function of TPB, a timing pulse which occurs when the data is valid, via *IC7B* and *IC10C*.

The RC network coupled to programming pin 18 of the 2708 shapes the programming pulse so that voltage spikes will not occur inside the 2708 possibly creating an error in the programmed data.

Timing. The 2708 timing must be programmed for a minimum of 100 ms for each bit, and each bit can be programmed only for a maximum of 1 ms at any given time. This means that each bit must be programmed at least 100 times.

Another criterion for programming the 2708 is that, each time a portion of the memory is programmed, the remainder of the bits must also be reprogrammed. This will be described further under "Software." The only other timing consideration to account for is the minimum 10 μs setup time for the address and data information. All of these timing requirements are

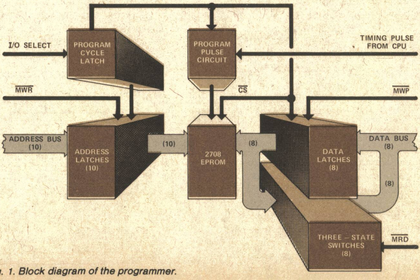

Fig. 1. Block diagram of the programmer.

handled by the programming software to keep the hardware simple.

Software. A fully erased 2708 contains all "ones" and the programmer replaces these with zeros where specified during the programming mode. Once a zero bit is programmed, it cannot be changed back to a one by programming. If you make an error and put a zero in the wrong location, the only way it can be rectified is erasing the EPROM with UV to produce all ones again, and then re-start the programming.

About 1K of RAM is required to assemble and hold the data to be programmed into the EPROM. This RAM space must be initially programmed with all ones to avoid any unwanted zeros from appearing when programming is started. This is accomplished by copying the contents of the erased 2708 in the programming socket into the RAM space.

This method is also convenient for adding data to an EPROM which has been partially programmed. In this case, the existing programs in the EPROM are also copied into RAM

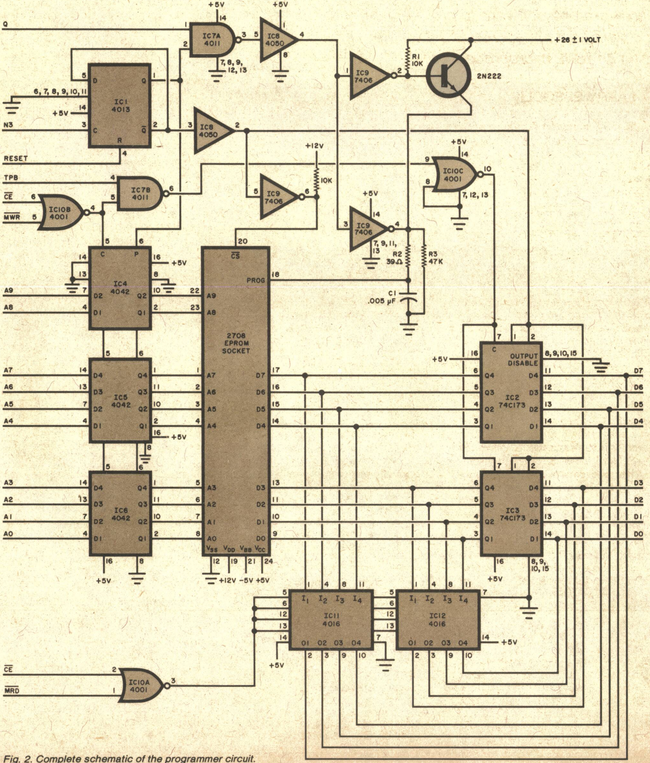

Fig. 2. Complete schematic of the programmer circuit.

and are reprogrammed back into the EPROM along with the added data. Keep in mind that, each time new data is added to the EPROM, all 1024 bytes must be programmed.

The three subroutines to be covered are called using conventional 1802 call and return techniques. The program locations are arbitrarily chosen. The items in parentheses are bytes that would have to be changed if any locations are modified. The COPY subroutine is shown in Listing 1. This is a simple move program of which many versions exist. In this case, the initiating routine sets pointers to the beginning address of the EPROM to be programmed and to the beginning address of the RAM area used to store the program. The bytes are then copied, one by one, from the EPROM into the RAM until all 1024 bytes in the EPROM have been copied.

New data to be programmed into the EPROM is placed in any available RAM space. When the new data has been entered into RAM, the BURN EPROM subroutine of Listing 2 is called to program data into the EPROM.

The BURN EPROM substitute should contain all the timing information needed to properly program a 2708 EPROM including the data and address setup times. When the subroutine is first entered, a counter is loaded with the number of times all 1024 words will be programmed. This number can vary from 100 to 1000 since the width of the programming pulse may be set from 0.1 to 1.0 ms, and the product must always be equal to or greater than 100 ms. An I/O pulse is then sent to the program-cycle-latch by way of line N3 to activate the programmer. Address pointers are then set to point to the starting addresses of both the EPROM to be programmed and RAM area holding the data. A byte, read from the RAM area, is written into the data-input latches, and simultaneously latches the address latches. Before application of the programming pulse, the 2708 needs a minimum of 10 μs to allow for data and address settling times. To accomplish this time delay, simply insert NOP instructions in the program before applying the programming pulse. The pulse-time-counter is then loaded with a number that describes the programming pulse width.

The Q line from the 1802 is then set high causing the programming pulse to begin. Next, the pulse-time-counter is decremented to zero, dictating the width of the programming pulse. The Q line is then set low, ending the pulse. The loop counter is decremented each time all 1024 words have been programmed; then a test for a zero in the loop counter is made. When the loop counter is zero, an I/O pulse is again sent to the programmer to take it out of the programming mode. It requires approximately 103 seconds to program all 1024 words into a 2708.

Some EPROMS may need more programming time to guarantee that all bits are properly burned. To do this, the number in the loop counter must be increased. If you have the BURN EPROM program already in the EPROM, simply burn the new one again using the same program.

To determine if you have burned all the bits properly, they can be tested using the VERIFY program shown in Listing 3. This routine compares each byte in the newly burned EPROM with the original data in RAM. If a mismatch is found, the Q line is set. The erroneous byte location can be shown on a monitor or a hexadecimal display. To determine if the VERIFY program is working properly, inset an intentional error in the RAM area and run the VERIFY program. ◇

LISTING 1—COPY

Location	Code	Comment
E4 1E	F8 (C8) B8	: Point R8 to RAM Area
E4 21	F8 (D0) B9	and
E4 24	F8 (00) A8 A9	R9 to beginning of EPROM
E4 28	09	: Get EPROM byte and
E4 29	58	put it in RAM
E4 2A	19 18	: Increment EPROM & RAM
E4 2C	99 FB (D4)	: If it's not the last
E4 2F	3A (28)	byte, get another
E4 31	D5	: RETURN

LISTING 2—BURN EPROM

Location	Code	Comment
E4 32	F8 65 AA	: Set loop counter to 101
E4 35	EB 63 2B	: Activate Programmer (N lines 3)
E4 38	F8 (C8) B8	: Point to starting locations
E4 3B	F8 (D0) B9	of RAM and EPROM
E4 3E	F8 (00) A9 A8	
E4 42	2A	: Decrement loop counter
E4 43	8A	: If loop counter is
E4 44	32 (5C)	zero then exit
E4 46	08	: Get RAM byte
E4 47	59	: Write byte into latches
E4 48	18 19	: Increment RAM & EPROM
E4 4A	C4 C4	: Waste time for settling data
E4 4C	F8 29 AE	: Load pulse time counter
E4 4F	7B	: Start programming pulse
E4 50	2E 8E	: Pulse width equals
E4 52	3A (50)	approx. 0.1 ms
E4 54	7A	: Stop programming pulse
E4 55	99 FB (D4)	: If it's not last
E4 58	3A (46)	byte get another byte
E4 5A	30 (38)	: Else do another loop
E4 5C	63 2B	: Deactivate EPROM
E4 5E	D5	: RETURN

LISTING 3—VERIFY BURN

Location	Code	Comment
E4 5F	F8 (C8) B8	: Point to start of
E4 62	F8 (D0) B9	RAM & EPROM
E4 65	F8 (00) A8 A9	
E4 69	E8	: Set X R8
E4 6A	99 FB (D4)	: If all bytes O.K.
E4 6D	32 (76)	then exit
E4 6F	09 F3	: Compare RAM byte with
E4 71	19 18	: EPROM and increment both
E4 73	32 (69)	if the same continue
E4 75	7B	: Else set Q
E4 76	D5	: RETURN

BUILD A HEADLIGHT MODULATOR FOR CYCLE SAFETY

Inexpensive circuit pulses the high beam to enhance visibility

BY STAN JONES

AS A safety precaution, riders of motorcycles and mopeds are required to have their headlights on when using public roads. Since even this is not always sufficient to ensure that they will be noticed by other drivers, devices have been developed to modulate the brightness of the headlight, enhancing its visibility. In most cases, the low beam is left on constantly, while the high beam is switched on and off at about a 4-Hz rate. When the headlight is switched to the high beam manually, the modulator is overridden and ceases to operate. In addition, if the circuit should fail to function properly, the normal headlight operation is not affected.

If motorcycles verge on being invisible to drivers of larger vehicles, bicycles are even harder to see. The modulator circuit described here can be easily modified to operate with the type of single-beam headlights commonly used on bicycles.

Circuit Operation. As shown in Fig. 1A, the circuit is based on a 555 timer operating as a slow astable square-wave generator. The ratio of *R1* to *R2* was selected to produce a nearly symmetrical waveform. Effectively, timing capacitors *C1* and *C2* charge through *R1* and *R2* and discharge through *R2* causing the output at pin 3 to be nearly square. The positive-going portion of the pulse turns switching transistor *Q1* on while the zero portion turns it off. When turned on, *Q1* acts as a closed switch to pass filament power from the dim to the bright headlight filament, causing it to glow as long as *Q1* is on. Diode *D1* passes only the positive-going excursions of the pulses.

Alternately, the circuit can be built around a relay as shown in Fig. 2. Just make sure that the selected relay will handle the current.

Power to operate the circuit comes from the low-beam circuit. When the

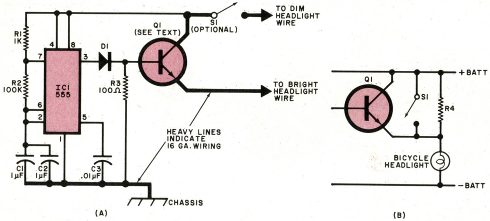

Fig. 1. Basic circuit (A) is based on a 555 timer. It can be modified as shown at (B) for a single-beam bicycle light.

PARTS LIST

C1, C2—1-μF, 34-V tantalum capacitor
C3—0.01-μF, 50-V disc ceramic capacitor
D1—1N914
IC1—NE 555 timer IC
Q1—ECG182 transistor (for 50-watt headlamp) or ECG184 transistor (for 30-watt headlamp)
R1—1-kΩ ½-W resistor
R2—100-kΩ, ½-W resistor
R3—100-Ω, ½-W resistor
S1—Optional spst toggle switch with 5-A contacts
Misc.—1½" × 1½" perf board, wire, solder, 8-pin socket (optional), short length of 16-gauge wire, mounting hardware.

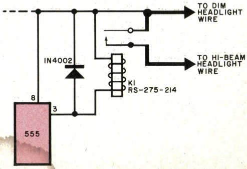

Fig. 2. A relay can be used instead of the output switching transistor.

$28

ONE OF THE

Finest Pen Watches in the World at the Lowest Price!

SOLD BY OTHERS FOR $69.95

The Original ARTRON Pen/Watch

The pen/watch is not a revolutionary new product. It has been on the market now for years. Unfortunately, from our experience, almost all were novelty-looking in appearance and cheaply constructed. Comparable pen/watches sell for $60 and more.

UNTIL NOW!

We engage in world trade. Being in the import/export business, we are aware of a countries outstanding products. The Artron Pen is sold worldwide and THE EGBERT CO. is the largest distributor of them in the U.S. Since we buy thousands at a time direct from the manufacturer, we can offer the Artron Pen/Watch at $28 . . . a truly wholesale price.

A UNIQUE COMBINATION

The Artron is an accurate, easy-to-read timepiece, combined with a quality writing instrument. The 100% stainless steel construction and classic styling of the Artron Pen/Watch offers you the quality of the undisputed leaders, such as Cross and Schaeffer, with the addition of an accurate LCD watch (accurate to ± 15 sec. a month). The finest quartz digital watches have comparable accuracies usually somewhere between ± 15 to ± 5 sec. a month.

THE WATCH

The LCD display constantly shows you the hour and minutes without any awkward button pushing. When you need the month and day, you just depress the top of the pen once or twice for seconds. An additional push returns it to the time. The watch is powered by a tiny silver oxide Eveready 392 battery that lasts about two years and is easily replaced.

Your Artron Pen/Watch comes with full instructions, a one year manufacturer's guarantee against defects and its battery in place. Included with every Pen/Watch is the beautiful presentation case shown. When you receive your Artron Pen/Watch, use it constantly for three full weeks. If, after you've thoroughly tested it, you don't agree that your

CONTINUOUS	1st PRESS	2nd PRESS
2:36	9:19	:07
TIME READOUT	MONTH DAY	SECONDS

Artron Pen/Watch represents a major breakthrough in price, quality and value, send it back.

We'll refund your entire investment, including the delivery charge. You can't lose . . . we guarantee it.

Time is of the essence.

We can only guarantee the continuation of this introductory price for a short time.

ORDER TODAY!

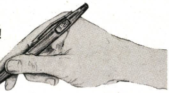

©1980 Egbert Co.

THE ULTIMATE PRACTICAL GIFT

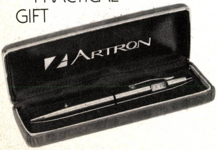

The Egbert Co.
11055 Sunset Blvd.
Los Angeles, CA 90049

The Egbert Company, Dept. PE-3
11055 Sunset Blvd. ● Los Angeles, CA 90049

RUSH the following Pen/Watches to me by first class insured mail:

☐ Stainless Steel Model . . . . . . $28 (2 for $52)
☐ Gold Plated model . . . . $38 (2 for $70)
A Generous 5 Micron
☐ Deluxe Stainless Steel & Gold Plated models. . . . . Both for $62
plus $1.50 postage & handling per order.
Calif. add 6% sales tax.

Enclosed find check or money order for $________.
Charge to my ☐ Visa ☐ Master Charge

Card # ____________ Exp. Date ______
Name: ____________
Address: ____________
City/State/Zip: ____________

For credit card orders only, call TOLL FREE, 24 hours, 7 days: 800-824-7880.
Ask for operator 107.
In Calif.: 800-852-7777 ● In Alaska/Hawaii: 800-824-7919

CIRCLE NO. 15 ON FREE INFORMATION CARD

project is wired to the motorcycle as shown, the high-beam indicator on the instrument panel will flash in-step with the strobe and serve as a visual indicator that it's working. Switch *S1* is an optional bypass switch that turns the entire unit off.

Figure 1B shows how the circuit can be modified to work with a single-beam bicycle headlight. Resistor *R4*, whose value and dissipation rating will depend on the particular headlight, is chosen to give an acceptable level of brightness when *Q1* is off. During the intervals when *Q1* is on, the lamp goes to full brightness. Switch *S1* has been connected to bypass the modulator when normal operation is desired. The additional power drawn by the pulsing circuitry is negligible.

Construction. Wiring of the modulator is not critical and any approach can be used. To allow mounting the finished unit inside the headlight housing, keep its size small. The finished project can be coated with a good silicone sealer, or protected inside a small plastic mini-box. Be sure to use good quality, low-leakage capacitors and test the unit before installation. Almost any npn power transistor will work fine for *Q1* as long as it can handle the required lamp current (5-7 amperes for a moped or small bike and 10 amperes or more for a bike with a 50-watt headlight). A heat sink will be required for *Q1*. Note the wire sizes called out in Fig. 1. As previously mentioned, a relay can be used in place of the transistor and the heat sink will not be needed. The relay drive current can be up to 150 mA and the contacts must, of course, be able to handle the lamp current.

The finished modulator can be mounted within the headlight housing, and all connections can be made without exposed wiring. If optional on/off switch *S1* is used, it can be mounted in a hole drilled in the modulator housing.

Operation. Dimming the headlight automatically starts strobing the high beam. On most motorcycles, the headlight switch can be set in the center position to provide both high and low beam illumination. If this position is used, the modulator is switched off.

Since materials for the unit cost only about $10, what excuse can there be for not building one for yourself? It might well save your life. ◇

Using the 4060 as a Timer

BY T.A.O. GROSS

MENTION timing circuits, and most people tend to think of the ubiquitous 555 IC. While the 555 is excellent for most timing applications, other devices are worthy of consideration. These are the CMOS CD4060A and SCL4060AB 14-stage ripple-carry binary counters from RCA and Solid State Scientific, respectively.

Among other advantages, the 4060-series devices can be less expensive to implement in a given application because they require less critical and less expensive resistors and capacitors. A second advantage is that 4060-series devices can deliver a number of output frequencies from the same RC components; the 555 delivers only one.

Technical Details. In a 555 timer circuit, external frequency-determining resistor and capacitor values must be selected to produce the desired oscillator frequency directly. As a result, in many cases where relatively long time constants (low frequencies) are desired, the RC product requires the use of bulky, expensive electrolytic capacitors with, often, inaccurate values and high losses. Devices of the 4060-series use oscillator frequencies much higher than what is required at the output. The oscillator frequency goes through a 14-stage binary counter that divides it by as much as 16,384 (2^{14}) before it is used as the final timing frequency.

Using a much higher oscillator frequency than the 555 timer to obtain the same timing frequency the 4060 has a correspondingly smaller RC product. Hence, there is no need to use inaccurate and unstable electrolytic capacitors or humidity-sensitive, very-high-value resistors.

While the CD4060A and SCL-4060AB are interchangeable in most cases, the two are different. In the CD

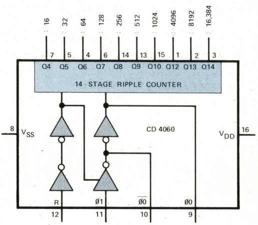

Fig. 1. Internal schematic arrangement of the RCA CD4060 timer integrated circuit.

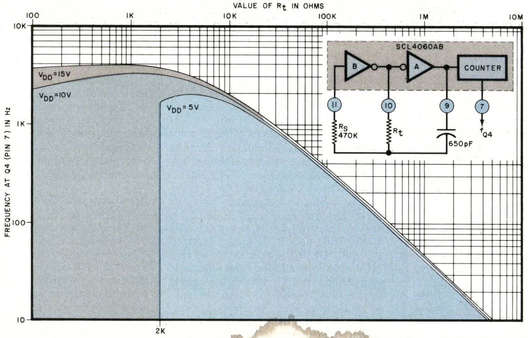

Fig. 2. With low values of timing resistor, R_t, the frequency of the circuit can vary with applied dc operating voltage.

ETCO

CABLE TV CONVERTERS AND OTHER GOOD STUFF!

SMASHING ALL SALES RECORDS – OUR NEW 30 CHANNEL CABLE TV CONVERTER!
Converts mid & super band cable channels for viewing on your TV set!
No. 335AE047
39.95
$34.95 ea. / 5

HOT NEW IMPORT! REMOTE CONTROL 30 CHANNEL CABLE TV CONVERTER!
89.95
$79.95 ea. / 5
$74.95 ea. / 10
Includes remote TV on/off switch and fine tuning control!
No. 335VA275

ETCO MKII WIRELESS – THE ULTIMATE CABLE TV CONVERTER!
Set TV to channel 3, and the hand-held remote control does it all!
No. 335ZA008
189.00

VIDCOR 2000 CONVERTER ELIMINATES PROBLEMS WHEN TAPING FROM CABLE TV
89.95
Restores your VCR's capability for programming. Restores remote channel control. Enables videotaping of one cable program while watching another.
No. 335VA950

UNUSUAL FACTORY SURPLUS MID-BAND – SUPER-BAND CABLE TV TUNER
Converts cable channels to a common IF frequency. Experimenters – build cable converters, decoders, etc. With schematic. No. 335VA342
19.95
$17.50 ea. / 10
335VA389- Detailed schematic & spec sheet - $1.50

FACTORY SURPLUS UHF TUNERS
4.95
$3.95 ea./10
Brand new production surplus. All solid state. Ideal for experimental work building, cable TV converters, etc. No. 335SU099

MINIATURE FM WIRELESS MICROPHONE
Hides in the palm of your hand. Reception on any standard FM radio or receiver.
No. 335VA482
29.95
$27.50 ea. / 5
$24.95 ea. / 10

QUARTER-MILE WIRELESS MICROPHONE & RECEIVER SYSTEM
69.95
$49.95 ea. / 5
FCC approved crystal controlled wireless mike & receiver. All battery operated. Electret wide-range response. VU meter.
No. 335VA093

ETCO GENERAL PURPOSE TUBE TESTER
IN KIT FORM. Checks for leakage, shorts, emission. 7, 9-pin, octal, loctal, compactrons, nuvistors. In portable case.
No. 335KT146
Wired: No. 335TE053 – $79.95
Pix tube adapter: 335TE344 - $19.95
49.95

DUMPING! NORELCO ENDLESS LOOP CASSETTES!
4.95
$4.49 ea./10
Impossible to find at any price!
3 minutes – No. 335VA605
6 minutes – No. 335VA606
ENDLESS!

IN STOCK – THE MURA CORDLESS TELEPHONE SYSTEM!
Answer & originate calls with this wireless pocketphone. 400 ft. range! Rechargeable! Last number recall! Paging feature! Use with rotary, touch systems!
No. 335VA724
144.88
$129.95 ea. / 5.

SALE OF QUARTZ BATTERY-OPERATED CLOCK MOVEMENTS!
9.95
$8.95 ea. / 5
Accuracy of 1 min. / year. up to 4 years operation on 1 alkaline "C" cell. Imported from West Germany. No. 335VA561
335VA565- Matching hands - $2.49/set. $1.95/set / 5

20 AMP REGULATED 12VDC POWER SUPPLY!
13.8 vdc no load, 12.5 vdc full load. Easily handles ham station, marine radio, SSB linears up to 400w P.E.P. Brand new, factory sealed cartons. No. 335VA394
59.88
$48.95 ea. / 5
335VA395- as above, 10 amps – $49.95. 39.95 ea. / 5.

FREE
OUR LATEST 98 PAGE FASCINATING CATALOG –jam-packed with unique items, electronic bargains and unusual offers. Write or circle the information card number below.

ETCO
ETCO ELECTRONICS
NORTH COUNTRY SHOPPING CENTER
PLATTSBURGH, N.Y. 12901

Check with order, please. Visa & Mastercard OK. (Sorry, no C.O.D.'s. Add 15% for UPS & Handling (Excess refunded). N.Y. State residents add 7% sales tax. Dealer & Export inquiries invited. Our telephone order desk never closes.
Call 1-518-561-8700.

CIRCLE NO. 19 ON FREE INFORMATION CARD

device, the oscillator is keyed by the reset input, whereas in the SCL device, the reset operates on the dividers, leaving the oscillator in continuous operation.

Basic internal logic of the CD4060A is shown in Fig. 1. Two of the four inverters serve as the active elements of the internal oscillator whose output is passed through the 14-stage ripple-carry binary counter. Oscillator frequency is set by an RC network, or an external crystal oscillator can be connected to pin 9 to eliminate the need for the internal oscillator. When the internal oscillator is used, the input at pin 12 is provided to reset the counter to zero and disable the oscillator.

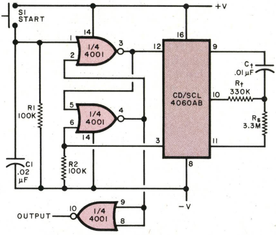

Fig. 3. With the values shown, this circuit has a one-minute delay period. The output strobe goes high after timeout.

It is not necessary to use all 14 stages of division. As shown in Fig. 1, you can select division factors of 16, 32, 64, 128, 256, 512, 1,024, 4,096, 8,192, or 16,384, simply by picking off the output from the appropriate pin of the IC.

Timing resistance values for 4060-series devices should not be less than 10,000 ohms to avoid changes in frequency with changes in applied dc operating voltages. As can be seen in Fig. 2, the frequency/resistance function reverses at about 4,500 ohms with a 5-volt supply at 1,300 ohms using 10 volts.

The frequency calculation formula for the 4060 given in manufacturer application notes is $F = 1/(2.2R_tC_t)$, where R_t and C_t are the values of the timing resistor and capacitor. This formula assumes V_{DD} is 10 volts, C_t is greater than 100 pF; R_t is greater than 1000 ohms, and R_s is larger than 10 times R_r. (R_s is the external stabilizing resistor, as shown in the inset schematic diagram in Fig. 2.) In this author's experience, this formula is accurate only when R_t is greater than 50,000 ohms. With values less than 50,000 ohms, observed frequency was lower than predicted by the formula.

Data given in Fig. 2 was obtained at the pin-7 (÷16) output from an SCL4060AB. With time delays of more than a few hours, it was determined that use of R_s is not necessary.

Practical Timer. Shown schematically in Fig. 3 is the circuit for a practical 1-minute timer built around a 4060-series device. A 330,000-ohm resistor and 0.01-μF capacitor are doing a job that would require a 60-megohm/microfarad *RC* product in a 555 circuit.

and

Momentary closure of START switch *S1* causes the set-reset flip-flop made up from two gates in a 4001 quad 2-input NAND IC to produce a high output at pin 12 of the 4060. After the timing interval (oscillator frequency) determined by R_t and C_t, pin 3 of the 4060 goes low and toggles the flip-flop to stop the counter. At the same time, the output of the bottom 4001 gate, held low during the timing interval, goes high. (Since the 4001 contains four on-chip gates, the fourth gate can be paralled with the output stage to provide more driving current for an external circuit.)

Much longer timing intervals can be obtained by cascading the pin-3 output of the 4060 with a 4020, a 14-stage counter that is similar to the 4060 but lacks the internal oscillator.

Capacitor *C1* and resistor *R1* improve the circuit's immunity to noise and are optional.

Summing Up. Once you start working with 4060-series devices, you will probably think of them as often as you do the 555 for your timing applications. Their easy implementation into circuit designs and reduced demands on frequency-determining resistors and capacitors make them particularly attractive where costs must be kept down and hardware space is at a premium. And they offer a number of different output frequencies from a given RC network that gives them an important advantage over single-frequency-only timing devices. ◇

Radio Shack is America's Parts Place™

No Minimum Order! No Waiting! Low Prices!

Low-Priced Precision Wire-Wrapping Tool

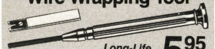

Long-Life Steel Bit **5.95**

This balanced 4½" all-metal tool speeds wiring of IC projects. It strips, wraps, and unwraps 30-gauge wire. Includes an easy-to-use stripper that stores in the handle. **276-1570** **5.95**

30-Gauge Kynar Wire

Color	Cat. No.	50-ft. Spool
Red	278-501	2.39
White	278-502	2.39
Blue	278-503	2.39

TV RF Modulator Board

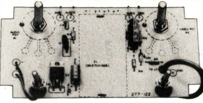

- *Prewired RF Module*
- *Ch. 2 or 3 Output*

16.95

Accepts b&w or color video, 30-15,000 Hz audio. With instructions, labeled and drilled board, parts list, RF module and antenna switch. PARTS EXTRA—all available at Radio Shack. **277-122** **16.95**

Shown built with recommended parts

20-Range LCD Multimeter

79.95

- *10-Meg Input*
- *Automatic Zero-Adjust & Polarity*

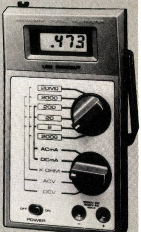

Carry Case

Only **6.95** **22-153**

Easy-to-read 0.4"-tall liquid crystal display with convenient low-battery and over-range indicators. Measures up to 500VAC in 4 ranges; 1000VDC in 4 ranges; 200 mA AC and DC current in 3 ranges each; 20 megohms resistance in 6 ranges. Size: 6¾x3¾x1¾". Leads and manual included. Requires 9V battery or AC adapter. **22-198** . **79.95**

AC Adapter. U.L. listed. **273-1431** **4.95**

Resistor Packs

100-Piece Assortments **2.99** Each

Great buy—keep a pack on hand! The most asked for values.

½W-10%. 271-306 Pkg. 100/2.99
¼W-5%. 271-308 Pkg. 100/2.99

Quad BiFET Op-Amp

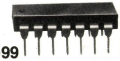

2.99 *13V/µS Slew Rate*

TL084C. Low-noise JFET inputs. Internally compensated. ±18V supply. 14-pin DIP. **276-1714** **2.99**

DPDT Switch

34% Off!

Reg. 3.19 **2.09**

Compact lever-type with contacts rated 6A at 125VAC. Mounts in 7/16" hole. **275-259 Sale 2.09**

6-Amp Triacs

Low As **99¢**

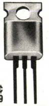

For lamp dimmers, heat element control, AC switching and more. TO-220 cases.
200V. 276-1001 . . . . **99¢**
400V. 276-1000 . . . . **1.19**

Card Connector

17% Off!

Reg. 5.95 **4.95**

40-pin insulation displacement type for digital boards. **276-1558** . . . **Sale 4.95**

Metal-Film Capacitors

Low As **39¢** Each

250WVDC. Aluminum deposited mylar for ultra-low leakage. Epoxy dipped for stability.

µF	Cat. No.	Each
.01	272-1051	.39
.047	272-1052	.49
.1	272-1053	.59
.22	272-1058	.69
.47	272-1054	.79
1.0	272-1055	.89

Micronta® Precision Panel Meters

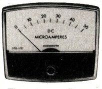

8.95 Each

These top-quality meters allow you to monitor critical circuits. Feature easy-to-read faces and D'Arsonval movements for ±5% accuracy, full scale. Require 1⅞" mounting hole.
0-50 µA DC. 270-1751 . . . . **8.95**
0-1 mA DC. 270-1752 . . . . . **8.95**

Micro Test Clips

NEW! *Package of 2* **1.49**

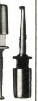

Insulated push-type—ideal for testing components on crowded boards. One red, one black. **270-370** . . . . . **Pkg. of 2/1.49**

Quad Timer IC

33% Off!

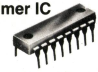

Reg. 2.99 **1.99**

Type 558. Four type 555 timers in a single 16-pin DIP. **276-1742** . . . **Sale 1.99**

Mini Amp with Built-In Speaker

Only **11.95**

- *200 mW Output*
- *1 mV Sensitivity*
- *10 to 10,000 Hz Response*

This compact, integrated-circuit amplifier with built-in speaker is ideal for use with a telephone pickup coil, a microphone or electric guitar. Use it as an intercom, the audio stage of a receiver project—or add a probe and it becomes a handy signal tracer! Has volume control with on/off switch, ⅛" jacks for input and external speaker or earphone. 2½x3⅞x1¾" molded case. Requires one 9V battery. **277-1008** **11.95**

12VDC Reed Relay

Only **99¢**

DPST. Encapsulated type with PC pins. Contacts rated 0.5A at 125VAC. 1⅛x9/16x7/16". **275-229** . . . . **99¢**

16K Hobby RAM

Cut $8

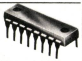

Reg. 13.95 **5.95**

4116 Dynamic RAM. 100% prime. Our lowest price ever! **276-2505** . . . **Sale 5.95**

Voltage Regulator

4.99

LM317. Adjustable, positive. Up to 1.5A output. TO-3 case. **276-1777** . . . . . **4.99** *1.2 to 37VDC*

Mercury Switch

NEW! 1.19

Tilt to close circuit. SPST contacts rated 5A at 125VAC. Wire leads. Style may vary. **275-027** **1.19**

Start Your Next Project at The Shack®

Radio Shack®

A DIVISION OF TANDY CORPORATION • FORT WORTH, TEXAS 76102
OVER 8000 LOCATIONS WORLDWIDE

Retail prices may vary at individual stores and dealers

BY M. T. VALESCU

AN APPLIANCE "OFF" REMINDER

A low-cost project provides an audible alert when an appliance indicator light goes off

IT IS often useful—sometimes vital—for the user of an appliance to know if and when it ceases to operate, whether by design or due to a power failure. Usually, this is not difficult to accomplish, since most appliances are equipped with indicator lights that show when they are working. But if the appliance is not in direct view, keeping track of it can be a great annoyance.

One solution to this problem is to use an electronic "eye" that senses the radiation from the indicator light and sounds an alarm when it is interrupted. For convenience, only the sensor is required to be physically at the monitoring point; the alarm can be located where it is easily heard.

The Lights-Out Alert described here provides the answer. It is battery powered and reliable; can be built from low-cost components; and is usable with almost any sort of power-on light indicator.

Circuit Operation. As shown in Fig. 1, phototransistor *Q1* and Darlington-connected *Q2* form a high-gain optical-to-electrical transducer that drives a charge pump made up of *Q3* and *Q4* and associated components.

When no light strikes *Q1*, its resistance should be high enough so that *Q2* is cut off. Any slight leakage from *Q2* should produce less than 0.7 volt across *R1*—not enough to turn on *Q3*. Assuming that capacitor *C1* has been discharged by the operation of *S1*, *Q4* also lacks the voltage required to turn it on. Thus, all four transistors are off and current from the battery is almost nil.

When light strikes *Q1*, its resistance drops, depending on the illumination level, and *Q2* is turned on. The voltage developed across *R1* turns *Q3* on provided *C1* is discharged. Thus *Q4* is driven deeper into cutoff. Current flows through *Q3* and *R2* to charge *C1*. When the voltage across *C1* rises to within 0.7 volt of that across *R1*, *Q3* is cut off. This condition will last as long as transistor *Q1* is illuminated.

When the illumination ceases, the voltage across *R1* drops. Since *C1* is charged high enough to reverse-bias *Q3*, this transistor cuts off and turns on *Q4*. Discharge current from *C1* now flows through *R2* and *Q4* to drive alarm *A1*.

After some time (about one minute per 10,000 microfarads of *C1*), *C1* becomes discharged and the alarm turns off. The circuit is then ready for the next illumination period, with no current drawn from *B1*. Switch *S1*, in conjunction with *R3*, provides manual silencing of the alarm. This switch should not be operated during the charging cycle of *C1* because this will tend to deplete the battery's charge.

Construction. The circuit consists of two physically independent sections—the light-sensitive portion and the alarm/power package, with the two interconnected by a length of flexible four-conductor cable.

The four transistors and two resistors that form the photosensor can be assembled on a small piece of perforated board or a small printed-circuit board. Make sure that the sensitive face of *Q1* is in the clear so that light can pass through a hole in the case and shine on this surface. Select a low-leakage device for *Q2*. If phototransistor *Q1* is a low-gain device (units vary with manufacturer), increase the value of *R1*. However, to avoid false alarms do not make the circuit too sensitive.

The board can be mounted in a small enclosure having a hole drilled so that external light can fall on the sensitive face of *Q1*. Another small hole can be used for the four-conductor cable. The alarm/power elements are mounted in a separate enclosure with holes near the alarm so that it can be heard.

To test the project, expose the photosensitive surface of *Q1* to an ordinary household light bulb at a distance of about 18 inches. When the light source is removed, the alarm should sound for approximately one minute. Changing the value of *C1* changes the alarm-on time. The alarm can be silenced by operating switch *S1*. ◇

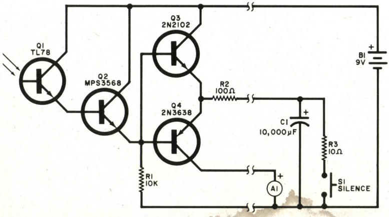

Fig. 1. Phototransistor Q1 senses when the light impinging on it goes off. The signal is then amplified to energize alarm A1.

PARTS LIST

A1—Alarm (Sonalert SC628 or similar)
B1—9-volt battery
C1—10,000-μF, 10-V capacitor (see text)
Q1—TL78 phototransistor (Radio Shack FPR-100)
Q2—MPS3568 transistor (Radio Shack S0015)
Q3—2N2102 transistor (Radio Shack S5026)
Q4—2N3638 transistor (Radio Shack S0029)
R1—10,000-Ω, ¼-W resistor
R2—100-Ω, ¼-W resistor
R3—10-Ω, ¼-W resistor
S1—Normally open pushbutton switch
Misc.—Length of four-conductor cable, suitable enclosures, perf board, printed-circuit board, mounting hardware, etc.

ALL THE PROGRAMS YOU'LL EVER NEED. FOR $600.

Say goodbye to the costs and frustrations associated with writing software: The Last One® will be available very soon.

More comprehensive and advanced than anything else in existence, The Last One® is a computer program that writes computer programs. Programs that work first time, every time.

By asking you questions in *genuinely* plain English about what you want your program to do, The Last One® uses those answers to generate a totally bug-free program in BASIC, ready to put to immediate use.

What's more, with The Last One,® you can change or modify your programs as often as you wish. Without effort, fuss or any additional cost. So as your requirements change, your programs can too.

In fact, it's the end of programming as you know it.

And if, because of the difficulties and costs of buying, writing and customising software, you've put off purchasing a computer system up to now, you need delay no longer.

The Last One® will be available very soon from better computer outlets. To place your order, take this ad into your local dealer and ask him for further details. Or in case of difficulty, please write to us direct.

THE LAST ONE®

YOU'LL NEVER NEED BUY ANOTHER PROGRAM.

D. J. 'AI' Systems Ltd., Ilminster, Somerset, England TA19 9BQ. Telephone: 011-44-4605-4117. Telex: 46338. ANYTYR G.

CIRCLE NO. 63 ON FREE INFORMATION CARD

SOLID-STATE DEVELOPMENTS

By Forrest M. Mims

Jellybean Op Amps

THE semiconductor industry makes many different kinds of operational amplifiers. Those companies that specialize in high performance or precision op amps, however, lump the mass-produced, inexpensive op amps into a catch-all category—*jellybeans.*

One of the most popular jellybean op amps is the 741/741C. This chip was introduced by Fairchild in 1968 as a successor to that company's μA709, the industry's first widely accepted op amp on a chip. The μA741 was also intended to compete with National Semiconductor's entry into the op amp market, the LM301. Unlike the μA709 and the LM301, the μA741 boasted an on-chip compensation capacitor. The other two required the use of external frequency compensation.

When the μA709, LM301 and μA741 were first introduced, they were considered major breakthroughs in semiconductor technology. They quickly became very popular among design engineers, who found that they could replace a number of discrete transistors and their associated passive components with a single chip, and a small handful of external components.

Fairchild's 1965 data sheet for its μA709C, the commercial version of the 709, billed the device as a "High Performance Operational Amplifier." In those days, "high performance" meant a minimum input impedance of 50 kilohms, a minimum open-loop voltage gain of 15,000 and a typical input-offset voltage (V_{os}) of two millivolts.

The μA741C offered even better performance. Its minimum input resistance was 300 kilohms (2 megohms typical), its minimum open-loop voltage gain was 50,000 (200,000 typical) and its typical V_{os} was one millivolt. Like the μA709C, the μA741C was designated a "high performance" operational amplifier.

Both the 709 and 741 (as well as other early op amps) are still in widespread use. They're cheap, readily available, and appear in hundreds of time-tested circuits in the literature

Operational-amplifier technology, however, has hardly stood still in the 13 years since the 741 was introduced. There now exists a wide range of op amps whose specifications are far superior to those of the old standbys.

These new devices are called *precision* or *high-performance* op amps to distinguish them from the 709, 741, 301 and the other general-purpose op amps, all of which now fall into the unglamorous category of jellybeans.

Precision op amps have considerably greater frequency responses than earlier chips. Devices with FET input stages can provide input impedances as great as 10^{12} ohms. Input-offset voltages can be as low as tens of microvolts. Not every op amp offers such exceptional performance in every category, but today's op amps are far more worthy of being termed high-performance devices than were their predecessors.

Experimenters have generally avoided using high-performance or precision op amps because of their cost. Jellybean chips like the 709 and 741 can be purchased for as little as 35 cents each, but precision op amps have sold for as much as $10 or more. Inevitably, however, the superior characteristics of precision and high-performance op amps have stimulated increased demand. More manufacturers have begun making such chips, and prices have begun to fall.

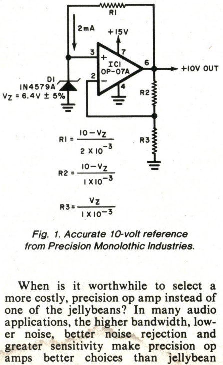
R1
2mA
+15V
3
7
+
IC1
OP-07A
6
2
−
4
+10V OUT
D1
1N4579A
V_Z = 6.4V ± 5%
R2
R3
$R1 = \frac{10 - V_Z}{2 \times 10^{-3}}$
$R2 = \frac{10 - V_Z}{1 \times 10^{-3}}$
$R3 = \frac{V_Z}{1 \times 10^{-3}}$

Fig. 1. Accurate 10-volt reference from Precision Monolothic Industries.

When is it worthwhile to select a more costly, precision op amp instead of one of the jellybeans? In many audio applications, the higher bandwidth, lower noise, better noise rejection and greater sensitivity make precision op amps better choices than jellybean chips. All of these advantages are equally desirable in instrumentation-amplifier applications.

Perhaps the best way to appreciate the advantages of precision op amps over the jellybean variety is to see how they are used in actual circuits. Precision Monolithic Industries (PMI), a leading manufacturer of precision analog integrated circuits, has published a number of application notes for its line of precision op amps. Note AN-13, by Donn Soderquist and George Erdi, is a detailed treatment of PMI's OP-07, a bipolar op amp with an input-offset voltage of only 25 microvolts. This ultra-low V_{os}, which eliminates the need for an offset-nulling potentiometer, is achieved during manufacture by a one-time, computer-controlled adjustment of an on-chip trimming network.

The circuit in Fig. 1 is a highly stable 10-volt reference described in AN-13. A 741 could be used in this circuit, but relatively frequent recalibration of an offset trimmer potentiometer would be required because of long-term drift of the 741's V_{os}. Long-term drift of the OP-07 is only about one microvolt per month, about 1% of that of the 741.

The circuit in Fig. 2, which is also from AN-13, is a precision large-signal voltage buffer with a worst-case accuracy of 0.005 percent. This high degree of accuracy is due to the ultra-low V_{os} of the OP-07 and the total absence of external components. See AN-13 for more details.

You can find out more about precision and high-performance op amps by contacting manufacturers. Some of the leading ones are: Advanced Micro Devices (901 Thompson Place, Sunnyvale, CA 94086); Fairchild Semiconductor (464 Ellis St., Mountain View, CA 94042); Harris Corporation (P.O. Box 883, Melbourne, FL 32901); Intersil (10710 N. Tantau Ave., Cupertino, CA 95014); Motorola (Box 20912, Phoenix, AZ 85036); National Semiconductor (2900 Semiconductor Drive, Santa Clara, CA 95051); Precision Monolithic Industries (1500 Space Park Drive, Santa Clara, CA 95050); RCA (Route 202, Somerville, NJ 08876); Raytheon (350 Ellis St., Mountain View, CA 94042); Signetics (P.O. Box 409, Sunnyvale, CA 94086) and Texas Instruments (P.O. Box 5012, Dallas, TX 75222).

Several excellent books on operational amplifiers are also available.

SUPER DISCOUNTS ON ALL COMPUTER EQUIPMENT

16K MEMORY .... ONLY $25.95! For **TRS-80** Keyboard or Expansion interface. KEYBOARD requires jumpers: $2.00 Extra. These are 200 ns tested RAM for the **TRS-80, APPLE** or **EXIDY.**

DISK DRIVES for the TRS-80 OR PMC-80:

All of our drives come complete with power supply and chassis. They may be used with existing Radio Shack drives on the same cable! 40 track drives store 102K bytes single density, and 175K double density. 80 track drives have 175K single density and 345K double density! All drives guaranteed 90 days, one year on power supply.

40 track MPI drives	**$319.95**
40 track TEAC drives	**$315.95**
40 track TANDON drives	**$319.95**
80 track MPI drives	**$449.95**
80 track TEAC drives	**$429.95**
2 drive cable	**$ 25.95**
4 drive cable	**$ 39.95**
NEWDOS 80 OPERATING SYSTEM	**$139.95**
NEWDOS 80 PATCH Patches **NEWDOS 80** to work with single or double density and the doubler	**$ 59.95**
PERCOM'S DOUBLER for double density operation!	**$219.95**

The **DOUBLER** works with the **TRS** or **PMC** expansion interfaces to allow you to use your drives in double density! You may still operate your drives as single density also! Comes with **DBLDOS** operating system which allows you to transfer single density files to double and vice versa! *GREAT BUY!*

DISKETTES: VERBATIM DATALIFE! *BOX OF TEN* SOFT OR HARD SECTORED 5¼′ **$32.50**

WE HAVE DRIVES AND CONTROLLERS FOR THE MODEL III. CALL FOR PRICES!!!

MODEMS AND TELE-COMMUNICATIONS

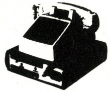

LYNX Telecommunication system for the TRS-80 and PMC-80 ....$279.95
Includes terminal software and connections for instant hookup! Can be connected to the **TRS-80** or **PMC-80** with or without an expansion interface!

LEXICOM MODEM 300 BAUD Requires RS-232	**$169.95**
THE SOURCE: Hook-up to the "SOURCE"	**$ 99.95**
ATARICONNECTION: Modem for 400/800, complete with software!	**$249.00**
APPLECONNECTION: Modem for APPLE II	**$279.95**

COMPLETE SYSTEMS:

PMC-80, 16K LEVEL II COMPUTER $739.00
The **PMC-80** is a work alike to the **TRS-80** mod I computer! Comes with Microsoft's **BASIC** in ROM. Built in cassette. 12″ green screen video monitor. Expandable to 48K.
Compatible to All **TRS-80 MOD I Programs.**

PMC 80 without monitor	**$595.00**
RF—MOD for PMC to TV hookup	**$39.95**
PMC-80 EXPANDER 100 SYSTEM	**$644.00**

INCLUDES: 32K memory, S-100 bus, RS-232 interface, Parallel printer driver, Disk controller. Fully compatable with **TRSDOS, NEWDOS, VTOS,** and all other **TRS-80 Mod I disk software!**

APPLE II COMPUTERS 16K	**$1195.00**
APPLE II COMPUTERS 48K	**$1299.00**
ATARI 400	**$ 495.95**
ATARI 800 COMPUTER	**$ 795.00**
ZENITH Z-89 48K, 1 DISK ALL IN ONE COMPUTER	**$2495.00**

VIDEO MONITORS

LEEDEX 100 12′ B/W MONITOR	**$139.95**
SANYO 9′ B/W MONITOR	**$199.95**

PRINTERS

OKIDATA MICROLINE 80 All OKI'S have TRS-80 Graphics!!! .... $ 499.00
Comes with friction and pin feed. upper/lower case, Graphics.

EPSON MX-80 PRINTER: Word Processing Quality Printout with Graphics!	**Call**
NEC SPINWRITER with Tractor Feed	**$2995.00**
DIABLO MODEL 1630 with Tractor	**$2695.00**
UNIVERSAL PRINTER STANDS	**$ 94.50**

Other Accessories:

SUP-R-MOD RF Modulator for APPLE	**$29.95**
ARCHBOLD SPEED-UP MOD FOR TRS MOD I. Allows up to 300% increase!	**$45.00**
MICROSOFT BASIC Decoded and other mysteries	**$29.95**
TRS-80 DISK and other mysteries	**$18.95**

ZBASIC BASIC COMPILER for MOD I and MOD III TRS-80 and PMC-80 Increase basic program speeds by up to 200 times!!!!!
Tape .... $79.95 Disk $89.95

Both For Only $99.95 Specify MOD I or MOD III

WE HAVE HUNDREDS OF PROGRAMS FOR ALL THE POPULAR COMPUTERS! CALL FOR OUR FREE CATALOG

Personal and Business Checks take 3 weeks to clear. For fastest delivery use Certified Checks, Money Orders, Credit Card, or C.O.D.

We will try and beat any published price on any system! Call!

SIMUTEK
COMPUTER PRODUCTS ™

4877 E. Speedway Blvd.
Tucson, Arizona 85712
(602) 323-9391: Technical Questions

CALL TOLL FREE TO ORDER
(800) 528-1149
Please mention this magazine when ordering
ARIZONA RESIDENTS ADD 6% SALES TAX.
WE TAKE VISA, MASTER CARD.

TRS-80 IS A TRADEMARK OF RADIO SHACK, A TANDY CORP. APPLE IS A TRADEMARK OF APPLE, INC.

Walter Jung has written two of them. The *IC Op Amp Cookbook* (Sams, 1975) covers just about everything you need to know about op amps in 591 pages. His *Audio IC Op Amp Applications* (Sams, 1978) is limited to audio uses for op amps.

Another excellent all-round book on op amps is David Stout's *Handbook of Operational Amplifier Circuit Design* (McGraw-Hill, 1976). This book is more expensive than the Sams volumes. If it's beyond your budget, you can probably find it at a well-stocked technical or engineering library.

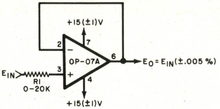

Fig. 2. A precision large-signal voltage buffer using an op amp.

More About Super LEDs. "Solid-State Developments" for February 1981 highlighted the new generation of (AlGa)As super LEDs which have twice the power output of comparable GaAs:Si LEDs. Several such LEDs made by Xciton were described.

I've since heard from Rich Fassler of General Electric that his company was the first to introduce commercial grade (AlGa)As LEDs. According to Rich, ". . . Xciton saw the light and followed *our lead* (please note the 11/78 date on our spec sheet)."

GE's (AlGa)As LEDs come in lensed (D suffix) and flat-window (E suffix) versions. The F5D1 and F5E1 emit at least 12 milliwatts at 100 milliamperes forward current. The power outputs at 100 miliamperes for the F5D2/F5E2 and F5D3/F5E3 are 9 and 10.5 milliwatts, respectively.

Figure 3 compares the optical output from the F5D1/F5E1 LEDs with that from GaAs:Si 1N6264/1N6265 emitters. Xciton's best (AlGa)As LED is the XC-88-FD (flat window) or XC-88-PD (lens). Its output is essentially identical to that of the GE diodes of the same type.

For some information and current pricing, contact a GE electronic-component sales representative or write to General Electric Semiconductor Products, West Genesee Street, Auburn, NY 13201. Xciton's address is Shaker Park, 5 Hemlock Street, Latham, NY 12110.

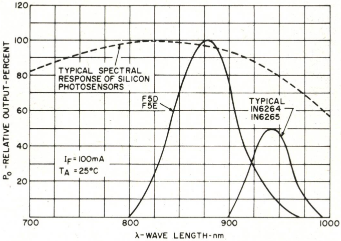

Fig. 3. Power output versus wavelength for General Electric's (AlGa)As LEDs.

Fighting Static Discharge. Regular readers of this column are well aware that certain solid-state devices are susceptible to damage from electrostatic discharge. Particularly vulnerable are CMOS ICs and those components with ultra-small active areas such as double-heterostructure lasers and tunnel diodes.

Manufacturers sometimes ship components and circuit boards that are vulnerable to electrostatic damage in antistatic polyethylene bags known as "pink poly." Ordinary polyethylene bags can develop surface potential gradients of many hundreds of volts from external friction or simply the movement of components inside the bag.

Although antistatic bags do prevent static-charge buildup, they do not prevent external, charged objects from discharging through the bag and across the terminals of sensitive components. Accordingly, last May, the Department of Defense issued a new standard requiring packaging that will not generate static charges *and* will protect against external fields and discharges.

3M Static Control Systems now

POLY PAKS
FREE!
1981
DISCOUNT
ELECTRONICS
CATALOG

JOIN THE PAK!

Send for our Free catalog and become a member of our exclusive Pak. Our members receive Poly Paks' exciting catalog several times a year. We offer: Penny Sales, Free Premiums and Low, Low Prices on a wide variety of Electronic Products such as Computer Peripherals, Integrated Circuits, Speakers, Audio Equipment, Rechargeable Batteries, Solar Products, Semiconductors, and much, much more! Take advantage of our 25 years as America's foremost Supplier of discount electronics.

Over 4.5 Million Satisfied Customers

RUSH ME YOUR FREE DISCOUNT CATALOG!
NAME: ____
ADDRESS: ____
CITY: ____
STATE: ____ ZIP: ____

CLIP AND MAIL COUPON TODAY TO:
POLY PAKS, INC.
P.O. BOX 942, PO6
S. LYNNFIELD, MA. 01940 (617) 245-3828

CIRCLE NO. 48 ON FREE INFORMATION CARD

IMPROVE YOUR COST/PERFORMANCE RATIO 3 DB*
PUT YOUR MONEY WHERE IT REALLY COUNTS, IN QUALITY
COMPONENTS AND A HIGH PERFORMANCE DESIGN.
BUY A PHOENIX SYSTEMS KIT.

FOR SALE: PRICE INCLUDES SHIPPING
PARAMETRIC EQUALIZER KIT .... P-94-S $ 99.00
ANALOG DELAY LINE KIT (MONO) P-25-DL $150.00
(STEREO) P-25-SDL $250.00
TAPE NOISE REDUCTION KIT .... P-518-S $ 65.00
HP/LPF (—12db/OCT) .... P-91-S $ 15.00
SAD-4096 ASR .... P-4096 $ 45.00

SEND FOR SPECS/CATALOG
PHOENIX SYSTEMS/91 ELM ST./MANCHESTER, CT 06040
*3DB FIGURE BASED ON APPROXIMATE DOUBLING OF DBS (DOLLAR POWER) (203) 643-4484

CIRCLE NO. 45 ON FREE INFORMATION CARD

makes such a bag. It consists of an inner layer of antistatic polyethylene and a polyester strength layer coated with a 10-micron-thick film of nickel. According to 3M, the nickel film provides "full Faraday cage protection from external static charge." These new bags cost some 15 cents more than ordinary antistatic bags, but 3M claims that one company is already saving some $2500 on each shipment of 100 circuit boards by using the new bags. Previously, as many as half the firm's boards were reportedly damaged by static discharge during shipment!

This new product serves as a reminder of the care one must exercise when working with components vulnerable to static damage. The best protection is to make sure all leads of vulnerable components and chips are shorted together. This can be done by inserting them into foam plastic which is either electrically conductive or covered with one or two layers of aluminum foil.

Even assembled products can be vulnerable to static discharge damage. John Miklosz passed on a warning from Keats Pullen to readers of John's column in *Electronic Engineering Times* (Feb. 16, 1981) that the face of a digital multimeter should be cleaned with a damp cloth to avoid the buildup of a static charge which results from wiping plastic with a dry cloth. As John concluded, "The fact that wiping with a dry cloth can damage an IC *in situ* with at least 1/4 inch between the circuit board and the panel should be of concern to all of your readers."

Indeed it should. I cannot verify the need for this precaution, but will pass along the personal experiences of readers who have damaged instruments by wiping their displays with a dry cloth. My initial reaction is that relatively few instruments are vulnerable to such damage. Otherwise, not many pocket calculators and digital watches would be in working order today. ◇

"Look at this new micro-mini-switch. It's invisible to the naked eye."

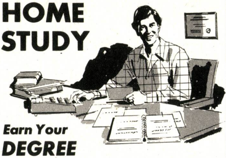

Put Professional Knowledge and a
COLLEGE DEGREE
in your Electronics Career through
HOME STUDY

Earn Your DEGREE

No commuting to class. Study at your own pace, while continuing your present job. Learn from easy-to-understand lessons, with help from your home-study instructors whenever you need it.

In the Grantham electronics program, you first earn your A.S.E.T. degree, and then your B.S.E.T. These degrees are *accredited* by the Accrediting Commission of the National Home Study Council.

Our *free* bulletin gives full details of the home-study program, the degrees awarded, and the requirements for each degree. Write for *Bulletin ET-81.*

Grantham College of Engineering
2500 So. LaCienega Blvd.
Los Angeles, California 90034

ELECTRONIC COMPONENTS

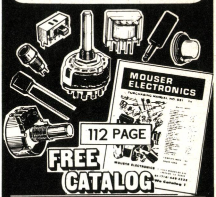

MANUFACTURERS OF QUALITY ELECTRONIC COMPONENTS

Battery Clips & Holders
Cable Sets Connectors Capacitors
Displays, LED Fuses Jacks & Plugs
Knobs Lamps Potentiometers
RF Coils Relays Resistors
Switches Semiconductors Speakers
Test Equipment Transformers Tools
Wire & Cable

WE STOCK What We Catalog !

- Sales and Order Desk Open from 6:00a.m.(PST)
- TERMS: C.O.D., Visa, MasterCharge (Open Accounts Available)
- Phone and Mail Orders Welcome
- Over 10,000 Different Items in Stock

MOUSER ELECTRONICS
11433 WOODSIDE AVE., SANTEE, CA 92071
PHONE: (714)449-2222 TWX: 910-331-1175

CIRCLE NO. 38 ON FREE INFORMATION CARD

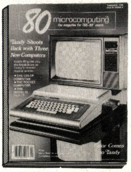

Looking for Good TRS-80* Programs?

How about ways to save hundreds or even thousands of dollars on buying accessories and software? The TRS-80* is the **only** computer with a major monthly magazine supporting it (and not published by Radio Shack, either!). 80 MICROCOMPUTING is running over 200 pages, with 30-40 articles, providing lots of programs, technical explanations, news of new products, reviews of products and software etc. You'll get many times the information available from Radio Shack. 80 MICROCOMPUTING is an encyclopedia of the TRS-80*. . . you really can't do without it.

Try it. A one year subscription is $18 (going up soon, obviously) and it will quickly save you many times that price. Send in the coupon and we'll send your first copy and an invoice. If you aren't absolutely delighted just cancel the subscription and keep the issue.

*Trademark of Tandy Corp.

☐ YES! I am looking . . . bill me $18 for one year.

Name ____________________

Address ____________________

City ____________________ State ________ Zip ________

Canadian $20/1 year only. Foreign $28/1 year only, US funds.
Please allow 6-8 weeks for delivery.
80 MICROCOMPUTING•PO Box 981•Farmingdale NY 11737

71JBP

CIRCLE NO. 16 ON FREE INFORMATION CARD

HOBBY SCENE

By John McVeigh,
Technical Editor

RS232-to-20-mA Converter

Q. ***Do you have the schematic diagram of a simple circuit that I can use to interface an RS-232 data output port to a 20-mA current-loop printer?—Michael Harbison, Falls Church, VA.***

A. The circuit shown in the figure will allow you to use your 20-mA printer with your output port. It can be assembled for next to nothing if you have a decent junk box. Even if you have to buy all the components at retail, total construction cost will be less than $5.00. Transistor type numbers are not critical—just about any garden-variety npn and pnp silicon devices can be used. Transistor *Q1* and its associated passive components function as an RS-232-to-TTL level converter. Inversion is performed by *Q2*; *Q3* is a keyed 20-mA current source. Power for the circuit can usually be tapped from one of the system components. Current demand is very small.

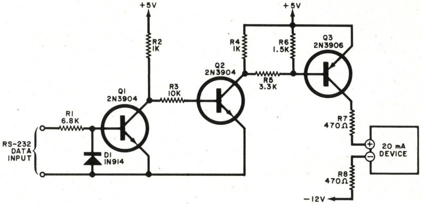

Open-Collector Logic

Q. ***What is the difference between "normal" TTL gates such as the 7400 or***

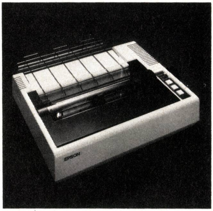
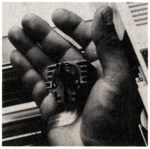
The printer you always wanted but could never afford, now you can afford. Epson.

The most revolutionary thing about the Epson MX-80 isn't the bidirectional printing or the logical seeking function. It isn't even the disposable print head—although that's pretty revolutionary. The most revolutionary thing about the MX-80 is the price. How, you may ask, could a printer that does as much as the MX-80 cost less than $650?

Frankly, it wasn't easy. But the MX-80 could only have come from the world's largest manufacturer of print mechanisms. Epson.

The world's first disposable print head. When it wears out, just throw it away. A new one costs less than a third the price of conventional heads, and you can install it yourself with one hand.

We spent three long years designing the MX-80 from the ground up to have all the functions people wanted, to be reliable like all Epson Printers, and to be produced on a scale that would allow us to charge less for each one. The MX-80 is our proof that it can be done.

Among its features, the MX-80 prints 96 ASCII, 64 graphic and eight international characters in a tack-sharp 9x9 matrix. It prints bidirectionally at 80 CPS with a logical seeking function to maximize throughput. And it has the world's first *disposable* print head.

If you've ever wanted a printer that could do it all at a price you could afford, you've got to see the Epson MX-80.

Because seeing is believing.

EPSON
EPSON AMERICA, INC.
23844 Hawthorne Boulevard, Torrance, California 90505 • Telephone (213) 378-2220

CIRCLE NO. 18 ON FREE INFORMATION CARD

7404 and "open-collector" gates such as the 7401 and the 7405?—Edward Cassidy, Los Angeles

A. Shown at (A) in the figure is the schematic diagram of a standard 2-input TTL NAND gate (type 7400). Two noteworthy characteristics of this gate are *Q1*, the multiple-emitter input transistor, and the *totem pole* output comprising *R4, Q3, D1* and *Q4*. When either input A or B is at logic 0, *Q1* saturates, cutting off *Q2* and *Q4*. Transistor *Q3* acts like an emitter follower and couples a logic 1 to the output. When both inputs are logic 1, forward current through the base/collector diode of *Q1* forces *Q2* and *Q4* into saturation, resulting in a logic-0 output. Diode *D1* prevents *Q3* from conducting when *Q4* is saturated by decreasing the base-to-emitter voltage drop to a value below the turn-on threshold of the transistor.

The major advantage of the totem-pole output is its low output impedance. When *Q3* is conducting, it acts as an emitter follower with an equivalent (Thevenin) output impedance of 70 ohms. When *Q4* is saturated, it has an equivalent (Thevenin) output impedance of approximately 12 ohms. In either case, the output impedance is low. This makes it possible to avoid excessive loading when it is connected to other TTL gates. A low output impedance also keeps switching speeds high. The voltage at the output of the gate cannot change state until all load and stray capacitances have been charged or discharged. Because the gate's output impedance is low in either state, the overall RC time constant is small and the output can change rapidly.

Shown schematically at (B) is an open-collector 2-input TTL NAND gate (type 7401). It lacks a totem-pole output. The gate will not work unless a *pull-up resistor* is connected externally between its output (the collector of *Q3*) and the positive supply voltage. Transistor *Q3* provides active pull-down when its saturates (as *Q4* does in the gate shown at A). However, when it cuts off, there is no upper transistor to pull up the output voltage. Any load and stray capacitances have to charge up through the pull-up resistor. Because the charging occurs through a passive component, the transition from logic 0 to logic 1 is called "passive pull-up." The value of this pull-up resistor is typically hundreds or thousands of ohms, so passive pull-up is considerably slower than active pull-up. This makes passive pull-up unsuitable for certain applications.

There is one principal advantage of open-collector logic. The outputs of a number of similar gates can be tied together through a common pull-up resistor. This direct connection produces the effect of an AND gate and eliminates the need for a separate AND gate. This application is sometimes called *WIRE-AND* logic, or, because of an elementary principle of Boolean algebra (DeMorgan's first theorem), *WIRE-OR* logic. ◇

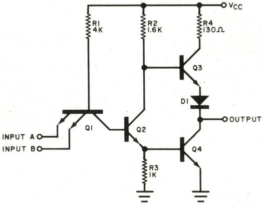

A

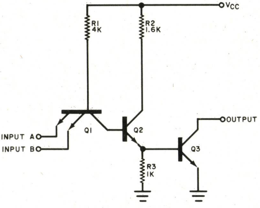

B

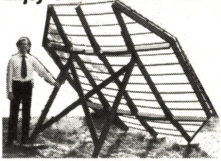

Enjoy SATELLITE TV Now

Save thousands of dollars!
Now you can choose from three complete systems, which have the same superb electronics. Prices are: 10 ft. dish **$2495,** 13 ft. dish **$2595,** and our 16 ft. (5 m.) dish system for only **$2695.** Complete system has dish antenna, feed horn, polarity rotor, LNA, cables, receiver and TV modulator—everything. Why pay more? Our 16 ft. system will outperform any 10 ft. system—even those costing thousands of dollars more. Satellite TV is so much better than simple Cable TV. More selection, news, movies, sports, Vegas shows, Spanish, French, Russian, religious, plenty of family and adult entertainment. Over 20 program services on just one satellite. You get perfect color and crystal clear reception, especially with our larger dishes that connect to any TV set. And to a whole condo or apartment complex! Have your local dealer install one or do-it-yourself in a weekend.

Don't wait any longer. Our big (8×11 in.) Handbook is loaded with details, photos, aiming data, and signal strength maps. Explains how much system you need. For the do-it-yourselfer, we show where to find full schematic plans and circuit boards. **Satisfaction Guaranteed.**

GLOBAL TV ELECTRONICS, INC.
235 S. Maitland Avenue
P. O. Box 219-K, Maitland, Florida 32751

Send $7.95 Today! Add $2.00 for first class (airmail). Canadian send $10.10 US or $12.50 Canadian, Foreign send $12.00 US funds - airmail only. Or in the USA, call our 24 hour C.O.D. order line **1-305-862-5068** now.

Name ____________________
Full Address ____________________
____
____________ Zip/PC ________

EXPERIMENTER'S CORNER

By Forrest M. Mims

Do-It-Yourself Batteries

YOU can conduct a fascinating demonstration of electrical power generation by chemical means with a silver coin, a strip of magnesium and a piece of paper towel the size of a postage stamp. Dip the paper in lemon juice, place it over the coin and lay the magnesium strip on the paper. Then touch the cathode lead of a red LED to the magnesium. When the LED's anode lead is touched to the coin as in Fig. 1, the LED will glow brightly.

With the exception of the LED, this simple demonstration would have seemed fairly routine to pre-World War I experimenters. In those days many experimenters constructed their own primary and secondary (storage) cells. Commercial power cells were relatively expensive, and only a few kinds were available.

Today, literally hundreds of different kinds of batteries are available in a wide range of voltages and physical configurations. Nevertheless, for some special-purpose applications, a homemade battery may be more satisfactory than a commercial battery!

One example is powering a telemetry transmitter in an instrumented model rocket. The upward flight of such a rocket might last only a few seconds, yet a commercial battery could supply the necessary power continuously for days or even weeks. The penalty for this unnecessary capacity is excessive size and mass, both of which should be kept to a minimum.

This month, we will experiment with several electrochemical power cells that you can make from readily available materials. These cells are suitable for powering CMOS and other low-power circuits. Whether you assemble any of these cells or not, you may gain a better understanding of how conventional batteries work. If you do build cells of your own, you will certainly gain an appreciation for the convenience and drip-free operation of commercial power cells and batteries.

Some Definitions. Before proceeding any further, it is important to define a few basic terms:

Anode—The negative electrode of a cell.
Battery—Two or more electrically connected cells.
Cathode—The positive electrode of a cell.
Cell—A single two-electrode electrochemical generator.
Electrolyte—An ionized, electrically conductive paste, gel or liquid.
Primary Cell—A nonrechargeable cell.
Secondary Cell—A rechargeable cell.
Storage Cell—A secondary cell.

Electrochemical Generators. Alessandro Volta, an Italian physicist, invented the chemical generator. In March 1800, he demonstrated two of his generators before the Royal Society in London. One, called the Crown of Cups, consisted of a circular pattern of cups containing a solution of water and salt. One strip each of silver and zinc were immersed in each cup, and the zinc strip in one cup was connected to the silver strip in the adjacent cell. This arrangement formed a series connection of *wet cells*.

Volta's second generator was a stack of alternating disks of dissimilar metals separated by disks of paper soaked in brine. This device could produce more electromotive force in a smaller space than the clumsier Crown of Cups arrangement.

The electrochemical generators invented by Volta were used with little variation until about 1860, when other kinds of cells were developed. One such cell, patented by French scientist Georges LeClanche in 1868, was the predecessor of the modern zinc-carbon *dry cell*.

The basic design of the zinc-carbon dry cell (such as those used to power radios, flashlights and toys) has remained largely unchanged for more than sixty years. Each cell consists of a zinc cup or can (the anode) filled with a moist compound whose composition has changed through the years. One 1924 recipe called for a mixture of one ounce each of zinc-chloride and ammonium-chloride, two ounces of water, and three ounces of plaster of paris, which served as a filler. Sawdust was also used as a filler material in some early cells. A

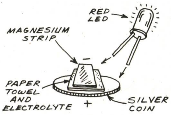

Fig. 1. An ultra-simple homemade power cell.

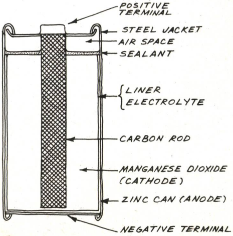

Fig. 2. Simplified internal view of a modern dry cell.

carbon rod inserted into the compound serves as the positive electrode.

The moist compound of the 1924 recipe served as the cell's electrolyte. In today's cells, the electrolyte is a paper liner impregnated with ammonium- or zinc-chloride that slides inside the zinc can. The space between the liner and the cell's carbon rod is packed with a mixture of granulated carbon and manganese dioxide. The latter compound serves as the cell's cathode. It is considered a *depolarizer* because it prevents *polarization*, the formation of an insulating layer of hydrogen bubbles around a cell's positive electrode.

Figure 2 is a pictorial view of the inner construction of a typical zinc-carbon dry cell. Most such cells are well sealed to prevent leakage which might occur should the zinc become corroded. The zinc seal also keeps the electrolyte from drying out. Drying of the electrolyte and subtle chemical reactions at the electrodes over time eventually degrade a cell whether or not it is used.

A Homemade Wet Cell. Figure 3 shows how you can make a simple wet cell from a plastic container such as a 35-mm film holder, a strip of copper and a strip of zinc. The metal strips are inserted through slits cut in the container's cap or lid. The container is then filled with an electrolyte such as salt water or lemon juice, and the cap and the electrodes are installed. This cell will produce about 0.7 volt.

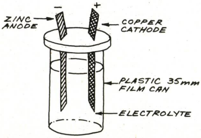

Fig. 3. Sketch of a homemade wet cell.

If you connect a voltmeter to the cell's electrodes and pull the electrodes partially out of the electrolyte, the output voltage will remain unchanged. Even when only a few millimeters of each electrode remain immersed in the electrolyte, the output voltage will remain unchanged. The cell's capacity to deliver current, however, is directly proportional to the area of the electrodes immersed in the electrolyte.

Electrode Materials. Any two dissimilar metals immersed in a suitable electrolyte will generate a voltage. Here are the voltages I measured for all possible pairs selected from the following group: a copper penny, a nickel, a silver dime, a magnesium strip, a zinc strip, and aluminum foil.

Cathode (+)	Anode (−)	Open-Circuit Voltage
Nickel	Copper	0.04
Magnesium	Zinc	0.05
Aluminum	Zinc	0.15
Silver	Nickel	0.19
Silver	Copper	0.20
Copper	Aluminum	0.70
Nickel	Aluminum	0.70
Copper	Zinc	0.72
Aluminum	Magnesium	0.78
Nickel	Zinc	0.81
Silver	Aluminum	0.84
Silver	Zinc	1.01
Nickel	Magnesium	1.44
Copper	Magnesium	1.45
Silver	Magnesium	1.65

(Continued overleaf)

POLY PAKS

Free!
Look at this fantastic offer from Poly Paks!!
BUY SEVEN JUMBO PAKS AND CHOOSE TWO FREE!!
All JUMBO PAKS PRICED AT $2.99 ea.
Indicate your free JUMBO PAKS with letter "F"

____400-PRE-FORMED ½ WATTERS, popular values, some 5 & 10%ers, ... (#6246)
____50-UPRIGHT ELECTROS. 100%, assorted values & voltages, marked........ (#3226)
____75-CABLE TIES, 4" non-slip white plastic, like Ty-wrap, ... (#5218)
____50-MINI POTS, pc style, single turn, assorted values....................... (#3345)
____150-PC. CAPACITOR SPECIAL, asst. mylars, polys, micas, etc. 100% good... (#6264)
____175-¼ WATT RESISTORS, asstd. carbons, carbo-films, some 5%ers........ (#5797A)
____125-POLYSTYRENE CAPS, assorted types, styles & sizes, all good,.......... (#2729)
____SURPRISE PAK Assortment of IC's, caps, pots and parts of every description (#6648)
____175-HALF WATTERS, 100% color coded resistors, asst. values,............ (#3046)
____175-MOLEX SOCKETS, "on a strip", make your own pc sockets,............. (#6255)
____400-PREFORMED ¼ WATTERS, assorted values, precut for PC appl.......... (#6622)
____24-MINI-BULBS, ASST. VOLTAGES & base styles, some colored. .... (#6757)
____125-LONG LEAD DISC, prime, marked caps, assorted material.............. (#2598)
____50-SLIDE SWITCHES, various shapes, sizes and types .... (#2726)
____25-MICRO MINI REED SWITCHES, 1" long, for alarms, relay systems, etc.... (#6263)
____50-THERMISTORS, various types & styles, neg. coefficient, 100% .... (#4089)
____100-DTL IC's, mostly dual JK flip flops, marked, 100% prime, ... (#6444)
____200-PRE-FORMED DISCS, caps w/leads for PC use, mixed values,............ (#2605)
____40-TRANSISTOR SOCKETS, assortment may include; TO-19,5,66,3, etc. ...... (#3845)
____50-AXIAL ELECTROS, asst. values, volts, sizes, what a buy! .... (#3227)
____100-PLESSY CAPS, ceramic blocks in assorted sizes & vlues, ... (#6221)
____3-WATCH GUTS, 5-function, LED style, assorted sizes, untested .... (#6287)
____6-TIME DELAYS, solid state, asst. from 450 mSec to 8 Sec. .... (#6758)
____65-PLASTIC TRANSISTORS, untested, to-92, asst. types..................... (#2604)
____50-TRANSISTOR ELECTROLYTICS, epoxy encapsulated, asst. values, ... (#2747)
____20-SLIDE VOLUME CONTROLS, various values & types, for Hi-Fi, etc. .... (#3057)
____500-PC.-HARDWARE SURPRISE, (approx.) 1 lb. asst. screws, washers, etc.... (#6271)
____100-POWER RESISTORS, 3 to 7 power resistors, ... (#6281)
____100-2 WATT RESISTORS, assorted carbons, films etc. some 5%ers, ... (#6238)
____10-NE-2 BULBS, w/resistors, neon, plugs right into 110VAC.................. (#6620)

6 VOLT 9 A.H. RECHARGEABLE SOLID-GEL BATTERY
- Safe, High Impact Polystyrene Case
- System Consists of Fully Gelled Lead Dioxide Electrolyte
- Top Mounted Spade Terminals

Cat. No. 6790 $15.09 Qty. ☐

LED BAR GRAPH DISPLAY
- Ideal Replacement For Analog Meters
- More Accurate Than Traditional Meters
- Uses Include: VU Meters, Power Level indicators, SWR Meters and More!

Unit consists of 10 bright Red LED's encased in a 1 3/8" x 1/4" x 3/4" plastic enclosure, and terminating in 3/16" PC-style leads. Common Anode device operates on 2V max. ' between 20-265mA. Requires driver circuitry appropriate for intended application (not included). Comes with hookup instructions & typical driver circuit schematic.
$5.98 ea. 2 for $11. Cat. No. 6922 Qty. ☐

"BLOCK" FANS
- 115 VAC • 15 WATTS
- ONLY 4-11/16" SQ.
- 1-1/2" DEEP!
- 75 CFM OR BETTER

Cat. No. 3108
$11.88 2/$23 Qty. ☐

ULTRASONIC TRANSDUCER SET
- Build your own burglar alarm
- Set includes 1 receiving and 1 transmitting transducer

Tiny element measures only 5/8" in diameter, and can be mounted virtually anywhere. A "must have" item for hobbyists everywhere.
$10. per set Qty. ☐
$19.50 for 2 sets Qty. ☐
Cat. No. 6876
Transmitting transducer only. Cat. No. 6951 $5. Qty. ☐

TOXIC GAS TRANSDUCER
- Indispensable In Trailers & Motor Homes
- Ideal Bilge Monitor For Boats!

The Figaro Toxic Gas Sensor utilized advanced semiconductor technology to provide detection, and subsequent warning of toxic gases such as carbon monoxide, methane, natural gases, LPG, butane, etc. Long Life (up to 10 years). High Reliability, and compact dimensions (only 5/8" dia. x 3/8". Requires a stabilized 5V heater supply and circuit voltage not exceeding 24 volts. Comes with complete specs and hookup instructions. Order Today!
Cat. No. 6836
$7.95 ea. 2 for $15.00 Qty. ☐

PANA-VISE WORK STATION
PANAVISE tilts, turns, and rotates. One quick turn of the control knob and you securely position your work exactly where you want it.
ONLY $29.95 Cat. No. 6434 Qty. ☐

MOTOROLA AM AUTO RADIO
Features include: 5-station pushbutton tuning, concentric control knobs for; ON/OFF/VOLUME & SPKR BALANCE/MANUAL TUNING, as well as an attractive black faceplate with chrome-colored trim. Requires 12 VDC, Neg. Gnd., 4 to 8 ohm speakers.
$16.88 Cat. No. 6920 Qty. ☐

ELECTRONIC COMPUTER GAME BOARD
- Free Case With Every Purchase
- 4 Different Skill Levels
- Electronic Lights & Sounds
- Includes Microprocessor Chip, plus all Necessary Circuitry& Components
- Fully Assembled in Case
- Game plays like "SIMON or EINSTEIN"

Board size: 4¾" x 2". Case size: 8¾" x 3¾" x 3¾".
$8.49 ea. 2 for $16. Cat. No. 6913 Qty. ☐

POLY PAKS®
P.O. BOX 942, PE-6
S. LYNNFIELD, MA. 01940

Total Amount of Order $ ____________

INCLUDE SHIPPING AND HANDLING: U.S., ADD $3.; FOREIGN, ADD $7. MASS. RES. ADD 5% SALES TAX.

NAME ____________
ADDRESS ____________
CITY ____________
STATE ________ ZIP ________
Enclosed is ☐ CHECK, ☐ MONEY ORDER
Charge my ☐ MASTERCARD ☐ VISA
ACCT. # ____________ EXP. DATE ____
Order By Phone 1-617-245-3828

ORDERING INSTRUCTIONS • Indicate quantity on line or box near item desired • Complete coupon section • Cut out Ad and mail to Poly Paks, Inc.
■ Send me your FREE catalog

CIRCLE NO. 47 ON FREE INFORMATION CARD

For these measurements, I used as a combined electrolyte and separator several layers of paper towel soaked in salt water. The values you measure may differ slightly from mine, particularly if you use an acid electrolyte, in which case the values will be higher.

Note that the highest voltages are produced by pairing magnesium with nickel, copper or silver. Nickel and copper can be found in pocket change, but silver coins have not been minted in the U.S. since the mid-Sixties and are rarely found in everyday circulation. You can purchase magnesium strips at toy and hobby shops that sell Perfect brand chemicals.

Magnesium is highly reactive. I tried a magnesium strip in a lemon-juice wet cell and found that although the cell could easily power a LED, the magnesium was soon covered by a frothy layer of hydrogen bubbles. The cell functioned well in spite of the bubbles until the reaction with the citric acid in the lemon juice coated the magnesium with a black film.

Zinc is the next-best substitute for magnesium. You can get free zinc by cutting open a discarded zinc-carbon flashlight cell. If the cell is covered by an outer steel jacket, use pliers or diagonal cutters to peel it off. Be careful! The edges of the metal envelope will be very sharp.

When the zinc can has been exposed (it may be covered with a layer of paper or black pitch), secure the cell in a vise and use a hacksaw to remove the top half-inch of the cell. Remove the carbon rod, the filler compound and the electrolyte-impregnated paper liner from inside the can. The carbon in the compound will stain clothing, so be careful. Watch out for the sharp edges of the zinc can and clean any remaining compound from the can with detergent, water and an old toothbrush.

When the zinc is clean, use a file to remove the sharp edges left by the hacksaw. Then cut the can into strips with shears or a nibbling tool. Remove any corrosion from the strips with sandpaper.

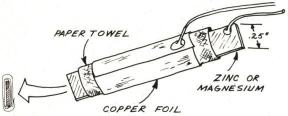

Fig. 4. How to make a simple 1.45-volt "moist" cell.

Homemade "Moist" Cells. Figure 4 shows a simple 1.45-volt cell made from a 1/4-inch wide strip of magnesium or zinc wrapped with two layers of paper towel previously dipped in a solution of salt and water. A piece of copper foil (available at craft and hobby shops) the size of a postage stamp is wrapped over the paper towel.

For best results, the paper towel should be dried before the cell is assembled. When the cell is to be used, it can be activated by dipping it in water. Alternatively, a few drops of water can be applied to the exposed ends of the paper towel.

The cell shown in Fig. 4 is merely one of many possible configurations. You can make round, square or triangular cells. You can even cut the zinc or magnesium anode into long, narrow strips and make ultra-thin, cylindrical cells. You can increase the current capacity of a cell by increasing the area of its electrodes. Two or more cells can be connected in series to achieve higher voltages.

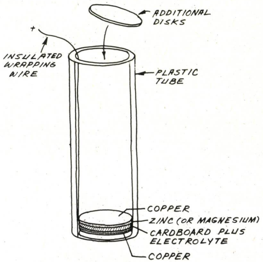

Fig. 5. Construction of a multi-cell stacked battery using zinc or magnesium.

If a discharged cell is disconnected, in time it will gradually recover. Add moisture, and the cell will again deliver power. After several discharge cycles, you can rejuvenate a cell by unwrapping the copper foil and cleaning both the anode and cathode with steel wool. Reassemble the cell with a fresh, salt-impregnated separator layer.

There are two ways to attach wires to the cell. The simplest is to use miniature clip leads. I prefer to solder short lengths of wrapping wire to the electrodes prior to assembly. Copper foil is easily soldered. Zinc must be sanded for best results. Solder will not adhere to magnesium, so you will have to use a clip lead if you use this anode material.

Homemade Stacked Batteries. You can assemble a miniature version of Volta's stacked battery, which was called

MODEL II

$\$459^{00}$ DISCOUNT
Off List
64K 1 DRIVE $3440.00
No Taxes on Out of State Shipments
Immediate Shipment On Most Items

$DISCOUNT$
TRS-80® DEALER A301

FREE COMPUTER CATALOG UPON REQUEST

26-3001 4K Color	$353.00
26-1145 RS-232 Board	84.00
26-1140 "O" K Interface	249.00
26-1160 Mini Disk	419.00
26-1172 Modem	135.00
Fast 100 CPS Centronics 730 Printer	577.00
Text Quality Centronics 737 Printer	737.00

26-1061 4K I	$629.00
26-1062 16K III	865.00
26-1063 32K III 2 Drives, RS232	2225.00

1-800-841-0860 Toll Free Order Entry
MICRO MANAGEMENT SYSTEMS, INC.
DOWNTOWN PLAZA SHOPPING CENTER
115 C SECOND AVE. S.W.
CAIRO, GEORGIA 31728
GA. & EXPORT PHONE NO. (912) 377-7120

Largest Inventory in S.E. U.S.A.

CIRCLE NO. 36 ON FREE INFORMATION CARD

a *Voltaic pile*, with the help of a 1/4-inch paper punch. Punch a dozen or so holes in a piece of *thin* cardboard like that used for shoe boxes and soak the cardboard disks in salt water or lemon juice. Then punch an identical number of disks out of sheets of copper foil and magnesium or zinc. Solder a six-inch length of wrapping wire to one copper disk and one zinc disk. If you use magnesium, make an extra copper disk and solder a wire to it.

For best results, assemble the cell inside a hollow plastic tube. I used a small tube which originally contained the point of a drafting pen. Flexible tubing can also be used.

Install the copper disk with an attached wire lead first. Then, install alternating disks of cardboard, zinc (or magnesium), copper, cardboard, etc. The final disk should be zinc with an attached wire. If magnesium is used in place of zinc, top off the stack with the other copper disk to which a lead has been attached.

You may need to press the disks lightly against the end of the tube to achieve maximum output from the battery. Too much pressure, however, will squeeze electrolyte from the cardboard disks. Free electrolyte can short adjacent cells and reduce the battery's output voltage.

Incidentally, you will find it very helpful to use pointed tweezers when assembling a battery like this. Also, be sure to blot excess electrolyte from the cardboard disks before installing them in the tube.

Figure 5 shows how a 12-cell stack is assembled. This battery delivers 5.8 volts open circuit and is able to drive a LED with built-in flasher. The load of the LED and flasher circuit drops the voltage from the battery to a few volts, so the LED is not very bright. I used zinc and copper disks and lemon juice electrolyte.

Unfortunately, the battery in Fig. 5 is not suitable for post-assembly water activation. Adding water to the battery would short all the cells together.

Additional Reading. Because of the volume of mail I receive, it will not be possible to answer individual reader's questions about homemade batteries. Fortunately, however, there are many good books on the subject.

For best results, visit a library which has lots of old books. Some large libraries keep such books in a separate section. Small-town libraries tend to keep such books longer than big libraries.

One typical example is *Electricity and Magnetism and Their Applications* by Dugald Jackson and John Jackson. This text was originally published by the Macmillan Company in 1902. It was revised by N. Henry Black in 1919 and republished in 1920. It contains an excellent chapter on early battery technology.

Another old book is *The Amateur Electrician's Handbook* by A. Frederick Collins (Thomas Y. Crowell Company, 1924). It contains instructions for making everything from wet cells to X-ray systems. I would not advise you to try the latter because much has been learned about the hazards of ionizing radiation since 1924.

Many newer books also discuss batteries. One is *Basic Electronics* by Abraham Marcus and Samuel Gendler (Prentice-Hall, 1971). Another is *Handbook for Electronics Engineering Technicians* by Milton Kaufman and Arthur Seidman (McGraw-Hill, 1976). ◇

TO OUR READERS. . .

POPULAR ELECTRONICS does not publicize the home addresses or telephone numbers of its authors, nor can we compel them to reply to inquiries they may receive. Letters to authors sent to the magazine will be forwarded by us, and there is a good chance that those accompanied by a stamped, self-addressed envelope will receive replies.

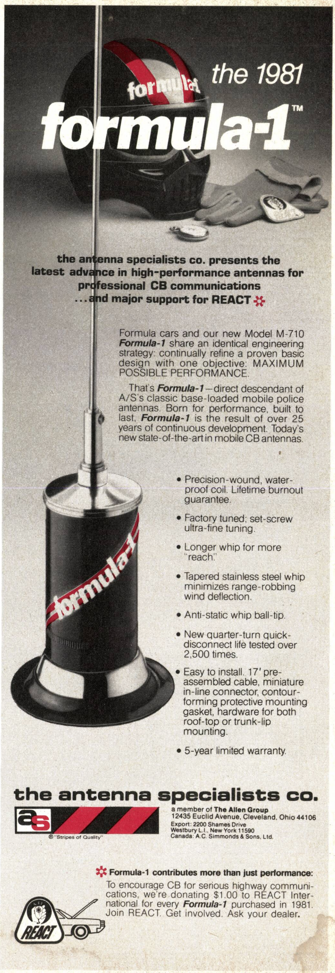

the 1981

formula-1™

the antenna specialists co. presents the latest advance in high-performance antennas for professional CB communications ...and major support for REACT ✲

Formula cars and our new Model M-710 ***Formula-1*** share an identical engineering strategy: continually refine a proven basic design with one objective: MAXIMUM POSSIBLE PERFORMANCE.

That's ***Formula-1***—direct descendant of A/S's classic base-loaded mobile police antennas. Born for performance, built to last, ***Formula-1*** is the result of over 25 years of continuous development. Today's new state-of-the-art in mobile CB antennas.

- Precision-wound, waterproof coil. Lifetime burnout guarantee.
- Factory tuned; set-screw ultra-fine tuning.
- Longer whip for more "reach."
- Tapered stainless steel whip minimizes range-robbing wind deflection.
- Anti-static whip ball-tip.
- New quarter-turn quick-disconnect life tested over 2,500 times.
- Easy to install. 17' pre-assembled cable, miniature in-line connector, contour-forming protective mounting gasket, hardware for both roof-top or trunk-lip mounting.
- 5-year limited warranty.

the antenna specialists co.

®"Stripes of Quality"

a member of **The Allen Group**
12435 Euclid Avenue, Cleveland, Ohio 44106
Export: 2200 Shames Drive
Westbury L.I., New York 11590
Canada: A.C. Simmonds & Sons, Ltd.

✲ **Formula-1 contributes more than just performance:**
To encourage CB for serious highway communications, we're donating $1.00 to REACT International for every ***Formula-1*** purchased in 1981. Join REACT. Get involved. Ask your dealer.

CIRCLE NO. 4 ON FREE INFORMATION CARD

Save on Calculators

Olympic Sales is an HP authorized dealer.

HEWLETT PACKARD
HP 41CV

Model	Retail	Your Cost
New Hp-41CV 2.2K bytes, 4 mem. modules built-in, slanted keybrd	$325.00	**$269.95**
System One, HP41CV & Card Reader	495.00	**394.95**
System Two, HP41CV-Card Redr & Prntr	840.00	**669.95**
Card reader for 41C/41CV	215.00	179.95
Printer for 41C/41CV	385.00	299.95
HP-41C new price	250.00	**189.95**
Quad Ram to upgrade HP41C to 2.2K bytes leaving 3 ports...Plugs into the 41C	95.00	84.95
Optical Wand for 41C/41CV	125.00	109.95
Memory Modules for 41C/41CV	39.50	27.95
HP-34C Scientific	150.00	119.95
HP-38C Bus./R.E.	150.00	119.95
HP-33C Scientific	90.00	78.95
HP-32E Adv. Scientific	55.00	49.95
HP-37E Bus. Calc.	75.00	63.95
HP-67 Progrmable Sci.	375.00	299.95
HP-97 Prog Printer Sci.	750.00	579.95
HP-85 Computer	3250.00	**2495.00**
New HP-83 Computer, similar to HP-85 without printer & cassette		1795.00

"C" stands for continuous memory.
One year guarantee by HP on all calcs, 90 days on computers.

apple computer

APPLE II and APPLE III
Huge inventory of Apple II computers. 16K-32K-48K. Disk drives, monitors, 80 column card. Dow Jones & Quote Reporter. Pascal-Fortran—DOS 3.3, etc. You name it...we've got it at super low prices.

Call us!

Immediate delivery on Apple III computers 96K and 128K systems.

Computers at unbeatable prices
Texas Instruments

99/4 console computer	449.95
TI-5230 printer (was $495)	169.95
TI-59	199.95
PC 100C	149.95
Epson MX80 printer	499.95
Epson MX70 printer	399.95
Atari 800 16K cnsle compu	759.95
Atari TV Game	144.95
Mattel Intel TV Game	239.95
Mattel Race Horse Anlyzr	59.95

Call us for best prices

Centronics printer PI for **Apple & Radio Shack** computers.	189.95
Centronics printers	17 models
Novation models CD-CAT/CAT	7 models
Shugart disk drives	6 models
Paper Tiger printers	5 models
Hazeltine video display terminals	7 models
Diablo printers	4 models
DEC VT100 & VT103	2 models

Casio watches at unbelievably low prices. Call us.
RCA VideoDisc SFT 100 player $459.95
(Many motion picture discs available) Call us
SCM Typewriters • **Royal** • **Victor** • **Canon** • **Sharp** • **Casio**
320models **Seiko** watches

Prices f.o.b. L.A. Minimum freight & handling charge—$4.95. In CA, add 6% sales tax. Goods subject to availability. We'll beat any advertised price if competitor has goods on hand.
Request our famous 100 page catalog, in writing.
Call Mon-Sat Outside CA, toll free **800-421-8045**
7AM-6PM. Inside CA, toll free **800-252-2153**

VISA

master charge

OLYMPIC SALES COMPANY, INC.
216 South Oxford Ave • P.O. Box 74545 • Los Angeles, CA 90004
Orders (213) 739-1130 • Customer Serv (213) 739-1100 • Telex 67-3477

CIRCLE NO. 43 ON FREE INFORMATION CARD

SEE YOUR DEALER TODAY

DEMAND THE ORIGINAL

'Firestik®'

The #1 Helically Wire-Wound and Most Copied Antenna in the World!

27MHz AM/FM/SSB CB

2 METER • MARINE TELEPHONE
LAND MOBILE TELEPHONE

FIBERGLASS ANTENNAS AND ACCESSORIES.

NEW CORDLESS TELEPHONE ANTENNA
INCREASES DISTANCE
5 TO 20 TIMES

Dealer & Distributor Inquiries Invited
SEND FOR FREE CATALOG

'Firestik' Antenna Company
2614 East Adams/Phoenix, AZ 85034

Name ____________________
Street ____________________
City ____________________
State ____________ Zip ____________

Serving the CB and Communications Market Since 1962.

5-YEAR REPLACEMENT WARRANTY

CIRCLE NO. 21 ON FREE INFORMATION CARD

English Broadcasts Audible in No. America

by Glenn Hauser

TIME EST/CDT	TIME UTC/GMT	STATION	QUAL.[2]	FREQUENCIES, kHz[3]
4:00-4:15 a.m.	0900-0915	BBC	A	15070, 11955, 11750, 9640, 9510, 6195
4:00-4:15 a.m.	0900-0915	R. Japan[4]	B	9505
4:00-4:30 a.m.	0900-0930	UN Radio	B	15250, 9565, 9350-SSB (Sat.)
4:00-5:00 a.m.	0900-1000	R. Andorra	C	15021 (varies) (Sun.)
4:00-5:30 a.m.	0900-1030	R. Australia	B	15115
4:00-6:00 a.m.	0900-1100	AFRTS, Los Angeles	A	11805, 9700, 9590, 9530, 6030
4:15-6:00 a.m.	0915-1100	BBC	C	17790, 17695, 15070, (21660 Sat. & Sun. and daily from 10:30)
4:30-5:15 a.m.	0930-1015	V. of the Malayan Revolution	C	15790, 11830
4:30-5:30 a.m.	0930-1030	V. of Germany	C	17780, 11850
5:00-5:15 a.m.	1000-1015	UN Radio	A	15250, 11090-LSB†, 9565 (Sat.)
5:00-5:15 a.m.	1000-1015	R. Japan	B	9505
5:00-5:30 a.m.	1000-1030	V. of Vietnam	C	12033, 10010
5:00-6:00 a.m.	1000-1100	R. Korea	C	11725, 9570, 9870, 15575
5:00-fade out	1000-	R. Australia	B	6045, 5995
5:00-8:00 a.m.	1000-1300	R. Moscow (via Cuba)	B	9600, 600 (5045 -1100)
5:00-11:02 a.m.	1000-1602	ABC, Perth	B	9610, 6140
5:15-5:55 a.m.	1050-1055	UAE Radio, Dubai	C	21695, 21640, 17775
5:20-5:30 a.m.	1020-1030	V. of Guatemala	B	6180, 640 (time varies widely)
5:28-8:00 a.m.	1028-1300	CBC Northern Service	B-C	9625, 6065 (not all Eng.)
5:30-6:30 a.m.	1030-1130	Sri Lanka Br. Corp.	C	17850, 15120, 11835 (not all Eng.)
5:55-6:55 a.m.	1055-1155	R. Thailand	C	11905, 9655
6:00-6:15 a.m.	1100-1115	R. Japan	B	9505
6:00-6:30 a.m.	1100-1130	V. of Vietnam	C	12035, 10010
6:00-6:30 a.m.	1100-1130	R. Mogadishu	D	9585
6:00-6:56 a.m.	1100-1156	R. RSA	C	25790, 21535
6:00-7:00 a.m.	1100-1200	V. of Asia, Taiwan	C	5980 (not Sun.)
6:00-7:00 a.m.	1100-1200	V. of Nigeria	C	17800, 15120
6:00-7:00 a.m.	1100-1200	AFRTS, Los Angeles	A	6030
6:00-7:30 a.m.	1100-1230	TWR-Bonaire	A	11815 (Sat. 1100-1330; Sun. 1100-1415)
6:00-7:50 a.m.	1100-1250	R. Pyongyang	C	9977
6:00-8:00 a.m.	1100-1300	R. Australia	A	9580
6:00-8:30 a.m.	1100-1330	BBC	A-B	25650, 21710, 21660, 21550, 11775, 11750, 9740, 9510, 6195
6:00-9:00 a.m.	1100-1400	4VEH, Haiti	C	11835, 9770
6:00-10:00 a.m.	1100-1500	VOA	B	11715, 9565
6:00-11:00 a.m.	1100-1600	AFRTS, Los Angeles	A	15430, 15330, 11805, 9700
6:15-6:30 a.m.	1115-1130	Vatican R.	C	21485, 17840 (not Sun.)
6:30-6:55 a.m.	1130-1155	R. Nacional, Angola	D	11955, 9535 (Mon.-Fri.)
7:00-7:15 a.m.	1200-1215	V. of Kampuchean People	C	11938, 9694 (vary)
7:00-7:20 a.m.	1200-1220	Vatican R.	B	21485, 17840 (not Sun.)
7:00-7:20 a.m.	1200-1220	R. Canada International	A	17820, 15440, 11955, 9650 (Mon.-Fri.)
7:00-7:30 a.m.	1200-1230	Kol Israel	C	25640, 17612.5, 21675
7:00-7:30 a.m.	1200-1230	R. Finland	B	15400
7:00-7:30 a.m.	1200-1230	R. Norway	C	21730 (Sun.)
7:00-7:30 a.m.	1200-1230	R. Tashkent	C	15460, 11785, 9750, 9715, 5950
7:00-7:30 a.m.	1200-1230	R. Japan	B	9505
7:00-7:30 a.m.	1200-1230	HCJB, Ecuador	A	26020, 15115, 11740
7:00-7:45 a.m.	1200-1245	V. of Germany	B	21600, 17875, 17765, 15410
7:00-7:55 a.m.	1200-1255	R. Peking	B	15520
7:00-8:00 a.m.	1200-1300	V. of Turkey	D	9560†
7:00-10:00 a.m.	1200-1500	R. Moscow World Service	B	17810, 15490, 12010
7:20-7:50 a.m.	1220-1250	R. Ulan Bator, Mongolia	C	12070 or 11825, 6383 or 4850 or 7235† (not Sun.)
7:30-7:55 a.m.	1230-1255	R. Tirana	D	11960, 9515
7:30-7:57 a.m.	1230-1257	Austrian R.	B	21655†
7:30-8:00 a.m.	1230-1300	R. Sweden	C	21690
7:30-8:00 a.m.	1230-1300	BBC (English by radio)	C	21695
7:30-8:00 a.m.	1230-1300	R. Bangladesh	D	21670, 15285
7:30-8:25 a.m.	1230-1325	R. Finland	B	15400 (Sun.)
7:30-8:30 a.m.	1230-1330	R. Korea	C	11830, 7550
7:30-8:30 a.m.	1230-1330	R. Maldives	D	4754
7:30-9:30 a.m.	1230-1430	HCJB, Ecuador	A	26020, 17890, 15115, 11740
7:30-9:30 a.m.	1230-1430	SLBC, Sri Lanka	C	15425
7:30-10:51 a.m.	1230-1551	WYFR, Family Radio	A	21545, 17785 (Sun. only)
7:35-7:45 a.m.	1235-1245	V. of Greece	C	21455, 17830, 11730 (Mon.-Fri.)
8:00-8:15 a.m.	1300-1315	R. Japan	B	9505
8:00-8:30 a.m.	1300-1330	R. Bucharest	C	17850, 15250, 11940
8:00-8:45 a.m.	1300-1345	R. Berlin International	C	21540, 21465, 17700
8:00-9:00 a.m.	1300-1400	R. Australia	C	11705, 9770, 6080
8:00-10:57 a.m.	1300-1557	R. RSA	B	25790, 21535, 15220
8:00-11:00 a.m.	1300-1600	CBC Southern Service	A	17820, 11955, 9575 (Sun.)
8:00-12:00 a.m.	1300-1700	WYFR, Family Radio	A	11830
8:00 a.m.-6:00 p.m.	1300-2300	CBC Northern Service	B-C	11720, 9625 (not all Eng.)
8:15-8:45 a.m.	1315-1345	Swiss R. International	B	21570, 21520
8:30-9:00 a.m.	1330-1400	R. Finland	B	21475, 15400
8:30-9:05 a.m.	1330-1405	BRT, Belgium	B	21525 (Mon.-Fri.)
8:30-9:00 a.m.	1330-1400	NYAB, Bhutan	D	4692 (Wed. & Fri.)
8:30-9:20 a.m.	1330-1420	R. Nederland	C	17605
8:30-9:30 a.m.	1330-1430	V. of Turkey	C	15125
8:30-9:30 a.m.	1330-1430	V. of Vietnam	C	10010
8:30-10:00 a.m.	1330-1500	All India R.	C	15335, 11810
8:30-11:00 a.m.	1330-1600	BBC	B-C	25650, 21710, 21660, 21550, 21470, 15400 (from 1430), 15070
8:30 a.m.-fade	1330-	R. Australia	C	6060

8:30 a.m.-5:00 p.m.	1330-2200	R. Moscow World Service (via Cuba)	B	11840 or 11860
8:57-11:55 a.m.	1357-1655	V. of Philippines	D	9578 (Sun.-1555) (not all English)
9:00-9:15 a.m.	1400-1415	R. Japan	B	9505
9:00-9:30 a.m.	1400-1430	R. Sweden	B	21615
9:00-9:30 a.m.	1400-1430	R. Norway	B	25730, 21730, 17840 (Sun. only)
9:00-9:30 a.m.	1400-1430	V. Rev. Party, N. Korea	D	4557, 4109
9:00-9:30 a.m.	1400-1430	R. Tashkent	C	15460, 11785, 9750, 9715, 5950
9:00-10:00 a.m.	1400-1500	V. of Indonesia	C	15200 or 15150, 11790
9:00-12:30 a.m.	1400-1730	R. Australia	C	17795, 9770
9:30-10:00 a.m.	1430-1500	KTWR, Guam	B	9510†
9:30-10:25 a.m.	1430-1525	R. Nederland	B	21480, 11735
9:30-11:00 a.m.	1430-1600	HCJB, Ecuador	A	26020, 17890, 15115
9:30-11:00 a.m.	1430-1600	Burma Br. Ser.	D	5985, 5040
9:30 a.m.-5:00 p.m.	1430-2200	UN Radio	A	21670, 15410 (when in session)
9:35-10:20 a.m.	1435-1520	R. Nepal	D	3425 or 7105 or 9589
9:50-10:35 a.m.	1450-1535	V. of the Malayan Revolution	C	15790, 11830
10:00-10:15 a.m.	1500-1515	R. Japan	C	9505
10:00-10:30 a.m.	1500-1530	V. of Asia, Taiwan	D	5980
10:00-11:00 a.m.	1500-1600	V. of Rev. Ethiopia	D	9560
10:00-11:00 a.m.	1500-1600	BBC	B	17830, 15260 (Sat, Sun)
10:00-11:00 a.m.	1500-1600	R. Moscow	B	24020, 12010
10:00-12:30 a.m.	1500-1730	BSHKJ, Jordan	D	9560
10:30-11:00 a.m.	1530-1600	R. Afghanistan	D	4775 or 6230
10:30-11:00 a.m.	1530-1600	R. Yugoslavia	C	15300, 15240
10:30-11:00 a.m.	1530-1600	Swiss R. International	B	21570
10:30-11:30 a.m.	1530-1630	V. of Vietnam	C	15010, 10040
10:35-10:45 a.m.	1535-1545	V. of Greece	C	21455, 17830, 11730 (Mon.-Fri.)
10:45-11:00 a.m.	1545-1600	R. Canada International	A	(17820 Mon.-Sat.), 15160, 15325
11:00-11:15 a.m.	1600-1615	R. Japan	C	9505
11:00-11:15 a.m.	1600-1615	Vatican R.	C	17730
11:00-11:15 a.m.	1600-1615	R. Pakistan	C	21755, 21605, 21486, 17910, 17660†
11:00-11:30 a.m.	1600-1630	R. Norway	B	25730, 21730 (Sun. only)
11:00-11:30 a.m.	1600-1630	R. Portugal	C	21530 or 21475 (not Sun.)
11:00-12:00 a.m.	1600-1700	R. Korea	C	11830, 9720
11:00 a.m.-12:09 p.m.	1600-1709	BBC	B	21710, 17830, 15260
11:00 a.m.-1:00 p.m.	1600-1800	AFRTS, Los Angeles	A	17765, 15430, 15330, 11805
11:00 a.m.-4:00 p.m.	1600-2100	R. Moscow World Service	B	24020, 15535, 12010, 11860†
11:00 a.m.-6:00 p.m.	1600-2300	VOA	A	26040, 21660, 21485, 17870, (15250 from 1900) 15445, (15410 to 2200)
11:05-11:55 a.m.	1605-1655	R. France International	B	25820, 21620, 21580, 21515, 17860
11:10-11:55 a.m.	1610-1655	BRT, Belgium	C	21525†
-11:30 a.m.	-1630	R. Singapore	C	11940, 5052, 5010 (fade-in time varies)
11:30-12:00 a.m.	1630-1700	UAE Radio, Dubai	B	21700, 21655, 21625†
11:45-12:00 a.m.	1645-1700	R. Canada International	A	(17820 Mon.-Sat.), 15325
11:45-12:45 p.m.	1645-1745	R. Pakistan	C	15495, 9460†
12:00-12:15 p.m.	1700-1715	R. Japan	C	9505
12:00-12:30 p.m.	1700-1730	HCJB, Ecuador	B	26020, 21480, 17790†
12:00-12:45 p.m.	1700-1745	BBC	C	18080
12:00-1:00 p.m.	1700-1800	WYFR, Family Radio	A	21615, 21465, 17845, 15440, 11830
12:00-3:00 p.m.	1700-2000	4VEH, Haiti	C	11835, 9770 (Sun.)
12:00-3:00 p.m.	1700-2000	BSK, Saudi Arabia	C	11856 (varies)
12:00-5:00 p.m.	1700-2200	VOA	B	17785, 15205, 11760, 9760, (15140 from 1830)
12:09-12:45 p.m.	1709-1745	BBC	B	17830, 15260 (Sat. & Sun.)
12:15-1:05 p.m.	1715-1805	V. of Germany	C	21600
12:45-3:00 p.m.	1745-2000	BBC	C	(21710 to 1830), 15400, 15070, 12095
12:45-5:30 p.m.	1745-2230	All India R.	C	11620
1:00-1:15 p.m.	1800-1815	R. Japan	C	9505
1:00-1:30 p.m.	1800-1830	R. Canada International	A	17820, 15260 (Sat. & Sun. - 1900)
1:00-1:30 p.m.	1800-1830	R. Norway	C	25730, 21730, 17840 (Sun only)
1:00-2:00 p.m.	1800-1900	V. of Vietnam	C	10040, 15010
1:00-2:00 p.m.	1800-1900	WYFR, Family Radio	A	21615, 17845
1:00-2:00 p.m.	1800-1900	V. of Nigeria	C	15120, 15185, 17800
1:00-3:00 p.m.	1800-2000	R. Australia	C	17795
1:00-4:00 p.m.	1800-2100	R. Kuwait	C	11650
1:00-5:00 p.m.	1800-2200	AFRTS, Los Angeles	A	21570, 17765, 15430, 15330, 15345
1:15-1:45 p.m.	1815-1845	Swiss R. International	C	21570, 17830, 17850
1:15-2:15 p.m.	1815-1915	R. Bangladesh	D	15100, 11765 (both vary)†
1:30-1:35 p.m.	1830-1835	UN Radio	A	19505-SSB, 15410, 11960, 17740, 15305 (Mon.-Fri.)
1:30-1:57 p.m.	1830-1857	Austrian Radio	C	15560 (Sun. from 1805)
1:30-2:00 p.m.	1830-1900	V. of Revolution, Guinea	C	15313 (varies) 9650 (Mon. Wed. and Fri.) (irregular)
1:45-2:15 p.m.	1845-1915	Sri Lanka Br. Corp.	C	17850, 15120, 15115, 11870
2:00-2:30 p.m.	1900-1930	R. Japan	B	17755
2:00-2:30 p.m.	1900-1930	R. Canada International	A	21630, 17875, 15325 (Sat. & Sun.-2000)
			A	17820, 15260 (Mon.-Fri.)
2:00-2:30 p.m.	1900-1930	R. Afghanistan	C	15079 (varies) or 17742†
2:00-2:45 p.m.	1900-1945	UN Radio	A	15410, 15305 (Fri.)
2:00-3:00 p.m.	1900-2000	HCJB, Ecuador	C	26020, 21480, 17790†, 15295†
2:00-3:00 p.m.	1900-2000	WYFR, Family Radio	A	21615, 17845, 11830
2:00-3:00 p.m.	1900-2000	R. Nacional, Brazil	C	17810, 15125
2:30-3:30 p.m.	1930-2030	V. of Iran	D	9022
2:35-5:00 p.m.	1935-2200	TIFC, Costa Rica	C	9645 (Sun.)
2:45-4:15 p.m.	1945-2115	R. Free Grenada	C	15104 (time varies and irregular)
3:00-3:15 p.m.	2000-2015	R. Japan	B	17755
3:00-3:30 p.m.	2000-2030	R. Norway	C	25730, 17840 (Sun.)
3:00-3:30 p.m.	2000-2030	R. Algiers	C	Some of: 25700, 25680, 21725, 21635, 17745, 15365, 15307, 11810
3:00-3:30 p.m.	2000-2030	R. Canada International	A	21630, 17875, 17820, 15325 (Mon.-Fri.)
3:00-3:30 p.m.	2000-2030	Kol Israel	C	17685, 17645, 15582.6, 12025, 11637, 9009
3:00-4:00 p.m.	2000-2100	WYFR, Family Radio	A	21615, 21525, 17845, 11830
3:00-4:15 p.m.	2000-2115	BBC	B	21560, 15260, 15070, 11750
3:00-12:00 p.m.	2000-0500	R. Moscow (via Cuba)	C	600

NEW!!! THE ELECTRIC MOUTH*

for S100, Elf II, Apple, TRS-80 Level II*

From $99.95 kit

Now — teach your computer to talk, dramatically increasing the interaction between you and your machine.

That's right: the ELECTRIC MOUTH actually lets your computer talk! Installed and on-line in just minutes, it's ready for spoken-language use in office, business, industrial and commercial applications, in games, special projects, R&D, education, security devices — there's no end to the ELECTRIC MOUTH's usefulness. Look at these features:

- ★ Supplied with 143 words/letters/ phonemes/ numbers, capable of producing hundreds of words and phrases.
- ★ Expandable on-board up to thousands of words and phrases (just add additional speech ROMs as they become available).
- ★ Four models, which plug directly into S100, Apple, Elf II and TRS-80 Level II computers.
- ★ Get it to talk by using either Basic or machine language (very easy to use, complete instructions with examples included).
- ★ Uses National Semiconductor's "Digitalker" system.
- ★ Includes on-board audio amplifier and speaker, with provisions for external speakers and amplifier.
- ★ Adds a new dimension and excitement to programming; lets you modify existing programs and games to add spoken announcements of results, warnings, etc.
- ★ Installs in just minutes.

Principle of Operation: The ELECTRIC MOUTH stores words in their digital equivalents in ROMs. When words, phrases, and phonemes are desired, they are simply called for by your program and then synthesized into speech. The ELECTRIC MOUTH system requires none of your valuable memory space except for a few addresses if used in memory mapped mode. In most cases, output ports (user selectable) are used.

Spoken Material Included

one	eighteen	at	dollar	inches	number	ss	c	t
two	nineteen	cancel	down	is	of	second	d	u
three	twenty	case	equal	it	off	set	e	v
four	thirty	cent	error	kilo	on	space	f	w
five	forty	400hertz tone	feet	left	out	speed	g	x
six	fifty	80hertz tone	flow	less	over	star	h	y
seven	sixty	20ms silence	fuel	lesser	parenthesis	start	i	z
eight	seventy	40ms silence	gallon	limit	percent	stop	j	
nine	eighty	80ms silence	go	low	please	than	k	
ten	ninety	160ms silence	gram	lower	plus	the	l	
eleven	hundred	320ms silence	great	mark	point	time	m	
twelve	thousand	centi	greater	meter	pound	try	n	
thirteen	million	check	have	mile	pulses	up	o	
fourteen	zero	comma	high	milli	rate	volt	p	
fifteen	again	control	higher	minus	re	weight	q	
sixteen	ampere	danger	hour	minute	ready	a	r	
seventeen	and	degree	in	near	right	b	s	

"Elf II" and "The Electric Mouth" are reg. trademarks of Netronics R&D Ltd. "Apple" is a reg. trademark of Apple Computer Inc. "TRS-80 Level II" is a reg. trademark of Tandy Corp.

Continental U.S.A. Credit Card Buyers Outside Connecticut
CALL TOLL FREE 800-243-7428
To Order From Connecticut Or For Technical Assistance, Etc.,
Call (203) 354-9375

NETRONICS R&D LTD. Dept PE
333 Litchfield Road, New Milford, CT 06776

Please send the items checked below:

☐ **S100 "Electric Mouth" kit $99.95**
☐ **Elf II "Electric Mouth" kit $99.95**
☐ **Apple "Electric Mouth" kit.............. $119.95**
☐ **TRS-80 Level II "Electric Mouth" kit..... $119.95**

Add $20.00 for wired & tested units. All plus $3.00 postage & insurance. Conn res. add sales tax.

Total Enclosed $ ____________

☐ **Personal Check** ☐ **Cashier's Check/Money Order**

☐ **Visa** ☐ **Master Charge (Bank No.** ________)

Acct. No. ____________

Signature ____________ **Exp. Date** ________

Print Name ____________

Address ____________

City ____________

State ____________ **Zip** ________

4PDT RELAY
POTTER BRUMFIELD
- 14 pin style
- 3 amp contacts
- 24 volt d.c. or 120 volt a.c. coil
- Used but fully tested

$1.50 each
specify coil voltage
LARGE QUANTITIES AVAILABLE
SOCKETS FOR RELAY 50¢ each

FLASHER L E D
Litronix FRL-4403
diffused red led with built in flashing unit 1 1/4 package
pulse rate 3hz @ 5v 20 ma.
2 for $1.70

COMPUTER GRADE CAP.
1,700mfd NEW
150 VDC $2.00
2 1/2" DIA X 4 3/4'
6,400mfd
60 VDC $2.50
1 3/8" DIA X 4 1/4"
22,000mfd 15 VDC $2.50
2" DIA X 2 1/2" HIGH
CLAMPS TO FIT CAPACITORS 50¢ ea.

SUB MINI L.E.D.
.079" X .098" - 20mA @ 1.75v
10 for $1.00
200 for $18.00
400 for $32.00
1000 for $70.00

7-17vdc
S.S. BUZZER
STAR #CMB-12
- Fits dip socket
- CMOS compatible
- Max current 14mA
- Sound output 70dB @ 20 cm

$1.25 each

SUPER SMALL
PHOTO-FLASH
170 MFD 330 VOLT
1 1/4" X 7/8"
2 for $1.50
10 for $14.00

TRANSFORMERS
120 volt primaries
6 VOLTS at 150 mA $1.25
12 V.C.T. at 500 mA $2.50
16.5 V. at 3 AMPS $6.50
30 V.C.T. at 3 AMPS $5.50

40 MFD 350 VOLTS
2 1/8 INCH X 3/4 INCH
2 for $1.50

DPDT 12VDC
ENCLOSED RELAY
KUP SERIES
10 AMP CONTACTS
AVAILABLE WITH NO FLANGE. CAN BE SOCKETED.
$3.00 EACH
10 FOR $27.50
SOCKETS $1.00

22/44 EDGE CONNECTOR
TIN SOLDERTAIL .156" x .200"
$1.35 each 10 for $12.50

50K SLIDE POT
Knobs for Slide Pots 20¢ each
75¢ each
audio taper
- 3-1/2 inch long
- 2-3/4 inch slide

ALL ELECTRONICS CORP.

905 S. Vermont Ave.
Los Angeles, CA 90006
(213) 380-8000

Store & Warehouse Hours
9 AM - 5 PM
Monday thru Friday
Saturday
10 AM - 3 PM

SEND FOR OUR FREE CATALOG

TERMS
- Quantities Limited
- Min. Order $10.00
- Add $2.00 Shipping USA
- Calif. Res. Add 6%
- Prompt Shipping

CIRCLE NO. 3 ON FREE INFORMATION CARD

apple computer
Complete Microprocessors line, peripherals & Terminals.
APPLE II PLUS, 48K $1215.00
LANG SYS. W/PASCAL 395.00
Z-80 SOFT CARD 299.00
Leedex 100 Mon 139.00
IDS 445G .... call us
TI-745 .... 1440.00
Disk 130K controller $575.00
SOROC IQ140 .... 1195.00
TI-99/4 .... 499.00
Epson MX-80 .... call us
Power Monitor .... call us
TI-810 .... 1695.00

Texas Instruments
TI-55 .... $ 29.95
Accessories .... Call us
TI-58C 84.50
PC100C 149.95
TI-59 .... 199.00
TI-55 II 39.95
Speak & Spell 49.95
TI Programmer 47.95
MBA 49.95

HEWLETT-PACKARD
System I .... call us
System II .... call us
HP-33C 75.00
HP-34C 119.00
HP-38C 114.99
HP-41C Prog 189.00
HP-41C Printer 289.00
HP-41C CRD RDR 169.00
HP-41C Mem Module 26.00
HP-41CV .... call us
HP-67 .... 299.00
HP-97 .... 579.00
Quad Ram .... call us
Application Pac .... call us
HP-83, HP-85 and accessory - call us for prices

SCM TYPEWRITER SPECIALS
SCM-2200 $269.00
SCM-2500 285.00
INTREPID $274.00
CLASSIC 12 144.00

All units shipped in original cartons with accessories according to manufacturer's specification. Send money orders, personal check (2 weeks to clear). In Illinois add 6% sales tax. Add $5.95 minimum shipping & handling charges per unit. We ship UPS. Subject to availability. Written warranty for specific products can be obtained free upon request. Above prices are for mail order and prepaid only. Prices and specifications subject to change without notice. Send mail orders

Nabik's, Inc.
519 DAVIS, EVANSTON, ILL. 60201 TEL.: 312-869-6144

3:10-4:40 p.m.	2010-2140	R. Habana Cuba	A	15155 or 11920
3:30-4:20 p.m.	2030-2120	R. Nederland	B	21685, 17695, 17605, 15220, 9715
3:30-4:30 p.m.	2030-2130	V. of Vietnam	C	15010, 10040
3:30-4:30 p.m.	2030-2130	V. Turkey	C	9615
3:45-5:30 p.m.	2045-2230	All India R.	C	15110
3:50-4:00 p.m.	2050-2100	R. Free Europe	C	21720, 17835, 15255, 15420 or 15290, 11825, 9725, 9565 (Fri.)
3:50-4:40 p.m.	2050-2140	R. Habana Cuba	C	17750, 9770
4:00-4:15 p.m.	2100-2115	R. Japan	B	17755
4:00-4:50 p.m.	2100-2150	R. RSA	B	17780, 15155, 11900
4:00-5:00 p.m.	2100-2200	V. of Nigeria	C	15185, 15120, 17800
4:00-5:00 p.m.	2100-2200	R. Moscow	C	21530, 15455
4:00-5:00 p.m.	2100-2200	WYFR, Family Radio	A	21615, 21525, 17845
4:00-6:00 p.m.	2100-2300	CBC Radio	A	17875, 15325 (Mon.-Fri.)
4:15-5:00 p.m.	2115-2200	BBC	A	21690, 15420, 15260, 15070, 9510, 6175
4:15-7:30 p.m.	2115-2430	R. Free Grenada	B	15045 (time varies)
4:30-5:00 p.m.	2130-2200	R. Canada International	A	17820, 15150, 11945 (17875, 15325 Sat. & Sun. only)
4:30-5:00 p.m.	2130-2200	KGEI, San Francisco	C	15280
4:30-5:00 p.m.	2130-2200	HCJB Ecuador	C	26020, 21480, 17795†, 15295†
4:30-5:00 p.m.	2130-2200	R. Sofia	B	11920, 11860†
4:30-5:30 p.m.	2130-2230	R. Baghdad	C	9745
4:40-5:40 p.m.	2140-2240	V. of Free China	C	17890, 15270, 11825
4:45-5:15 p.m.	2145-2215	Swiss R. International	B	21585
4:55 p.m.-1:30 a.m.	2155-0630	R. New Zealand	C	17860
5:00-5:15 p.m.	2200-2215	R. Japan	B	17755, (via Portugal 11955†)
5:00-5:30 p.m.	2200-2230	R. Argentina	C	11710 (Mon.-Sat.)
5:00-5:30 p.m.	2200-2230	R. Norway	C	17795, 15345, 15175 (Sun. only)
5:00-5:30 p.m.	2200-2230	R. Vilnius	B	17870, 17845, 15100, 11790, 11770
5:00-6:00 p.m.	2200-2300	WYFR, Family Radio	A	21615, 21525, 17845, 9535
5:00-6:00 p.m.	2200-2300	R. Moscow	A	21530, 17720, 15455, 15140, 12050, 12010, 11960, 11920, 11860, 11735, 9765, 9710, 9685, 9610
5:00-6:00 p.m.	2200-2300	V. of Turkey	B	9725, 7215†
5:00-6:00 p.m.	2200-2300	R. Clarin, Dom. Rep.	B	11700 (Sat. & Sun.; irregular)
5:00-6:00 p.m.	2200-2300	BBC	A	21690, 15420, 15260, 15070, 11750, 9590, 9510, 6175, 6120
5:00-7:00 p.m.	2200-2400	CBC Southern Service	A	9755, 5960 (Sat. 2200-2230; Sun. 2200-2300)
5:00-7:00 p.m.	2200-2400	AFRTS, Los Angeles	A	25615, 21570, 15430, 15345, 15330
5:00-11:30 p.m.	2200-0430	VOA	A	21460, 17740, (26000 – 2400), (17820 -0100)
5:15-5:30 p.m.	2215-2230	UN Radio	A	15305, 11830 (Fri.)
5:15-5:30 p.m.	2215-2230	R. Yugoslavia	C	9620
5:30-6:00 p.m.	2230-2300	Kol Israel	A	15583, 12025, 11638, 9815
5:30-6:00 p.m.	2230-2300	R. Nacional, Angola	D	9535 (Mon.-Fri.)
5:30-6:25 p.m.	2230-2325	R. Mexico	B	15430 (Sun., time varies)
5:30-6:30 p.m.	2230-2330	R. Sofia	B	15330, 15110
5:45-6:00 p.m.	2245-2300	SODRE, Uruguay	C	11885, 9515 (time varies)
6:00-6:30 p.m.	2300-2330	R. Japan	C	17755
6:00-6:30 p.m.	2300-2330	R. Sweden	B	15380, 11705
6:00-7:00 p.m.	2300-2400	4VEH, Haiti	B	11835, 9770
6:00-7:00 p.m.	2300-2400	WYFR, Family Radio	A	21525, 9535
6:00-7:00 p.m.	2300-2400	R. Mexico	B	15430 (Thurs., time varies)
6:00-7:30 p.m.	2300-2430	BBC	A	15420, 15260, 15070, 11910, 9590, 9580, 9410, 7325, 6175, 6120, 5975
6:00-7:50 p.m.	2300-2450	R. Pyongyang	C	9977
6:00-8:00 p.m.	2300-0100	R. Moscow	A	21530, 17720, 15455, 15140, 12050, 12010, 11960, 11860, 11780, 11735, 9765, 9710, 9685, 9610
6:00-12:07 p.m.	2300-0507	CBC Northern Service	B-C	9625, 6195 (not all English)
6:25-7:00 p.m.	2325-2400	SODRE, Uruguay	C	11885, 9515 (time varies)
6:30-7:00 p.m.	2330-2400	HCJB, Ecuador	B	26020, 15350
6:30-7:00 p.m.	2330-2400	R. Kiev	B	17870, 17845, 15100, 11790, 11770
6:30-7:00 p.m.	2330-2400	V. of Vietnam	C	12035, 10080, 10040, 10010
6:45-7:45 p.m.	2345-2445	R. Japan	C	17825, 15430
7:00-7:15 p.m.	0000-0015	R. Japan	C	17755
7:00-7:25 p.m.	0000-0025	R. Tirana	B	9750, 7065
7:00-7:30 p.m.	0000-0030	R. Mexico	C	17765, 15430, 11770 (Sat.)
7:00-7:30 p.m.	0000-0030	R. Canada International	A	9755, 5960
7:00-7:30 p.m.	0000-0030	Kol Israel	A	15583, 11638, 9815
7:00-7:30 p.m.	0000-0030	R. Norway	C	15345, 9605 (Mon. only)
7:00-7:45 p.m.	0000-0045	R. Berlin International	C	11970, 9730
7:00-7:55 p.m.	0000-0055	R. Peking	B	17855, 17680, 15125
7:00-8:00 p.m.	0000-0100	WYFR, Family Radio	A	17845, 5985
7:00-8:00 p.m.	0000-0100	R. Sofia	B	15110, 11830
7:00-8:00 p.m.	0000-0100	AFRTS, Los Angeles	A	25615, 21570, 15345, 15330, 11790
7:00-9:00 p.m.	0000-0200	R. Luxembourg	C	6090 (Time varies)
7:00-9:00 p.m.	0000-0200	VOA	A	17730, 15205, 11740, 9650, 6130, 5995
7:00-12:00 p.m.	0000-0500	R. Moscow (via Cuba)	A	9600
7:00 p.m.-4:00 a.m.	0000-0900	UN Radio	A	6055 (when in session)
7:05-8:55 p.m.	0005-0155	Spanish Foreign R.	B	11880, 9630
7:15-8:00 p.m.	0015-0100	BRT, Belgium	C	15385, 15175
7:25-7:40 p.m.	0025-0040	SODRE, Uruguay	C	11885, 9515 (time varies)
7:30-8:00 p.m.	0030-0100	R. Prague	C	6055
7:30-8:00 p.m.	0030-0100	R. Budapest	B	17710, 15220, 11910, 9835, 9585 (Wed. and Fri.)
7:30-8:00 p.m.	0030-0100	La Cruz del Sur, Bolivia	D	4875 (Mon. only)
7:30-9:00 p.m.	0030-0200	HCJB, Ecuador	A	15155
7:30-9:30 p.m.	0030-0230	SLBC, Sri Lanka	C	15425
7:30-9:30 p.m.	0030-0230	BBC	A	15260, 11835, 11750, 9580, 9410, 7325, 6175, 6120, 5975
7:35-9:30 p.m.	0035-0230	HCJB, Ecuador	B	26020, 15360, 9745
7:55-8:35 p.m.	0055-0135	TWR-Bonaire	B	11745
8:00-8:15 p.m.	0100-0115	R. Japan	C	17755
8:00-8:15 p.m.	0100-0115	Vatican R.	B	11845, 9605, 6015
8:00-8:20 p.m.	0100-0120	RAI, Italy	B	11800, 9575
8:00-8:25 p.m.	0100-0125	Kol Israel	A	15583, 11638, 9815

8:00-8:30 p.m.	0100-0130	R. Argentina	B	11710 (not Mon.)
8:00-8:30 p.m.	0100-0130	R. Mexico	B	15430 (Sun.)
8:00-8:30 p.m.	0100-0130	R. Budapest	B	17710, 15220, 11910, 9835, 9585 (not Mon.)
8:00-8:30 p.m.	0100-0130	R. Canada International	A	17820, 9755, 5960
8:00-8:55 p.m.	0100-0155	R. Prague	B	11990, 9740, 9540, 7345, 5930
8:00-8:55 p.m.	0100-0155	R. Peking	B	17855, 17680, 15125
8:00-9:00 p.m.	0100-0200	V. of Free China	C	17890, 15345, 11825
8:00-9:00 p.m.	0100-0200	R. Moscow	A	21530, 17720, 15455, 15140, 12050, 12010, 11960, 11860, 11780, 9765, 9710, 9685, 9610, 9530 (9700 from 0130)
8:00-9:00 p.m.	0100-0200	AFRTS, Los Angeles	A	25615, 21570, 15345, 15330, 11790
8:00-9:00 p.m.	0100-0200	WYFR, Family Radio	B	9715
8:00-10:30 p.m.	0100-0330	R. Australia	B	21740, 17795
8:00-11:50 p.m.	0100-0450	R. Habana Cuba	B	11930, 11725
8:20 p.m.-12:10 a.m.	0120-0510	R. Belize	C	3285, 834
8:20-8:50 p.m.	0120-0150	V. of Germany	A	15105, 11865, 9590, 9565, 9545, 6145, 6085, 6040
8:30-8:45 p.m.	0130-0145	V. of Greece	B	11730, 9655, 9515 (not Sun.)
8:30-8:57 p.m.	0130-0157	Austrian Radio	B	9770, 5945
8:30-8:55 p.m.	0130-0155	R. Tirana	B	9750, 7120
8:30-9:15 p.m.	0130-0215	R. Berlin International	C	11970, 9730
8:30-9:30 p.m.	0130-0230	R. Japan	C	21640, 17825, 17725, 15235
8:45-9:15 p.m.	0145-0215	Swiss R. International	A	15305, 11715, 9725, 6135
9:00-9:15 p.m.	0200-0215	R. Japan	C	17755
9:00-9:25 p.m.	0200-0225	Kol Israel	A	15583, 11638, 9815
9:00-9:30 p.m.	0200-0230	R. Canada International	A	11940, 9755, 5960
9:00-9:30 p.m.	0200-0230	R. Norway	B	11870, 11860, 9610 (Mon. only)
9:00-9:30 p.m.	0200-0230	R. Kiev	B	17870, 15100, 11790, 9665
9:00-9:30 p.m.	0200-0230	R. Budapest	B	17710, 15220, 11910, 9835, 9585, 6000†
9:00-9:40 p.m.	0200-0240	R. Polonia	B	15120, 11815, 9525, 7270, 7145, 6135, 6095 (length varies)
9:00-9:50 p.m.	0200-0250	R. RSA	B	11900, 9585, 5980
9:00-9:55 p.m.	0200-0255	R. Bucharest	C	11940, 11840, 11735, 9690, 9570, 5990
9:00-9:55 p.m.	0200-0255	R. Peking	B	17855, 17680, 15120
9:00-10:00 p.m.	0200-0300	R. Nacional, Brazil	A	15290, 17830,
9:00-10:00 p.m.	0200-0300	R. Moscow	A	17720, 15455, 15240, 15140, 12050, 12010, 11960, 11860, 11780, 9710, 9700, 9685, 9610, 9530,
9:00-10:30 p.m.	0200-0330	R. Cairo	B	12050, 9475
9:00-11:00 p.m.	0200-0400	VOA	A	15205, 9650, 5995
9:00-11:30 p.m.	0200-0430	AFRTS, Los Angeles	A	21570, 17765, 11790, 9755, 6030
9:00-12:00 p.m.	0200-0500	WYFR, Family Radio	A	9715, 5985
9:30-9:45 p.m.	0230-0245	R. Pakistan	C	21590, 17835, 21745†
9:30-9:45 p.m.	0230-0245	UN Radio	A	15240, 6035, 15685-SSB 10869-SSB (Sat.)
9:30-9:55 p.m.	0230-0255	R. Tirana	B	9750, 7120
9:30-10:00 p.m.	0230-0300	R. Lebanon	C	15170 or 11820† (time varies)
9:30-10:00 p.m.	0230-0300	R. Finland	B	11755, 15400
9:30-10:00 p.m.	0230-0300	R. Sweden	B	15315, 11705
9:30-10:15 p.m.	0230-0315	R. Berlin International	B	11975, 11890, 11840
9:30-10:25 p.m.	0230-0325	R. Nederland	A	9590, 6165
9:30-10:30 p.m.	0230-0330	R. Korea	C	15575, 11810
9:30-10:30 p.m.	0230-0330	BBC	A	11750, 9580, 9510, 9410, 7325, 6175, 6120, 5975
9:30-12:00 p.m.	0230-0500	HCJB, Ecuador	A	15155, 9745
9:51-9:58 p.m.	0351-0358	V. of Yerevan	C	17870, 17845, 15100
10:00-10:15 p.m.	0300-0315	R. Japan	C	17755
10:00-10:15 p.m.	0300-0315	R. Budapest	B	17710, 15220, 11910, 9835, 9585, 6000† (Wed. & Fri.; Mon. -0330)
10:00-10:25 p.m.	0300-0325	R. Polonia	B	15120, 11815, 9525, 7270, 7145, 6135, 6095 (length varies)
10:00-10:30 p.m.	0300-0330	R. Canada International	A	11940, 11845, 9755, 9535, 5960
10:00-10:30 p.m.	0300-0330	R. Portugal	B	11925, 6185 or 15125†
10:00-10:30 p.m.	0300-0330	R. Australia	C	15260 (Fri.)
10:00-10:50 p.m.	0300-0350	V. of Free China	C	17890, 15270, 11825
10:00-10:55 p.m.	0300-0355	R. Prague	B	11990, 9740, 9540, 7345, 5930
10:00-10:55 p.m.	0300-0355	R. Peking	B	17680, 15120
10:00-11:00 p.m.	0300-0400	R. Moscow World Service	A	17765, 15460,11960, 11860, 11780, 9700, 9610, 9530
10:00-11:00 p.m.	0300-0400	TIFC Costa Rica	C	9645, 5055, (Mon. 0235-0435)
10:00-11:00 p.m.	0300-0400	R. Baghdad	D	11935
10:00-11:15 p.m.	0300-0415	R. Uganda	B	15325 (irregular)
10:00-11:26 p.m.	0300-0426	R. RSA	B	11900, 9585, 7270, 5980
10:00-11:30 p.m.	0300-0430	R. Cultural, Guatemala	B	3300 (Mon. 0030–)
10:00 p.m.-1:00 a.m.	0300-0600	HRVC, Honduras	B	4820
10:00 p.m.-2:00 a.m.	0300-0700	R. Moscow	A	17845, 15470, 15455, 15420, (15140 and 15100 to 0400), 12050, 12010, 9790, 9580
10:00 p.m.-2:30 a.m.	0300-0730	VOA	A	15240, 9670, 6040, 6035, 5995
10:25 p.m.-fade	0325-	R. One, Zimbabwe	C	3396 (exc. Sun.)
10:30-10:55 p.m.	0330-0355	R. Tirana	B	7300, 6200
10:30-10:57 p.m.	0330-0357	U.A.E. Radio, Dubai	B	15320, 11755†
10:30-10:57 p.m.	0330-0357	Austrian Radio	C	9770, 5945
10:30-11:00 p.m.	0330-0400	R. Australia	B	21680, 17890, 17870, 17795, 17725
10:30-11:45 p.m.	0330-0445	BBC	A	15070, 9410, 6175, 5975
10:30-12:00 p.m.	0330-0500	AWR Guatemala	C	5980
10:30 p.m.-1:00 a.m.	0330-0600	R. Habana Cuba	A	11760, 11725
10:40-10:47 p.m.	0340-0347	V. of Greece	B	11730, 9650, 9515 (not Sun.)
10:50-11:10 p.m.	0350-0410	RAI, Italy	C	21560, 17795, 15330
11:00-11:15 p.m.	0400-0415	R. Japan	C	17755
11:00-11:30 p.m.	0400-0430	R. Bucharest	C	11940, 11840, 11735, 9690, 9570, 5990
11:00-11:30 p.m.	0400-0430	R. Canada International	A	11845, 9755, 9535, 5960
11:00-11:30 p.m.	0400-0430	R. Norway	C	21730, 15175, 11860 (Mon. only)

SAVE!

MONEY • TIME • FREIGHT

QUALITY STEREO EQUIPMENT AT LOWEST PRICES.

YOUR REQUEST FOR QUOTATION RETURNED SAME DAY.

FACTORY SEALED CARTONS— GUARANTEED AND INSURED.

SAVE ON NAME BRANDS LIKE:

PIONEER SANSUI
KENWOOD DYNACO
SHURE SONY
MARANTZ KOSS

AND MORE THAN 50 OTHERS
BUY THE MODERN WAY
BY MAIL—FROM

ia
illinois audio

BANK CARDS ACCEPTED
12 East Delaware
Chicago, Illinois 60611
312-664-0020
800-621-8042

CIRCLE NO. 29 ON FREE INFORMATION CARD

AMAZING
DEVICES

(((((PHASERS)))))

PPF-1 *PHASER PAIN FIELD* — This device recently developed and patented in our labs is being evaluated by law enforcement agencies for riot and crowd control. It is now available but soon will come under the jurisdiction of weapons and infernal machine control making it unavailable to the public. The device is hand-held and looks like a BUCK ROGERS ray gun. It is hazardous if not used with discretion.
PPF-1 .... PLANS **$15.00**

IPG-1 *INVISIBLE PAIN FIELD GENERATOR* — This amazing, simple hand-held device is about the size of a pack of cigarettes and generates a directional field of moderate to intensive pain in the lower part of the head up to a range of 50'. Device is simple and economical to make.
IPG-1 PLANS **$7.00** **IPG-1K** ALL PARTS **$39.50**
IPG-10 ASSEMBLED&TESTED FOR ANIMAL CONTROL **$49.50**

LASERS

RUBY LASER RAY PISTOL — Produces highly intense red beam, capable of burning. A hazardous device. PLANS, PARTS, SOURCES **$15.00**

HIGH POWERED CARBON DIOXIDE BURNING AND CUTTING. Complete plans and all parts sources **$15.00**

SOLID STATE IR 12 WATTS with built in power supply plans **$8.00** Complete kit with collimator **$74.00**

POCKET LASER pulsed, visible red ...... plans **$7.00**
Complete kit ... **$39.50** Also complete plans and parts sources for RUBY, YAG, NEODYNIUM, HeNe ARGON, DYE, NITROGEN and many more lasers.

SECURITY

SNP-2. *SNOOPER PHONE* — Dial home or office phone while on vacation activating sensitive mike without phone ringing. Excellent property protection and intrusion device.
SNP2 .... PLANS **$7.00**
SNP2K .... ALL PARTS **$49.50**
SNP20 .... ASSEMBLED AND TESTED **$99.50**

LONG RANGE XMTR PLANS **$7.00**
SEE-IN-THE-DARK PLANS **$10.00**
DIRECTIONAL SHOTGUN MIKE PLANS **$8.00**
SUPER SENSITIVE PARABOLIC MIKE PLANS **$8.00**
SOUND & TELEPHONE OPERATED TAPE RECORDER **$7.00**
CATALOG ON PLANS, KITS & FINISHED UNITS **$1.00**

Send check or money order to
SCIENTIFIC SYSTEMS, Dept. Q1, Box 716
AMHERST, N.H. 03031

CIRCLE NO. 51 ON FREE INFORMATION CARD

ESP

DON'T BLAME THE SOFTWARE!

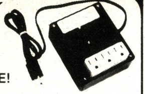

Power Line Spikes and Hash often cause memory loss or erratic operation. Often floppies, printer & processor interact!

OUR unique ISOLATORS eliminate equipment interaction AND curb damaging Power Line Spikes, Surges and Hash.

3 filtered 3-prong sockets and integral Spike Suppression. 125 VAC, 15 Amp, 1875 W Total — 1 KW per socket.

ISO-1 ISOLATOR. 3 Filtered Sockets; 1000 Amp 8/20 usec Spike Suppressor $62.95

ISO-4 ISOLATOR. 6 Filtered Sockets; 1000 Amp 8/20 usec Spike Suppressor $106.95

ISO-3 SUPER-ISOLATOR. 3 DUAL filtered Sockets; 2000 Amp 8/20 usec Spike Suppressor $95.95

ISO-7 SUPER-ISOLATOR. 5 DUAL filtered Sockets; 2000 Amp 8/20 usec Spike Suppressor $154.95

Master-Charge, Visa, American Express
TOLL FREE ORDER DESK 1-800-225-4876
(except AK, HI, MA, PR & Canada)

Electronic Specialists, Inc.
171 South Main Street, Natick, MA 01760
Technical & Non-800: 1-617-655-1532

CIRCLE NO. 17 ON FREE INFORMATION CARD

RemoveVocals

Remove the lead vocal and substitute your own voice with most stereo recordings using our new, low cost VOCAL ZAPPER™. Great for practice, professional demos or just for fun.

WITH THE

VOCAL ZAPPER™

FROM
PAIA Electronics, Inc.
1020 W. Wilshire, Oklahoma City, OK 73116 · (405)843-9626

☐ Rush my Vocal Zapper Kit, $24.95 plus $3 postage & handling enclosed.
☐ Send assembled Vocal Zapper, $39.95 plus $3 postage & handling enclosed.
☐ Send Free Catalog

name ____________________
address ____________________
city ____________ state ____ zip ________
Visa☐MC☐ card no. ____________________
PAIA Electronics, dept. 6P, 1020 W. Wilshire, Okla. City, OK 73116

CIRCLE NO. 44 ON FREE INFORMATION CARD

11:00-11:30 p.m.	0400-0430	R. Mozambique	C	4855, 3265
11:00-11:55 p.m.	0400-0455	R. Peking	B	17680, 15120
11:00-12:00 p.m.	0400-0500	R. Sofia	C	11860†
11:00-12:00 p.m.	0400-0500	R. Australia	B	21680, 21650, 21525, 17890, 17870, 17795, 17755, 17725, 15320, 15240, 15160
11:00-12:00 p.m.	0400-0500	R. Moscow World Service	A	17765, 15460, 12055, 11960, 11790, 9610, 9530
11:00 p.m.-1:00 a.m.	0400-0600	TWR, Bonaire	A	9755
11:05-11:50 p.m.	0405-0450	FEBA, Seychelles	C	15400†
11:30-11:57 p.m.	0430-0457	Austrian R.	B	12015
11:30-12:00 p.m.	0430-0500	Swiss R. International	B	11715, 9725
11:30 p.m.-1:00 a.m.	0430-0600	AFRTS, Los Angeles	A	17765, 11790, 15330, 9755, 6030
11:45-12:00 p.m.	0445-0500	Vatican Radio	C	6210 or 6190
11:45 p.m.12:45 a.m.	0445-0545	BBC	A	15070, 9510, 9410, 6175, 5975
11:55 p.m.-1:00 a.m.	0455-0600	V. of Nigeria	C	7255
12:00-12:15 a.m.	0500-0515	Kol Israel	B	17710, 15105, 15583, 11638
12:00-12:15 a.m.	0500-0515	R. Japan	C	15430
12:00-12:30 a.m.	0500-0530	R. Portugal	B	9575 or 11925, 6185
12:00-1:00 a.m.	0500-0600	R. Australia	C	21680, 17890, 17870, 17725, 15240, 15160
12:00-1:00 a.m.	0500-0600	WYFR, Family Radio	A	9705, 5985
12:00-1:00 a.m.	0500-0600	R. Moscow World Service	B	17730, 15460, 11790
12:00-2:00 a.m.	0500-0700	HCJB, Ecuador	B	9745, 6095, 11915
12:00-3:00 a.m.	0500-0800	R. Kuwait	C	21545 or 15345
2:00-3:00 a.m.	0500-0800	R. Nigeria, Kaduna	B	4770 (not all Eng.)
12:00-5:00 a.m.	0500-1000	V. of Cuba	B	550
12:10-12:45 a.m.	0510-0545	UAE Radio, Dubai	C	17810, 17775†
12:15-1:15 a.m.	0515-0615	Spanish Foreign R.	B	11880, 9630
12:22-12:30 a.m.	0522-0530	UN Radio	A	9540, 6055 (Tue.-Sat.)
12:30-12:40 p.m.	0530-0540	R. Garoua, Cameroon	C	5010
12:30-12:50 a.m.	0530-0550	V. of Germany	A	11905, 9650, 9545, 6100, 5960
12:30-fade	0530-	R. Ghana	C	3366, 4915
12:30-1:25 a.m.	0530-0625	R. Nederland	A	9715, 6165
12:45-1:00 a.m.	0545-0600	UN Radio	A	9540, 6055 (Tue.-Sat.)
12:45-1:30 a.m.	0545-0630	R. Berlin Int.	B	17700, 15100
12:45-2:30 a.m.	0545-0730	BBC	B	15070, 11955, 11860, 9640, 9510, 9410, 7150, 6175
1:00-1:15 a.m.	0600-0615	R. Japan	C	15430
1:00-1:30 a.m.	0600-0630	V. of Germany	C	17875, 15275, 11905, 11765, 9700
1:00-1:30 a.m.	0600-0630	R. Norway	B	21655, 15170, 11860 (Mon. only)
1:00-1:30 a.m.	0600-0630	R. Australia	C	21680, 21525, 17870, 17795, 17755, 17725, 15240, 15160
1:00-2:00 a.m.	0600-0700	AFRTS, Los Angeles	B	11790, 9755, 6030
1:00-2:00 a.m.	0600-0730	HCJB, Ecuador	C	11835, 15225
1:00-3:00 a.m.	0600-0800	V. of Nigeria	C	15185, 15120, 17800
1:15-1:30 a.m.	0615-0630	R. Canada International	B	17860, 15325, 11960, 11825, 11775, 9760, 9590, 7135, 6140, 6045 (Mon-Fri)
1:25-3:00 a.m.	0625-0800	TWR, Monte Carlo	B	9495† (Sun. to 1000)
1:25-3:55 a.m.	0625-0855	V. of Malaysia	C	15295, 12350, 9750
1:30-2:00 a.m.	0630-0700	R. Australia	B	21680, 17870, 17725, 15240, 15115
1:30-2:00 a.m.	0630-0700	Radio Polonia	B	9675, 7270
1:30-2:30 a.m.	0630-0730	R. RSA	B	21535, 17780, 15220
1:30-3:00 a.m.	0630-0800	R. Habana Cuba	A	9525
1:40-7:25 a.m.	0640-1225	R. New Zealand	C	11945
1:45-2:00 a.m.	0645-0700	R. Canada International	B	17860, 15325, 11960, 11825, 11775, 9760, 9590, 7135, 6140, 6045 (Mon-Fri)
1:45-2:00 a.m.	0645-0700	UN Radio	A	15125, 11735 (Sat.)
1:57-4:55 a.m.	0657-0955	V. of Philippines	C	9578 (not all English)
2:00-2:15 a.m.	0700-0715	R. Japan	C	15430, (15170† via Portugal)
2:00-2:20 a.m.	0700-0720	R. Nederland	C	25650, 21480, 17605, 11720, 9895
2:00-2:30 a.m.	0700-0730	Swiss Radio Int.	C	21520, 15305, 9535, 9560
2:00-3:00 a.m.	0700-0800	Xandir Malta	C	9670 (Sat.) (irregular)
2:00-3:00 a.m.	0700-0800	ELWA, Liberia	C	11830
2:00-3:00 a.m.	0700-0800	V. of Vietnam	C	7512, 9840, 6383
2:00-4:00 a.m.	0700-0900	R. Australia	B	21680, 17725, 15115, 11740, 9570
2:00-5:30 a.m.	0700-1030	HCJB, Ecuador	C	11900, 9745, 6130
2:07-2:15 a.m.	0707-0715	UN Radio	A	17815, 15195 (Sat.)
2:30-3:25 a.m.	0730-0825	R. Nederland	B	9770, 9715
2:30-4:00 a.m.	0730-0900	BBC	B	15070, 11955, 9640, 9510
2:30-6:30 a.m.	0730-1130	Solomon Isl. Broadcasting	C	9545 or 5020 (Not all Eng.)
2:30-9:00 a.m.	0730-1400	NBC, Papua New Guinea	C	4890, 3925 (not all Eng.)
2:30-9:02 a.m.	0730-1402	ABC Melbourne	C	9680
2:37-2:45 a.m.	0737-0745	UN Radio	A	17815, 15195 (Sat.)
2:45-4:30 a.m.	0745-0930	KTWR, Guam	B	11840
2:55 a.m.-fade	0755-	Action Radio, Guyana	C	5950
2:55-3:05 a.m.	0755-0805	V. of Guatemala	B	6180, 640 (time varies)
3:00-3:15 a.m.	0800-0815	R. Japan	B	9505
3:00-3:30 a.m.	0800-0830	R. Norway	C	15135, 11850 (Sun.)
3:00-315 a.m.	0800-0815	UN Radio	A	17860, 15235, 15125, 11735 (Sat.)
3:00-4:00 a.m.	0800-0900	R. Korea	B	15575, 11810, 9870
3:00-9:00 a.m.	0800-1400	R. East Coast Commercial	D	11578† (Sat.)
3:30-3:35 a.m.	0830-0835	UN Radio	A	15250, 10385, 9565 (Sat.)
3:30-4:25 a.m.	0830-0925	R. Nederland	B	9715
3:30-5:00 a.m.	0830-1000	FEBC, Philippines	C	11890 or 11765
24 Hours	24 Hours	CFRX, Toronto	C	6070

Explanatory Notes.

1. Times in first column are EST/CDT. For ADT add 2 hours; EDT add 1 hour; MDT, subtract 1 hour, MST/PDT, subtract 2 hours. Days of week are in GMT.
2. Quality. A—strong signal and very reliable reception. B—regular reception. C—occasional reception under favorable conditions. D—rarely audible. These ratings are for locations in the central USA. European and African stations are in general, more reliably received in eastern North America. Asian and Pacific stations are more reliably received in western North America. North American stations are received well except in areas too close to the transmitter site.
3. The information in this listing is correct to press time. However, frequencies and schedules are constantly changing. Listen to "DX Digest" on R. Canada International for late changes, Saturday at 2130; Sunday at 1930; GMT Mondays at 0100 and 0400.
4. R.—Radio; V.—Voice

† = frequent changes

TIPS & TECHNIQUES

Memory Circuit for Alarm Systems

Many simple alarm systems offer reliable performance but lack one convenience—a memory circuit. Such a memory circuit would alert the owner upon arriving at his premises that the alarm system has been triggered and that he should enter cautiously (if at all). Shown in the figure is a memory circuit that I added to my alarm system. It takes advantage of the system's continuously available +6-volt supply and the +6 volts that appears on the local-alarm bus during the alerting interval. The 5-kΩ linear-taper potentiometer functions as a voltage divider. It is adjusted to keep the voltage applied to the gate of the SCR within the +1.5-volt maximum rating of the Radio Shack device used. The lamp is installed near the garage door where it is easily checked upon returning home. Although the alarm system resets itself automatically after a fixed time interval, the remote lamp continues to glow until switch *S1* is momentarily opened.—*Edward B. Harris, Spring Valley, NY.*

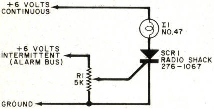

Perforated Construction Aid

Those who assemble electronic projects using perforated board and point-to-point wiring techniques can obtain more professional results in less time if the board is photocopied before it is wired. Such photocopies will contain arrays of dots corresponding to the board's holes, and the spacing between adjacent dots will be almost exactly the same as that between adjacent board perforations. Prototype component layouts and wiring pictorials can be drawn on photocopies of the board using full-size renditions of the components to be mounted on it.

Working out the "bugs" of a circuit board on paper at the proper scales reduces assembly time and results in improved project appearance. Component spacing on the board will be perfect if the art-work is used as a guide during construction. What's more, a permanent record is generated, simplifying circuit duplication should that be necessary in the future.—*J.C. Smolski, Wilton, NH.*

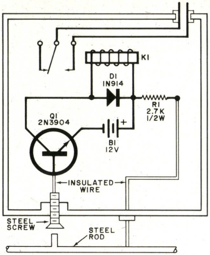

A

Basement Flood Alarm

This circuit is intended for those people who are unlucky enough to have leaky basements. It is designed to give a resident early warning of rising water so that he can take the necessary steps to correct the problem. It is shown schematically in Fig. A. Battery *B1* is a 12-volt power source and can be two 6-volt lantern batteries or 8 D cells connected in series. When the rising water causes the steel rod to contact the screw (by means of a flotation device as shown in Fig. B), base current flows through *Q1*. The transistor then conducts and energizes relay *K1*. The relay contacts can be connected to an alarm, a pump, or any combination of devices.

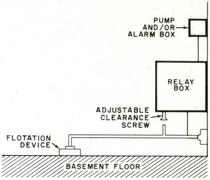

B

The only precautions that must be observed are that the relay contacts are rated to handle the current drawn by the load(s) connected to them and that the coil current does not exceed the rated collector current of *Q1* (200 mA). The best location for the flood alarm is either in a corner of the basement or at a low spot where water should most likely collect. The screw is adjustable so that the relay will be energized when the water reaches a predetermined level.—*Donald R. Swenson, Webster, WI.*

Do you want Advertising or Information?

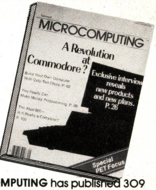
MICROCOMPUTING
A Revolution at Commodore?
Exclusive interview reveals new products and new plans. P.26
Special PET Focus

Sure ads in a magazine are helpful . . . in fact, few will be more helpful to you than this one, which can save you hundreds of dollars . . . but you want to get as much information as you can. This is why **Kilobaud MICROCOMPUTING** bears some investigation.

To put it right on the line . . . so far this year **MICROCOMPUTING** has published 309 articles (technical programs you can use, mostly written for the newcomer to computing). Compare that with #2 in the field, **80 MICROCOMPUTING**, which has only published 257 articles. Number three is **Byte** with 93 articles . . . way down the list when it comes to giving you information.

Remember that it is solely through magazine articles that you can keep up with the state of the art. Books are a year behind. Only through magazines can you have an invaluable encyclopedia of microcomputer information. **MICROCOMPUTING** has published 1148 articles during the past year. No other magazine has even come close to giving you so much valuable information.

Send in the coupon below and we'll send you an issue of **MICROCOMPUTING** plus an invoice for $25 (you save about one-third the cost of the magazine in the stores). If you aren't absolutely delighted with that first issue, just cancel the subscription. What could be fairer than that?

☐ YES! . . . Bill me $25 for one year.

Name____________________

Address____________________

City__________ State________ Zip________

Canadian $27/1 year only. Foreign $35/1 year only, US funds.
Please allow 6-8 weeks for delivery.
Kilobaud Microcomputing•PO Box 997•Farmingdale NY 11737

71JBP

CIRCLE NO. 34 ON FREE INFORMATION CARD

FREE
48-Page
Catalog

A new, free 48-page catalog is free from Creative Computing and Peripherals Plus. To help buyers make intelligent purchasing decisions, the product descriptions are exceptionally comprehensive and include screen photos in the software section.

The catalog describes 20 books on programming, games, and educational applications; 160 software packages for Apple, Atari, TRS-80, PET, CP/M, TI, Sorcerer and Sol computers; 3 magazines (*Creative Computing*, *Microsystems*, and *SYNC*); 5 graphics and music peripherals; an LP record; board game; 8 T-shirts and an eclectic assortment of other products for the personal computer user.

To get your free copy, simply drop a card or note to the address below.

creative computing
Attn: Charlene
39 East Hanover Avenue
Morris Plains, NJ 07960

CIRCLE NO. 9 ON FREE INFORMATION CARD

CALCULATOR SAVINGS

HEWLETT PACKARD

HP-32E Scientific	$42.95
HP-33C Programmable	68.95
HP-34C Adv. Program.	114.95
HP-37E Financial	58.95
HP-38C Adv. Financial	114.95
HP-41C Alpha Program.	187.95
HP-41CV (Full Memory)	237.95
HP-41CV Syst.I (w/crd.rdr)	379.95
HP-41CV Syst.II (C.R.,Prtr)	639.95
Card Reader/41	164.95
Printer/41	289.95
Optical Wand/41	92.95
Memory Module/41C	23.95
Quad Memory/41C	76.95
HP-67 Programmable	287.95
HP-97 Desk Program.	579.95
HP-85 Desk Computer	2495.00

Call for Low Prices on all Calculator and Computer Accessories.

TEXAS INSTRUMENTS

TI-35	$19.95	TI-59	$209.95	TI-99/4 Console	$449.95
TI-55	32.95	PC-100C	159.95	Language Tutor	129.95
TI-57	39.95	Progrmr	49.95	Speak & Spell	59.95
TI-58C	99.95	TI-5040	67.95	Business Analyst II	39.95

Call for Low Prices on All TI Calculators and Watches

Sharp	PC-1211 Handheld Computer	CALL
	EL-5100 Alphanumeric scientific programmable	69.95
	EL-5101 Alphanumeric scientific programmable	39.95
	EL-6200 Compact message center, 37 alarms	84.95
	EL-7000 Miniature typewriter and calculator	99.95
	CT-660E Talking digital alarm clock	59.95
Casio	FX-602P Slim programmable, 500 steps	79.95
	FX-3500P Slim programmable, 38 steps	34.95
	ML-75 12 melody credit card calc. w/alarm	34.95
	M-10 Compact musical keyboard	124.95
	W-100 Water sports alarm chrono, 325 feet	34.95
	M-12 12 melody alarm chrono	39.95
	CA-90 Calculator alarm chrono watch	44.95
Pearlcorder	S202 Microcassette tape recorder	79.95
	S802 Two-speed, two-hour recorder	99.95
	S801 Olympus' smallest, two-hour	139.95
Craig	M100 Language translator	69.95
Canon	P5-D Smallest rechargeable print and display	49.95
	P10-D World's most popular mini printer	69.95

For faster delivery use cashier's check or money order. Add shipping: 1% of your order ($2.75 min.). East of Missp Riv. add $1.50. CA Res add 6%. Subject to availability. VISA and MC accepted.

ORDER TOLL-FREE **800-421-5188** Outside CA, AK, HI
Information line (213) 633-3262

tam's INCORPORATED

Tam's Dept. PE-5
14932 Garfield Ave.
Paramount, CA 90723
(213) 633-3262

CIRCLE NO. 57 ON FREE INFORMATION CARD

Experience
The World's Most
Versatile Microcomputer

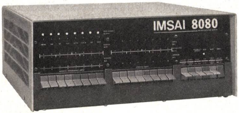

IMSAI T.M
8080

Kit *$599.00*
Assembled *$799.00*

Includes:
- 22-Slot Motherboard with Sockets
- 28 Amp Power Supply
- MPU-A 8080 2 Mhz. Processor
- Programmer's Front Panel

Send Check or Money Order to

IMSAI Computer Division of the Fischer-Freitas Corporation
910 81st Avenue, Bldg. 14 • Oakland, CA 94621
415/635-7615

Imsai is a trademark of the Fischer-Freitas Corporation

CIRCLE NO. 56 ON FREE INFORMATION CARD

ELECTRONICS LIBRARY

Digital Electronics

by Christopher E. Strangio

This book can serve as a comprehensive introduction to digital electronics. It ranges from basic concepts right on up complex to digital computers. Early chapters are devoted to entry-level discussions of logic concepts, boolean algebra, combinational logic circuits and Karnaugh mapping, binary number operations, and the octal and hexa-decimal codes. Details for analyzing and designing flip-flop, counter, and sequential circuits are then discussed, followed by practical digital-circuit fault analysis. *Published by Prentice-Hall, Inc., Englewood Cliffs, NJ 07632. Hard cover. 523 pages. $24.95.*

CRT Controller Handbook

by Gerry Kane

Here's a reference book for the person who wants to understand design of controller circuits for displaying alphanumerics and graphics on the screen of a cathode ray tube. The first chapter provides general information on the basics of CRT operation. After covering technical details of the CRT itself, it delves into such topics as character-generation logic, screen memory, manipulation of screen data, etc., and finishes up with a section that compares five popular LSI controller chips. Each of the remaining five chapters is devoted to detailed descriptions of one of these controller chips. *Published by Osborne/McGraw-Hill, 630 Bancroft Way, Berkeley, CA 94710. Soft cover. 216 pages. $6.99.*

Pascal

by David L. Heiserman

If you're thinking of moving up to Pascal programming with your microcomputer, this book offers a painless way of learning how to use and manipulate this powerful high-level computer language. The example used in the text is Tiny Pascal written for a TRS-80 II microcomputer. (Tiny Pascal for microcomputers is an abbreviated form of Standard Pascal that can be run only in large computer systems.) Except for a few graphics commands unique to the TRS-80, the material covered in this book is equally applicable to almost any other microcomputer/Pascal system. The text makes no assumption that the reader is conversant with Pascal. To this end, every step is clearly spelled out, from powering up the TRS-80 to running programs written in Pascal.
Published by Tab Books, Blue Ridge Summit, PA 17214. Soft cover. 350 pages. $9.95.

OPERATION ASSIST

If you need information on outdated or rare equipment—a schematic, parts list, etc.—another reader might be able to assist. Simply send a postcard to Operation Assist, POPULAR ELECTRONICS, 1 Park Ave., New York, NY 10016. For those who can help readers, please respond directly to them. They'll appreciate it. (Only those items regarding equipment not available from normal sources are published.)

Hickok model 610A alignment signal generator (serial #4211032), **Precision** model #-200-C signal generator and **Pioneer** model QL600 quadralizer amplifier. Need operation manuals and schematics. David Gettys, 3305 Wayside, Ft. Worth, TX 76110.

Borg Warner model EI-1 electronic ignition kit. Need schematic and parts list. Robert Seward, 808 Shoreham, Grosse Pointe Woods, MI 48236.

Test model 1006-007 converter. Need schematic and service manual. E.Smith, Box 688, Greenwood, IN 46142.

National NC57M and **Hallicrafters** S-38 general coverage receivers. Need schematics, operating manuals and alignment manuals. Michael O'Neil, 43 Spring Garden St., Valley Stream, NY 11580.

Electronic Research Associates, model TR36-4M power supply and **Atwater Kent** model 60 radio. Need any information available. Paul B. Shelton, 9004 E. 29th Pl., Tulsa, OK 74129.

Grundig model S0121 stereo console. Need schematic. Nils Kinne, 2 Stark St., Nashua, NH 03060.

Chicago Industrial Instrument Co., VTVM model 504. Need schematic or bridge circuit information. C. Bischoff, 533 Forest Rd., Wayne, PA 19087.

E&R Research Co., power supply model 138A3A. Need schematic. E.M. Crush, 9302 Ledbury Rd, Richmond, VA 23229.

Sony superscope model 555-A. Need operating manual and schematic. Herbert W. Klumpe, III, Box 32, Catskill Turnpike, Meredith, NY 13805.

Mostek series MK50310 calculator. Need spec sheet and printed circuit board. Duane Kincheloe, Box 287, Iola, KS 66749.

U.S. Navy OS-8 scope. Need manual and schematic. Randall Keils, 127 Elm St., Kalamazoo, MI 49007.

Sears Silvertone model 6026, service #132.602601 TV. Need schematic and service literature. Vaughn Dade, 225 Gale St., Akron, OH 44302.

Melcor model SC535 calculator. Need schematic and repair instruction. Moe Lynn, 10644-146 St., Edmonton AB, Canada T5N3A7.

RCA WV-98-B senior voltohmyst. Need schematic. C. Mazurek, 1963 Evergreen Ave., Chicago, IL 60622.

Dynamic Instrumentation model 4132 micrometer and **Sorenson** dc power supply, model DCR150-15. Need servicing information. J.A. Call, 1876 E. 2990 So., Salt Lake City, UT 84106.

Koss Pro 4AA stereophones. Need diaphragm and voice coil. Timothy Hu, 906 N. Ash St., Gordon, NB 69343.

B&K Precision model 960 transistor radio analyst. Need operating manual and realignment guide. Wilfrid Joseph Cote III, 704 So. Filbert St., Stockton, CA 95205.

Fisher solid state stereo model A-192. Need schematic. Norman Cizek, 1212 Kinne St., East Syracuse, NY 13057.

National model NC-57 transceiver. Need schematic and owner's manual. Paul Cesario, 192-2 Bolton St., Marlboro, MA 01752.

Knight model KG-2000 scope. Need schematic and instruction manual. Craig Suhr, Page, NC 58064.

Texas Instruments model TI-58 programmable calculator. Need schematic. Bernard Eisenkratt, 1043 E. 81 St., Brooklyn, NY 11236.

Allied Radio #83Y125 305009 VTVM. Need schematic and manual. G.L. Jones, 10071 N.E. South Beach Dr., Bainbridge Island, WA 98110.

Eico model 360 signal generator and B & K model 177 VTVM. Need parts, service data and schematics. Victor S. Lopez Avila, N. Garcia y Lastres 258-260, Urb. Ingenieria, Lima, Peru.

Lafayette model 99-33094 antenna impedance meter and **Hallicrafters** model SW-100 receiver. Need service manuals. Peter Calendo, 968 Hertel Avenue, Buffalo, NY 14216.

Umtech videobrain computer. Need schematic and source for cartridges and interface. Bruce North, 2477 Dalton, Ann Arbor, MI 48104.

Instrument Designs, Inc. model 657 engine analyzer. Need service information. Paul Fleming, 8008 Comet Dr., Oxon Hill, MD 20022.

Kinsman model E organ. Need any information available. John D. Guerard, 306 N. 2nd St., Alhambra, CA 91801.

Lavoie Labs military surplus U.S. Navy OS-62B/USM SO oscilloscope. Need schematics and manuals. Tom Jasinski, 503 Jensen, Shorewood, IL 60436.

Claricon Products 36-215 (tuner) and 36-155 (amplifier). Need schematics. Howard Karsh, 97 Third Avenue, New York, NY 10003.

Allied Radio model 498 receiver. Need schematic and operation manual. G. Hill, 8109 St. David Ct., Springfield, VA 22153.

Hallicrafters S-120 receiver. Need schematic, alignment information and manual. Kurt R. Warner, 1332 S.E. Center St., Portland, OR 97202.

Midland 13-880 23 channel CB. Need pc board. L. Harrison, 205 Stone, Joliet, IL 60435.

RCA model 73B mono record master cutting machine. Need instruction manual, parts or any information available. Thomas Squidd, Box 261, Madison Hts., MI 48071.

Knight-Kit model KG-2000 oscilloscope. Need calibration and maintenance manual and schematic. Melvin Thomas, 1793 S. Hamilton Blvd., Pomona, CA 91766.

Hallicrafters model SW-500 receiver. Need schematic and alignment procedures. F.C. Lester, 2610 W. Verdugo Ave., Burbank, CA 91505.

Manke Instruments ac volt meter. Need instruction book. Donald Bisbee, 685 S. Roys Ave., Columbus, OH 43204.

Precision electronic tube tester, series 10-12 and 1015. Need tube charts form MRC-C2A. Peter J. Cotte, 372 W. Scott Ave., Rahway, NJ 07065.

Lectrotech model V-7 generator. Need all information available. Ernest Evans, Box 275A Kittatiny, R.D. 4, Lehighton, PA 18235.

Vox Essex bass amplifier. Need schematic. David Doyle, 4515 Benhurst Ave., San Diego, CA 92122.

Elan model 2 ignition scope. Need schematic. Kurt Bendit, 3927 19th St., San Francisco, CA 94114.

B&K model 400 cathode rejuvenator tester and model 700 tube tester. Need schematics, service manuals and operation manuals. Steven Black, 1810 S. Perkins Rd., #4, Stillwater, OK 74074.

Tektronix 585 oscilloscope and type CA plug-in unit. Schematics and manuals needed. Philip Stevens, 5001 Bull Creek #117, Austin, TX 78731.

Sears & Roebuck Co. Silvertone color TV model 4288, chassis #52972480. Need schematic diagram and service manual. Ed Herbert, 410 N. Third St., Minersville, PA 17954.

Components Corp. ring modulator for model TD-687/URR demultiplexer needed. Charles T. Huth, 146 Schonhardt St., Tiffin, OH 44883.

Allied Radio Knight Star Roamer SWR. Need schematic or assembly manual. Paul Yoder, 1438 Lathrop Ave., Racine, WI 53405.

EAST / WEST
ΩMEGA SALES CO

SPECIAL OF THE MONTH!

ATARI 800
16K
$ 759

APPLE II Plus 48K
$1169

EPSON MX-80 PRINTER
Call for Price
INTERFACES: IEEE $55,
TRS•80 $35, RS • 232 $70
APPLE INTERFACE
+ CABLE $90.

RADIO SHACK
16K Level II Model 3
$ 875

NEC 5510 SPINWRITER	**$2495**
INTERTEC SUPERBRAIN 64K RAM	$2849
OKIDATA MICROLINE - 83	$ 899
OKIDATA MICROLINE - 80	$ 469
APPLE DISK w/3.3 DOS Controller	$ 545
APPLE DISK w/o Controller	$ 435
BASE II Printer	$ 649
DIABLO 630	**$1995**
w/Tractor Option	**$ 200**
HAZELTINE 1420	$ 799
NORTHSTAR HORIZON 32K QD	$2975
ATARI 400 8K	$ 399
ATARI 400 16K	$ 499
RADIO SHACK 64K Model 2	$3449
ANADEX DP - 9500	$1249
NEC MONITOR	**$ 219**
TELEVIDEO 912C	$ 669
TELEVIDEO 920C	$ 729
TELEVIDEO 950	$1049
ATARI 825 Printer	$ 729
ATARI 850 Interface	$ 169
ATARI 810 Disk	$ 449

TWO WAREHOUSE LOCATIONS TO ENSURE FAST DELIVERY!

EAST COAST
1-800-556-7586
12 Meeting Street
Cumberland, RI 02864
1-401-722-1027

WEST COAST
1-800-235-3581
3353 Old Conejo Road
Newbury Park, CA 91320
1-805-499-3678

ΩMEGA SALES CO

PROJECT OF THE MONTH

By Forrest M. Mims

Steam Engine and Whistle Sound Synthesizer

THIS month's project is for model railroaders and anyone else who appreciates the sounds of old-fashioned steam locomotives. A circuit that recreates those nostalgic sounds is shown in Fig. 1.

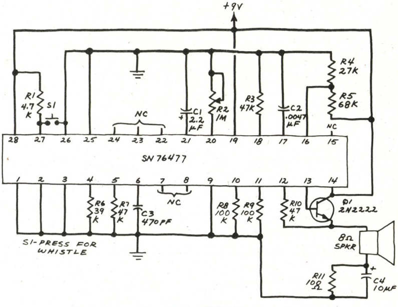

Fig. 1. Schematic using the SN76477 sound-effects chip to generate sounds of a steam locomotive.

Originated at Texas Instruments, the circuit is designed around the SN76477 sound-effects chip. In operation, the output of the chip's noise generator is switched on and off by its super-low-frequency (SLF) oscillator. Potentiometer *R2* controls the switching rate, hence the speed of the engine sound.

When *R2*'s resistance is high, the sound resembles that of a stopped train whose engine is idling. As the potentiometer's effective resistance is reduced, the sound speeds up and resembles that produced by an accelerating train.

The sound of the train's whistle is derived from the output of the voltage controlled oscillator (vco) in the SN76477. The values of *C2* and *R3* control the whistle's pitch. Pressing *S1* activates the whistle.

The output of the SN76477 is amplified by *Q1*, which in turn drives a small 8-ohm speaker. Resistor *R11* controls the amplitude of the sound from the speaker. If you prefer, you can drive an external audio power amplifier with the signal voltage appearing between pin 13 of the IC and ground.

For a little more money, you can buy the SN76488. This chip has everything that the SN76477 has, as well as a built-in amplifier, but it has a different pinout. If you use this chip, omit *Q1* from the circuit in Fig. 1 and connect pin 13 directly to one terminal of the speaker. Connect the second speaker terminal to ground through *C4*. Resistors *R10* and *R11* should be omitted.

A drawback of the circuit in Fig. 1 is that the steam-engine sound generator is disabled when the whistle is activated. This problem can be remedied by adding a simple whistle-multiplexer circuit (Fig. 2) and by removing *S1* from the circuit of Fig. 1.

When activated, the whistle multiplexer, which was also suggested by Texas Instruments, switches the whistle on and off at a rate of 26 kHz. Even though the steam-engine sound is turned off when the whistle is on, the switching rate is far too fast for the ear to detect. Consequently, the whistle seems to be superimposed on the sound of the engine. The only audible effect of the whistle multiplexer on the steam-engine sound is a slight reduction in volume when the whistle is activated.

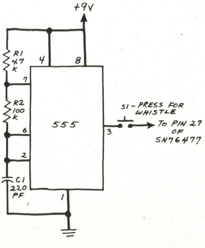

Fig. 2. Whistle multiplexer for steam-engine simulator.

Model railroaders might want to modify this circuit so that the engine sound speeds up *automatically* when a model train is accelerating. This can be done with the help of a homemade optoisolator made from a small lamp and a cadmium-sulfide photocell. Use black electrical tape or heat-shrinkable tubing to mount the lamp adjacent to the photocell and to block ambient light.

Connect the lamp in the optoisolator to the train's transformer. Remove *R2* from the circuit of Fig. 1 and connect the photocell in its place. As the train's speed is increased, the lamp will glow more brightly. This will reduce the resistance of the photocell and increase the rate at which the sound-effects generator is switched on and off by the SLF oscillator.

It might be necessary to add a series resistor between the photocell and the circuit to match the sound of the engine with the speed of the train. You can achieve the same result by blacking out part of the photocell's window. ◇

MICROPROCESSOR SUPPORT I.C.'S

WE GUARANTEE FACTORY PRIME PARTS

We are going to become the largest supplier of prime microprocessor support I.C.'S. We guarantee that our I.C.'S are purchased from manufacturer authorized distributors. This is the only way to deliver prime parts at the lowest possible prices. Our committment is to offer the best price and the fastest delivery to our customer. We give many thanks to our valued customers who have helped us grow.

NEC 16Kx1 DYNAMIC RAM 200 N.S.

These are prime 4116's from one of the best MOS RAM manufacturers in the world.

4116	**200ns**
8 for $25.00	**32 for 96.00**

8080A	**CPU**	**4.95**
8085A	**CPU**	**8.95**
8086	**CPU**	**99.95**
8088	**CPU**	**44.95**
Z-80	**CPU**	**10.50**
Z-80A	**CPU**	**12.95**

2708	**EPROM**	**1Kx8**	**4.95**
2716	**EPROM**	**2Kx8**	**8.95**
2732	**EPROM**	**4Kx8**	**21.00**
4118	**STATIC**	**1Kx8**	**15.00**
4164	**200ns**	**64Kx1**	**Call**
Z80B	**CPU**		**21.00**

NEC 1Kx4 STATIC RAM 250 N.S.

These are prime low power static ram's NEC for the finest in MOS MEMORY.

2114L	**250ns**
8 for $25.00	**32 for $96.00**

Z80-P10	7.75	8755	49.95	4050	.69	4531	.99	74C925	6.95	74LS107	.45	74LS244	1.95
Z80A-P10	9.75	4000	.35	4051	1.10	4532	1.25	74LS00	.35	74LS109	.45	74LS245	4.95
Z80-CTC	7.75	4001	.35	4052	1.10	4539	.99	74LS01	.28	74LS112	.49	74LS247	1.10
Z80ACTC	9.75	4002	.35	4053	1.10	4543	1.99	74LS02	.28	74LS122	.55	74LS248	1.10
Z80-DMA	22.25	4006	1.39	4055	3.95	4553	3.50	74LS03	.28	74LS123	1.19	74LS249	1.69
Z80A-DMA	27.75	4007	.29	4056	2.95	4555	.75	74LS04	.39	74LS125	1.35	74LS251	1.79
Z80-S10/0	24.95	4008	1.39	4059	9.95	4556	.75	74LS05	.28	74LS126	.89	74LS253	.98
Z80A-S10/0	29.95	4009	.49	4060	1.39	4581	1.99	74LS08	.39	74LS132	.79	74LS257	.98
Z80-S10/1	24.95	4010	.49	4066	.75	4582	1.01	74LS09	.39	74LS136	.59	74LS258	.98
Z80A-S10/1	29.95	4011	.35	4068	.35	4584	.55	74LS10	.28	74LS138	.89	74LS259	2.95
Z80-S10/2	24.95	4012	.29	4069	.35	4585	.99	74LS11	.39	74LS139	.89	74LS260	.69
Z80A-S10/2	29.95	4013	.49	4070	.49	4702	9.95	74LS12	.39	74LS145	1.25	74LS261	2.49
3205	3.95	4014	1.39	4071	.35	74C00	.39	74LS13	.47	74LS148	1.49	74LS266	.59
3242	10.00	4015	1.15	4072	.35	74C02	.39	74LS14	1.25	74LS151	.79	74LS273	1.75
8155	11.25	4016	.59	4073	.35	74C04	.39	74LS15	.39	74LS153	.79	74LS275	4.40
8185	29.95	4017	1.19	4075	.35	74C08	.49	74LS20	.26	74LS155	1.19	74LS279	.59
8185-2	39.95	4018	.99	4076	1.29	74C10	.49	74LS21	.38	74LS156	.99	74LS283	1.10
8202	45.00	4019	.49	4078	.35	74C14	1.65	74LS22	.38	74LS157	.99	74LS290	1.29
8205	3.95	4020	1.19	4081	.35	74C20	.39	74LS26	.39	74LS158	.75	74LS293	1.95
8212	2.00	4021	1.19	4082	.35	74C30	.39	74LS27	.39	74LS160	.98	74LS295	1.10
8214	3.95	4022	1.15	4085	1.95	74C32	.99	74LS28	.39	74LS161	1.15	74LS298	1.29
8216	1.85	4023	.38	4086	.79	74C42	1.85	74LS30	.26	74LS162	.98	74LS324	1.75
8224	2.65	4024	.79	4093	.99	74C48	2.39	74LS32	.39	74LS163	.98	74LS347	1.95
8226	1.85	4025	.38	4099	2.25	74C73	.85	74LS37	.79	74LS164	1.19	74LS348	1.95
8228	5.00	4026	2.50	4104	1.99	74C74	.85	74LS38	.39	74LS165	.89	74LS352	1.65
8238	5.45	4027	.65	4501	.39	74C85	2.49	74LS42	.79	74LS166	2.49	74LS353	1.65
8243	4.65	4028	.85	4502	1.65	74C89	4.95	74LS47	.79	74LS170	1.99	74LS363	1.49
8251A	5.55	4029	1.29	4503	.69	74C90	1.85	74LS48	.79	74LS173	.89	74LS365	.99
8253	9.85	4030	.45	4505	8.95	74C93	1.85	74LS51	.26	74LS174	.99	74LS366	.99
8255A	5.40	4031	3.25	4506	.75	74C95	1.85	74LS54	.35	74LS175	.99	74LS367	.73
8255A-5	5.40	4032	2.15	4507	.95	74C107	1.19	74LS55	.35	74LS181	2.20	74LS368	.73
8257	9.25	4033	2.15	4508	3.95	74C151	2.49	74LS73	.45	74LS190	1.15	74LS373	2.75
8257-5	9.25	4034	3.25	4510	1.39	74C154	3.50	74LS74	.59	74LS191	1.15	74LS374	2.75
8259A	7.30	4035	.95	4511	1.39	74C157	2.10	74LS75	.68	74LS192	.98	74LS375	.69
8271	60.00	4037	1.95	4512	1.39	74C160	2.39	74LS76	.45	74LS193	.98	74LS377	1.95
8275	32.95	4040	1.29	4514	3.95	74C161	2.30	74LS78	.65	74LS194	1.15	74LS385	1.95
8279	10.80	4041	1.25	4515	3.95	74C163	2.39	74LS83	.99	74LS195	.95	74LS386	.65
8279-5	10.80	4042	.95	4516	1.69	74C164	2.39	74LS85	1.19	74LS196	.89	74LS390	1.95
8282	6.70	4043	.85	4519	.99	74C173	2.59	74LS86	.45	74LS197	.89	74LS393	1.95
8283	6.70	4044	.85	4520	1.39	74C174	2.75	74LS90	.75	74LS221	1.49	74LS395	1.70
8284	5.85	4046	1.75	4522	.99	74C175	2.75	74LS92	.75	74LS240	1.95	74LS399	2.95
8286	6.70	4047	1.25	4526	1.15	74C192	2.39	74LS93	.75	74LS241	1.90	74LS424	2.95
8287	6.70	4048	.99	4527	1.75	74C193	2.39	74LS95	.88	74LS242	1.95	74LS668	1.75
8288	25.40	4049	.69	4528	.99	74C195	2.39	74LS96	.98	74LS243	1.95	74LS670	2.29
8289	49.95												

MAIL ORDERS SHOULD BE SENT TO:
P.O. Box 21432 Seattle, Washington 98111
Telephone Orders & Inquiries (206) 453-0792
Minimum Order $10.00 Add $3.00 Shipping

HANLEY ENGINEERING

RETAIL STORE
1644 116th NORTHEAST
BELLEVUE, WASHINGTON 98005

FOR THE FINEST IN MICROPROCESSOR SUPPORT I.C.'S

CIRCLE NO. 24 ON FREE INFORMATION CARD

7400

Part	Price
SN7400N	.25
SN7401N	.20
SN7402N	.25
SN7403N	.25
SN7404N	.25
SN7405N	.29
SN7406N	.35
SN7407N	.35
SN7408N	.29
SN7409N	.29
SN7410N	.25
SN7411N	.29
SN7412N	.35
SN7413N	.40
SN7414N	.69
SN7416N	.29
SN7417N	.29
SN7420N	.25
SN7421N	.29
SN7422N	.45
SN7423N	.29
SN7425N	.29
SN7426N	.29
SN7427N	.25
SN7428N	.49
SN7430N	.25
SN7432N	.29
SN7437N	.25
SN7438N	.40
SN7439N	.25
SN7440N	.20
SN7441N	.89
SN7442N	.59
SN7443N	1.10
SN7444N	1.10
SN7445N	.89
SN7446N	.79
SN7447N	.69
SN7448N	.79
SN7450N	.20
SN7451N	.20
SN7453N	.20
SN7454N	.20
SN7459A	.25
SN7460N	.20
SN7470N	.29
SN7472N	.29
SN7473N	.35
SN7474N	.35
SN7475N	.49
SN7476N	.35
SN7479N	5.00
SN7480N	.50
SN7482N	.99
SN7483N	.69
SN7485N	.89
SN7486N	.35
SN7489N	1.75
SN7490N	.49
SN7491N	.59
SN7492N	.45
SN7493N	.45
SN7494N	.69
SN7495N	.69
SN7496N	.69
SN7497N	3.00
SN74100N	1.49
SN74107N	.35
SN74109N	.39
SN74116N	1.95
SN74121N	.39
SN74122N	.55
SN74123N	.59
SN74125N	.49
SN74126N	.49
SN74132N	.75
SN74136N	.75
SN74141N	.99
SN74142N	3.25
SN74143N	3.49
SN74144N	3.49
SN74145N	.79
SN74147N	1.95
SN74148N	1.29
SN74150N	1.25
SN74151N	.69
SN74152N	.69
SN74153N	.79
SN74154N	1.25
SN74155N	.79
SN74156N	.79
SN74157N	.69
SN74160N	.89
SN74161N	.89
SN74162N	.89
SN74163N	.89
SN74164N	.89
SN74165N	.89
SN74166N	1.25
SN74167N	2.79
SN74170N	1.95
SN74172N	4.95
SN74173N	1.39
SN74174N	.99
SN74175N	.89
SN74176N	.79
SN74177N	.79
SN74179N	1.49
SN74180N	.79
SN74181N	2.25
SN74182N	.79
SN74184N	2.49
SN74185N	2.49
SN74190N	1.25
SN74191N	1.25
SN74192N	.89
SN74193N	.89
SN74194N	.89
SN74195N	.69
SN74196N	.89
SN74197N	.89
SN74198N	1.49
SN74199N	1.49
SN74221N	1.25
SN74251N	.99
SN74276N	1.95
SN74279N	.79
SN74283N	1.49
SN74284N	3.95
SN74285N	3.95
SN74365N	.69
SN74366N	.69
SN74367N	.69
SN74368N	.69
SN74390N	1.49
SN74393N	1.49

74LS

Part	Price
74LS00	.29
74LS01	.29
74LS02	.29
74LS03	.29
74LS04	.35
74LS05	.35
74LS08	.29
74LS09	.35
74LS10	.29
74LS11	.75
74LS12	.35
74LS13	.59
74LS14	.99
74LS15	.35
74LS20	.29
74LS21	.35
74LS22	.35
74LS26	.35
74LS27	.35
74LS28	.35
74LS30	.29
74LS32	.35
74LS33	.59
74LS37	.45
74LS38	.49
74LS40	.35
74LS42	.89
74LS47	.89
74LS48	1.15
74LS49	1.15
74LS51	.29
74LS54	.29
74LS55	.29
74LS73	.45
74LS74	.45
74LS75	.59
74LS76	.45
74LS78	.49
74LS83	.89
74LS85	1.25
74LS86	.45
74LS90	.59
74LS92	.75
74LS93	.75
74LS95	.99
74LS96	1.15
74LS107	.45
74LS109	.45
74LS112	.45
74LS113	.49
74LS114	.49
74LS122	.89
74LS123	1.25
74LS125	.89
74LS126	.55
74LS132	.99
74LS133	.89
74LS136	.49
74LS138	.89
74LS139	.89
74LS151	.89
74LS153	.89
74LS154	1.75
74LS155	1.19
74LS156	1.19
74LS157	.89
74LS158	.99
74LS160	1.15
74LS161	1.15
74LS162	1.15
74LS163	1.15
74LS164	1.25
74LS165	1.25
74LS168	1.19
74LS169	1.19
74LS170	2.49
74LS173	1.39
74LS174	.99
74LS175	.99
74LS181	2.95
74LS190	1.25
74LS191	1.25
74LS192	1.15
74LS193	1.15
74LS194	1.15
74LS195	1.15
74LS197	1.19
74LS221	1.19
74LS240	1.95
74LS241	1.95
74LS242	1.95
74LS243	1.95
74LS244	1.95
74LS245	2.95
74LS247	1.19
74LS248	1.19
74LS249	1.19
74LS251	1.49
74LS253	.99
74LS257	.89
74LS258	.99
74LS260	.69
74LS266	.69
74LS273	1.95
74LS279	.75
74LS283	1.09
74LS290	.99
74LS293	.99
74LS298	1.25
74LS352	1.29
74LS353	1.29
74LS365	.75
74LS366	.75
74LS367	.75
74LS368	.75
74LS373	1.95
74LS374	1.95
74LS375	.89
74LS386	.69
74LS393	2.49
74LS399	2.49
74LS670	2.49
81LS95	1.95
81LS97	1.95

74S

Part	Price
74S00	.50
74S02	.50
74S03	.50
74S04	.55
74S05	.55
74S08	.50
74S09	.50
74S10	.50
74S11	.50
74S15	.50
74S20	.50
74S22	.50
74S30	.50
74S32	.55
74S40	.55
74S51	.50
74S64	.50
74S65	.50
74S74	.79
74S86	.79
74S112	.79
74S113	.79
74S114	.79
74S133	.55
74S134	.69
74S135	1.19
74S136	1.75
74S138	1.35
74S139	1.35
74S140	1.15
74S151	1.35
74S153	1.35
74S157	1.35
74S158	1.35
74S174	1.59
74S175	1.59
74S188	4.95
74S194	1.95
74S195	1.95
74S196	3.95
74S240	2.95
74S241	2.95
74S242	3.25
74S243	3.25
74S244	3.25
74S251	1.45
74S253	1.45
74S257	1.35
74S258	1.35
74S260	.79
74S280	2.95
74S287*	4.95
74S288*	4.95
74S373	3.49
74S374	3.49
74S387*	5.95
74S471*	19.95
74S472*	19.95
74S473*	19.95
74S474*	21.95
74S475*	21.95
74S570*	7.95
74S571*	7.95
74S572*	19.95
74S573*	19.95
74S940	3.15
74S941	3.15

* LIMITED AVAILABILITY ON THESE PROMS

CA–LINEAR

Part	Price
CA3013H	2.15
CA3023H	3.25
CA3039H	1.35
CA3046N	1.30
CA3059N	3.25
CA3060N	3.25
CA3080H	1.25
CA3081N	2.00
CA3082N	2.00
CA3083N	1.60
CA3086N	.85
CA3089N	3.75
CA3096N	3.95
CA3130H	1.39
CA3140H	1.25
CA3160H	1.25
CA3401N	.59
CA3600N	3.50

CD–CMOS

Part	Price
CD4000	.39
CD4001	.39
CD4002	.39
CD4006	1.19
CD4007	.25
CD4009	.49
CD4010	.49
CD4011	.39
CD4012	.25
CD4013	.49
CD4014	1.39
CD4015	1.19
CD4016	.59
CD4017	1.19
CD4018	.99
CD4019	.49
CD4020	1.19
CD4021	1.39
CD4022	1.19
CD4023	.29
CD4024	.79
CD4025	.23
CD4026	2.95
CD4027	.69
CD4028	.89
CD4029	1.49
CD4030	.49
CD4035	.99
CD4040	1.49
CD4041	1.49
CD4042	.99
CD4043	.89
CD4044	.89
CD4046	1.79
CD4047	2.50
CD4048	1.35
CD4049	.49
CD4050	.69
CD4051	1.19
CD4052	1.19
CD4053	1.19
CD4056	2.95
CD4059	9.95
CD4060	1.49
CD4066	.79
CD4068	.39
CD4069	.45
CD4070	.55
CD4071	.49
CD4072	.49
CD4073	.39
CD4075	.39
CD4076	1.39
CD4078	.55
CD4081	.39
CD4082	.39
CD4093	.99
CD4098	2.49
CD4506	.75
CD4507	.99
CD4508	3.95
CD4510	1.39
CD4511	1.29
CD4514	3.95
CD4515	2.95
CD4516	1.49
CD4518	1.79
CD4519	.89
CD4520	1.29
CD4526	1.79
CD4528	1.79
CD4529	1.95
CD4543	2.79
CD4562	11.95
CD4566	2.79
CD4583	2.49
CD4723	1.95
CD4724	1.95
MC14409	14.95
MC14410	14.95
MC14411	14.95
MC14412	11.95
MC14419	4.95
MC14433	13.95

A P PRODUCTS

DIP JUMPERS

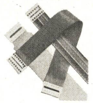

- Mate with Standard IC Sockets
- Fully Assembled and Tested
- Integral Molded-On Strain-Relief
- Line-By-Line Probeability

Dip Jumpers are used for jumpering within a PC Board; interconnecting between PC Boards, backplanes and mother boards; and interfacing input/output signals.

Part Number	No. of contacts	Description	Wire Length	Price
924102-12	14	single end	12"	$1.51
924102-24	14	single end	24"	1.92
924102-36	14	single end	36"	2.33
924106-12	14	double end	12"	2.61
924106-24	14	double end	24"	3.02
924106-36	14	double end	36"	3.43
924112-12	16	single end	12"	1.67
924112-24	16	single end	24"	2.13
924112-36	16	single end	36"	2.59
924116-12	16	double end	12"	2.88
924116-24	16	double end	24"	3.34
924116-36	16	double end	36"	3.80
924122-12	24	single end	12"	2.60
924122-24	24	single end	24"	3.30
924122-36	24	single end	36"	4.00
924126-12	24	double end	12"	4.50
924126-24	24	double end	24"	5.20
924126-36	24	double end	36"	5.90
924132-12	40	single end	12"	4.35
924132-24	40	single end	24"	5.53
924132-36	40	single end	36"	6.71

DISCRETE LEDS

Part	Size	Color	Price
XC556R	.200"	red	5/$1
XC556G	.200"	green	4/$1
XC556Y	.200"	yellow	4/$1
XC556C	.200"	clear	4/$1
XC22R	.200"	red	5/$1
XC22G	.200"	green	4/$1
XC22Y	.200"	yellow	4/$1
MV10B	.170"	red	4/$1
MV50	.085"	red	6/$1
XC209R	.125"	red	5/$1
XC209G	.125"	green	4/$1
XC209Y	.125"	yellow	4/$1
XC526R	.185"	red	5/$1
XC526G	.185"	green	4/$1
XC526Y	.185"	yellow	4/$1
XC526C	.185"	clear	4/$1
XC111R	.190"	red	5/$1
XC111G	.190"	green	4/$1
XC111Y	.190"	yellow	4/$1
XC111C	.190"	clear	4/$1

XC556 RED LED, METAL MTG. HDW. 2-6" LEADS.

RL-2 . . $.39 ea. or 3/$1.00

DISPLAY LEDS

C.A. — Common Anode C.C. — Common Cathode

Type	Polarity	Ht	Price
MAN 1	C.A.—red	.270	2.95
MAN 2	5x7 D.M.—red	.300	4.95
MAN 3	C.C.—red	.125	.25
MAN 52	C.A.—green	.300	1.25
MAN 54	C.C.—green	.300	1.25
MAN 71	C.A.—red	.300	.75
MAN 72	C.A.—red	.300	.75
MAN 74	C.C.—red	.300	1.25
MAN 82	C.A.—yellow	.300	.49
MAN 84	C.C.—yellow	.300	.99
MAN 3620	C.A.—orange	.300	.49
MAN 3630	C.A.—orange ± 1	.300	.99
MAN 3640	C.C.—orange	.300	.99
MAN 4610	C.A.—orange	.400	.99
MAN 6610	C.A.—orange—DD	.560	.99
MAN 6630	C.A.—orange ± 1	.560	.99
MAN 6640	C.C.—orange—DD	.560	.99
MAN 6650	C.C.—orange ± 1	.560	.99
MAN 6660	C.A.—orange	.560	.99
MAN 6710	C.A.—red—DD	.560	.99
MAN 6750	C.C.—red ± 1	.560	.99
MAN 6780	C.C.—red	.560	.99
DLO304	C.C.—orange	.300	1.25
DLO307	C.A.—orange	.300	1.25
DLG500	C.C.—green	.500	1.25
DLG507	C.A.—green	.500	1.25
DL704	C.C.—red	.300	1.25
DL707	C.A.—red	.300	1.25
DL728	C.C.—red	.500	1.49
DL741	C.A.—red	.600	1.25
DL746	C.A.—red ± 1	.630	1.49
DL747	C.A.—red	.600	1.49
DL750	C.C.—red	.600	1.49
DLO847	C.A.—orange	.800	1.49
DLO850	C.C.—orange	.800	1.49
DL33B	C.C.—red	.110	.35
FND358	C.C. ± 1	.357	.99
FND359	C.C.	.357	.75
FND503	C.C. (FND500)	.500	.99
FND507	C.A. (FND510)	.500	.99
HDSP-3401	C.A.—red	.800	1.50
HDSP-3403	C.C.—red	.800	1.50
5082-7751	C.A., R.H.D.—red	.430	1.25
5082-7760	C.C., R.H.D.—red	.430	1.75
5082-7300	4x7 sgl. dig. RHD	.600	22.00
5082-7302	4x7 sgl. dig. LHD	.600	22.00
5082-7304	Overnge. char. (±1)	.600	19.95
4N28	Photo Xsistor Opto-Isol.		.99
LIT-1	Photo Xsistor Opto-Isol.		.69
MOC3010	Optically Isol. Triac Driver		1.25

SOCKETS RECEPTACLES

Test TEXTOOL Sockets

ZERO INSERTION FORCE

- ★ Nickel Boron Plating
- ★ G.F. PSF Plastic Body
- ★ For testing IC's

Part No.	Pins	Price
214-3339	14 pin	5.95
216-3340	16 pin	6.49
218-3341	18 pin	7.95
220-3342	20 pin	8.95
222-3343	22 pin	9.95
224-3344	24 pin	9.75
228-3345	28 pin	11.95
240-3346	40 pin	12.95

- ★ Nickel Boron Plating
- ★ G.F. PSF Plastic Body
- ★ Wire Wrap Contacts

Part No.	Pins	Price
214-3592	14 pin	9.75
216-3593	16 pin	9.95
218-3594	18 pin	10.95
220-3595	20 pin	11.95
222-3596	22 pin	12.95
224-3597	24 pin	12.75
228-3598	28 pin	13.95
240-3599	40 pin	15.95

LOW PROFILE (TIN) SOCKETS

	1-24	25-49	50-100
8 pin LP	.17	.16	.15
14 pin LP	.20	.19	.18
16 pin LP	.22	.21	.20
18 pin LP	.29	.28	.27
20 pin LP	.34	.32	.30
22 pin LP	.37	.36	.35
24 pin LP	.38	.37	.36
28 pin LP	.45	.44	.43
36 pin LP	.60	.59	.58
40 pin LP	.63	.62	.61

SOLDERTAIL STANDARD (TIN)

	1-24	25-49	50-100
14 pin ST	.27	.25	.24
16 pin ST	.30	.27	.25
18 pin ST	.35	.32	.30
24 pin ST	.49	.45	.42
28 pin ST	.99	.90	.81
36 pin ST	1.39	1.26	1.15
40 pin ST	1.59	1.45	1.30

SOLDERTAIL (GOLD) STANDARD

	1-24	25-49	50-100
8 pin SG	.39	.35	.31
14 pin SG	.49	.45	.41
16 pin SG	.54	.49	.44
18 pin SG	.59	.53	.48
24 pin SG	.79	.75	.69
28 pin SG	1.10	1.00	.90
36 pin SG	1.65	1.40	1.26
40 pin SG	1.75	1.59	1.45

WIRE WRAP SOCKETS (GOLD) LEVEL #3

	1-24	25-49	50-100
8 pin WW	.59	.54	.49
10 pin WW	.69	.63	.58
14 pin WW	.79	.73	.67
16 pin WW	.85	.77	.70
18 pin WW	.99	.90	.81
20 pin WW	1.19	1.08	.99
22 pin WW	1.49	1.35	1.23
24 pin WW	1.39	1.26	1.14
28 pin WW	1.69	1.53	1.38
36 pin WW	2.19	1.99	1.79
40 pin WW	2.29	2.09	1.89

1/4 WATT RESISTOR ASSORTMENTS – 5%

ASST. 1	5 ea.	10 Ohm 27 Ohm	12 Ohm 33 Ohm	15 Ohm 39 Ohm	18 Ohm 47 Ohm	22 Ohm 56 Ohm	50 pcs.	$1.95
ASST. 2	5 ea.	68 Ohm 180 Ohm	82 Ohm 220 Ohm	100 Ohm 270 Ohm	120 Ohm 330 Ohm	150 Ohm 390 Ohm	50 pcs.	$1.95
ASST. 3	5 ea.	470 Ohm 1.2K	560 Ohm 1.5K	680 Ohm 1.8K	820 Ohm 2.2K	1K 2.7K	50 pcs.	$1.95
ASST. 4	5 ea.	3.3K 8.2K	3.9K 10K	4.7K 12K	5.6K 15K	6.8K 18K	50 pcs.	$1.95
ASST. 5	5 ea.	22K 56K	27K 68K	33K 82K	39K 100K	47K 120K	50 pcs.	$1.95
ASST. 6	5 ea.	150K 390K	180K 470K	220K 560K	270K 680K	330K 820K	50 pcs.	$1.95
ASST. 7	5 ea.	1M 2.7M	1.2M 3.3M	1.5M 3.9M	1.8M 4.7M	2.2M 5.6M	50 pcs.	$1.95
ASST. 8R	Includes Resistor Assts. 1-7 (350 pcs.)							$10.95 ea.

$10.00 Min. Order — U.S. Funds Only
Calif. Residents Add 6% Sales Tax
Postage — Add 5% plus $1 Insurance

Spec Sheets — 25¢
Send 52¢ Postage for your
FREE 1981 JAMECO CATALOG

NEW 1981 CATALOG

Jameco ELECTRONICS

PHONE
ORDERS
WELCOME
(415) 592-8097

MAIL ORDER ELECTRONICS – WORLDWIDE
1355 SHOREWAY ROAD, BELMONT, CA 94002
PRICES SUBJECT TO CHANGE

6/81

INTERSIL

Part No.	Function		Price
7045IPI	CMOS Precision Timer		14.95
7045EV/Kit*	Stopwatch Chip, XTL		22.95
7106CPL	3½ Digit A/D (LCD Drive)		16.95
7106EV/Kit*	IC, Circuit Board, Display		34.95
7107CPL	3½ Digit A/D (LED Drive)		15.95
7107EV/Kit*	IC, Circuit Board, Display		28.95
7116CPL	3½ Digit A/D LCD Dis. HLD.		18.95
7117CPL	3½ Digit A/D LED Dis. HLD.		17.95
7201IDR	Low Battery Volt Indicator		2.25
7205IPG	CMOS LED Stopwatch/Timer		12.95
7205EV/Kit*	Stopwatch Chip, XTL		19.95
7206CJPE	Tone Generator		5.15
7206CEV/Kit*	Tone Generator Chip, XTL		9.95
7207AIPD	Oscillator Controller		6.50
7207AEV/Kit*	Freq. Counter Chip, XTL		11.10
7208IPI	Seven Decade Counter		17.95
7209IPA	Clock Generator		3.95
7215IPG	4 Func. CMOS Stopwatch CKT		13.95
7215EV/Kit*	4 Func. Stopwatch Chip, XTL		19.95
7216AIJI	8-Digit Univ. Counter C.A.		32.00
7216CIJI	8-Digit Freq. Counter C.A.		26.95
7216DIPI	8-Digit Freq. Counter C.C.		21.95
7217IJI	4-Digit LED Up/Down Counter		12.95
7218CIJI	8-Digit Univ. LED Drive		10.95
7224IPL	LCD 4½ Digit Up Counter DRI		11.25
7226AIJL	8-Digit Univ. Counter		31.95
7226AEV/Kit*	5 Function Counter Chip, XTL		74.95
7240IJE	CMOS Bin Prog. Timer/Counter		4.95
7242IJA	CMOS Divide-by-256 RC Timer		2.05
7250IJE	CMOS BCD Prog. Timer/Counter		6.00
7260IJE	CMOS BCD Prog. Timer/Counter		5.25
7555IPA	CMOS 555 Timer (8 pin)		1.45
7556IPD	CMOS 556 Timer (14 pin)		2.20
7611BCPA	CMOS Op Amp Comparator	5MV	2.25
7612BCPA	CMOS Op Amp Ext. Cmvr.	5MV	2.95
7621BCPA	CMOS Dual Op Amp Comp.	5MV	3.95
7631CCPE	CMOS Tri Op Amp Comp.	10MV	5.35
7641CCPD	CMOS Quad Op Amp Comp.	10MV	7.50
7642CCPD	CMOS Quad Op Amp Comp.	10MV	7.50
7660CPA	Voltage Converter		2.95
8069CCQ	50ppm Band—GAP Volt Ref. Diode		2.50
8211CPA	Volt Ref/Indicator		2.50
8212CPA	Volt Ref/Indicator		2.50

* INTERSIL'S EVALUATION KITS

74C

Part	Price
74C00	.39
74C02	.39
74C04	.39
74C08	.39
74C10	.39
74C14	.75
74C20	.39
74C30	.39
74C42	1.39
74C48	1.95
74C73	.79
74C74	.79
74C85	1.95
74C86	.99
74C89	6.95
74C90	1.29
74C93	1.29
74C95	1.59
74C106	.75
74C107	1.89
74C151	2.95
74C154	3.95
74C157	2.25
74C160	1.69
74C161	1.60
74C162	1.49
74C163	1.69
74C164	1.59
74C173	1.39
74C174	1.39
74C175	1.39
74C192	1.69
74C193	1.69
74C195	1.59
74C221	1.95
74C240	2.25
74C244	2.25
74C373	2.49
74C374	2.59
74C901	.89
74C903	1.15
74C911	10.95
74C912	10.95
74C915	1.69
74C917	10.95
74C922	5.49
74C923	5.75
74C925	7.50
74C926	7.50
80C95	.79
80C97	.79

LINEAR

Part	Price
LH0002CN	6.85
LM10CLH	4.50
LM11CLH	4.75
LH0070-OH	6.05
TL071CP	.79
TL072CP	1.39
TL074CN	2.49
LH0082CD	35.80
TL082CP	1.19
TL084CN	2.19
LH0094CD	36.80
LM300H	.99
LM301CN	.35
LM302H	1.95
LM304H	1.95
LM305H	.99
LM307CN	.45
LM308CN	1.00
LM309H	1.95
LM309K	1.25
LM310CN	1.75
LM311H	.90
LM312H	2.49
LM317MP	1.15
LM317T	1.75
LM317K	3.95
LM318CN	1.95
LM319N	1.95
LM320K-5	1.35
LM320K-12	1.35
LM320K-15	1.35
LM320T-5	1.25
LM320T-12	1.25
LM320T-15	1.25
LM323K-5	5.95
LM324N	.99
LM329DZ	.65
LM331N	3.95
LM334Z	1.30
LM335Z	1.40
LM336Z	1.75
LM337T	1.95
LM337MP	1.15
LM338K	6.95
LM339N	.99
LM340K-5	1.35
LM340K-12	1.35
LM340K-15	1.35
LM340T-5	1.25
LM340T-12	1.25
LM340T-15	1.25
LM341P-5	.75
LM341P-12	.75
LM341P-15	.75
LM342P-5	.69
LM342P-12	.69
LM342P-15	.69
LM348N	1.25
LM350K	5.75
LF351N	.60
LF353N	1.00
LF355N	1.10
LF356N	1.10
LM358N	1.00
LM359N	1.79
LM370N	4.49
LM373N	3.25
LM377N	2.95
LM380N	1.25
LM381N	1.95
LM382N	1.79
LM384N	1.95
LM386N-3	1.29
LM387N	1.45
LM389N	1.35
LM392N	.69
LF398N	4.00
LM399H	5.00
TL494CN	4.49
TL496CP	1.75
NE510A	6.00
NE529A	4.95
NE531H	3.95
NE536H	6.00
NE540H	6.00
NE544N	4.95
NE550A	1.30
NE555V	.39
LM556N	.99
NE564N	3.95
LM565N	1.25
LM566CN	1.95
LM567V	1.25
NE570N	4.95
LM702H	.79
LM703CN	.89
LM709N	.49
LM710N	.79
LM711N	.79
LM723N	.69
LM733N	1.00
LM739N	1.19
LM741CN	.35
MC1741SCG	3.00
LM747N	.79
LM748N	.59
LM1014N	2.75
LM1310N	1.95
LM1458CN	.59
LM1488N	1.25
LM1489N	1.25
LM1496N	1.95
LM1556V	1.75
LM1800N	2.95
LM1877N-9	3.25
LM1889N	3.20
LM1896N	1.75
LM2002T	1.49
LM2877P	2.05
LM2878P	2.25
LM2896P-1	2.25
LM3189N	2.95
LM3900N	.69
LM3905CN	1.25
LM3909N	1.15
LM3914N	3.95
LM3915N	3.95
LM3916N	3.95
RC4136N	1.25
RC4151NB	3.95
RC4194TK	5.95
RC4195TK	5.49
KB4428	4.25
KB4429	5.95
LM4500A	3.25
ICL8038B	4.95
LM13080N	1.29
LM13600N	1.49
75138N	1.95
75450N	.89
75451CN	.39

CAPACITOR CORNER

50 VOLT CERAMIC DISC CAPACITORS

Value	1-9	10-99	100+	Value	1-9	10-99	100+
10 pf	.08	.06	.05	.001µF	.08	.06	.05
22 pf	.08	.06	.05	.0047µF	.08	.06	.05
47 pf	.08	.06	.05	.01µF	.08	.06	.05
100 pf	.08	.06	.05	.022µF	.09	.07	.06
220 pf	.08	.06	.05	.047µF	.09	.07	.06
470 pf	.08	.06	.05	.1µF	.15	.12	.10

100 VOLT MYLAR FILM CAPACITORS

.001mf	.12	.10	.07	.022mf	.13	.11	.08
.0022mf	.12	.10	.07	.047mf	.21	.17	.13
.0047mf	.12	.10	.07	.1mf	.27	.23	.17
,01mf	.12	.10	.07	.22mf	.33	.27	.22

+20% DIPPED TANTALUMS (Solid) CAPACITORS

.1/35V	.39	.34	.29	1.5/35V	.41	.37	.29
.15/35V	.39	.34	.29	2.2/35V	.51	.45	.34
.22/35V	.39	.34	.29	3.3/25V	.53	.47	.37
.33/35V	.39	.34	.29	4.7/25V	.63	.56	.45
.47/35V	.39	.34	.29	6.8/25V	.79	.69	.55
.68/35V	.39	.34	.29	15/25V	1.39	1.25	.95
1.0/35V	.39	.34	.29	22/6V	.79	.69	.55

MINI. ALUMINUM ELECTROLYTIC CAPACITORS

Axial	1-99	100-499	500+	Radial	1-99	100-499	500+
.47/50V	.16	.14	.10	.47/25V	.15	.13	.12
1.0/50V	.19	.16	.12	.47/50V	.16	.14	.13
3.3/50V	.17	.15	.11	1.0/16V	.15	.13	.12
4.7/25V	.18	.15	.11	1.0/25V	.16	.14	.13
10/25V	.18	.15	.11	1.0/50V	.17	.15	.14
10/50V	.19	.16	.12	4.7/16V	.15	.13	.12
22/25V	.19	.16	.12	4.7/25V	.16	.14	.13
22/50V	.24	.20	.18	4.7/50V	.17	.15	.14
47/25V	.25	.21	.19	10/16V	.15	.13	.12
47/50V	.29	.25	.23	10/25V	.16	.14	.13
100/25V	.28	.24	.22	10/50V	.17	.15	.14
100/50V	.41	.37	.34	47/50V	.25	.21	.19
220/25V	.39	.34	.33	100/16V	.21	.17	.14
220/50V	.49	.45	.41	100/25V	.25	.23	.21
470/25V	.54	.49	.45	100/50V	.37	.34	.31
1000/16V	.79	.69	.61	220/16V	.25	.21	.19
2200/16V	.89	.79	.69	470/25V	.35	.31	.27

National Semiconductor Clock Modules

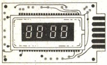

12VDC
AUTOMOTIVE/
INSTRUMENT
CLOCK

APPLICATIONS:
- In-dash autoclocks
- After-market auto/ RV clocks
- Aircraft-marine clks.
- 12VDC oper. instru.
- Portable/battery powered instrumnts.

Features: Bright 0.3″ green display. Internal crystal timebase. ± 0.5 sec./day accur. Auto. display brightness control logic. Display color filterable to blue, blue-green, green & yellow. Complete—just add switches and lens.

MA1003 Module $16.95

CLOCK MODULES

MA1023	.7″ Low Cost Digital LED Clock Module	8.95
MA1026	.7″ Dig. LED Alarm Clock/Thermometer	18.95
MA5036	.3″ Low Cost Digital LED Clock/Timer	6.95
MA1002	.5″ LED Display Dig. Clock & Xformer	9.95

TRANSFORMERS

XFMR1023	Xformer for MA1023 Clock Modules	3.49
XFMR1026	Xformer for MA1026 Clock Modules	3.49
XFMR5036	Xformer for MA5036 Clock Modules	3.49

Transistor Checker

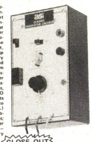

The *ASI Transistor Checker* is capable of checking a wide range of transistor types, either "in circuit" or out of circuit. It has been specially designed to take advantage of the newest concept of dynamic testing under current amplifier conditions. To operate, simply plug the transistor to be checked into the front panel socket, or connect it with the alligator clip test leads provided. No preliminary set-up is needed. The unit safely and automatically identifies low, medium and high-power PNP and NPN transistors. The ASI Transistor Checker also permits matching similar transistors in actual operating circuits, and provides a reliable GO/NO-GO test at practical collector currents (from 5mA on small signal types to 50mA and more on power types.) Match similar type transistors by observing and comparing dial readings; the higher the reading, the higher the gain. Completely assembled – battery operated. ("C" cell battery not included.)

CLOSE-OUT

Trans-Check $9.95

EPROM Erasing Lamp

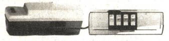

- Erases 2708, 2716, 1702A, 5203Q, 5204Q, etc.
- Erases up to 4 chips within 20 minutes.
- Maintains constant exposure distance of one inch.
- Special conductive foam liner eliminates static build-up.
- Built-in safety lock to prevent UV exposure.
- Compact – only 7-5/8″ x 2-7/8″ x 2″
- Complete with holding tray for 4 chips.

UVS-11E $79.95

JOYSTICKS

JS-5K

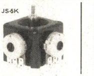

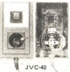

JVC-40

JS-5K	5K Linear Taper Pots	$5.25
JS-100K	100K Linear Taper Pots	$4.95
JVC-40	40K (2) Video Controller in case . . .	$5.95

6-Digit Clock Kit

- Bright .300 ht. comm. cathode display
- Uses MM5314 clock chip
- Switches for hours, minutes and hold modes
- Hrs. easily viewable to 20 ft.
- Simulated walnut case
- 115 VAC operation
- 12 or 24 hr. operation
- Incl. all components, case & wall transformer
- Size: 6¾″ x 3-1/8″ x 1¾″

JE701 .... $19.95

NEW! JE215 Adjustable Dual Power Supply

General Description: The JE215 is a Dual Power Supply with independent adjustable positive and negative output voltages. A separate adjustment for each of the supplies provides the user unlimited applications for IC current voltage requirements. The supply can also be used as a general all-purpose variable power supply.

FEATURES:
- Adjustable regulated power supplies, pos. and neg. 1.2VDC to 15VDC.
- Power Output (each supply): 5VDC @ 500mA, 10VDC @ 750mA, 12VDC @ 500mA, and 15VDC @ 175mA.
- Two, 3-terminal adj. IC regulators with thermal overload protection.
- Heat sink regulator cooling
- LED "on" indicator
- Printed Board Construction
- 120VAC input
- Size: 3-1/2″w x 5-1/16″L x 2″H

JE215 Adj. Dual Power Supply Kit (as shown) . . $24.95

(Picture not shown but similar in construction to above)

JE200 Reg. Power Supply Kit (5VDC, 1 amp) . .	$14.95
JE205 Adapter Brd. (to JE200) ±5,±9 & ±12V.	$12.95
JE210 Var. Pwr. Sply. Kit, 5-15VDC, to 1.5amp.	$19.95

MICROPROCESSOR COMPONENTS

8080A/8080A SUPPORT DEVICES

INS8080A	CPU	4.95
DP8212	8-Bit Input/Output	3.25
DP8214	Priority Interrupt Control	5.95
DP8216	Bi-Directional Bus Driver	3.49
DP8224	Clock Generator/Driver	3.95
DP8226	Bus Driver	3.49
DP8228	System Controller/Bus Driver	4.95
DP8238	System Controller	5.95
INS8243	I/O Expander for 48 Series	9.95
INS8250	Asynchronous Comm. Element	16.95
DP8251	Prog. Comm. I/O (USART)	7.95
DP8253	Prog. Interval Timer	14.95
DP8255	Prog. Peripheral I/O (PPI)	9.95
DP8257	Prog. DMA Control	19.95
DP8259	Prog. Interrupt Control	14.95
DP8275	Prog. CRT Controller	49.95
DP8279	Prog. Keyboard/Display Interface	19.95
DP8300	Octal Bus Receiver	6.95
DP8303	System Timing Element	6.95
DP8304	8-Bit Bi-Directional Receiver	3.95
DP8307	8-Bit Bi-Directional Receiver	3.95
DP8308	8-Bit Bi-Directional Receiver	3.95

6800/6800 SUPPORT DEVICES

MC6800	MPU	14.95
MC6802CP	MPU with Clock and RAM	19.95
MC6810API	128x8 Static RAM	4.95
MC6821	Peripheral Inter. Adapt (MC6820)	7.49
MC6828	Priority Interrupt Controller	10.95
MC6830L8	1024x8-Bit ROM (MC68A30-8)	14.95
MC6850	Asynchronous Comm. Adapter	6.95
MC6852	Synchronous Serial Data Adapter	6.95
MC6860	0-600bps Digital MODEM	10.95
MC6862	2400bps Modulator	12.95
MC6880A	Quad 3-State Bus. Trans. (MC8T26)	2.25

MICROPROCESSOR CHIPS

Z80 (780C)	CPU (MK3880N) (2MHz)	13.95
Z80A (780-1)	CPU (MK3880N-4) (4MHz)	15.95
CDP1802	CPU	19.95
2650	MPU	16.95
IDM2901ADC	CPU—4-Bit Slice (Com. Temp. Grade)	19.95
MCS6502	MPU w/Clock (65K Bytes Memory)	11.95
INS8035N-6	MPU—8-Bit (6MHz)	16.95
INS8039N-6	CPU—Sgl. Chip 8-Bit (128 bytes RAM)	19.95
INS8040N-6	CPU (256 Bytes RAM)	24.95
INS8070N	CPU—64 Bytes RAM	24.95
INS8073N	CPU w/Basic Micro Interpreter	29.95
P8085	CPU	19.95
INS8900	CPU—16-Bit	29.95
TMS9900JL	MPU—16-Bit	49.95

SHIFT REGISTERS

MM500H	Dual 25-Bit Dynamic	.50
MM503H	Dual 50-Bit Dynamic	.50
MM506H	Dual 100-Bit Static	.50
MM510H	Dual 64-Bit Accumulator	.50
MM1402	256-Bit Dynamic	3.95
MM5013	1024-Bit Dynamic/Accumulator	1.95
MM5016H	500/512-Bit Dynamic	.89
MM5034N	Octal 80-Bit	9.95
MM5035N	Octal 80-Bit	9.95
2504V (1404A)	1024-Bit Dynamic	3.95
2518N	Hex 32-Bit Static	4.95
2522V	Dual 132-Bit Static	2.95
2524V	512-Bit Dynamic	.99
2525V	1024-Bit Dynamic	2.95
2527V	Dual 256-Bit Static	2.95
2528V	Dual 250-Bit Static	4.00
2529V	Dual 240-Bit Static	4.00
2532N	Quad 80-Bit Static	2.95
3341PC	Fifo (Dual 80)	6.95

DATA ACQUISITION

AF100-1CN	Universal Active Filter 2.5%	5.95
AF121-1CJ	Touch Tone Low Pass Filter	19.95
AF122-1CJ	Touch Tone Low Pass Filter	19.95
LM308AH	Super Gain Op Amp	1.00
LM334Z	Constant Current Source	1.30
LM335Z	Temperature Transducer	1.40
LF356N	JFET Input Op Amp	1.10
LF398N	Sample & Hold Amplifiers	3.95
LM399H	Temp. Comp. Prec. Ref. (.5ppm/C°)	4.95
ADC0804LCN	8-Bit A/D Converter (1 LSB)	4.95
DAC0806LCN	8-Bit D/A Converter (0.78% Lin.)	2.25

DATA ACQUISITION (CONTINUED)

ADC0809CCN	8-Bit A/D Converter (8-Ch. Multi.)	5.25
ADC0817CCN	8-Bit A/D Converter (16-Ch. Multi.)	10.95
DAC1000LCN	10-Bit D/A Conv. Micro. Comp. (0.05%)	13.95
DAC1008LCN	10-Bit D/A Conv. Micro. Comp. (0.20%)	8.95
DAC1020LCN	10-Bit D/A Converter (0.05% Lin.)	8.49
DAC1022LCN	10-Bit D/A Converter (0.20% Lin.)	5.95
DAC1222LCN	12-Bit D/A Converter (0.20% Lin.)	9.95
CD4051N	8-Channel Multiplexer	1.19
AY-5-1013	30K BAUD UART	5.95

RAM'S

1101	256x1 Static	1.49
1103	1024x1 Dynamic	.99
2101 (8101)	256x4 Static	3.95
2102	1024x1 Static	1.75
21L02	1024x1 Static	1.95
2111 (8111)	256x4 Static	3.95
2112	256x4 Static MOS	4.95
2114	1024x4 Static 450ns	3.95
2114L	1024x4 Static 450ns Low Power	4.95
2114-3	1024x4 Static 300ns	4.95
2114L-3	1024x4 Static 300ns Low Power	5.95
2117	16,384x1 Dynamic 550ns (house marked)	4.95
4116 (UPD416)	16K Dynamic 250ns	3.95
4164	64K Dynamic 250ns	49.95
MM2147J	4096x1 Fast 70ns	19.95
5101	256x4 Static	7.95
MM5261	1024x1 Dynamic Fully Decoded	.99
MM5262	2Kx1 Dynamic	.25
MM5280/2107	4096x1 Dynamic	4.95
MM5290J-2(4116)	16K Dynamic 150ns	5.25
MM5298J-3A	8K Dyn. 200ns (lower ½ of MM5290J)	4.95
UPD414/MK4027	4K Dynamic 16-pin	4.95
TMS4044-45NL	4K Static	14.95
TMS4045	1024x4 Static	14.95

PROMS/EPROMS

1702A	2K UV Erasable PROM	5.95
2708	8K EPROM	5.95
TMS2716	16K EPROM (-5V, +5V, +12V)	19.95
2716 Intel (2516) TI	16K EPROM (Single +5V)	10.95
2732 Intel (2532) TI	32K EPROM	19.95
2758	8K EPROM (450ns) (Single +5V)	7.95
5203	2048 PROM	14.95
82S23 (74S188)	32x8 PROM (Open Collector)	4.95
82S115	4096 Bipolar PROM	19.95
82S123 (74S288)	32x8 Tri-State Bipolar PROM	4.95
82S185	8K PROM	29.95

ROM'S

2513(2140)	Character Generator (Upper Case)	9.95
2513(3021)	Character Generator (Lower Case)	9.95
2516N	Character Generator	10.95
MM5230N	2048-Bit Read Only Memory	1.95

NMOS READ ONLY MEMORIES

MCM66710P	128x9x7 ASCII Shifted w/Greek	13.50
MCM66740P	128x9x7 Math Symbol & Pictures	13.50
MCM66750P	128x9x7 Alpha. Control Char. Gen.	13.50

MICROPROCESSOR MANUALS

M-Z80	User Manual	7.50
M-CDP1802	User Manual	7.50
M-2650	User Manual	5.00

SPECIAL FUNCTION

DS0025CN	Dual MOS Clock Driver (5MZ)	3.50
DS0026CN	Dual MOS Clock Driver (5MZ)	1.95
INS1771N-1	Floppy Disc Controller	24.95
INS2651N	Communication Chip	19.95
MM58167N	Microprocessor Real Time Clock	8.95
MM58174N	Microprocessor Compatible Clock	11.95
COP402N	Microcontroller with 64-Digit RAM and Direct LED Drive	6.95
COP402MN	Microcontroller with 64-Digit RAM & Direct LED Drive w/N Buss Int.	7.49
COP470N	32-Seg. VAC Fluor. Driver (20-pin pkg.)	3.25

TELEPHONE/KEYBOARD CHIPS

AY-5-9100	Push Button Telephone Dialer	14.95
AY-5-9200	Repertory Dialer	14.95
AY-5-9500	CMOS Clock Generator	4.95
AY-5-2376	Keyboard Encoder (88 keys)	11.95
HD0165-5	Keyboard Encoder (16 keys)	7.95
74C922	Keyboard Encoder (16 keys)	5.49
74C923	Keyboard Encoder (20 keys)	5.75
MM53190N	Push Button Pulse Dialer	7.95
MM57499N	96/144-Key Serial Keyboard Encoder	8.95

ELECTRONIC TOY MOTORS

.937 O.D. X
1.201 Length

Typical Power Source	Operating Voltage Range	TYPICAL CHARACTERISTICS								SMALL TORQUE
			NO LOAD		AT MAXIMUM EFFICIENCY					
		Voltage	Speed	Current	Speed	Current	Torque	Output	Eff.	
			RPM	AMP	RPM	AMP	OZ. IN.	W	%	OZ. IN.
DRY CELL	1.5-6.0	3.0	9,200	0.20	6,750	0.90	0.260	1.30	57.0	0.97

MABUCHI RE280 $ .99 each . . .10/$7.50 . . .100/$50.00

DESIGNERS' SERIES
Blank Desk-Top Electronic Enclosures

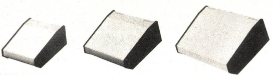

CONSTRUCTION:

The "DTE" Blank Desk Top Electronic Enclosures are designed to blend and complement today's modern computer equipment and can be used in both industrial and home. The end pieces are precision molded with an internal slot (all around) to accept both top and bottom panels. The panels are then fastened to ¼″ thick tabs inside the end pieces to provide maximum rigidity to the enclosure. For ease of equipment servicing, the rear/bottom panel slides back on slotted tracks while the rest of the enclosure remains intact. Different panel widths may be used while maintaining a common profile outline. The molded end pieces can also be painted to match any panel color scheme.

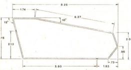

Enclosure Model No.	Panel Width	PRICE
DTE-8	8.00″	$29.95
DTE-11	10.65″	$32.95
DTE-14	14.00″	$34.95

$10.00 Min. Order – U.S. Funds Only
Calif. Residents Add 6% Sales Tax
Postage – Add 5% plus $1 Insurance

Spec Sheets – 25¢
Send 52¢ Postage for your
FREE 1981 JAMECO CATALOG

NEW 1981 CATALOG

Jameco ELECTRONICS

PHONE
ORDERS
WELCOME
(415) 592-8097

MAIL ORDER ELECTRONICS – WORLDWIDE
1355 SHOREWAY ROAD, BELMONT, CA 94002
PRICES SUBJECT TO CHANGE

6/81

Bourns Potentiometer

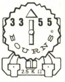

3/4 Watt Single Turn
(TOP ADJUSTMENT)

Values: 500Ω 1K 2.5K 5K 10K 25K 50K 100K 250K 500K 5Meg

INDIVIDUAL PRICING:

1-49	50-99	100-999	1K-up
.19	.17	.15	.12

GB174 ...... $1.95/lot
(25 pieces all 11 asst. values)

To order: Specify Bourns 3355 – (Value desired)

AC and DC Wall Transformers

Ideal for use with clocks, games, power supplies or any other type of AC or DC application.

Part No.	Input	Output	Price
AC 250	117V/60Hz	12 VAC 250mA	$3.95
AC 500	117V/60Hz	12 VAC 500mA	$4.95
AC1000	117V/60Hz	12 VAC 1 amp	$5.95
AC1700	117V/60Hz	9 VAC 1.7 amp	$6.95
DV 9200	117V/60Hz	9 VDC 200mA	$3.25
DC 900	120V/60Hz	9 VDC 500mA	$3.95

CONNECTORS

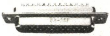

DB25P	D-Subminiature Plug	$2.95
DB25S	D-Subminiature Socket	$3.50
DB51226	Cover for DB25P/S	$1.75
22/44SE	P.C. Edge (22/44 Pin)	$2.95
UG88/U	BNC Plug	$1.79
UG89/U	BNC Jack	$3.79
UG175/U	UHF Adapter	$ .49
SO239	UHF Panel Recp.	$1.29
PL258	UHF Adapter	$1.60
PL259	UHF Plug	$1.60
UG260/U	BNC Plug	$1.79
UG1094/U	BNC Bulkhead Recp.	$1.29

TRS-80
16K Conversion Kit

Expand your 4K TRS-80 System to 16K.
Kit comes complete with:
★ 8 ea. MM5290 (UPD416/4116) 16K Dyn. Rams (*NS)
★ Documentation for Conversion

TRS-16K2 *150 NS **$39.95**
TRS-16K4 *250 NS **$29.95**

GLOBAL SPECIALTIES

EXPERIMENTOR SOCKETS

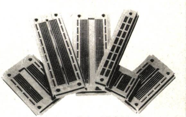

Model	Length	Width	Center Channel	5 Tie Point Terminals	Bus Strips	Price
EXP4B	6.0″	1.0″	n/a	n/a	4(160)	$ 4.75
EXP300	6.0″	2.1″	.3″	94(470)	2(80)	$12.00
EXP325	1.8″	2.1″	.3″	22(110)	2(20)	$ 3.50
EXP350	3.6″	2.1″	.3″	46(230)	2(40)	$ 6.75
EXP600	6.0″	2.4″	.6″	94(470)	2(80)	$14.75
EXP650	3.6″	2.4″	.6″	46(230)	2(40)	$ 8.75

Quick Test Sockets & Bus Strips

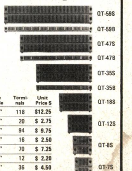

MANY OTHER GLOBAL ITEMS

	Length	Hole to-hole	Terminals	Unit Price $
QT-59S	6.5″	6.2″	118	$12.25
QT-59B	6.5″	6.2″	20	$ 2.75
QT-47S	5.3″	5.0″	94	$ 9.75
QT-47B	5.3″	5.0″	16	$ 2.50
QT-35S	4.1″	3.8″	70	$ 7.25
QT-35B	4.1″	3.8″	12	$ 2.20
QT-18S	2.4″	2.1″	36	$ 4.50
QT-12S	1.8″	1.5″	24	$ 3.75
QT-8S	1.4″	1.1″	16	$ 3.00
QT-7S	1.3″	1.0″	14	$ 2.75

CIRCLE NO. 31 ON FREE INFORMATION CARD

PULSAR COMPONENTS

FOR ALL YOUR I.C. NEEDS

SPECIALS

2708	$5.95	2114	$4.25
2716	$8.95	4116	$6.95
2732	$24.95	1702A	$4.95

PROMS

74S188	$3.95	74S471	$15.95
74S287	$3.95	74S472	$15.95
74S288	$3.95	74S474	$18.95
74S387	$4.95	74S571	$7.75

74LS

74LS00	.27	74LS107	.39	74LS194	1.09
74LS02	.27	74LS109	.49	74LS195	1.09
74LS04	.29	74LS113	.49	74LS240	1.89
74LS05	.29	74LS123	.99	74LS241	1.19
74LS08	.29	74LS138	.79	74LS244	1.19
74LS10	.27	74LS139	.79	74LS245	1.99
74LS11	.49	74LS151	.79	74LS258	.89
74LS12	.40	74LS153	.79	74LS259	1.99
74LS14	.49	74LS156	1.19	74LS266	.59
74LS20	.27	74LS157	.79	74LS279	.69
74LS26	.33	74LS161	.99	74LS367	.69
74LS27	.33	74LS163	.99	74LS368	.69
74LS30	.33	74LS165	1.19	74LS373	1.79
74LS32	.37	74LS166	1.19	74LS374	1.79
74LS37	.49	74LS169	1.99	74LS390	1.79
74LS38	.49	74LS174	.89	74LS393	1.79
74LS51	.27	74LS175	.89	74LS644	2.49
74LS74	.39	74LS191	1.19	74LS645	2.49
74LS85	.99	74LS193	1.09	74LS670	1.99
74LS86	.39				

74S

74S00	.45	74S86	.75	74S174	1.59
74S02	.45	74S112	.75	74S175	1.59
74S04	.45	74S133	.50	74S194	1.59
74S08	.45	74S134	.69	74S195	1.59
74S10	.45	74S138	1.19	74S200	6.95
74S20	.45	74S140	.99	74S225	6.95
74S32	.50	74S151	.99	74S240	2.95
74S37	.99	74S161	1.99	74S251	1.55
74S51	.99	74S169	3.99	74S253	.99
74S74	.75			74S257	.99
				74S374	2.95

7400

7400	.25	7426	.30	74191	.95
7402	.25	7438	.35	74193	.85
7405	.25	7485	.85	74197	.85
7406	.30	74109	.45	74259	1.95
7410	.25	74123	.45	74368	.65
7417	.35	74128	.45		
7420	.30				

ALSO

DIODES
TRANSISTORS
LINEARS
MICROPROCESSOR
VECTOR BOARDS

PULSAR COMPONENTS INC.

125 JERICHO TPKE.
JERICHO, N.Y. 11753

Send Mail Order or Call
(516) 334-7593 or (213) 390-4461
$20 Minimum Order
N.Y. Residents add 7% sales tax
Please add $2.50 shipping charges

CIRCLE NO. 49 ON FREE INFORMATION CARD

NEW LITERATURE

Transistor Catalog

A 52-page booklet from TRW describes its family of 15 small-signal, low-noise transistors, complete with specifications, performance graphs, photographs, circuit diagrams, and dimensions. All devices are npn silicon bipolar transistors with gold metallization. Address: TRW RF Semiconductors, 14520 Aviation Blvd., Lawndale, CA 90260.

Word Processing Booklet

"CPT Takes the Mystery Out of Word Processing" is a 20-page booklet explaining what word processors do—and how they do it. Helps the reader decide whether he needs word processing and lists criteria for prospective buyers of equipment such as screen size, memory capacity, etc. Address: CPT Corp., Box 17, Minneapolis, MN 55440.

Test Probe Catalog

A new catalog from Test Probes, Inc. describes 16 models of probe kits and test lead sets. Specifications and applications are given for probes for scopes, DVMs, DMMs, VOMs, and special meters. Address: Test Probes, Inc., Box 2113, La Jolla, CA 92038.

Digital Switches

Ordering instructions, option information, truth tables to illustrate circuit connections, and prices are given on 16 series of digital switches in two six-page brochures. No. 1-0071C covers commercial and industrial switches. No. 1-0072C is for sealed, QPL, and general-purpose units. Address: Digitran Co., 855 S. Arroyo Pkwy., Pasadena, CA 91105.

Acoustic-Coupled Modems

Bulletin 5273 describes two new acoustic-coupled modems (ACM300 and ACM300/1200) which operate asynchronously over the DDD network. The publications contains photographs, a system diagram and technical notes. Address: Rixon Inc., 2120 Industrial Pkwy., Silver Spring, MD 20904.

Software Catalog

"Micro Yellow Pages" is a 20-page newsletter and catalog describing Micro Architect software. It describes software packages for the Model I, Model II, and Model III TRS-80*, CP/M, and Heath HDOS. Send long, SASE (30 cents) to: Micro Architect Inc., 96 Dothan St., Arlington, MA 02174.

BULLET
ELECTRONICS, Inc.
PO Box 401244P Garland TX 75040
(214) 278-3553

Super Music Maker Kit REVISION 2 **$24.95**

Now you can play hundreds of songs using the Bullet **Super Music Maker.** The unit **features a single factory programmed microprocessor IC** that comes with 20 preprogrammed short tunes. By adding the additional PROMS (2708's) the system can be expanded to play up to **1000 notes per PROM.** Just think . . . a compact electronic instrument that will play dozens, hundreds or even thousands of selections of music. The kit comes with **all electronic components (less the PROM),** and a drilled, plated and screened PC Board which measures 4" x 4¾". The **7 watt amplifier** section is on the same PC board and drives an 8 ohm speaker (not included), from a whisper to ear splitting volume. Since the unit works on **12 VDC** or **12 VAC***, vehicle or portable operation is possible. **What do you get for $24.95? Everything but a speaker, transformer, case, switches,** and **PROM.** Additional 2708 albums containing popular tunes are available for **$15.00** each or you can program your own PROMS using information provided with the kit instructions. Lists of available PROM albums are available on request. *(Note: Unit plays electronic music one note at a time, it is not possible to play chords or a melody with harmony simultaneously.)*

OPTIONAL ACCESSORIES

DIP Switches	One 8 pos., One 5 pos. (Can be **directly soldered** to PC Bd. to access tunes)	**2.00/Set**
Rotary Switches	Two 5 position (For **remote wiring** to PC Bd. to access tunes)	**2.50 /Set**
Attractive	**Plastic Case**	**6.50**
Wallplug Transformer	(For operation on 117VAC house voltage)	**3.00**

Sound Effects Kit $18.50

The **SE-01 Sound Effects Kit** is a complete kit: all you need to build a programmable sound effects machine except a battery and speaker. Our kit is designed to really ring out the **TI 76477** Sound Chip. Only the SE-01 provides you with additional circuitry that includes a **PULSE GENERATOR, MUX OSCILLATOR and COMPARITOR** to make more complex sounds a snap. We help you in building the kit with a clear, easy-to-follow construction manual and we show you how to easily program the unit. Other dealers will sell you the chip or a "kit" of parts but you are on your own to do the most difficult part...make neat sounds! Within a short time after you build the SE-01 you can easily create **Gunshots, Explosions, Space Sounds, Steam Trains** and much more. We think the Bullet SE-01 is the best deal on the market but don't ask us. — ask the **15,000** happy SE-01 owners!

Complete Kit With Quality Plated PC Board **$18.50**
(Less battery & speaker)

7 Watt Audio Amp Kit $5.95

SMALL, SINGLE, HYBRID IC AND COMPONENTS FIT ON A 2" x 3" PC BOARD (INCLUDED). RUNS ON 12 VDC. GREAT FOR ANY PROJECT THAT NEEDS AN INEXPENSIVE AMP. LESS THAN 3% THD @ 5 WATTS. COMPATIBLE WITH SE-01 SOUND KIT.

AY3-8910 PROGRAMMABLE SOUND GENERATOR

The AY3-8910 is a 40 pin LSI chip with three oscillators, three amplitude controls, programmable noise generator, three mixers, an envelope generator, and three D/A converters that are controlled by 8 BIT WORDS. No external pots or caps required. This chip hooked to an 8 bit microprocessor chip or Buss (8080, Z80, 6800 etc.) can be software controlled to produce almost any sound. It will play three note chords, make bangs, whistles, sirens, gunshots, explosions, bleets, whines, or grunts. In addition, it has provisions to control its own memory chips with two IO ports. The chip requires +5V @ 75ma and a standard TTL clock oscillator. A truly incredible circuit.

12.95 W/Basic Spec Sheet (4 pages)
60 page manual with S-100 interface instructions and several programming examples, **$3.00 extra**

AM-FM STEREO RECEIVER

Complete chassis, (no case) with pushbutton switches and tuning dial. Has phono and tape inputs. Requires 12-14VDC.

$12.95 Order: BEM-0001

PLUG-IN AMPLIFIER and DC Power Supply for above. Has tone, balance and volume slide controls. Low distortion IC audio driver 2 watts per channel RMS. Requires 12VDC transformer at 1/2 A.

$6.95 Order: BEM-0002

4" Speakers for small systems. 8 ohm.
2/$3.50

COMPUTER GRADE CAPS

Compact high grade filter cap. 6000 mfd at 50WV. Low ESR 2" diameter x 3 3/16H.

$2.30 $2/3.90

Call or write for FREE catalog.

POLICIES

NO C.O.D.'s SEND CHECK,MONEY ORDER, CREDIT CARD #
ADD 5% FOR SHIPPING. TX. RES. ADD 5% TAX. FOREIGN ORDERS ADD 30% FOR SHIPPING.
U. S. FUNDS ONLY
PHONE ORDERS ON MASTER CHARGE & VISA ONLY
(214) 278-3553

DIODES/ZENERS

QTY				
	1N914	100v	10mA	.05
	1N4005	600v	1A	.08
	1N4007	1000v	1A	.15
	1N4148	75v	10mA	.05
	1N4733	5.1v	1 W Zener	.25
	1N4749	24v	"	.25
	1N753A	6.2v	500 mW Zener	.25
	1N758A	10v	"	.25
	1N759A	12v	"	.25
	1N5243	13v	"	.25
	1N5244B	14v	"	.25
	1N5245B	15v	"	.25
	1N5349	12v	3W Zener	.25

SOCKETS/BRIDGES

QTY				
	8-pin	pcb .20	ww	.40
	14-pin	pcb .25	ww	.60
	16-pin	pcb .30	ww	.70
	18-pin	pcb .35	ww	.95
	20-pin	pcb .45	ww	1.05
	22-pin	pcb .50	ww	1.15
	24-pin	pcb .55	ww	1.25
	28-pin	pcb .60	ww	1.45
	40-pin	pcb .70	ww	1.75
	Molex pins .01		To-3 Sockets	.35
	2 Amp Bridge		200-prv	1.35
	25 Amp Bridge		200-prv	2.25

TRANSISTORS, LEDS, etc.

QTY			
	2N2222M (Metal)	.25	(2N2222 Plastic .20)
	2N2222A	NPN	.35
	2N2907A	PNP	.35
	2N3906	PNP (Plastic)	.25
	2N3904	NPN (Plastic)	.25
	2N3054	NPN 4A 90v	.60
	2N3055	NPN 15A 60v	.75
	TIP125	PNP Darlington	1.95
	LED	Green Red Clear Yellow	.19
	DL747	7 seg ⅝" High com-anode	2.25
	DL 728B	doub 7 seg 5" com-cathode	2.50
	MA6740	doub 7 seg 5" com-cathode	2.50
	MAN72	7 seg com-anode (Red)	1.50
	MAN3630	7 seg com-anode ±1	1.00
	MAN82A	7 seg com-anode (Yellow)	1.50
	MAN74	7 seg com-cathode (Red)	1.50
	FND359	7 seg com-cathode (Red)	1.50

9000 SERIES

QTY			QTY		
	9301	1.95		9322	.65
	9309	1.25		9601	.40
	9316	1.50		9602	1.35

MICROs, RAMS CPUs, E-PROMS

1771 Disc Controller $29.50	
8T13	1.50
8T23	2.50
8T24	3.00
8T97	1.50
74S188	6.50
1488	1.75
1489	1.75
1702A	8.50
AM9050/TMS4050	5.00
ICM7207	6.95
ICM7208	13.95
MM5314	4.50
MM5311	4.50
MM5316	4.50
MM5387	4.50
MM5369	3.95
TR1602B/6011	4.95
UPD414/TMS4027	3.50
Z80A	15.00
Z80	9.50
Z80PIO(A)	10.50
2102	1.45
2102L	1.75
2107B-4	5.95
2114	5.00
2513 (5V) Up/Lo	9.50
2708	6.95
2716TI	9.00
2716(5V)	12.00
TMS2532/2732	35.00
3242	12.50
4116	6.50
6800	11.50
6802	15.50
6820/6520	8.00
6850	9.95
8080	5.50
8085	14.50
8212	3.50
8214	4.95
8216	4.50
8224	4.25
8228	5.95
8251	9.50
8253	14.50
8255	9.50
TMS4044	9.95

— T T L —

4/1/81

QTY			QTY			QTY			QTY		
	7400	.35		7493	.60		74H11	.45		74LS74	.95
	7401	.25		7494	.75		74H15	.45		74LS75	.95
	7402	.35		7495	.60		74H20	.35		74LS76	.90
	7403	.35		7496	.55		74H21	.35		74LS86	.95
	7404	.45		74100	2.75		74H22	.40		74LS90	1.85
	7405	.35		74107	.55		74H30	.40		74LS93	1.00
	7406	.55		74121	.55		74H40	.45		74LS107	.90
	7407	.65		74122	.55		74H50	.40		74LS109	1.00
	7408	.50		74123	.70		74H51	.40		74LS123	1.20
	7409	.35		74125	.75		74H52	.40		74LS138	1.00
	7410	.35		74126	.75		74H53	.45		74LS151	1.00
	7411	.35		74132	.75		74H55	.45		74LS153	1.15
	7412	.35		74141	.90		74H72	.45		74LS154	2.00
	7413	.45		74145	1.35		74H74	1.50		74LS157	1.75
	7414	.65		74150	1.15		74H101	.95		74LS160	1.65
	7416	.35		74151	.95		74H103	.55		74LS161	1.50
	7417	.40		74153	.95		74L00	.80		74LS164	1.90
	7420	.45		74154	1.40		74L02	.75		74LS193	2.00
	7426	.35		74156	.70		74L03	.35		74LS195	2.00
	7427	.40		74157	.95		74L04	.90		74LS196	2.50
	7430	.40		74161	1.50		74L10	.30		74LS244	1.50
	7432	.65		74163	1.50		74L20	.45		74LS245	3.50
	7437	.55		74164	1.50		74L30	.55		74LS253	1.95
	7438	.70		74165	1.10		74L47	1.95		74LS298	1.50
	7440	.40		74166	1.10		74L51	.65		74LS367	1.50
	7441	.95		74175	.95		74L55	.85		74LS368	1.95
	7442	.95		74176	1.15		74L72	.65		74LS373	1.50
	7443	.75		74177	1.10		74L73	.70		74S00	.70
	7444	.75		74180	1.10		74L74	1.95		74S02	.90
	7445	.75		74181	2.25		74L75	1.05		74S03	.45
	7446	.90		74182	.75		74L85	3.00		74S04	.70
	7447	1.50		74190	1.25		74L93	2.95		74S05	.65
	7448	1.50		74191	1.25		74L123	2.95		74S08	1.80
	7450	.35		74192	1.50		74LS00	.50		74S10	.95
	7451	.25		74193	1.50		74LS01	.60		74S11	.75
	7453	.25		74194	.95		74LS02	.50		74S20	.75
	7454	.35		74195	.95		74LS03	.60		74S22	.75
	7460	.40		74196	1.75		74LS04	.60		74S40	.70
	7470	.35		74197	.95		74LS05	.60		74S50	.70
	7472	.40		74198	1.50		74LS08	.60		74S51	.75
	7473	.40		74221	1.50		74LS09	.60		74S64	.35
	7474	.45		74298	2.50		74LS10	.60		74S74	1.50
	7475	.45		74367	1.15		74LS11	.60		74S86	1.25
	7476	.95		75107A	1.50		74LS20	.65		74S112	1.90
	7480	.60		75451	.85		74LS21	.50		74S114	.85
	7481	.95		75452	.85		74LS22	.45		74S133	.85
	7482	.95		75491	1.50		74LS27	.60		74S140	.95
	7483	.75		75492	1.50		74LS32	.80		74S151	1.50
	7485	.95		74H00	.50		74LS37	.60		74S153	2.25
	7486	.55		74H01	.50		74LS38	.95		74S157	2.95
	7489	1.95		74H04	.90		74LS40	.70		74S158	1.75
	7490	.75		74H05	.55		74LS42	.75		74S194	1.75
	7491	.60		74H08	.90		74LS47	1.95		74S196	2.00
	7492	.50		74H10	.45		74LS51	.95		74S257(8123)	1.95
										74S287	5.95
										8131	2.75

C MOS

QTY			QTY			QTY			QTY		
	4000	.40		4019	1.15		4041	1.15		4081	.55
	4001	.35		4020	.95		4042	.65		4082	.60
	4002	.35		4021	.75		4043	.90		4093	.90
	4006	1.50		4022	.75		4044	.90		4098	2.25
	4007	.30		4023	.35		4046	1.50		4507	.95
	4008	.75		4024	.95		4047	2.50		4511	1.50
	4009	.40		4025	.35		4048	2.50		4512	1.25
	4010	.35		4026	1.95		4049	.50		4515	2.95
	4011	.65		4027	.65		4050	.65		4519	.85
	4012	.25		4028	.95		4052	.75		4522	1.10
	4013	.65		4029	1.50		4053	1.50		4526	.95
	4014	.75		4030	.45		4066	.75		4528	1.50
	4015	.75		4033	1.50		4069/74C04	.45		4529	.95
	4016	.55		4034	2.75		4070	.60		MC14409	14.50
	4017	1.50		4035	.95		4071	.40		MC14419	4.85
	4018	.95		4040	1.50		4072	.50		74C151	2.50

I^{2}L, LINEARS, REGULATORS, etc.

QTY			QTY			QTY		
	MCT2(E)	1.25		LM320K24	1.65		LM373	3.95
	8038	4.50		LM320T5(7905)	1.65		LM377	2.95
	LM201	2.00		LM320T12	1.65		78L05	.95
	LM301	.95		LM320T15	1.65		78L12	.95
	LM308	1.25		LM323K	7.95		78L15	.95
	LM309H	1.50		LM324	1.00		78M05	.95
	LM309(340K-5)	1.50		LM337T	2.25		LM380(8-14Pin) 386N	1.19
	LM310	.85		LM339	.95		LM709(8-14Pin)	.75
	LM311(8-14Pin)	1.50		7805(340T5)	1.50		LM711	.45
	LM317T	2.25		LM340T12	1.50		LM723	.75
	LM318N	2.15		LM340T15	1.50		LM725	3.95
	LM320H6	.89		LM340T18	1.50		LM739	1.50
	LM320H15	.89		LM340T24	1.50		LM741(8-14)	.75
	LM320H24	.89		LM340K12	1.50		LM747	1.25
	LM320K5	1.65		LM340K15	1.50		LM1307	1.75
	LM320K12	1.65		LM340K18	1.50		LM1458	.65
	LM320K15	1.65		LM340K24	1.50		LM3900	.75
							LM3909	1.50
							NE555	.50
							NE556	1.00
							NE565	1.50
							NE566	1.75
							NE567	1.50
							TA7205	4.95
							76477	2.95
							95H90	9.95
							TL081CP	.75

INTEGRATED CIRCUITS UNLIMITED, INC.
7889 Clairemont Mesa Blvd., San Diego, California 92111

Out of State 1-800-854-2211
California 1-800-542-6239

(714) 278-4394

Telex: 697-827
TWX 910-335-1577

Name ______________________________

Street Address ______________________________

City ______________ State ______________ Zip ______________

Phone ______________ Charge card # AE VISA BA MC ______________ Exp. Date ______________

☐ C.O.D. ☐ Will Call ☐ UPS ☐ Post ☐ Net 30 Days ☐ P.O. # ______________

Add $2.00 Shipping on all U.S. Orders - $5.00 Minimum - C.O.D. Orders Accepted - Most Orders Shipped Same Day

Commerical Accounts Invited - California Residents Add 6% Sales Tax - PRICES SUBJECT TO CHANGE WITHOUT NOTICE

24 Hour Phone Service - We Accept American Express/Visa/BankAmeriCard/Master Card/Barclav Card/Access • 15% Restocking Charge After 10 Days

All Prices in U.S. Dollars - Foreign Orders F.O.B. San Diego

CIRCLE NO. 30 ON FREE INFORMATION CARD

DIGI-KEY CORPORATION 800-346-5144

In Mn., Ak., Hi. Call 218-681-6674

VISA

Capacitors•Real-Time Clock/Calendar• E F Johnson •Terminal Strips•T.I. Connectors•Wire Wrapping Supplies•CMOS•Rectifiers•Powerace•Sams Books•Diamond Tools•Panavice AP Products•Batteries•ZNR's•Books•Zenier Diodes•Breadboarding•Wire•Buzzers•Vises •Templates•Diodes•Switches•Drafting Aids•Soldering Supplies•Edge Connectors•IC Socket •Enclosures•Resistors & Resistor Networks•Hardware•Power Supplies•Hobby Blox•Phono Plugs & Jacks•Integrated Circuits•Optoelectronics•Lamps•Multimeter•LED's•Data Books Microprocessor & Support•Luxo Lamps•Clock Bezels•PC Layout Supplies•Lithium Batteries•Tantalum Capacitors•Time-Temperature Clock•A/D & D/A•Nickle-Cadmium Batteries Electrolytic Capacitors•Potentiometers•Car Clock•Transistors•Home Clock Kits•Tools • Fuse Holder Boards•Ungar Products•Heat Sinks & Accessories•Solder Wick•AND MORE

master charge

DIGI-KEY — DIGI-KEY — DIGI-KEY — DIGI-KEY — DIGI-KEY — DIGI-KEY — DIGI-KEY — DIGI-KEY *The Big DIGI-KEY Discount makes a Big Price Difference* (SEE BELOW) DIGI-KEY — DIGI-KEY — DIGI-KEY — DIGI-KEY — DIGI-KEY — DIGI-KEY — DIGI-KEY — DIGI-KEY

INTEGRATED CIRCUITS

7400 TTL

7400 TTL	
7400N	.32
7401N	.32
7402N	.32
7403N	.32
7404N	.35
7405N	.35
7406N	.41
7407N	.41
7408N	.35
7409N	.37
7410N	.32
7411N	.35
7413N	.48
7414N	.85
7416N	.41
7417N	.41
7420N	.32
7423N	.40
7425N	.37
7426N	.37
7427N	.37
7430N	.32
7432N	.37
7437N	.41
7438N	.41
7440N	.32
7442N	.73
7445N	.93
7446N	1.06
7447N	1.06
7448N	1.06
7450N	.32
7451N	.32
7453N	.32
7454N	.32
7460N	.35
7470N	.49
7472N	.49
7473N	.46
7474N	.46
7475N	.62
7476N	.46
7483N	.85
7485N	.95
7486N	.46
7489N	1.75
7490N	.53
7491N	.89
7492N	.60
7493N	.57
7495N	.71
7496N	.79
74107N	.46
74109N	.46
74121N	.55
74123N	.71
74125N	.64
74126N	.64
74132N	.82
74141N	1.19
74145N	.93
74147N	1.73
74148N	1.33
74150N	1.12
74151N	.73
74153N	.73
74154N	1.21
74155N	.79
74156N	.79
74157N	.73
74160N	.93
74161N	1.02
74162N	.93
74163N	.93
74164N	.98
74165N	1.15
74166N	1.26
74170N	1.87
74173N	1.35
74174N	.90
74175N	.84
74176N	.96
74177N	.96
74180N	1.00
74181N	2.00
74182N	1.10
74190N	1.01
74191N	1.01
74192N	1.03
74193N	.95
74194N	.93
74195N	.88
74196N	.91
74197N	.91
74198N	1.49
74199N	1.49
74251N	1.12
74365N	.80
74366N	.80
74367N	.80
74368N	.80

74LS00 LS TTL	
74LS00N	.36
74LS01N	.36
74LS02N	.36
74LS03N	.36
74LS04N	.38
74LS05N	.38
74LS08N	.36
74LS09N	.38
74LS10N	.36
74LS11N	.38
74LS12N	.36
74LS13N	.59
74LS14N	1.25
74LS15N	.38
74LS20N	.36
74LS21N	.38
74LS22N	.36
74LS26N	.37
74LS27N	.36
74LS30N	.36
74LS32N	.41
74LS37N	.37
74LS38N	.37
74LS40N	.38
74LS42N	.85
74LS47N	1.08
74LS48N	1.08
74LS49N	1.18
74LS51N	.36
74LS54N	.36
74LS55N	.36
74LS73N	.49
74LS74N	.46
74LS75N	.59
74LS76N	.54
74LS78N	.49
74LS83N	1.08
74LS85N	1.28
74LS86N	.50
74LS90N	.73
74LS93N	.73
74LS107N	.46
74LS113N	.49
74LS114N	.49
74LS122N	.75
74LS123N	1.03
74LS125N	.64
74LS126N	.64
74LS132N	.93
74LS136N	.49
74LS138N	.84
74LS139N	.84
74LS151N	.77
74LS153N	.84
74LS154N	1.44
74LS155N	.91
74LS156N	.91
74LS157N	.77
74LS158N	.86
74LS160N	1.07
74LS161N	1.07
74LS162N	1.07
74LS163N	1.07
74LS164N	1.18
74LS168N	1.51
74LS169N	1.51
74L170N	1.84
74LS173N	1.34
74LS174N	1.22
74LS175N	.90
74LS190N	1.30
74LS191N	1.30
74LS192N	1.17
74LS193N	1.17
74LS196N	1.34
74LS197N	1.34
74LS221N	1.37
74LS247N	1.19
74LS248N	1.19
74LS249N	1.19
74LS253N	1.02
74LS257N	.89
74LS258N	.97
74LS266N	.50
74LS283N	1.03
74LS290N	1.12
74LS293N	1.12
74LS352N	1.30
74LS353N	1.44
74LS365N	.70
74LS366N	.70
74LS368N	.70
74LS386N	.55
74LS670N	2.59
81LS95N	1.76
81LS96N	1.76
81LS97N	1.76
81LS98N	1.76

4000 CMOS	
4000	.40
4001	.31
4002	.35
4006	1.36
4007	.49
4008	1.12
4009	.56
4010	.56
4011	.33
4012	.35
4013	.62
4014	1.08
4015	1.08
4016	.55
4017	1.08
4018	1.08
4019	.56
4020	1.30
4021	1.14
4022	1.08
4023	.35
4024	.94
4025	.38
4027	.74
4028	.99
4029	1.19
4030	.46
4034	2.75
4035	1.42
4040	1.24
4041	1.07
4042	1.08
4043	1.08
4044	1.08
4046	1.79
4047	1.45
4048	.80
4049	.58
4050	.58
4051	1.19
4052	1.19
4053	1.19
4060	1.58
4066	.79
4071	.35
4073	.35
4075	.35
4081	.37
4089	2.75
4093	.76
4099	2.10
4503	.69
4510	1.17
4511	1.28
4512	1.39
4514	2.80
4515	2.80
4516	1.23
4518	1.17
4519	.63
4520	1.17
4522	1.75
4526	1.75
4527	1.68
4528	1.61
4723	1.53
4724	1.53
40106	.90
40160	1.19
40161	1.19
40162	1.19
40163	1.19
40174	1.16
40175	1.16
40192	1.30
40193	1.30
40195	1.19

74C00 CMOS	
74C00N	.35
74C02N	.35
74C04N	.35
74C08N	.35
74C10N	.35
74C14N	.90
74C20N	.35
74C30N	.35
74C32N	.35
74C42N	1.03
74C48N	1.28
74C73N	.72
74C74N	.48
74C76N	.72
74C83N	1.51
74C85N	1.51
74C86N	.46
74C90N	1.14
74C93N	1.14
74C95N	1.39
74C107N	.70
74C150N	3.66
74C151N	2.41
74C154N	3.66
74C157N	2.41
74C160N	1.19
74C161N	1.19
74C162N	1.19
74C163N	1.19
74C164N	1.16
74C165N	1.19
74C173N	1.30
74C174N	1.16
74C175N	1.16
74C192N	1.38
74C193N	1.38
74C195N	1.19
74C221N	1.90
74C901N	.48
74C902N	.48
74C908N	1.22
74C909N	2.26
74C914N	1.50
74C922N	5.70
74C923N	5.90
74C925N	7.80
74C926N	7.80
74C927N	7.80
74C928N	7.80
80C95N	.69
80C96N	.69
80C97N	.69
80C98N	.69

LINEAR I.C.'S	
LF347N	3.57
LF351N	.78
LF353N	1.40
LF356N	1.48
LF357N	1.48
LF13741N	.76
LM301AN	.58
LM307N	.68
LM308N	1.00
LM311N	.90
LM317K	5.23
LM317MP	2.06
LM317T	3.00
LM318N	2.58
LM320MP-5	1.74
LM320MP-6	1.74
LM320MP-8	1.74
LM320MP-9	1.74
LM320MP-12	1.74
LM320MP-15	1.74
LM320MP-18	1.74
LM320MP-24	1.74
LM322N	2.08
LM323K	8.98
LM324N	.92
LM325N	3.44
LM326N	3.44
LM327N	3.44
LM331N	5.46
LM334Z	1.52
LM335Z	2.25
LM336Z	2.27
LM337K	6.98
LM337T	2.47
LM338K	9.49
LM339N	1.15
LM340KC-5	2.10
LM340T-5	1.32
LM340T-6	1.32
LM340T-12	1.32
LM340T-15	1.32
LM340T-18	1.32
LM340T-24	1.32
LM341P-5	1.04
LM341P-6	1.04
LM341P-8	1.04
LM341P-10	1.04
LM341P-12	1.04
LM341P-15	1.04
LM341P-18	1.04
LM341P-24	1.04
LM348N	1.62
LM349N	1.82
LM350K	7.85
LM358N	1.10
LM377N	2.40
LM378N	3.15
LM392N	1.20
LM379S	5.60
LM380N-8	1.30
LM381N	2.25
LM382N	1.75
LM383AT	3.64
LM386N-1	1.10
LM387N	1.45
LM1310N	1.90
LM1458N	.80
LM1496N	.94
LM1800N	1.75
LM1801N	2.75
LM1812N	6.21
LM1830N	1.75
LM1889N	2.58
LM2111N	1.57
LM2907N	2.57
LM2917N	2.57
LM3046N	.82
LM3086N	.69
LM3089N	2.00
LM3302N	.92
LM3900N	1.07
LM3905N	1.83
LM3909N	.83
LM3911N	1.95
LM3914N	3.75
LM3915	4.55
LM3916	4.29
LM13600N	4.29
NE555CN	.70
NE556CN	1.07
NE565CN	1.33
NE566CN	1.58
NE567CN	1.33
NSM3914N	8.37
NSM3915N	8.37
NSM3916N	8.37
UA709CN	.82
UA723CN	.69
UA733CN	.94
UA741CN	.53
UA747CN	.82
UA748CN	.70
UA7805CK	2.10
UA7805CT	1.32
UA7806CT	1.32
UA7812CT	1.32
U7815CT	1.32
UA7818CT	1.32
UA7824CT	1.32
UA78L05ACZ	.45
UA78L06ACZ	.45
UA78L08ACZ	.45
UA78L10ACZ	.45
UA78L12ACZ	.45
UA78L15ACZ	.45
UA78L24ACZ	.45
UA7905CT	1.70
UA7906CT	1.70
UA7909CT	1.70
UA7912CT	1.70
UA7915CT	1.70
UA7924CT	1.70

INTERFACE I.C.'S	
8093N	.64
8094N	.64
8095N	.80
8096N	.80
8097N	.80
8098N	.80
75450N	.92
75451N	.65
75452N	.65
75453N	.65
75454N	.65
75491N	.84
75492N	.84
75493N	1.07
75494N	1.07
MC1488N	1.39
MC1489N	1.39

A/D & D/A CONVERTERS & MISCELLANEOUS	
ADC0804LCN	5.79
ACD0817CCN	14.35
ACD0816CCN	29.95
ACD3511CCN	12.02
ADC3711CCN	13.52
ADD3501CCN	11.98
ADD3701CCN	13.52
DAC0800LCN	3.87
DAC0808LCN	3.37
MM5314N	3.98
MM5369N	2.80
MM5837N	2.30

MEMORY	
1702A	10.49
2114N	8.33
21L02-1	2.24
2708	16.74
74S189N	2.49
74S570N	5.74
74S571N	5.74
9334N	1.90
93410PC	3.24
MM5257N	8.99
MM5280N-055	4.84
MM5290J-4	15.00
DAC1020LCN	11.37
DAC1022LCN	11.37

MICROPROCESSORS			
8228N	6.23	8060N	18.58
8238N	6.11	8080AN	9.97
8251N	8.73	8212N	3.25
8304N	6.75	8216N	3.25
ISP-8F/352	32.75	8224N	3.25
DP8226N	2.47	INS8255N	9.45

DIP IC INSERTION TOOLS WITH PIN STRAIGHTENER

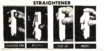

K153-ND	14-16 Pin Cip/IC Inserter	$3.49
K154-ND	14-16 Pin CMOS Safe Inserter	$7.95
K155-ND	24-28 Pin CMOS Safe Inserter	$7.95
K156-ND	36-40 Pin CMOS Safe Inserter	$7.95
K157-ND	Extractor Tool	$1.49

CMOS-SAFE DIP IC EXTRACTOR TOOL

K158-ND Extractor Tool $7.95

INSERTION & EXTRACTION KIT

K159-ND Insertion & Extraction Kit $29.95

5% CARBON FILM RESISTORS

¼ WATT RESISTOR ASSORTMENTS

RS125 Set of 5 each of the 73 standard 5% ¼ watt carbon film resistors in the series 1.0, 1.2, 1.5, 1.8, 2.2, etc., through 1.0 megohm (365 total pcs.) $9.90

RS225 Set of 5 each of the 72 standard 5% ¼ watt carbon film resistors in the series 1.1, 1.3, 1.6, 2.0, 2.4, etc., through 910 kilohm (360 total pcs.) $9.90

½ WATT RESISTORS ASSORTMENTS

RS150 Set of 5 each of the 73 standard 5% ½ watt carbon film resistors in the series 1.0, 1.2, 1.5, 1.8, 2.2, etc., through 1.0 megohm (365 total pcs.) $9.90

RS250 Set of 5 each of the 72 standard 5% ½ watt carbon film resistors in the series 1.1, 1.3, 1.6, 2.0, 2.4, etc., through 910 kilohm (360 total pcs.) $9.90

E.F. JOHNSON ALUMINUM SPACERS

Round Tubular

Cat. No.	I.D.	O.D.	Len.	10	100
J166	.115	.250	.187	$1.15	$9.90
J167	.115	.250	.250	1.25	10.80
J168	.140	.250	.125	1.05	9.00
J169	.140	.250	.250	1.25	10.80

Round Threaded

Cat. No.	Thread	O.D.	Len.	10	100
J170	4-40	.250	.375	$1.70	$14.40
J171	4-40	.250	.875	2.50	21.60
J172	4-40	.250	1.25	3.35	28.80
J173	6-32	.250	.625	1.80	15.30

Hex Threaded

Cat. No.	Thread	O.D.	Len.	10	100
J174	4-40	.250	.375	$1.90	$16.20
J175	4-40	.250	.625	2.30	19.80
J176	4-40	.250	.875	2.30	19.80
J177	6-32	.250	.250	1.45	12.30
J178	6-32	.250	.500	2.10	18.00
J179	6-32	.250	.625	2.30	19.80
J180	6-32	.250	.750	2.15	18.30
J181	6-32	.250	1.00	2.95	25.20

MOLEX I.C. SOCKET PINS

.95/C 9.10/M 42.00/5M 300.00/50M

TEXAS INSTRUMENTS I.C. SOCKETS

SOLDER TAIL DIP SOCKETS

- Low profile
- Face grip design for maximum rentention force
- Redundant contact points
- YOUR CHOICE — TIN OR GOLD* (*Minimum of 50 microinches gold inlay on gold sockets)
- TEXAS INSTRUMENTS QUALITY

TIN INLAY SOLDER TAIL Min. 200 Microinches Tin

Part No.	Description	1	10	100
C8508	8 pin solder tab, tin	.10	.88	8.00
C8514	14 pin solder tab, tin	.17	1.53	14.00
C8516	16 pin solder tab, tin	.20	1.76	16.00
C8518	18 pin solder tab, tin	.22	1.98	18.00
C8520	20 pin solder tab, tin	.25	2.21	20.00
C8522	22 pin solder tab, tin	.27	2.43	22.00
C8524	24 pin solder tab, tin	.30	2.65	24.00
C8528	28 pin solder tab, tin	.35	3.11	28.00
C8540	40 pin solder tab, tin	.49	4.41	40.00

GOLD INLAY SOLDER TAIL Min. 50 Microinches Gold

Part No.	Description	1	10	100
C9508	8 pin solder tab, gold	.28	2.48	22.00
C9514	14 pin solder tab, gold	.32	2.81	25.00
C9516	16 pin solder tab, gold	.37	3.26	29.00
C9518	18 pin solder tab, gold	.42	3.72	33.00
C9520	20 pin solder tab, gold	.47	4.16	37.00
C9522	22 pin solder tab, gold	.50	4.50	40.00
C9524	24 pin solder tab, gold	.54	4.84	43.00
C9528	28 pin solder tab, gold	.63	5.63	50.00
C9540	40 pin solder tab, gold	.90	8.10	72.00

WIRE WRAP DIP SOCKETS

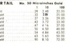

- Standard profile
- Universal mounting and packaging capabilities
- Contacts accommodate .015" through .021" rectangular or round dual-in-line leads
- Wire wrap posts held to true position of .015" providing a true position of .020" on boards for efficient automatic wire wrapping
- YOUR CHOICE — TIN OR GOLD* (*Minimum .50 microinch gold inlay on gold sockets)
- TEXAS INSTRUMENTS QUALITY

TIN PLATED WIRE WRAP Min. 200 Microinches Tin

Part No.	Description	1	10	100
C8108	8 pin wire wrap, tin	.33	2.93	26.00
C8114	14 pin wire wrap, tin	.38	3.70	36.00
C8116	16 pin wire wrap, tin	.47	4.10	40.00
C8118	18 pin wire wrap, tin	.55	4.95	44.00
C8120	20 pin wire wrap, tin	.78	6.98	62.00
C8122	22 pin wire wrap, tin	.80	7.20	64.00
C8124	24 pin wire wrap, tin	.83	7.43	66.00
C8128	28 pin wire wrap, tin	1.05	9.45	84.00
C8140	40 pin wire wrap, tin	1.58	14.18	126.00

GOLD INLAY WIRE WRAP Min. 50 Microinches Gold

Part No.	Description	1	10	100
C9108	8 pin wire wrap, gold	.49	4.35	41.10
C9114	14 pin wire wrap, gold	.82	7.45	69.95
C9116	16 pin wire wrap, gold	.91	8.20	77.15
C9118	18 pin wire wrap, gold	.99	8.95	84.40
C9120	20 pin wire wrap, gold	1.30	11.25	111.00
C9122	22 pin wire wrap, gold	1.33	11.95	113.05
C9124	24 pin wire wrap, gold	1.36	12.25	115.40
C9128	28 pin wire wrap, gold	1.81	16.35	154.10
C9140	40 pin wire wrap, gold	2.58	23.20	218.90

SILICON TRANSISTORS

	1	10	100	1000
2N3904	.20	1.79	16.25	146.25
2N3906	.20	1.79	16.25	146.25
2N4124	.21	1.93	17.50	157.50
2N4126	.22	2.01	18.25	164.25
2N4401	.21	1.93	17.50	157.50
2N4403	.21	1.93	17.50	157.50
2N4410	.30	2.70	24.38	219.38
2N5087	.24	2.20	20.00	180.00
2N5089	.24	2.20	20.00	180.00
2N5210	.27	2.48	22.50	202.50
2N5457	.54	4.86	43.88	394.88
92PU01A	.38	3.42	30.88	277.88
92PU10	.38	3.42	30.88	277.88
92PU45A	.41	3.69	33.32	299.82
92PU51A	.38	3.42	30.88	277.88
MJ2955	1.47	13.48	122.50	1102.25
MJE172	.74	6.66	60.13	541.13
MJE182	.72	6.48	58.50	526.50
MJE3439	.56	4.80	40.00	360.00
MJE344	.68	6.12	55.25	497.25
MJE370	.89	8.01	72.32	650.82
MJE371	1.10	9.90	89.38	804.38
MJE520	.86	7.74	69.88	628.88
MJE521	.86	7.74	69.88	628.88
MJE703	1.13	10.17	91.82	826.31
MJE712	.74	6.66	60.13	541.13
MJE722	.74	6.66	60.13	541.13
MJE803	1.01	9.09	82.07	738.57
MPF102	.54	4.95	45.00	405.00
MPS2222A	.21	1.93	17.50	157.50
MPS2369A	.24	2.20	20.00	180.00
MPS2907A]	.24	2.20	20.00	180.00
MPS3392	.23	2.07	18.75	169.00
MPS3393	.21	1.93	17.50	157.50
MPS3394	.24	2.20	20.00	180.00
MPS3395	.24	2.20	20.00	180.00
MPS3563	.21	1.93	17.50	157.50
MPS3565	.21	1.93	17.50	157.50
MPS3638A	.21	1.93	17.50	157.50
MPS3641	.21	1.93	17.50	157.50
MPS3643	.21	1.93	17.50	157.50
MPS918	.22	1.98	17.88	160.88
MPS930	.21	1.93	17.50	157.50
MPSA13	.27	2.48	22.50	202.50
TIP112	.98	8.40	70.00	630.00
TIP117	1.12	10.08	91.00	819.00
TIP120	1.17	10.73	97.50	877.50
TIP122	1.54	13.20	110.00	990.00
TIP127	1.54	13.20	110.00	990.00
TIP132	2.32	20.88	188.50	1696.50
TIP135	2.32	20.88	188.50	1696.50
TIP29C	.81	6.90	57.50	517.50
TIP30C	.81	6.90	57.50	517.50
TIP31C	.98	8.40	70.00	630.00
TIP32C	1.02	8.70	72.50	652.50
TIP61C	.81	6.90	57.50	517.50
TIP62C	.81	6.90	57.50	517.50

ITT RECTIFIERS

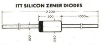

Cat. No.	Description	Pkg.	10	100	1000	10,000
1N4001	1 Amp 50 PIV Silicon Rectifier	DO-41	.80	7.00	60.00	540.00
1N4002	1 Amp 100 PIV silicon Rectifier	DO-41	.80	7.00	60.00	540.00
1N4003	1 Amp 200 PIV Silicon Rectifier	DO-41	.80	7.50	64.00	576.00
1N4004	1 Amp 400 PIV Silicon Rectifier	DO-41	.80	7.90	68.00	612.00
1N4005	1 Amp 600 PIV Silicon Rectifier	DO-41	1.00	9.00	74.00	666.00
1N4006	1 Amp 800 PIV Silicon Rectifier	DO-41	1.00	9.00	80.00	720.00
1N4007	1 Amp 1000 PIV Silicon Rectifier	DO-41	1.00	9.00	88.00	800.00
1N4148	Ultra Fast Switching Diode (1N914 equiv.)	DO-41	.60	5.00	32.00	276.60

ITT SILICON ZENER DIODES

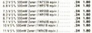

Catalog Number	Description	Unit Price	10
1N5226B	3.3 V 5% 500mW Zener (1N746A equiv.)	.24	1.80
1N5227B	3.6 V 5% 500mW Zener (1N747A equiv.)	.24	1.80
1N5228B	3.9 V 5% 500mW Zener (1N748A equiv.)	.24	1.80
1N5229B	4.3 V 5% 500mW Zener (1N749A equiv.)	.24	1.80
1N5230B	4.7 V 5% 500mW Zener (1N750A equiv.)	.24	1.80
1N5231B	5.1 V 5% 500mW Zener (1N751A equiv.)	.24	1.80
1N5232B	5.6 V 5% 500mW Zener (1N752A equiv.)	.24	1.80
1N5233B	6.0 V 5% 500mW Zener	.24	1.80
1N5234B	6.2 V 5% 500mW Zener (1N753A equiv.)	.24	1.80
1N5235B	6.8 V 5% 500mW Zener (1N957B equiv.)	.24	1.80
1N5236B	7.5 V 5% 500mW Zener (1N958B equiv.)	.24	1.80
1N5237B	8.2 V 5% 500mW Zener (1N959B equiv.)	.24	1.80
1N5238B	8.7 V 5% 500mW Zener	.24	1.80
1N5239B	9.1 V 5% 500mW Zener (1N960B equiv.)	.24	1.80
1N5240B	10 V 5% 500mW Zener (1N961B equiv.)	.24	1.80
1N5241B	11 V 5% 500mW Zener (1N962B equiv.)	.24	1.80
1N5242B	12 V 5% 500mW Zener (1N963B equiv.)	.24	1.80
1N5243B	13 V 5% 500mW Zener (1N964B equiv.)	.24	1.80
1N5244B	14 V 5% 500mW Zener	.24	1.80
1N5245B	15 V 5% 500mW Zener (1N965B equiv.)	.24	1.80
1N5246B	16 V 5% 500mW Zener (1N966b equiv.)	.24	1.80
1N5247B	17 V 5% 500mW Zener	.24	1.80
1N5248B	18 V 5% 500mW Zener (1N967B equiv.)	.24	1.80
1N5249B	19 V 5% 500mW Zener	.24	1.80
1N5250B	20 V 5% 500mW Zener (1N968B equiv.)	.24	1.80
1N5251B	22 V 5% 500mW Zener (1N969B equiv.)	.24	1.80
1N5252B	24 V 5% 500mW Zener (1N970B equiv.)	.24	1.80
1N5253B	25 V 5% 500mW Zener	.24	1.80
1N5254B	27 V 5% 500mW Zener (1N971B equiv.)	.24	1.80
1N5255B	28 V 5% 500mW Zener	.24	1.80
1N5256B	30 V 5% 500mW Zener (1N972B equiv.)	.24	1.80
1N5257B	33 V 5% 500mW Zener (1N973B equiv.)	.24	1.80

Call or Write for your Free DIGI-KEY Catalog

HOBBY-BLOX

THE NEW MODULAR CIRCUIT BUILDING SYSTEM

Whether you're a beginner or an advanced hobbyist, Hobby-Blox is the right system for you. The Hobby-Blox System takes you as far as your imagination will go. Begin at the beginning with a Hobby-Blox starter pack. You can expand the Hobby-Blox System with a complete line of modules.

BASIC INTEGRATED CIRCUIT STARTER PACK
The IC Starter Pack includes two terminal strips, two distribution strips and a spacer/support strip, already in a Hobby-Blox tray, ready for use. A free project booklet containing ten IC projects with step-by-step instructions completes the pack. Purchase of the IC Starter Pack saves you one dollar over price of modules purchased separately.
Part No. 921490-R **$5.97**

INTEGRATED CIRCUIT STARTER PACK COMPONENTS
Order Part No. 921491-R **$11.86**

BASIC DISCRETE COMPONENT STARTER PACK
This starter pack contains a tray, discrete component strip, battery holder and connector (battery not included) and project booklet with ten projects. Purchase of the Discrete Component Starter Pack saves you one dollar over price of modules purchased separately.
Part No. 921480-R **$6.57**

DISCRETE COMPONENT STARTER PACK COMPONENTS
Order Part No. 921481-R **$6.25**

TRAY Part No. 921500-R **$1.99**
All modules fit easily into the Hobby-Blox tray which is the basis for the entire Hobby-Blox system.

DISTRIBUTION STRIPS Part No. 921510-R **$1.99**
Includes two distribution strips, each of which has two continuous 26 tie-point terminals. With the Hobby-Blox distribution strips, it's easy to connect your circuitry to power and ground.

3x36 TERMINAL STRIPS Part No. 921505-R **$2.99**
Two terminal strips and a spacer/support strip make up this pack. Each terminal strip contains 26 3 tie-point terminals.

BLANK PANEL PACK Part No. 921550-R **$1.69**
A custom piece for any hobbyist. The blank panel allows you to drill holes in any manner of configuration to suit any mounting you desire.

BUS STRIP Part No. 921520-R **$2.99**
This Hobby-Blox module contains two continuous rows of 60 tie-point terminals for easy power and ground busing the entire length of the tray and also between trays with its unique tray interlocking features.

3x16 TERMINAL STRIP Part No. 921525-R **$2.99**
Consists of three patterns of terminals with each pattern containing two rows of eight contracts. This strip will accept three each 7 segment displays, 14 or 16 pin DIPS.

L.E.D. STRIP Part No. 921530-R **$1.99**
Accepts six LEDs and includes a common BUS for current limiting resistor

DISCRETE COMPONENT STRIP Part No. 921515-R **$2.99**
This module is the answer to breadboarding circuits with larger components. It contains 14 terminals, each with five tie-points. The tie-points are spaced .2" apart both vertically and horizontally.

BINDING POST STRIP Part No. 921560-R **$3.59**
Includes three five-way binding posts. Each binding post is electronically connected to a solderless plug-in tie-point.

TRAY EXTENDER CLIPS Part No. 921570-R **$1.29**
Expandability is not only side-by-side with the Hobby-Blox system. The tray extender clips allow you to attach trays end-to-end also! Includes four clips.

CONTROL PANEL PACK Part No. 921545-R **$1.69**
Includes two control panels and two spacer/support strips. Accepts a wide varity of switches and indicators.

SPEAKER PANEL PACK Part No. 921540-R **$1.69**
Includes two speaker panels and two spacer/support strips. Readily accepts a 2" or smaller diameter speaker.

BATTERY HOLDER PACK Part No. 921555-R **$2.59**
Includes battery holder and connector for a 9-volt battery. (Battery not included)

VERTICAL TRAY PACK Part No. 921535-R **$1.69**
Includes a smaller tray and an adaptor strip that allows you to mount the tray perpendicular to the horizontal tray.

SUPER-STRIPS

UNIVERSAL BREADBOARDING ELEMENTS WITH SOLDERLESS PLUG-IN TIE POINTS

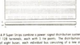

The A P Super-Strips combine a power/signal distribution system with a matrix of 128 terminals, each with 5 tie points. The distribution system consists of eight buses, each individual bus consisting of a line of 25 tie points. All tie points are the solderless, plug-in type of the same design used on A P terminal Strips and A P Distribution Strips.

923252	(Alloy 770 Terminals)	$18.50
923748	(Gold-plated Terminals)	$33.95

POWERACE

For faster and easier prototyping. They have built in power supplies

Powerace 101
With plus-5 to plus-15 VDC adj power supply. No. 923101 $ 96.95

Powerace 103
Triple-output power supply for digital & linear. No. 923103 $149.95
Other equipment, too numerous to mention, available.

Powerace 102
A digital lab including a logic probe & clock. No. 923102 $149.95

For complete AP Products specifications get your FREE DIGI-KEY catalog today

TEXAS INSTRUMENTS GOLD EDGEBOARD CONNECTORS

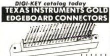

RELIABLE, COST-EFFICIENT CONTACT DESIGN

- 50 (Wire Wrap) to 50 (solder Tail) micro-inches gold inlay over a nickel diffusion barrier.
- Copper-nickel-tin CA 725 alloy.
- Bifurcated contact points.
- Preloaded, cantilever spring design.
- Contacts are user removable.

*NOTE — Dimensions below are the pin center to center measurement followed by the distance separating the two pin rows.

H4 SERIES .100"x.200" EDGEBOARD CONNECTORS

Positions Contacts	Part No. Wire Wrap	1	10	100	Part No. Solder Tail	1	10	100
10/20	C6-10	2.22	20.40	167.00	C5-10	2.10	19.30	158.00
15/30	C6-15	2.55	23.40	191.00	C5-15	2.37	21.70	178.00
17/34	C6-17	2.73	25.00	205.00	C5-17	2.52	23.10	189.00
18/36	C6-18	2.88	26.40	216.00	C5-18	2.61	23.90	196.00
20/40	C6-20	3.09	28.30	232.00	C5-20	2.76	25.30	207.00
22/44	C6-22	3.36	30.80	252.00	C5-22	2.97	27.20	223.00
25/50	C6-25	3.75	34.40	281.00	C5-25	3.27	30.00	245.00
28/56	C6-28	3.99	36.60	299.00	C5-28	3.54	32.50	266.00
30/60	C6-30	4.14	38.00	311.00	C5-30	3.75	34.40	281.00
31/62	C6-31	4.32	39.60	324.00	C5-31	3.84	35.20	288.00
35/70	C6-35	4.89	44.80	367.00	C5-35	4.20	38.50	315.00
36/72	C6-36	4.95	45.40	371.00	C5-36	4.32	39.60	324.00
40/80	C6-40	5.49	50.30	412.00	C5-40	4.71	43.20	353.00
43/86	C6-43	5.91	54.20	443.00	C5-43	4.98	45.70	374.00
49/98	C6-49	6.72	61.60	504.00	C5-49	5.58	51.20	419.00
50/100	C6-50	6.81	62.40	511.00	C5-50	5.64	51.70	423.00

for polarizing keys order P/N CR1164-2 .10/ea. 7.50/100

H4 SERIES .125"x.250" EDGEBOARD CONNECTORS

Positions Contacts	Part No. Wire Wrap	1	10	100	Part No. Solder Tail	1	10	100
10/20	C4-10	2.37	21.70	178.00	C3-10	2.13	19.50	160.00
15/30	C4-15	2.73	25.00	205.00	C3-15	2.46	22.60	185.00
18/36	C4-18	2.97	27.20	223.00	C3-18	2.67	24.50	200.00
20/40	C4-20	3.24	29.70	243.00	C3-20	2.85	26.10	214.00
22/44	C4-22	3.48	31.90	261.00	C3-22	3.00	27.50	225.00
25/50	C4-25	3.90	35.80	293.00	C3-25	3.39	31.10	254.00
28/56	C4-28	4.11	37.70	308.00	C3-28	3.69	33.80	277.00
30/60	C4-30	4.29	39.30	322.00	C3-30	3.81	34.90	286.00
31/62	C4-31	4.44	40.70	333.00	C3-31	4.05	37.10	304.00
35/70	C4-35	5.01	45.90	376.00	C3-35	4.50	41.30	338.00
36/72	C4-36	5.10	46.80	383.00	C3-36	4.56	41.80	342.00
40/80	C4-40	5.64	51.70	423.00	C3-40	5.04	46.20	378.00
44/88	C4-44	6.09	55.80	457.00	C3-44	5.49	50.30	412.00
50/100	C4-50	6.90	63.30	518.00	C3-50	6.18	56.70	464.00

for polarizing keys order P/N CR1164-2 .10/ea. 7.50/100

H4 SERIES .156"x.200" EDGEBOARD CONNECTORS

Positions Contacts	Part No. Solder Tail	1	10	100	Part No. Solder Eye	1	10	100
10/20	C1-10	2.49	22.80	187.00	C2-10	4.08	37.40	306.00
12/24	C1-12	2.64	24.20	198.00	C2-12	4.32	39.60	324.00
15/30	C1-15	2.94	27.00	221.00	C2-15	4.71	43.20	353.00
18/36	C1-18	3.18	29.20	239.00	C2-18	4.98	45.70	374.00
22/44	C1-22	3.54	32.50	266.00	C2-22	5.49	50.30	412.00
25/50	C1-25	3.84	35.20	288.00	C2-25	5.91	54.20	443.00
28/56	C1-28	4.29	39.30	322.00	C2-28	6.36	58.30	477.00

for polarizing keys order P/N CR1164-1 .10/ea. 7.50/100

ELECTRONIC HARDWARE KIT

1600 pieces of zinc plated hardware complete with divided plastic box for easy storage.

ELECTRONIC HARDWARE KIT CONTAINS:

100 2-56x1/4 Machine Screws	100 8-32x5/8 Machine Screws
100 2-56x1/2 Machine Screws	100 2-56 Hex Nuts
100 4-40x1/4 Machine Screws	100 4-40 Hex Nuts
100 4-40x1/2 Machine Screws	100 6-32 Hex Nuts
100 6-32x1/4 Machine Screws	100 8-32 Hex Nuts
100 6-32x1/2 Machine Screws	100 No. 2 Internal Tooth Lock Washers
100 8-32x3/8 Machine Screws	100 No. 4 Internal Tooth Lock Washers
	100 No. 6 Internal Tooth Lock Washers
	100 No. 8 Internal Tooth Lock Washers

CAT. NO. 1600 KIT
$14.95

"NEW" MA1032 Clock

Digital LCD Clock Module

- Operates from a single 1.5V Battery
- 0.5" LCD Display

Instructions Included In All Orders

- User selectable 12 or 24-hour mode
- 24-hour alarm with ON-OFF control
- Presetable 59-minute sleep timer with reset to zero
- 7-minute snooze timer
- Fast/Slow setting controls
- Seconds display
- 90 mA hour battery will typically last one year
- Minimum external parts required for travel clock/clock radio
- Backlighted Display

Catalog No.	Description	Cost
MA1032M	LCD Clock Module only	$24.95
MA1032C	Switch for MA1032M	$2.85
MA1032R	MA1032M, MA1032C, & AA battery holder	$28.20

TIME-TEMPERATURE PROGRAMMABLE MODULE

USER PROGRAMMABLE FOR:

- 12 or 24 Hour Display
- °F and or °C, as well as virtually any number of temperature sensors
- Fixed or flashing colon format
- 50/60 Hz line frequency operation

MA 1026 by National Semiconductor

Instruction included with all orders

FEATURES

- Giant 0.7 inch — 4 digit LED display with red lens.
- PM, colon, degree and alarm "ON" LED indicators.
- 6 display modes - temperature, time, seconds, alarm, sleep and lamp test.
- Exclusive Digi-Key switching panel available to simplify hook-up.
- Leading zero blanking.
- time is normal display mode, with temperature display at push of switch.
- displays temperatures in range of -40°C to 90°C.
- Power fail condition indicated by flashing.
- Addition of simple circuit will allow switching of small to medium AD loads.

Cat. No.	Description	Cost
MA1026M	MA1026 Clock Module (Assembled and tested)	$19.95
MA1026P	Digi-Key Switching Panel Kit for MA1026M (includes P.C. Board, switches, hardware, two temperature sensors, two potentiometers)	11.95
MA1026T	Special transformer for MA1026M	2.95
MA1026B	Alarm buzzer for MA1026M	3.00
MA1026K	Includes MA1026M P, T, and B	34.95
MA1026X	3.58 Megahertz Crystal	3.95
MA1026C	Conventional Switch Set for applications where MA1026P is not used includes one 501PB and ten 502PB switches	3.95
MA1026R	Includes MA1026M, MA1026C, MA1026T, two temperature sensors and two potentiometer	29.95

For each additional sensor unit, the following are suggested:

LM334	Temperature transducer for MA1026M module	1.53
KOA32	300 ohm potentiometer for LM334 transducer	.32
502PB	Normally open switch	.45

THE "PROGRAMMABLE" CLOCK MODULES

USER PROGRAMMABLE FOR:

- 12 or 24 hour display
- Fixed or flashing colon
- 50/60 Hz line frequency operation

NEW! Two Giant Sizes — 0.7" and 0.84"

FEATURES:

- Display brightness can be controlled by introduction of potentiometer
- Back-up time keeping with introduction of 5M potentiometer & 9V battery
- Alarm involves adding buzzer—no intervening circuitry
- Your Choice — 0.7" or 0.84" red LED display
- Low power consumption
- Leading zero blanking
- Optional switching panel to simplify hook-up

MA1023 — 0.7" HIGH DIGITS

Cat. No.	Description	Cost
MA1023M	MA1023 Clock Module Only (Assembled and tested)	$ 9.95
MA1023P	Digi-key Switching Panel Kit for MA1023 (Includes P.C. Board, Switches, Hardware and Components)	6.95
MA1023T	Special Transformers for MA1023	2.95
MA1023B	Alarm Buzzer for MA1023	3.00
MA1023K	Includes MA1023M, P, T, & B.	19.95
MA1023C	Conventional switch set for applications, where MA1023P is not used; includes one 501PB and ten 502PB	3.10
MA1023R	Clock Module, Conventional Switches, Transformer	14.95

MA1020 — 0.84" HIGH DIGITS

Cat. No.	Description	Cost
MA1020M	MA1020 Clock Module (Assembled and tested)	$13.95
MA1020P	Digi-key Switching Panel Kit for MA1020 (Includes P.C. Board, Switches, Hardware, Components)	7.95
MA1020T	Special Transformer for MA1020M	3.25
MA1020B	Alarm Buzzer for MA1020M	3.00
MA1020K	Includes MA1020M, P, T, & B.	26.95
MA1020C	Conventional switch set for applications where MA1020P is not used, includes one 501PB and six 502PB and a 3M ohm resistor, trimmer, battery snaps.	3.50
MA1020R	Includes MA1020M, MA1020C & MA1020T	19.95

DIGITAL CLOCK BEZEL

THE J.M.J. DIGITAL DISPLAY BEZEL

WITH RED FILTER
Part No. 400

UNIVERSAL SIZE
HANDLES MOST REQUIREMENTS

Be Sure to Order the Proper Adapter for Your Digital Clock

Part	Description	Price
400	Digital Display BEZEL with Red Filter	$ 4.95
420	Mounting Adapters for MA1001, MA1002, etc.	.69
421	Mounting Adapters for MA1010, MA1020, MA1026	.69
422	Universal PC Board Mounting Adapters	.69
423	Mounting Adapter for MA1023	.69

DIGI-CLOCK KIT

- 12 VDC — Ideal for Car, Van or Boat!

- Trouble-free Module!
- 270° Swivel Mount
- Inlaid Walnut Chrome Trim Bezel!
- Ideal for Car, Van or Boat!
- 3-5/8"x2-3/16" Tall x 2-1/8" Deep!
- Quick and Easy to Install!

Part No. 5001K
ONLY $24.95

Do you need spacers, Banana plugs and jacks, or tip plugs and jacks? You can get these and more E. F. JOHNSON products from DIGI-KEY.

HEAT SINKS from TO-92 2W coolers to TO-3 100W sinks.

PANASONIC ELECTROLYTIC CAPACITORS

Value UF	WV D.C.	Axial 1	Axial 10	Axial 100	Radial 1	Radial 10	Radial 100
22	/6.3	.18	1.54	12.83	—	—	—
33	/6.3	.20	1.68	14.04	.14	1.12	9.31
47	/6.3	.21	1.74	14.48	.14	1.16	9.59
100	/6.3	.22	1.83	15.22	.16	1.33	11.05
220	/6.3	.28	2.34	19.53	.21	1.78	14.80
330	/6.3	.29	2.46	20.48	.23	1.92	15.95
470	/6.3	.33	2.78	23.15	.23	1.97	16.34
1000	/6.3	.49	4.20	35.00	.36	3.08	25.62
2200	/6.3	.60	5.13	42.75	.54	4.56	37.95
3300	/6.3	.81	6.94	57.83	.75	6.38	53.10
4700	/6.3	1.04	8.89	74.07	.93	7.95	66.20
6800	/6.3	1.27	10.87	90.58	1.13	9.68	80.62
10000	/6.3	1.54	13.17	109.77	1.54	13.13	109.40
22	/10	.18	1.54	12.83	.13	1.08	8.94
33	/10	.21	1.74	14.48	.14	1.16	9.59
47	/10	.21	1.77	14.78	.14	1.19	9.90
100	/10	.24	2.00	16.65	.17	1.39	11.58
220	/10	.29	2.46	20.48	.23	1.92	15.95
330	/10	.33	2.78	23.15	.24	2.06	17.10
470	/10	.44	3.72	30.97	.35	2.97	24.69
1000	/10	.55	4.63	38.62	.41	3.42	28.45
2200	/10	.78	6.63	55.28	.70	5.93	49.42
3300	/10	.99	8.45	70.38	.90	7.71	64.22
4700	/10	1.28	10.94	91.18	1.13	9.68	80.62
6800	/10	1.55	13.26	110.52	1.54	13.20	109.40
10000	/10	1.99	17.00	141.63	—	—	—
10	/16	.18	1.54	12.83	.13	1.08	8.94
22	/16	.21	1.74	14.48	.14	1.15	9.52
33	/16	.21	1.77	14.77	.14	1.19	9.90
47	/16	.24	2.00	16.65	.16	1.36	11.31
100	/16	.28	2.34	19.53	.21	1.78	14.80
220	/16	.33	2.78	23.15	.24	2.06	17.10
330	/16	.44	3.72	30.97	.35	2.97	24.69
470	/16	.50	4.22	35.14	.38	3.19	26.58
1000	/16	.60	5.09	42.45	.50	4.21	35.08
2200	/16	.92	7.85	65.39	.87	7.46	62.10
3300	/16	1.16	9.91	82.62	1.17	10.01	83.48
4700	/16	1.57	13.40	111.68	1.57	13.43	111.87
6800	/16	1.99	17.00	141.63	—	—	—
2.2	/25	.18	1.54	12.83	—	—	—
3.3	/25	.18	1.54	12.83	.13	1.08	8.94
4.7	/25	.18	1.54	12.83	.13	1.08	8.94
10	/25	.18	1.54	12.83	.14	1.15	9.52
22	/25	.22	1.83	15.22	.15	1.22	10.17
33	/25	.24	2.00	16.65	.17	1.38	11.50
47	/25	.28	2.34	19.53	.21	1.73	14.42
100	/25	.33	2.78	23.15	.23	1.90	15.77
220	/25	.44	3.75	31.24	.40	3.42	28.45
330	/25	.50	4.26	35.47	.52	4.45	37.08
470	/25	.58	4.95	41.24	.64	5.42	45.13
1000	/25	.84	7.18	59.84	.83	7.06	58.78
2200	/25	1.16	9.91	82.62	1.17	10.02	83.47
3300	/25	1.61	13.77	114.71	1.66	14.17	118.03
4700	/25	1.99	17.00	141.63	—	—	—
2.2	/35	.18	1.54	12.83	—	—	—
3.3	/35	.18	1.54	12.83	.13	1.11	9.20
4.7	/35	.18	1.54	12.83	.13	1.11	9.20
10	/35	.21	1.77	14.78	.14	1.19	9.90
22	/35	.24	2.00	16.65	.19	1.60	13.30
33	/35	.28	2.34	19.53	.21	1.78	14.80
47	/35	.33	2.78	23.15	.23	1.90	15.77
100	/35	.43	3.65	30.40	.24	2.06	17.10
220	/35	.51	4.34	36.17	.40	3.42	28.45
330	/35	.57	4.85	40.40	.52	4.45	37.08
470	/35	.65	5.51	45.89	.64	5.42	45.13
1000	/35	.98	8.38	69.80	.92	7.84	65.32
2200	/35	1.61	13.77	114.71	1.66	14.17	118.03
3300	/35	1.99	17.00	141.63	—	—	—
4700	/35	2.61	22.31	185.88	—	—	—
0.47	/50	.18	1.54	12.83	.13	1.08	8.94
1	/50	.18	1.54	12.83	.13	1.08	8.94
2.2	/50	.18	1.54	12.83	.13	1.08	8.94
3.3	/50	.18	1.54	12.83	.14	1.15	9.52
4.7	/50	.21	1.77	14.77	.14	1.18	9.78
10	/50	.24	2.00	16.65	.16	1.35	11.20
22	/50	.28	2.34	19.53	.22	1.83	15.19
33	/50	.32	2.69	22.43	.23	1.90	15.77
47	/50	.36	3.04	25.33	.24	2.05	17.03
100	/50	.45	3.78	31.54	.36	3.08	25.62
220	/50	.61	5.18	43.15	.52	4.45	37.08
330	/50	.76	6.50	54.14	.83	7.06	58.78
470	/50	.92	7.87	65.55	.92	7.84	65.32
1000	/50	1.25	10.71	89.27	1.31	11.16	92.93
2200	/50	1.99	17.00	141.63	—	—	—
0.47	/63	.18	1.54	12.83	.13	1.12	9.32
1	/63	.18	1.54	12.83	.13	1.12	9.32
2.2	/63	.18	1.54	12.83	.14	1.15	9.32
3.3	/63	.21	1.77	14.77	.15	1.25	10.35
4.7	/63	.24	2.00	16.65	.16	1.34	11.13
10	/63	.28	2.34	19.53	.18	1.50	12.43
22	/63	.33	2.78	23.15	.24	2.02	16.79
33	/63	.37	3.12	26.04	.27	2.24	18.60
47	/63	.53	4.51	37.62	.38	3.18	26.45
100	/63	.56	4.76	39.64	.50	4.24	35.27
220	/63	.76	6.50	54.14	.78	6.61	55.02
330	/63	.92	7.87	65.55	.92	7.84	65.32
470	/63	1.05	8.94	74.52	.99	8.43	70.19
1000	/63	1.36	11.59	96.55	1.66	14.17	118.03
2200	/63	2.61	22.31	185.89	—	—	—
0.47	/100	.18	1.54	12.83	.14	1.19	9.90
1	/100	.18	1.54	12.83	.14	1.19	9.90
2.2	/100	.22	1.83	15.22	.15	1.25	10.35
3.3	/100	.24	2.00	16.65	.17	1.38	11.50
4.7	/100	.28	2.34	19.53	.17	1.41	11.70
10	/100	.33	2.78	23.15	.22	1.83	15.19
22	/100	.43	3.65	30.40	.27	2.27	18.90
33	/100	.45	3.85	32.12	.34	2.88	24.00
47	/100	.54	4.62	38.49	.41	3.50	29.14
100	/100	.74	6.29	52.43	.57	4.83	40.22
220	/100	1.09	9.26	77.18	.96	8.22	68.47
330	/100	1.30	11.10	92.53	1.25	10.70	89.13
470	/100	1.81	15.46	128.80	1.78	15.25	127.04
1000	/100	3.16	27.09	225.72	—	—	—

PANASONIC METALLIZED POLYESTER CAPACITORS

250 VDC plus minus 10% TOLERANCE

NEW! KIT
170 METALIZED POLYESTER CAPACITORS
Price includes convenient divided plastic box with bin guide for easy storage and quick access.
ASSORTMENT OF 15 POPULAR VALUES PANASONICQUALITY

CAT. NO. E-KIT
ONLY
$54.95

PART NO.	CAP (UFD)	1	10	100	1000
E2103	.01	.19	1.64	13.68	123.08
E2123	.012	.19	1.64	13.68	123.08
E2153	.015	.19	1.64	13.68	123.08
E2183	.018	.19	1.64	13.68	123.08
E2223	.022	.19	1.64	13.68	123.08
E2273	.027	.19	1.64	13.68	123.08
E2333	.033	.19	1.64	13.68	123.08
E2393	.039	.19	1.64	13.68	123.08
E2473	.047	.22	1.85	15.43	138.83
E2563	.056	.22	1.85	15.43	138.83
E2683	.068	.22	1.85	15.43	138.83
E2823	.082	.22	1.85	15.43	138.83
E2104	.10	.23	1.94	16.13	145.13
E2124	.12	.25	2.12	17.63	158.63
E2154	.15	.26	2.28	18.95	170.55
E2184	.18	.29	2.49	20.73	186.53
E2224	.22	.32	2.68	22.28	200.48
E2274	.27	.34	2.90	24.25	218.25
E2334	.33	.37	3.18	26.47	238.17
E2394	.39	.41	3.44	28.67	257.85
E2474	.47	.43	3.68	30.65	275.85
E2564	.56	.47	4.02	33.45	301.05
E2684	.68	.52	4.43	36.93	332.33
E2824	.82	.58	4.94	41.13	370.13
E2105	1.0	.63	5.35	44.52	400.62
E2125	1.2	.68	5.82	48.50	436.50
E2155	1.5	.85	7.22	60.97	548.67
E2185	1.8	.94	8.64	72.00	648.00
E2225	2.2	1.03	8.85	73.68	663.08

PANASONIC K-SERIES CAPACITORS

New Panasonic Kseries are miniature, low cost aluminum electrolytic capacitors. Their size and performance characteristics make them viable alternatives to tantalums in many applications.

CAPACITANCE TOLERANCE: 20%
D.C. LEAKAGE CURRENT, MAX. 1 0.01 C V OR 3uA
ALL K-SERIES CAPACITORS WE CARRY ARE RADIAL

DIGI-KEY PART NO.	CAPACITANCE UF	WORKING VOLTAGE DC	1	10 PAK
P800	22		.24	2.03
P801	33	6.3	.25	2.13
P802	47		.26	2.18
P803	100		.30	2.56
P804	22		.25	2.13
P805	33	10	.26	2.23
P806	47		.28	2.37
P807	10		.25	2.07
P808	22	16	.25	2.28
P809	33		.29	2.45
P810	47		.32	2.72
P811	3.3		.24	2.03
P812	4.7		.24	2.03
P813	10	25	.25	2.13
P814	22		.29	2.45
P815	33		.33	2.76
P816	3.3		.24	2.03
P817	4.7	35	.25	2.07
P818	10		.26	2.23
P819	22		.32	2.72
P820	.1		.24	2.72
P821	.22		.24	2.03
P822	.33		.24	2.03
P823	.47		.24	2.03
P824	1.0	50	.24	2.03
P825	2.2		.24	2.03
P826	3.3		.25	2.07
P827	4.7		.25	2.13
P828	10		.28	2.38

PANASONIC POLYESTER CAPACITORS

100 VDC plus minus 10% TOLERANCE

NEW! KIT
150 POLYESTER CAPACITORS
Price includes convenient divided plastic box with bin guide for easy storage and quick access.
ASSORTMENT OF 15 POPULAR VALUES PANASONICQUALITY

CAT. NO. M-KIT
ONLY
$34.95

PART NO.	CAP (UFD)	PRICES 1	PAK OF 10	PAK OF 100	PAK OF 1000
M1102	.001	.14	1.17	8.34	75.04
M1122	.0012	.14	1.17	8.34	75.04
M1152	.0015	.14	1.17	8.34	75.04
M1182	.0018	.14	1.17	8.34	75.04
M1222	.0022	.14	1.17	8.34	75.04
M1272	.0027	.14	1.17	8.34	75.04
M1332	.0033	.14	1.17	8.34	75.04
M1392	.0039	.14	1.17	8.34	75.04
M1472	.0047	.14	1.17	8.34	75.04
M1562	.0056	.14	1.17	8.34	75.04
M1682	.0068	.14	1.17	8.34	75.04
M1822	.0082	.14	1.17	8.34	75.04
M1103	.01	.14	1.17	8.34	75.04
M1123	.012	.14	1.22	8.65	77.85
M1153	.015	.14	1.22	8.65	77.85
M1183	.018	.15	1.24	8.80	79.20
M1223	.022	.15	1.26	8.94	80.44
M1273	.027	.15	1.26	8.94	80.44
M1333	.033	.15	1.28	9.10	81.80
M1393	.039	.16	1.32	9.40	84.60
M1473	.047	.16	1.35	9.60	86.18
M1563	.056	.17	1.46	10.38	93.38
M1683	.068	.18	1.51	10.74	96.64
M1823	.082	.18	1.55	11.07	99.57
M1104	.1	.18	1.58	11.28	101.48
M1124	.12	.21	1.80	12.85	115.65
M1154	.15	.23	2.01	14.30	128.70
M1184	.18	.26	2.26	16.09	144.79
M1224	.22	.28	2.38	16.98	152.78
M1274	.27	.32	2.72	19.40	174.60
M1334	.33	.34	2.96	21.12	190.02
M1394	.39	.39	3.35	23.88	214.88
M1474	.47	.41	3.58	25.57	230.02

PLESSEY "MINI-BOX"

Metalized Poly. Cap. Kit

140 CAPACITORS
Price includes convenient divided plastic box with bin guide for easy storage and quick access.
ASSORTMENT OF 14 POPULAR "MINI-BOX" CAPACITORS

CAT. NO. 3050P-Kit
ONLY
$35.95

PANASONIC ELECTROLYTIC KIT

150 CAPACITORS
Price includes convenient divided plastic box with bin guide for easy storage and quick access.
ASSORTMENT OF 15 POPULAR CAPACITORS

Cat. No. P6200-Kit
ONLY
$35.95

E. F. JOHNSON PLUG & JACK KIT

150 COMPONENTS
Price includes convenient divided plastic box with bin guide for easy storage and quick access.
ASSORTMENT OF 150 POPULAR JACKS & PLUGS

Cat. No. J100-Kit
ONLY
$69.95

PANASONIC DISC CAPACITORS

NEW! KIT
310 DISC CAPACITORS
Prices includes convenient divided plastic box with bin guide for easy storage and quick access.
ASSORTMENT OF 18 POPULAR VALUES PANASONICQUALITY
(Tolerance: A — plus/minus 5%, B — plus/minus 10%, C — plus 80%/minus 20%)

CAT. NO. DH-KIT
ONLY
$24.95

Part Number	Capacitance	Tolerance	Voltage	1	10	100
DH100	10PF	A	500V	.74	5.46	45.50
DH150	15PF	B	500V	.52	3.60	30.00
DH220	22PF	B	500V	.52	3.60	30.00
DH330	33PF	B	500V	.52	3.60	30.00
DH470	47PF	B	500V	.61	4.30	35.75
DH680	68PF	B	500V	.61	4.30	35.75
DH101	100PF	B	500V	.74	5.46	45.50
DH151	150PF	B	500V	.74	5.46	45.50
DH221	220PF	B	500V	.74	5.46	45.50
DH331	330PF	B	500V	.74	5.46	45.50
DH471	470PF	B	500V	.74	5.46	45.50
DH681	680PF	B	500V	.74	5.46	45.50
DH102	.001UFD	C	50V	.60	4.20	35.00
DH152	.0015UFD	C	50V	.60	4.20	35.00
DH222	.0022UFD	C	50V	.60	4.20	35.00
DH332	.0033UFD	C	50V	.60	4.20	35.00
DH472	.0047UFD	C	50V	.60	4.20	35.00
DH682	.0068UFD	C	50V	.61	4.29	35.75
DE103	.01UFD	C	25V	.84	6.30	50.00
DE223	.022UFD	C	25V	.84	6.30	52.50
DE333	.033UFD	C	25V	1.14	7.98	66.50
DE473	.047UFD	C	25V	1.09	8.40	70.00
DE104	.1UFD	C	25V	1.80	15.10	125.75

PANASONIC RESIN DIPPED TANTALUM CAPACITORS

NEW! KIT
180 TANTALUM CAPACITORS
Prices includes convenient divided plastic box with bin guide for easy storage and quick access.
ASSORTMENT OF 15 POPULAR VALUES PANASONICQUALITY

CAT. NO. F-KIT
ONLY
$79.95

Part No.	Cap (uF)	Voltage (V. DC)	Prices 1	Pak of 10	Pak of 100	Pak of 1000
F35ER1	0.1	35	.38	3.21	26.70	240.30
F35ER15	0.15	35	.38	3.21	26.70	240.30
F35ER22	0.22	35	.38	3.21	26.70	240.30
F35ER33	0.33	35	.38	3.21	26.70	240.30
F35ER47	0.47	35	.38	3.21	26.70	240.30
F35ER68	0.68	35	.38	3.21	26.70	240.30
F35E1	1.0	35	.43	3.64	30.33	272.93
F16E1R5	1.5	16	.38	3.21	26.70	240.30
F16E2R2	2.2	16	.42	3.56	29.63	266.63
F16E3R3	3.3	16	.47	4.02	33.43	300.83
F16E4R7	4.7	16	.55	4.65	38.70	348.30
F16E6R8	6.8	16	.65	5.54	46.14	415.24
F16E10	10	16	.81	6.91	57.53	517.73
F16E15	15	16	1.06	9.06	75.50	679.50
F16E22	22	16	1.41	12.05	100.36	903.26

DIGI-KEY Precut/Prestripped Wire

Precut/Prestripped 100 Wire Package
Bulk Wire Wrap Wire

Wire Assortment No. WK-1-A
900 Precut/Prestripped No. 30 Wire Wrap Wire. Assortment consists of following lengths and quantities.
250—3" 100—4½"
250—3½" 100—5"
100—4" 100—6"
Catalog No. WK-1-A $17.95

Wire Assortment No. WK-2-A
2800 Precut/prestripped No. 30 Wire Wrap Wire. Assortment consists of following lengths and quantities.
250—2½" 250—5"
500—3" 100—5½"
500—3½" 100—6"
500—4" 100—6½"
500—4½" 100—7"
Catalog No. WK-2-A $42.95

Wire Stripped 1" both ends
PRECUT/PRESTRIPPED WIRE 100 Wires/Package

Part No.	Color	Length	Cost
B3	30-AWG Blue Wire,	3" Overall Length	$2.25
Y3	30-AWG Yellow Wire,	3" Overall Length	2.25
W3	30-AWG White Wire,	3" Overall Length	2.25
R3	30-AWG Red Wire,	3" Overall Length	2.25
B4	30-AWG Blue Wire,	4" Overall Length	2.40
Y4	30-AWG Yellow Wire,	4" Overall Length	2.40
W4	30-AWG White Wire,	4" Overall Length	2.40
R4	30-AWG Red Wire,	4" Overall Length	2.40
B5	30-AWG Blue Wire,	5" Overall Length	2.65
Y5	30-AWG Yellow Wire,	5" Overall Length	2.65
W5	30-AWG White Wire,	5" Overall Length	2.65
R5	30-AWG Red Wire,	5" Overall Length	2.65
B6	30-AWG Blue Wire,	6" Overall Length	2.90
Y6	30-AWG Yellow Wire,	6" Overall Length	2.90
W6	30-AWG White Wire,	6" Overall Length	2.90
R6	30-AWG Red Wire,	6" Overall Length	2.90
B7	30-AWG Blue Wire,	7" Overall Length	3.50
Y7	30-AWG Yellow Wire,	7" Overall Length	3.50
W7	30-AWG White Wire,	7" Overall Length	3.50
R7	30-AWG Red Wire,	7" Overall Length	3.50
B8	30-AWG Blue Wire,	8" Overall Length	3.75
Y8	30-AWG Yellow Wire,	8" Overall Length	3.75
W8	30-AWG White Wire,	8" Overall Length	3.75
R8	30-AWG Red Wire,	8" Overall Length	3.75

30 AWG Kynar Insulated in Bulk Continuous Length

Part No.	Color	Length	Cost
100 RD	Red	100 feet	$ 3.10
100 BK	Black	100 feet	3.10
100 BU	Blue	100 feet	3.10
500 RD	Red	500 feet	13.50
500 BK	Black	500 feet	13.50
500 BU	Blue	500 feet	13.50
1000 RD	Red	1000 feet	23.75
1000 BK	Black	1000 feet	23.75
1000 BU	Blue	1000 feet	23.75

The Digi-Key volume discount and Service charges are simple to apply. Most items sold by Digi-Key may be combined for a volume discount. Items that are not discountable are identified by the suffix-ND following the part number. After writing your order, total all of the discountable items and apply the appropriate discount. To this subtotal, add the non-discountable items. Then add the Service charge. We pay all shipping and insurance to addresses in the U.S.A., Canada and Mexico when payment accompanies order.

WHEN ORDERING BY PHONE, CALL: 1-800-346-5144 (Mn., Ak., Hi., call 218-681-6674) By mail send your order to: DIGI-KEY, Highway 32 South, Thief River Falls, MN 56701

You may pay by check, money order, Master Charge, VISA or C.O.D. ***DIGI-KEY GUARANTEE:*** Any parts or products purchased from Digi-Key that prove to be defective will be replaced or refunded if returned within 90 days from receipt with a copy of your invoice.

SERVICE	CHARGES	VOLUME DISCOUNT	
$ 0.00-$ 9.99	Add $2.00	$ 0.00-$ 99.99	NET
$ 10.00-$25.00	Add $0.75	$ 100.00-$249.99	Less 10%
$ 25.00-$49.99	Add $0.50	$ 250.00-$499.99	Less 15%
$ 50.00-$99.99	Add $0.25	$ 500.00-$999.99	Less 20%
$100.00 & Up	No Charge	$1000.00 & Up	Less 25%

CIRCLE NO. 11 ON FREE INFORMATION CARD

16K Memory 8/$19.95

4116 200ns

NEC Mostek

ALL MERCHANDISE 100% GUARANTEED!

CALL US FOR VOLUME QUOTES

LS SERIES

74LS00	.32	74LS155	1.19
74LS01	.28	74LS156	.95
74LS02	.38	74LS157	.79
74LS03	.32	74LS158	.82
74LS04	.35	74LS160	.94
74LS05	.28	74LS161	.99
74LS08	.38	74LS162	.99
74LS09	.38	74LS163	.99
74LS10	.32	74LS164	.99
74LS11	.29	74LS165	.99
74LS12	.29	74LS166	2.40
74LS13	.38	74LS168	1.79
74LS14	.99	74LS169	1.79
74LS15	.35	74LS170	1.89
74LS20	.26	74LS173	.82
74LS21	.30	74LS174	1.19
74LS22	.34	74LS175	1.09
74LS26	.40	74LS181	2.19
74LS27	.35	74LS190	1.15
74LS28	.39	74LS191	1.31
74LS30	.35	74LS192	.88
74LS32	.39	74LS193	.98
74LS33	.54	74LS194	1.80
74LS37	.78	74LS195	1.39
74LS38	.39	74LS196	.82
74LS40	.25	74LS197	.82
74LS42	.79	74LS221	1.28
74LS47	.78	74LS240	1.89
74LS48	.78	74LS241	1.89
74LS51	.35	74LS242	1.89
74LS54	.35	74LS243	1.89
74LS55	.32	74LS244	1.79
74LS73	.44	74LS245	2.89
74LS74	.48	74LS251	1.32
74LS75	.58	74LS253	.89
74LS76	.50	74LS257	.89
74LS78	.59	74LS258	.89
74LS83	.90	74LS259	2.89
74LS85	1.23	74LS260	.68
74LS86	.45	74LS266	.68
74LS90	.70	74LS273	1.69
74LS92	.82	74LS275	3.39
74LS93	.71	74LS279	.59
74LS95	1.11	74LS283	1.03
74LS96	.86	74LS290	1.25
74LS107	.43	74LS293	1.89
74LS109	.49	74LS295	1.09
74LS112	.48	74LS298	1.24
74LS113	.48	74LS352	1.59
74LS114	.55	74LS353	1.59
74LS122	.55	74LS363	1.39
74LS123	.99	74LS365	.99
74LS124	2.99	74LS366	.99
74LS125	.99	74LS367	.99
74LS126	.88	74LS368	.99
74LS132	.69	74LS373	1.85
74LS136	.58	74LS374	1.81
74LS138	.79	74LS377	1.48
74LS139	.79	74LS385	1.90
74LS145	1.19	74LS386	.65
74LS148	1.39	74LS390	1.90
74LS151	.79	74LS393	1.90
74LS153	.79	74LS395	1.69
74LS154	2.39	74LS670	2.20

SPRING MEMORY SALE

RAMS			100pcs	EPROMS			100pcs
2101	(450ns)	2.49	2.29				
2102-1	(450ns)	.99	.95	1702	(1us)	4.95	4.75
21L02-1	(450ns)	1.29	1.15	2708	(450ns)	4.95	4.75
2111	(450ns)	2.99	2.49	2758(5v)	(450ns)	9.95	Call
2112	(450ns)	2.99	2.79	2716(5v)	(450ns)	7.95	6.95
2114	(450ns)	2.95	2.85	2716-1(5v)	(350ns)	12.95	10.95
2114L-2	(200ns)	8/29.95	3.10	TMS2516	(450ns)	9.95	9.50
2114L-3	(300ns)	8/24.95	2.95	TMS2716	(450ns)	9.95	8.95
4027	(250ns)	4.95	3.95	2732	(450ns)	29.95	Call
4116-15	(150ns)	8/21.95	2.65	TMS2532	(450ns)	21.95	Call
4116-20	(200ns)	8/19.95	2.35	TMS25L32	(450ns)	29.95	Call
4116-30	(300ns)	8/18.99	2.29	TMS2564	(500ns)	179.95	Call

NEED YOUR ORDER SHIPPED TODAY? THEN CALL TOLL FREE

800-538-5000

IN CALIF.

800-662-6233

(effective 4-14-81)

BEFORE YOU BUY, CALL US.
WE WILL BEAT
ANYONE'S PRICES

6800

6800	11.75
6810	4.60
6820	5.75
6821	6.40
6828	9.95
6834	19.95
6850	5.75
6852	5.75
6875	6.95

8080

8080A	3.95
8085A	12.95
8212	2.75
8214	5.25
8216	2.75
8224	2.95
8226	3.49
8228	4.95
8238	5.50
8251	6.95
8253	12.95
8255	6.50
8257	16.95
8259	14.95
8275	49.95
8279	15.95

Z80

Z80	9.95
Z80A	12.95
Z80-CTC	7.65
Z80-DMA	18.00
Z80-PIO	7.60
Z80-SIO/2	27.50
Z80-SIO/9	20.50

T.V. CIRCUITS

MC1330	1.89
MC1350	1.29
MC1358	1.79
LM380	1.29
LM565	.99
LM741	.29
LM1310	**2.90**
LM1800	**2.99**
LM1889	2.49

MISC.

1771-B01	24.95
3242	9.95
AY5-1013	4.99
8T26	2.49
8T28	2.49
8T97	1.69
8T98	1.69

7400 SERIES

7400	.19	7450	.19	74123	.59
7402	.19	7472	.29	74151	.69
7404	.24	7473	.34	74153	.59
7406	.29	7474	.35	74154	1.49
7407	.29	7475	.49	74156	.69
7408	.24	7476	.35	74157	.69
7410	.19	7483	.65	74161	.79
7420	.19	7486	.35	74163	.89
7430	.19	7490	.49	74164	.89
7432	.29	7491	.69	74173	1.39
7440	.19	7492	.59	74174	.89
7442	.49	7493	.49	74175	.89
7445	.69	7496	.74	74176	.89
7446	.69	74100	1.19	74192	.79
7447	.59	74107	.34	74193	.79
7448	.69	74121	.34	74196	.79

IC SOCKETS

8 pin ST	**10/1.29**	8 pin WW	.59
14 pin ST	**10/1.49**	14 pin WW	.69
16 pin ST	**10/1.69**	16 pin WW	.69
18 pin ST	**10/1.99**	18 pin WW	.99
20 pin ST	**10/2.89**	20 pin WW	1.09
22 pin ST	**10/2.99**	22 pin WW	1.39
24 pin ST	**10/2.99**	24 pin WW	1.49
28 pin ST	**10/3.99**	28 pin WW	1.69
40 pin ST	**10/4.99**	40 pin WW	1.99

ST = SOLDERTAIL   WW = WIREWRAP

VOLTAGE REG's

7805T	.89	7905T	.99
7812T	.89	7912T	.99
7815T	.99	7915T	1.19
7824T	.99	7924T	1.19
7805K	1.39	7905K	1.49
7812K	1.39	7912K	1.49
78L05	.69	79L05	.79
78L12	.69	79L12	.79
78L15	.69	79L15	.79

TRANSISTORS

2N2222	10/1.00	100/8.99
2N3904	10/1.00	100/8.99
2N3906	10/1.00	100/8.99
2N3055	.79	10/6.99

LEDS

Jumbo Red	10/1.00
Jumbo Green	6/1.00
Jumbo Yellow	6/1.00
5082-7760 .43'CC	.79
MAN74 .3'CC	.99
MAN72 .3'CA	.99

CMOS

4001	.35	4024	.99	4070	.49
4002	.39	4025	.29	4071	.49
4007	.25	4027	.65	4072	.49
4009	.49	4040	1.29	4081	.39
4010	.49	4042	.99	4093	.99
4011	.35	4046	1.79	4098	2.49
4012	.29	4047	2.49	4503	.69
4013	.49	4049	.49	4508	3.95
4016	.59	4050	.69	74C04	.39
4017	1.19	4060	1.39	74C14	1.49
4020	1.19	4066	.79		
4023	.29	4069	.39		

LINEAR

LM301v	.34	LM556	.69	LM1488	1.39
LM308v	.98	LM565	.99	LM1489	1.39
LM309K	1.49	LM566v	1.49	LM1800	2.99
LM311v	.64	LM567v	1.29	LM1889	2.49
LM317t	2.29	LM723	.49	LM3900	.59
LM318v	1.49	LM733	.98	75451v	.39
LM323k	4.95	LM741v	.29	MC1330v	1.89
LM324	.59	LM747	.79	MC1350v	1.29
LM339	.99	LM748v	.59	MC1358	1.79
LM377	2.29	LM1310	**2.90**		
LM380	1.29	LM1414	1.59		
LM555v	.39	LM1458v	.69		

T = TO-220   V = 8 pin   K = TO-3

DIP SWITCHES

4 position	.99
5 position	1.02
6 position	1.06
7 position	1.09
8 position	1.14

74S00 SERIES

74S00	.50	74S124	3.95	74S288	4.75
74S02	.50	74S174	1.49	74S387	5.75
74S04	.50	74S188	4.75	74S471	18.75
74S08	.50	74S195	1.95	74S472	18.75
74S37	.55	74S240	2.95	74S474	19.95
74S74	.80	74S260	1.80	74S570	7.80
74S113	.79	74S287	4.75	74S571	7.80

master charge   VISA®

JDR MICRODEVICES, INC.
1101 South Winchester Blvd.
San Jose, California 95128
800-538-5000 408-247-4852

TERMS: Include $2.00 for shipping. $10.00 minimum order. Send SASE for complete catalog. Bay Area Residents add 6½% sales tax Calif. Residents add 6% sales tax. We reserve the right to limit quantities and substitute manufacturer. Prices subject to change without notice. Foreign orders add suff. postage.

HAND HELD GAME BOARD SPECIALS

These are the complete functional circuit boards from popular hand held games — no case or batteries supplied.

Computer Perfect

Has 10 LEDS and tone signals. You try to guess correct button sequence to light LEDS in order. Requires two 9V batteries. With instructions. C24404
$4.50

Computer Mind

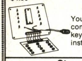

You guess the secret number stored in computer chip memory. Has 10 LEDS and keyboard. Requires one 9V battery. With instructions.
C24405 **$3.75**

Starsound Board

Unique board uses IC circuitry and gravity switch to produce space engine sounds. Point the board downwards and it produces "idle" sounds. Point upwards and the sound increases in pulsating frequency to produce "Blastoff" sounds. Originally had LED circuitry but this has been removed. Sound portion is 100% perfect. Requires 9V battery and speaker. C24406 **$2.50**

2" Speaker for above. C24311 **99¢**

120 VAC Xenon Strobe Kit

Complete variable rate strobe light kit. Contains all parts, PC board, line cord and instructions. C23071 **$7.50**

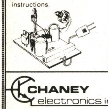

Super LED Flasher Kit

Great for Robot projects this simple to build kit uses IC circuitry to randomly flash 4 LEDS; 2 red, 1 yellow, 1 green. Complete with all parts, PC board and instructions. Size: 2" x 2". Operates on 9VDC.
C24407 **$4.98**

CHANEY electronics inc.

P.O. BOX 27038
DENVER, COLORADO 80227

Phone Orders
303-781-5750

- Minimum AD Order $6.00
- Please include $1.50 for postage
- VISA MC accepted
- Phone orders are welcome

Send for our free catalog of unique items

CIRCLE NO. 7 ON FREE INFORMATION CARD

EIGHT 16K DYNAMIC RAMS FOR $24.50

Fast/low power RAMs expand memory in TRS-80* I/II/III and Color Computers, Heath H89, Apple, newer PETs, etc. 1 year limited warranty. Add $3 for two dip shunts & conversion instructions for TRS-80* I.

*TRS-80 is a trademark of the Tandy Corporation

POWER SUPPLIES

12 VOLT 8 AMP: $44.50. With crowbar overvoltage protection, current limiting, adjustable output 11-14V, RF suppression, easy assembly. Does not include enclosure and line cord. Allow $10 for shipping; excess refunded.

1/2 AMP POWER SUPPLY: $8.00 (specify 5, 6, 8, or 12 Volt operation). Regulated, short-proof, thermally limited, 1 A intermittent operation. Less case and hardware.

BIPOLAR SUPPLY #13-XX: $15.00 (specify ±5V, ±6V, ±8V, ±9V, ±12V, or ±15V operation). Regulated, very simple assembly, virtually blow-out proof, delivers +250 mA minimum per side.

SOLDERTAIL SOCKETS

8 pin	**100/$5.95**
14, 16 & 18 pin	**50/$4.95**
20 pin	**40/$4.95**
24, 28 pin	**30/$4.95**
40 pin	**20/$4.95**

SALE PRICE! AP Products solderless breadboard kit. With 1,032 solderless plug-in tie point capacity. Was $24.95, now **$19.95**

SALE!! MA1003 12V Clock Module **$10.95,** Module plus Case **$14.80.**

TERMS: Cal res add tax. Allow 5% shipping; excess refunded. Orders under $15 add $2 handling. VISA® and Mastercard® orders ($25 min) call (415) **562-0636**, 24 hrs. Include street address for UPS. Prices subject to change without notice; limited quantity on most items.

GODBOUT ELECTRONICS
BOX 2355, OAKLAND AIRPORT, CA 94614

SEMICONDUCTOR

CMOS

4012	12/$2
4020	4/$2
4023	12/$2
4044	4/$2
4046	2/$2
4071	4/$2
4093	4/$2
4507	2/$2
4510	3/$2
4511	4/$2
4512	12/$2
5101	10/$17.50

TO-220 NEGATIVE VOLTAGE REGULATORS

7906	2/$2
7908	2/$2
7912	2/$2
79M15	2/$2
7918	2/$2
7924	2/$2

LINEARS

(package type: H = TO99, M = minidip, D = dip, TK = TO66)

301H	10/$2
308H	6/$2
703H	6/$2
723D	6/$2
741M	15/$2
1458M	10/$2
4195TK	2/$2

TTL

7403	21/$2
7410	21/$2
7413	6/$2
7428	13/$2
7438	21/$2
7444	8/$2
7450	21/$2
7472	21/$2
7493	10/$2
7496	12/$2
74122	18/$2
74151	8/$2
74155	8/$2
74159	4/$2
74161	8/$2
74163	8/$2
74164	6/$2
74190	4/$2
74192	4/$2
74194	4/$2
74195	6/$2
74198	4/$2

SPECIAL! EPROMS AT A GREAT PRICE: 2708 EPROM $3.50 EACH; 2716 EPROM $8.50 EACH. LIMITED QUANTITY.

OTHER COMPONENTS

1000 uF 35V axial capacitor	**10/$2.00**
10,000 uF 10V axial capacitor	**5/$2.00**
S-100 card edge connectors	**10/$29.50**
Resistor asst. (cut & bent leads)	**1000/$5**
2102 low power 1K static RAM	**10/$9.90**
General purpose silicon signal diodes	**50/$2**
GT5306 NPN darlington, min gain 17000, 25V 200 mA, TO92 package	**100/$8.95**
NPN transistor similar 2N3904	**100/$7.95**
PNP transistor similar 2N3906	**100/$8.95**
MCT-2/IL-1 pinout	**5/$2**
SN76477 complex sound generator	**1/$2.50**
Opto-Isolator Grab Bag - 50 mixed opto-isolators from a major manufacturer. Unmarked 6 and 8 lead minidips include single and dual types with diode, transistor, and darlington outputs. Test them yourself and save! Not recommended for beginners.	**50/$4**

send for our flyer!

CIRCLE NO. 22 ON FREE INFORMATION CARD

Quest ELECTRONICS

P.O. Box 4430C
Santa Clara, CA 95054
Will calls: 2322 Walsh Ave.
(408) 988-1640 TWX 910-338-2139

Same day shipment. First line parts only. Factory tested. Guaranteed money back. Quality IC's and other components at factory prices.

INTEGRATED CIRCUITS

74LS00 TTL	
74LS00N	.29
74LS02N	.29
74LS04N	.35
74LS05N	.25
74LS08N	.35
74LS10N	.35
74LS13N	.55
74LS14N	1.00
74LS20N	.35
74LS22N	.35
74LS28N	.35
74LS30N	.35
74LS33N	.60
74LS38N	.50
74LS74N	.45
74LS75N	.65
74LS90N	.60
74LS93N	.75
74LS95N	1.00
74LS107N	.45
74LS112N	.45
74LS113N	.45
74LS132N	.89
74LS136N	.50
74LS151N	.75
74LS155N	.79
74LS157N	1.10
74LS162N	1.10
74LS163N	1.10
74LS174N	1.15
74LS190N	1.25
74LS221N	1.25
74LS258N	1.00
74LS367N	.89

Linear CMOS and 7400 complete lines in stock. Send for catalog.

MOS/MEMORY RAM	
2101-1	3.85
2102-1	.95
2102AL-4	1.45
2102AN-2L	1.65
2104A-4	4.95
2107B-4	3.75
2111-1	3.75
2112-2	3.95
2114A-5 250ns	3.75
2114L 300ns	4.00
4116 200ns	3.75
8/4116 200ns	23.95
MM5262	.40
MM5280	3.00
MM5320	9.95
MM5330	5.94
PD411D-3	4.00
PD411D-4	5.00
P5101L	8.95
4200A	9.95
82S25	2.90
91L02A	1.50
HD0165-5	6.95
MM57100	4.50
GIAY38500-1	9.95
MCM66751A	9.95
9368	3.50
410D	10.00
416	16.00

PROM	
1702A	8.95
2708	6.10
2716T1	18.00
2716 5 Volt	10.50
8/2716 5 Volt	72.00
2732	29.50
2758	19.50
8741A	55.00
8748	55.00
8748-8	55.00
8755A	55.00
N82S23	2.95
N82S123	4.75
N82S126	4.75
N82S129	4.75
N82S131	6.50
N82S136	8.75
N82S137	8.75
DM8577	2.90
8223	3.50

INTERFACE	
8095	.65
8096	.65
8097	.65
8098	.65
8T09	1.25
8T10	4.50
8T13	3.00
8T20	5.50
8T23	3.10
8T24	3.50
8T25	3.20
8T26	1.69
8T28	2.75
8T97	1.69
8T98	1.69

MICROPROCESSOR	
6502	10.95
6504	9.95
6522	9.95
6800	6.95
6802	11.95
6820	4.95
6850	5.95
8080A	3.95
8085	12.95
8086	75.00
Z80	9.95
Z80A	11.95
8212	2.90
8214	3.95
8216	2.90
8224	3.45
8228	4.95
8251	6.95
8253	15.00
8255	5.75
8257	10.95
8259	14.95
1802CP plas.	13.95
1802DP plas.	17.95
1861P	9.50
CDP1802CD	28.95
CDP1802D	35.00
CDP1861P	7.95

RESISTORS ¼ watt 5%

10 per type	.03
25 per type	.025
100 per type	.015
1000 per type	.012
350 piece pack 5 per type	6.75

½ watt 5% per type .05

IC SOCKETS

Solder Tin PIN	1 UP	Low Profile PIN	1UP
8	.15	22	.30
14	.14	24	.35
16	.16	28	.42
18	.27	36	.58
20	.29	40	.57

2 level 14 pin ww .20

WIRE WRAP LEVEL 3

PIN		PIN	
14	.46	24	.93
16	.49	28	1.00
18	.67	40	1.23

CRYSTALS	
1 MHz	4.50
2 MHz	4.50
4 MHz	4.25
5 MHz	4.25
10 MHz	4.25
18 MHz	3.90
20 MHz	3.90
32 MHz	3.90
32768 Hz	4.00
1.8432 MHz	4.50
3.5795 MHz	1.20
2.0100 MHz	1.95
2.097152 MHz	4.50
2.4576 MHz	4.50
3.2768 MHz	4.50
5.0688 MHz	4.50
5.185 MHz	4.50
5.7143 MHz	4.50
6.5536 MHz	4.50
14.31818 MHz	4.25
18.432 MHz	4.50
22.1184 MHz	4.50

DISPLAY LEDS			
MAN1	CA	.270	2.90
MAN3	CC	.125	.39
MAN72/74	CA/CA	.300	1.00
DL704	CC	.300	1.25
DL707/DL707R	CA	.300	1.00
DL727/728	CA/CC	.500	1.90
DL747/750	CA/CC	.600	1.95
FND359	CC	.357	.70
FND500/507	CC/CA	.500	1.35
FND503/510	CC/CA	.500	.90
FND800/807	CC/CA	.800	2.20
3 digit Bubble			.60
10 digit display			1.25
7520 Clairex photocells			.39
TIL311 Hex			9.50
MAN3640	CC	.30	1.10
MAN4610	CA	.40	1.20
MAN4640	CC	.40	1.20
MAN4710	CA	.40	.95
MAN4740	CC	.40	1.20
MAN6640	CC	.56	2.95
MAN6710	CA	.60	1.35
MAN6740	CC	.60	1.35

KEYBOARDS	
56 key ASCII keyboard kit	$67.50
Fully assembled	77.50
53 key ASCII keyboard kit	60.00
Fully assembled	70.00
Enclosure Plastic	14.95
Metal Enclosure	29.95

Votrax Speech Synthesizer 64 phonemes accessed by 6 bit code. Unlimited vocabulary SC01 $95. VSM/1 Speech Module $269.

Modem Kit $60.00

State of the art, orig., answer. No tuning necessary. 103 compatible 300 baud. Inexpensive acoustic coupler plans included. Bd. only $17.00.

Z80 Microcomputer

16 bit I/O, 2 MHz clock, 2K RAM, ROM Breadboard space. Excellent for control. Bare Board **$28.50.** Full Kit **$99.00.** Monitor **$20.00.** Power Supply Kit **$35.00. Tiny Basic $30.00**

Video Modulator Kit $9.95

Convert TV set into a high quality monitor w/o affecting usage. Comp. kit w/full instruc.

Multi-volt Computer Power Supply

8v 5 amp, ±18v .5 amp, 5v 1.5 amp, −5v .5 amp, 12v .5 amp, −12v option. ±5v, ±12v are regulated. Basic Kit **$29.95.** Kit with chassis and all hardware **$43.95.** Add $4.00 shipping. Kit of hardware **$14.00.** Woodgrain case **$10.00.** $1.50 shipping.

RCA Cosmac 1802 Super Elf Computer Kit $106.95

The Quest Super Elf is the right choice for the person who has a need to learn more about computers, from an understanding of the hardware and how it goes together to beginning programming with machine language on up through basic.

Tremendous Value

The Super Elf is a tremendous value as it combines video, digital displays, LED displays, and music, all on a single board for $106.95. Its unique ability for single step debugging, display of state and mode of the computer and display of addressing as an inexpensive option gives it an "easy to use" capability not available anywhere at the price.

Inexpensive Expansion

The Super Elf expansion capability is virtually unlimited and you can do it inexpensively one step at a time. Expansion includes cassette interface, additional memory, color video, Basic, ASCII keyboard, printer, floppy, S-100 bus, RS232, etc.

Strong Software Support

The Super Elf comes complete with power supply and detailed 127 page instruction manual which includes over 40 pages of software, including a series of lessons to help get you started and a music program and graphics target game. Many schools and universities are using the Super Elf as a course of study. OEM's use it for training and R&D. A monthly newsletter, Questdata is devoted exclusively to software for the Super Elf and there are many software books available at low cost. You can do a tremendous amount with the software available and there is more coming every day. Of course, you can do your own programming which is fun and very rewarding.

Free 14 Page Brochure

Send or call for a free brochure on all details and pricing of the Super Elf and its expansion. We will get it right out to you!

60 Hz Crystal Time Base Kit $4.40

Converts digital clocks from AC line frequency to crystal time base. Outstanding accuracy.

Rockwell AIM 65 Computer

4K version **$450.00**

Ohio Scientific Computer Products

CIP Series 2 **$447.00**
with monitor/TV combo **$599.00**
CIPMF Series 2 **$1225.00**
with monitor TV/combo **$1349.00**
Superboard II $289.00

TERMS: $5.00 min. order U.S. Funds. Calif residents add 6% tax.
$10.00 min. BankAmericard and Master Charge accepted. $1.00 insurance optional.
Postage: Add 5%. C.O.D. $10.00 min. order.

FREE: Send for your copy of our NEW 1981 QUEST CATALOG. Include 48¢ stamp.

CIRCLE NO. 50 ON FREE INFORMATION CARD

THE MICROCOMPUTER MART
COMPUTER RETAIL STORES

MICROCOMPUTER MART RATE: 1" x 1 Column (1-5/8") $150. 1-1/2" x 1 Column (1-5/8") $225.00. 2" x 1 Column (1-5/8") $300.00. **GENERAL INFORMATION:** Frequency rates available. Payment must accompany copy except credit card—Am. Ex., Diners, MC, VISA (supply Expiration date)—or accredited ad agency insertions. Orders are not acknowledged. They will appear in next available issue after receipt. Closing date: 1st of the 2nd month preceding cover date (for example, April issue closes February 1st). Send order and remittance to MicroComputerMart, **POPULAR ELECTRONICS,** One Park Avenue, New York, NY 10016. Direct inquiries to (212) 725-3485.

CALIFORNIA

OHIO SCIENTIFIC
MICRO-COMPUTERS
A.A. Office
Equipment Company
2140 American Avenue
Hayward, CA 94545
(415) 782-6110

The Original
ByteShop®
1415 W. El Camino Real
Mountain View, CA 94040
(415) 969-5464

Disc/3
MART, INC.

WE SPECIALIZE IN LOW COST PRINTERS

Call Us For Quotes On Centronics, Anadex, Epson And Any Others. Try Us For The Best Prices On Diskettes, Cartridges And Accessories.

Centronics Printer 737 (Parallel).. $775.00
Anadex Printer DP-9500/9501... $1,350.00

1840 Lincoln Blvd.
Santa Monica, CA 90404
(213) 450-5911

NEW HAMPSHIRE

As advertised in 73 Amateur Radio, 80 Microcomputing & Kilobaud Microcomputing magazines

COMPUCRUISE
WITH CRUISE CONTROL
Regular list $199.95
$159.95
+ $8.00 shipping & handling
FREE CATALOG

MOM'S
MAIL ORDER MICROS
Dept. P7, 603-924-3041
P.O. Box 427, Marlboro, N.H. 03455

- Northstar
- Exidy
- OSI
- TRS-80
- Apple
- PET
- Heath
- TI 99/4
- Atari

Free Software Catalog

Instant Software Inc.
Dept. PE-1
Peterborough, NH 03458

ILLINOIS

FARNSWORTH
COMPUTER
Apple. Hewlett-Packard
I.D.S. Printers
Monthly Specials
1891 N. Farnsworth Ave.
Aurora, IL 60505. (312) 851-3888

RHODE ISLAND

WHOLESALE COMPUTER PRICES DIRECT TO THE PUBLIC!

Apple • Atari •
HP-85 • Intertec •
Soroc • TRS-80II •
NEC Spinwriter

CALL TOLL FREE
1-800-556-7586

ΩMEGA Sales Co.
12 Meeting St.
Cumberland, RI
(401) 722-1027

NEW YORK

Cromemco

Tomorrow's Computers Today!
BEST PRICING—WARRANTY SERVICE
COMPUTER CENTER
31 E. 31st St & 480 Lex. Ave
N.Y., NY 10016 N.Y., N.Y. 10167
(212) 889-8130

WISCONSIN

OHIO SCIENTIFIC SYSTEMS

We'll Beat Any Price!
We also carry
Apple Computers

Write or call for prices
TOLL FREE 1-(800) 558-4237
COMPUTERS PLUS INC.,
2749 South 108th St.
Milwaukee, WI 53227
(414) 321-1770

MASSACHUSETTS

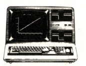

Model 111 16 K • $859
TOLL FREE
1-800-343-8124

THIS is only one of hundreds of unusual values . . .
Get your **FREE CATALOG** today!

computer plus
245A Great Road
Littleton,
MA 01460

TEXAS

TEXAS COMPUTER SYSTEMS
a **Radio Shack**
Authorized Sales Center, OFFERS
LOWEST PRICES on
TRS-80®
COMPUTERS

Call **TOLL FREE** for the **BEST PRICES** on all Radio Shack® Computers and accessories
- ★ **FREE SHIPPING** on most items.
- ★ No out of state sales tax charged.

NEW—Percom **DOUBLE DENSITY** for Model I. Twice the disk space. Easy to install, no modifications. Copies single density to **DOUBLE DENSITY** to convert existing software. Less than $200.

TOLL FREE 800-351-1473
Texas Residents 915-597-0673
TEXAS COMPUTER SYSTEMS
106 E. 10th, Brady, Tx. 76825
Radio Shack® Authorized Sales Center F701
TRS-80® is a trademark of Tandy Corp

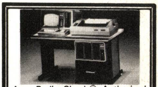

As a Radio Shack® Authorized Sales Center owned & operated by Pan American Electronics, Inc., we can sell them for less. *No taxes* collected on out-of-state shipments. *We pay* shipping & insurance.
TOLL FREE 800/531-7466
Texas & Main No.
512/581-2765
1117 Conway
Mission, Texas 78572

COMPUTER RETAILERS

Increase Your Sales Responses!!!

Your computer store ad in **THE MICROCOMPUTER MART** will enable you to reach **POPULAR ELECTRONICS'** Electronics Activist audience . . . an audience that utilizes microcomputer equipment for business AND personal purposes. For further details, call **(212) 725-3485.**

VECTOR SLIT-N-WRAP T.M.
MEETS PAR. 5.6 MIL-STD-1130A

4 TIMES FASTER WITH
NO PRECUTTING
NO PRESTRIPPING

SLIT-N-WRAP TO BE SURE
DON'T JUST WRAP AND WONDER
IF THE POST CUT THE INSULATION

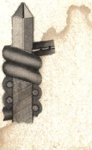
cross section on diagonal on bottom and unwrapped wire on top

Vector Electronic Company INCORPORATED
12460 Gladstone Ave., Sylmar, CA 91342

CIRCLE NO. 59 ON FREE INFORMATION CARD

Electronics Classified

CLASSIFIED RATES: Per Word, 15 Word Minimum. **COMMERCIAL:** $3.00. **EXPAND-AD®:** $4.50. **DISPLAY:** 1" x 2¼", $370.00. 2" x 2¼", $740.00. 3" x 2¼", $1,110.00. **GENERAL INFORMATION:** Frequency rates and prepayment discounts available. Payment must accompany order except credit card—Am. Ex., Diners, MC, VISA (include exp. date)—or accredited ad agency insertions. Copy subject to publisher's approval; must be typewritten or printed. First word set in caps. Advertisers using P.O. Boxes MUST supply permanent address and telephone number. Orders not acknowledged. They will appear in next available issue after receipt. Closing date: 1st of the 2nd month preceding cover date (e.g., Mar. issue closes Jan. 1). Send order & remittance to: Classified Advertising, Popular Electronics Magazine, 1 Park Avenue, New York, NY 10016. Direct inquiries to Rose Lynch (212) 725-7686.

FOR SALE

FREE! Bargain Catalog—I.C.'s, LED's, readouts, fiber optics, calculators parts & kits, semiconductors, parts. Poly Paks, Box 942PE, Lynnfield, Mass. 01940.

GOVERNMENT and industrial surplus receivers, transmitters, snooperscopes, electronic parts, Picture Catalog 25 cents. Meshna, Nahant, Mass. 01908.

ELECTRONIC PARTS, semiconductors, kits. FREE FLYER. Large catalog $1.00 deposit. BIGELOW ELECTRONICS, Bluffton, Ohio 45817.

RADIO—T.V. Tubes—49 cents each. Send for free catalog. Cornell, 4213 University, San Diego, Calif. 92105.

SAVE UP TO 50% on name brand test equipment. Free catalog and price list. Salen Electronics, Box 82, Skokie, IL 60077.

SOUND SYNTHESIZER KITS — Surf $16.95, Wind $16.95, Wind Chimes $22.95, Musical Accessories, many more. Catalog free. PAIA Electronics, Box J14359, Oklahoma City, OK 73114.

BUILD AND SAVE TELEPHONES, TELEVISION, DETECTIVE, BROADCAST Electronics. We sell construction plans with an Engineering Service. Speakerphones, Answering Machines, Carphones, Phonevision, Dialers, Color TV Converters, VTR, Games, $25 TV Camera, Electron Microscope, Special Effects Generator, Time Base Corrector, Chroma Key. Engineering Courses in Telephone, Integrated Circuits, Detective Electronics. PLUS MUCH MORE. NEW Super Hobby Catalog PLUS year's subscription to Electronic News Letter, $1.00. Don Britton Enterprises, 6200 Wilshire Blvd., Los Angeles, Calif. 90048.

UNSCRAMBLERS FOR any scanner. Several models available. Free literature. Capri Electronics, 8753T Windom, St. Louis, MO 63114.

UNSCRAMBLERS, seven models available to decode police, ambulance, and fire coded transmissions. Other scanner devices. Tone encoders/decoders. Telephone accessories, etc. Free Catalog. KRYSTAL KITS, Box 445, Bentonville, AR 72712. (501) 273-5340.

POLICE/FIRE SCANNERS, crystals, antennas, CBs, Radar Detectors. HPR, Box 19224, Denver, CO 80219.

PRINTED CIRCUIT supplies, chemicals, tools, artwork, plating solutions. Major credit cards. Catalog $2.00, refundable. CIRCOLEX, Box 198, Marcy, NY 13403.

RECONDITIONED TEST EQUIPMENT $1.00 for catalog. WALTER'S TEST EQUIPMENT, 2697 Nickel, San Pablo, CA 94806, (415) 758-1050.

Buy Gov't Surplus SAVE To 85%.

Send 60¢ For Big Bargain Catalog

1000's Of Bargains; Surplus, Excess Inventory, Brand Name New Equipment

COMPRESSORS • WINCHES • GEAR MOTORS
TELEPHONES • WELDERS • POWER PLANTS
SURVEYING INSTRUMENTS • ELECTRONICS
FIRE/BURGLAR ALARMS • PAINT GUNS
TARPS • BINOCULARS • TOOL BOXES
HYDRAULICS • AIR TOOLS • PUMPS

SURPLUS CENTER Box 82209-PE Lincoln, Nebraska Zip Code 68501

NEW ELECTRONIC PARTS. Continuously stocked. Stamp brings catalog. Daytapro Electronics, 3029 N. Wilshire Ln., Arlington Hts., IL 60004.

ELECTRONIC CATALOG. Over 4,500 items. Parts, & components. Everything needed by the hobbyist or technician. $2.00 (U.S. funds) $4.00 Foreign Postage & handling, refundable with first $15.00 order. T & M Electronics, 472 East Main St., Patchogue, NY 11772. (516) 289-2520.

SPEAKERS SAVE 50%. Build your own speaker system. Write: McGee Radio Electronics, 1901 McGee Street, Kansas City, Missouri 64108.

PRINTED CIRCUIT BOARDS, your artwork. Quick delivery. Reasonable. Atlas Circuits, Box 974, Waynesville, NC 28786. (704) 456-3739.

HAMS, CBERS, SWLS, ELECTRONICS BUFFS! Parts, kits and plans now available for Popular Electronics projects. MORSE-A-WORD: Circuit boards $24.00; Essential parts kit $99.95; Complete four character kit $149.95; Eight character kit $169.95; Wired $249.95. RTTY READER: Boards $24.00; Complete kit $169.95; Wired $249.95. S&H $5.00 kits; $1.50 boards. Use VISA/Mastercard. (414) 241-8144. Write for catalog. MICROCRAFT, POB 513PE, Thiensville, WI 53092.

CABLE TV DESCRAMBLERS AND CONVERTERS. MICROWAVE ANTENNAS AND DOWN CONVERTERS. Plans and parts. Build or buy. For information send $2.00. C&D Company, P.O. Box 21, Jenison, MI 49428.

FIBER OPTIC SPECIALS—100 foot spool of fiber $3.00—Experimenter's kit $6.00—High Power LED with matched Detector $10.00—Data Link construction plans (detailed) $5.00. Catalog with samples $1.00. FIBERTRONICS, Box 322-A, Primos, PA 19018.

SCRAMBLED TELEVISION—Encoding/Decoding. New publication. Complete theory, circuits. $9.95. Workshop, Box 393PEH, Bethpage, NY 11714.

Telephone Listening Device

Record telephone conversations in your office or home. Connects between any cassette or tape recorder and your telephone or telephone LINE. Starts automatically when phone is answered. Records both sides of phone conversation. Stops recorder when phone is hung up. This device is not an answering service.

Each $18.95

Qty Disc Avail

Super Powerful

Wireless Mic

10 times more powerful than other mics. Transmits up to ¼ mile to any FM radio. Easy to assemble kit. 15V battery (not incl.)

Call (305) 725-1000 or send $18.95 + $1.00 shipping per item to USI Corp., P.O. Box PE-2052, Melbourne, FL 32901. COD's accept. For catalog of transmitters, voice scramblers and other specialty items, enclose $2.00 to USI Corp.

CHEMICALS, Apparatus, Project Books, Wide Selection. Catalog send $1.00 to Pioneer Corp., 14a Hughey Street, Nashua, NH 03060.

TEST EQUIPMENT, new and used. Catalog $1.00. PTI, Box 8756; White Bear Lake, MN 55110.

QUALITY AUDIO COMPONENTS, Multi-Track Equipment, Programmable Calculators, Accessories. Competitive Pricing! Prompt Delivery! Knowledgeable staff! Service Facility! Credit Cards accepted. FREE catalog. SOUND IDEAS, Dept. SR, PO Box 340, Cary, N.C. 27511. 1-800-334-2483 (N.C. 919-467-8462).

SATELLITE TELEVISION INFORMATION—Build or buy your own Earth Station. U.S.$4.00 Satellite Television, RD 3, Oxford, NY 13830.

UNSCRAMBLE CODED MESSAGES from police, fire and medical channels. Also telephone recording adaptor. Same day service. Satisfaction guaranteed. Don Nobles Electronics, Inc. Rt. 7, Box 610-A, Hot Springs, AR 71901. (501) 623-6027.

DECODER KIT, TV UHF CHANNELS. Sine Wave Decoder System. Model 7 + 11 SWD, complete kit $139.00, plus 5% for shipping and handling. Also parts etc. Catalog $1.00. Visa, Master Charge acceptable. Simple Simon Electronic Kits, 11852 S. Hawthorne Blvd., Hawthorne, California 90250. TEL: (213) 675-2335.

PCB as low as 15¢ sq-in. FREE DRILLING. International Enterprise, 6452 Hazel Circle, Simi Valley, CA 93065.

SUBSCRIPTION TELEVISION EDUCATION MANUAL! Two scrambling decoding systems, theory, circuits. Decoder dealers listed. $14.95. Kits available. Satisfaction guaranteed. ABEX, P.O. Box 26601-P4, San Francisco, CA 94126.

TELEVISION DOWNCONVERTERS and decoders $99.95 up. Details for Stamp. GW Electronics, POB 688, Greenwood, IN 46142.

POLICE SCANNERS AT WHOLESALE PRICES. VISA/MC Phone orders accepted. (415) 573-1624. Free catalog write: Scanners Unlimited, 1199A Laurel Street, San Carlos, CA 94070.

SUBSCRIPTION TV. 2300MHz Microwave Antenna Plans. Fully Guaranteed. $9.95. DynaComp Electronics, Dept. GF-4, P.O.B. 4181, Scottsdale, AZ 85258.

TUBES, IC'S, ni-cads, FiresTick antennas, multimeters, amateur-short wave receivers, scanners, radar, and metal detectors, A+E. C.O.D.'s 1-800-531-5405.

TOP QUALITY SPEAKERS AND KITS. Send $2.00. Speaker Warehouse, 809 North Route 441, Hollywood, FL 33021.

ROBOT DESIGN BREAKTHROUGH, Easily Built, Untrappable, Controlled with 4 Bit Input, Microprocessor Adaptable, Complete Plans with 24x36 Blueprint $6.95. FREE INFORMATION. Zamis Engineering, 251 First Street PE, Perrysburg, Ohio 43551.

RF POWER TRANSISTORS - TUBES SPECIAL PARTS for "HAM" linears. MRF454 $17.00, MRF455A $14.00, 8950 $9.00, 6LF6 $5.50, Catalog and cross-reference help available. C.O.D., VISA/MC Accepted. WESTCOM, 1320 Grand, San Marcos, CA 92069. (714) 744-0728.

RADIOTELETYPE WORLD PRESS stations list. Over 50 news services transmitting 24 hours in English worldwide. Much news confidential. Hundreds of frequencies and times. Simple Equipment. How to set up, sources. Book including three lists, $5.00 postpaid. UNIVERSAL ELECTRONICS, 1280 Aida Drive, Reynoldsburg, Ohio 43068.

SCRAMBLED TELEVISION TUNERS: Wideband UHF tuner, covers most of UHF to VHF channels. $24.95 plus $1.50 postage. Money order only. Quest Electronics, Box 1722, Costa Mesa, CA 92627.

AMATEUR SCIENTISTS, Electronics Experimenters . . . Construction plans - drawings, schematics, parts lists. Over 60 items. Catalog - $1.00. Technical Writers Group, Box 5994, University Station, Raleigh, NC 27650.

SHORTWAVE LISTENERS! Free catalog. High quality SWL equipment! Radio West, 2015 S. Escondido Blvd., Escondido, CA 92025. (714) 741-2891. The Only all SWL store in the Known World.

FREE TV DECODER PLANS — Send self addressed stamped envelope for free plans, parts list and price list to SCR Electronics, Inc., 9533 Valley View, Cypress, CA 90630.

TO RECEIVE FREE UNINTERRUPTED movies, Sports shows. Send $199.95 for complete ready to install AMATEUR MICROWAVE SUBSCRIPTION T.V. ANTENNA, or $9.95 for complete plans, fully guaranteed and refundable against purchase of Antenna. Phillps-Tech Electronics, Dept Sp-12, 5025 North 68th Street, Scottsdale, Arizona 85253.

PAY-TV UNSCRAMBLER plans $10.95, Board $12.95 plus $1.50 postage. Demex, 6221 Apache, Westminster, CA 92683.

MICROWAVE ANTENNAS. High quality commercial units available. Also complete plans and instructions for Amateur Microwave Antennas, Satellite T.V. and Radar Detectors. Write for information. MICROTRONICS, Box 32357, Washington, D.C. 20007.

VERY HIGH-FIDELITY, 30 watt, power-amp. Distortion way below audibility. $29.00 per channel, w/heat-sink. You supply power, etc. Send $1.00 for full line of multi-amp modules and accessory information; Bulletin Audio, P.O. Box 25781, Salt Lake City, Utah 84125.

ELECTRIC CAR CONVERSIONS. Drawings, pictures, and prices $2.00 to: Conversions, 2103-P Leeway, Roseville, CA 95678.

HOME STUDY COURSES bought-sold. $2.00 to add yours to list. List $6. EXCHANGE, Box 218, River Edge, NJ 07621.

PSYCHEDELIC LIGHT DRIVER. Converts music into flashing colors. EASY and INEXPENSIVE. Complete plans $2.00. Converters, P.O. Box 559, Foxboro, MASS. 02035.

VIDEO CATALOG - complete selection, recorders, cameras, accessories, electronic items, cabinets. Send $2.00 - refundable first order to: VIDEO MERCHANT, P.O. Box 5381, Dept. 103, Akron, Ohio 44313.

LOWEST PRICES ELECTRONIC PARTS, confidential catalog free. KNAPP, 4750 96th St. N., St. Petersburg, FL 33708.

SAVE - Thousands of unused capacitors - eg. 250 uf, 150 VDC, only 50¢. Weingart, Inc., Fort Wayne, Indiana 46818.

SPEAKERS! SPEAKERS! AM/FM CASSETTE RADIOS 4"x10", 5¼" Round 20oz, 25 watts coaxial speaker $27.95 pair, 6"x9" Triaxial 20oz, 30 watt speaker system, $32.88. Two pair fourway speaker system (8 total speakers!) 40oz Ceramic Magnetic circuit 30 watts, mounted in 6½"x10" Grills $44.95 pair. GOOD FOR HOME OR CAR! Coaxial speaker system in cast aluminum case (5w"x7½h"x4d") 50 watts $54.95 pair, Triaxial speakers in cast aluminum (Triangle enclosure 7w"x7d"x5h") $69.95 pair. AM/FM cassette in dash radio $54.95. INQUIRIES WELCOME. Send check or money order to: DIRECT WHOLESALE INC., 122 East 42nd Street, Suite 3303, N.Y., NY 10017. Please add $3.50 for shipping and handling. N.Y. State residents add Sales Tax.

SUPACLARIFIER SSB reception with AM CB's. Simple detailed instructions and parts list. Send $5.00 to: POBCO, Box 251, Azusa, CA 91702.

MICROWAVE TV downconverter, prebuilt $140.00. Specify output channel. Complete system. $294.95. Free information. TEM MICROWAVE, 22518 97th Ave. No., Corcoran, MN 55374. 612-498-8014.

"FONO-NET"® Accurate-quick test of phonograph amplifiers with any Audio Generator. Individually calibrated. Guaranteed. $29.95 postage paid. QUANTITY DISCOUNTS. R.C. Davidson Inc., 3005 Bagley Avenue, Los Angeles, CA 90034.

ELECTRONIC TELEPHONE RINGER replaces harsh bells with electronic tone at half ringer equivalency! Installs easily, $14.50. CONSUMERS' TELEPHONE, 69-C Smith St., Glen Head, NY 11545.

DIGITAL REVERB September 80 issue PE. PCB $18. Critical IC's $23. Memory set $50. SASE for reprint. Videoart, Box 10327, Stanford, CA 94305.

PICK UP SATELLITE TV BROADCASTS at home. Receiver under $1500. Complete system under $5000. Dealer inquiries welcome. CYM ASSOCIATES INC., Dept. P, 160 Tobin Rd., Henrietta, New York 14467. 716/482-5769.

PICTURE TUBE REBUILDING equipment new and used. ATOLL TELEVISION, 6425 Irving Park, Chicago, Illinois 60634.

SATELLITE PARABOLIC ANTENNA, including polar mount. Fiberglass and steel construction f/d-.45, 10'-39db - $1000.00. 12'-41db - $1100.00. Satronics Communications, P.O. Box 2924 St. A, Champaign, IL 61820. (217) 398-2873.

RESISTORS ½W, ¼W5% C.F. 3¢ea. NO MINIMUMS 1% Metalfilms. Send for details. Bulk pricing available. JR Industries, 5835-A Swancreek, Toledo, Ohio 43614.

ELECTRIC CAR PARTS. Catalog contains parts, plans, instructions. Send $3.00 to: Electric Vehicle Components Catalog, Flight Systems, Dept. EV8, Box 25, Mechanicsburg, PA 17055.

DOES YOUR PHONE RING WHEN YOU'RE NOT HOME? I have the answer. Send 50¢ to: KMR, Box 5262, Norman, OK 73070.

SATELLITE EARTH STATION - Build your own antenna for less than $200.00 with materials you can buy local. Complete instructions plus material list. Any handyman can do it. Send today $7.95 to: YOUNG SATELLITE SYSTEM, P.O. Box 79089, Fort Worth, TX 76179.

TV BAND MICROWAVE ANTENNAS

Factory Direct Fully Assembled

- *Many Uses*
- *10 Day Trial*
- *Usable Indoors*
- *Perfectly legal*

FROM $169⁰⁰

"Down Converts" microwave signals to VHF television band. Commercial rod or parabolic dish type.
NOTE: Many versions of our product are available. Let the buyer beware. We fully guarantee ours in writing. We want your recommendation. Weekdays 9-4:30. Sat. 10-2 PAC. STD. TIME.

CALL FOR FREE INFORMATION PACKET 1-800-634-6062

ATARI SPACE INVADERS is MORE FUN with the RAPID FIRE Variation. Doesn't LIMIT YOU to FIRING ONLY LASER each time. APPLIES INSTANTLY!! NO MODIFICATION TO YOUR COMPONENTS! NOW SPECIALLY PRICED! $5.98 COMPLETE. BALIS, Box 522, Brooklyn, NY 11215.

ETCHING SOLUTION Ammonium persulphate. $2.85/lb. A pound makes two gallons. P/H $.75 per pound. EV Electronics, Box 247, Perryville, MO 63775.

Satellite TV

FOR THE HOME

Sick of Network TV?

Our receiver lets you get over 75 channels of television directly from earth-orbiting cable TV satellites!: HBO, Showtime, super stations, sports and movies worldwide.

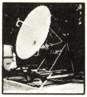

We don't just sell information! We Manufacture Hardware!

From offshore oil rigs, data links to hotels and backyard installations, we wrote the book. Constantly updated, our **94 Page** technical information book and catalog gives you all the facts. Inexpensive dishes, feeds, telemetry software, kits and more. Recommended reading by NASA, The Office of Consumer Affairs and quality companies like Rockwell/Collins. Send $7.95 today!

CALL
24-hrs. C.O.D. Hotline
(305) 339-7600

© *SPACECOAST*™
RESEARCH CORPORATION
P.O. Box 442-A, Altamonte Spgs, FL 32701

SATELLITE VISION
SATELLITE VISION
SATELLITE VISION

We manufacture the highest spec 3-meter data & video dish in the world 41db gain! We also sell direct. Immediate delivery or you pick up. Complete details including satellite TV information, aiming service and discount schedule. Send $1.25 for postage & handling to:

TIGER TENNAS
P. O. Box 561
Casselberry, Florida 32707

BUY DIRECT

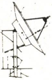

COMPUTER EQUIPMENT

SURPLUS COMPUTER PERIPHERALS: "Selectric" I/O typewriter bargains. World's largest selection. Send 25¢ for bargain-packed flyer. CFR, Box 144, Newton, NH 03858.

LEARN MICROCOMPUTERS on your own computer. Send $5.00 for 2 complete instruction manuals. Paccom, 14905 NE 40th, Dept. MPE021, Redmond, WA 98052.

WANTED — Sell your unwanted computer through us. Big savings for buyers in pre-owned equipment. Buyers/sellers — Send SASE or 25¢ for details, Autocomp, Box 246, Glenham, NY 12527.

RF MODULATORS! Special versions for SATELLITE TELEVISION, COMPUTERS, CCTV. Also Monitors, Cameras, Kits. FREE catalog. Phone (402) 987-3771. Dealers welcomed. ATV RESEARCH, 13-P Broadway, Dakota City, NE 68731.

INTERACT COMPUTERS — Software, service. Best prices. Send for catalog: MICRO VIDEO, Box 7357, Ann Arbor, Michigan 48107.

COMPUTERISTS AND COMPUTER CLUBS! Why pay full price for software? We have it all for most any system and will not be undersold! Guaranteed! Write for free listings. Pacific Discount Software, 3205 Production Circle, Oceanside, Cal. 92054. 714-439-6201.

FREE COMPUTER SUPPLIES CATALOG - 1600 field-proven products compatible with any mini or microcomputer. Tapes, disks, floppies, cartridges, cables, furniture, ribbons, more. Order by mail, phone, 24 hour shipment. Inmac, 2465 Augustine Drive, Dept. 200, Santa Clara, Cal. 95051. Call Sandy (408) 727-1970.

SOFTWARE FOR SMALL SYSTEMS. TRS-80, CPM, Northstar. This month's special: ALL OSBORNE CBASIC BUSINESS PROGRAMS on CPM disk . . . $100. Send system info for catalog. SOFTWARE REVIEW, 704 Solano Ave., Albany, California 94706. (415) 527-7730.

8 SOCKET AC POWER STRIP. Eliminate interaction between microcomputers, floppies, printers, memory caused by power line coupling. Varistors eliminate power line spikes that may cause memory loss, errors. Hash filters on each of 3 pairs. Lighted switch, fuse, 3 wire cord, 1875 watts total. Model MFJ-1107. Call or write for more information. To order call toll-free 800-647-1800. Charge VISA, MC or mail check, money order for $69.95 plus $4.00 shipping. MFJ Enterprises Inc., Drawer AJ, Mississippi State, MS 39762.

SAVE 90% Build Your own Minicomputer. Free Details. Digatek, 2723 West Butler Dr., Suite 20C, Phoenix, AZ 85021.

TRS-80 COLOR COMPUTER GAMES. 3 Games on 1 Cassette. Will run on 4 K Machines. (Z-WAR8) (KOLLECT) and (REMEMBER). Send $9.95 check/M.O.: Musiputer Co., P.O.B 9721-PE, Knoxville, Tenn. 37920.

USED COMPUTER TERMINALS, Printers, Modems, Surplus Electronic parts. Catalog $1.00, RONDURE COMPANY, THE COMPUTER ROOM, 2522 Butler St., Dallas, TX 75235. (214) 630-4621.

COMPUTER/DISK drive surplus and recycler electronics. Free catalogue. R.C.M.I., Box 533, Lafayette, Colorado 80026.

ATARI® GAME OWNERS

You already own a powerful hobby computer!

Realize its capabilities by plugging our MagiCard module into your unaltered Video Computer System T.M. console. Using our instruction manual, obtain direct control of your ATARI game's features through 6502 machine language programs and your keyboard controlers. Send check or money order for $49.88 (in Illinois, add 6% tax) to **Computer Magic, Inc., Box 3383, Fox Valley Center, Aurora, Illinois 60505.**

ATARI and Video Computer System are trademarks of ATARI Inc.

AMATEUR RADIO

MADISON DEEP HAM DISCOUNTS. Kenwood, Yaesu, Icom, Drake, Accessories—Stock. FREE flyer, Madison Electronics, 1508-P McKinney, Houston, TX 77010. (713) 658-0268.

RADIO AMATEUR CALLBOOKS 1981 Directories of Radio Amateurs around the world. U.S. Callbook $20.50; Foreign Callbook $19.50, shipping included. See your dealer or write for FREE catalog. Radio Amateurs Callbook, Dept. PE, 925 Sherwood Dr., Lake Bluff, IL 60044.

PLAY YOUR TAPES, records, T.V. on any F.M. radio in your house - wireless - simple hook-up. Satisfaction guaranteed, $24.95. Port-o-Sound Co., Box 279A, Howard Beach, NY 11414.

HAM REPEATER AUTOPATCH Speech proof Decoder. $498.00. Write for information: Monroe Electronics, Inc., 450 Housel, Lyndonville, NY 14098. (716) 765-2254.

C.B. EQUIPMENT

GET MORE CB CHANNELS AND RANGE! Frequency Expanders, boosters, speech processors, how-to-books, plans, modifications. Catalog $2. CB CITY, Box 31500PE, Phoenix, AZ 85046.

PALOMAR - PRIDE - ATLAS: Exclusive Repair Facility. Factory trained technicians, all work guaranteed. Palomar Electronics Repair Service, 1320 Grand, San Marcos, Cal 92069. (714) 744-0720.

CABLE TV

500 PHILIPS 32 CHANNEL CABLE TV converters and VCR programmers. $17,800 prepaid to your door. Sample $48. Birnbom, 3655 Ridgewood, Suite 103, Montreal, Canada H3V 1B4. (phone 514-739-0614). (U.S. inquiries).

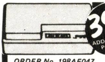

39⁹⁵ ADD $2.50 FOR POSTAGE

30 CHANNEL CABLE TV CONVERTER

ORDER No. 198AE047

ETCO ROUTE 9N,
PLATTSBURGH, N.Y. 12901
Tel.: (518) 561-8700.

FREE! UNUSUAL 96 PAGE ELECTRONIC PARTS & IDEAS CATALOG!

PLANS AND KITS

PRINTED CIRCUIT Boards from sketch or artwork. Kit projects. Free details. DANOCINTHS Inc., Dept. PE, Box 261, Westland, MI 48185.

LASERS HANDBOOK with burning, cutting, Ruby Reds, CO's complete plans, books, and parts. Send $4.00 to: Famco, Dept. PE, Box 1902, Rochester, NH 03867.

GIANT SCREEN TV projection system converts any television into 7-foot picture. Lens & instructions $14.95. (Dealers welcome). Bell Video, 4616 Belair Rd., Baltimore, MD 21206.

BUILD AN ORCHESTRA THE WERSI WAY

Preview the world's most advanced Do-It-Yourself Organs, Pianos, Synthesizers, Amps, etc. Send $6.00 for our famous "Sight & Sound" pack. WERSI Electronics, Inc., Dept. M2, P.O. Box 5318, 1720 Hempstead Rd., Lancaster, PA 17601.

DIGITAL AND SOUND EFFECTS PROJECTS. Send stamp for information. Waveform, 7 Bradford Ave., Pittsburgh, PA 15205.

IN-GROUND SWIMMING POOL KIT — Blue-prints — Vinyl Liner — Side-Walls — Skimmer — Filer — Pump — All materials Necessary for Construction — Except Local Materials — 16'x32' $1,995.00-FOB. Cheswick Pool Sales Inc., Rte. 28, Cheswick, PA 15024. (412) 274-6400. Call Collect.

UNIQUE TV DECODER plugs between UHF and VHF tuners on tube or solid-state sets. Plans $3.95; DECODER ANTENNA receives multi-polarized signals. Plans $3.95; Antenna Kit $19.95. Helico, P.O. Box 304, Bridgewater, MA 02324.

SUBSCRIPTION TV DECODER KIT. Includes parts, manual, and Etched Board. $39.00. Manual only $4.60. Catalog $2.00. JOE, P.O. Box 61, Cumberland, RI 02864.

ELECTRONICS WORKBENCH. 34 x 48 worktop, equipment risers, easily built. Hobbiest's must: Complete plans $2.00. Masterplans set 31-01, P.O. Box 24295, Columbus, Ohio 43224.

PLANS - Monophonic Organ Synthesizer $9.50. Kits available upon request. For information, SASE Mad 13, P.O. Box 6742, Concord, California 94524.

ROBOTIC CATALOG-MOTORS, gears, hardware, electronics, $3.00. Newsletter, $8.00/yr. MOUDY ELECTRONICS, R.D.2, Box 427, Hollidaysburg, PA 16648.

BUILD YOUR OWN SPEAKERS. Save 50%. Designs inlcude miniatures, subwoofers, satellites, multi-amp and State of The Art ultra speakers. Plans, parts, crossovers and kits available. No compromises - These are well engineered designs. High quality drivers and components. Write for free catalog. YE OLDE SOUNDE BOX, Box 75, Webster City, IA 50595.

SUBSCRIPTION TELEVISION DECODER: Best design available; no internal connections to television! Complete plans, $10.00. Negative Ion Generator, Telephone Memory Dialer, plans $4.00 each. PARTS AND KITS AVAILABLE! For info send SASE. COLLINS ELECTRONICS, Box 6424, San Bernardino, CA 92412.

TESLA COILS. 50,000V - 5,000,000V, 520W - 3,000KW, Arcs - 100". Illustrated Constructed Manual includes: 5 Powerful Coil Plans (Tube, Sparkgap), High-Voltage, High-Frequency Experiments, Design Theory, Ball Lightning . . . Manual $15.00. Information/Photo $2.00. B&L Scientific, 215 W. First St., Suite 105-47C, Tustin, CA 92680.

FM STEREO TRANSMITTER Module. Tunes FM band. Audiophile Specifications. Applications: Broadcasting, MPX alignments. Complete kit, $59.95. Stellatron, 4942 Whitsett — 205, N. Hollywood, CA 91607.

ALARMS

Burglar • Fire Protection

Protect Your Life, Home, Business, Auto, etc.

• Our catalog shows how. Install your own alarm systems and devices and save $$$$. We offer FREE write-in engineering service.

FREE CATALOG Lowest Prices on Reliable, High-Quality Alarm Systems and Devices

Burdex Security Co. Box 82802-PE Lincoln, Ne. 68501

BURGLAR, FIRE, CAR! Finest equipment! Save! Free Catalog. Refundable! AAS, 186A Oxmoor Road, B'ham, AL 35209.

WANTED

GOLD, Silver, Platinum, Mercury, Tantalum wanted. Highest prices paid by refinery. Ores assayed. Free circular. Mercury Terminal, Norwood, MA 02062.

TUBES

RADIO & T.V. Tubes — 49 cents each. Send for free Catalog. Cornell, 4213 University, San Diego, Calif. 92105.

TUBES: "Oldies", Latest. Supplies, components, schematics. Catalog Free (stamp appreciated). Steinmetz, 7519-PE Maplewood, Hammond, Ind. 46324.

TUBES-RECEIVING, Industrial and Semiconductors Factory Boxed. Free price sheet including TV, Radio and audio parts list. Transleteronic, Inc., 1365 39th St., Brooklyn, New York 11218. Telephone: (212) 633-2800. Toll free: 800-221-5802.

HUGE INVENTORY! Thousands of types. Wholesale prices. FREE CATALOG! ETCO Electronics, DEPT. 290, Plattsburgh, NY 12901.

TUBES-TUBES-TUBES: Radio-TV-Industrial. Antique & Obsolete tubes our specialty. Send $1.00 for comprehensive listing. Vacume Tubes, P.O. Box 13271, Tucson, Arizona 85732. (602) 299-5730.

HIGH FIDELITY

DIAMOND NEEDLES and Stereo Cartridges at Discount prices for Shure, Pickering, Stanton, Empire, Grado, Audio Technica, Osawa, Satin and ADC. Send for free catalog. LYLE CARTRIDGES, Dept. P, Box 69, Kensington Station, Brooklyn, New York 11218. Toll Free 800-221-0906 9AM - 8PM except Sunday.

A SINGER'S DREAM!

REMOVES VOCAL FROM MOST STEREO DISCS

The Thompson Vocal Eliminator can actually remove most or virtually all of a solo vocalist from a standard stereo record and yet leave most of the background music untouched! Not an equalizer! We can prove it works over the phone. Write for a brochure and demo record below. COST: $249.00

YOU SHOULD SEE US

For:

- Time Delay/Ambience
- Studio Echo/Reverb
- Tape Noise Reduction
- Parametric Equalization
- Electronic Crossovers
- Compressor/Expanders
- Mic Preamp/Mixers

We manufacture a full line of high quality audio and recording equipment. You will probably have to pay twice as much elsewhere to obtain comparable quality. Only Direct Sales make our prices and quality possible. Send $1 for a 20 page brochure and 20 minute demonstration record.

Write to: **LT Sound,** Dept. PE, P.O. Box 338, Stone Mountain, GA 30086, Phone (404) 493-1258

GOVERNMENT SURPLUS

MANUALS for Govt Surplus radios, test sets, scopes. List $1.00 (cash). Books, 7218 Roanne Drive, Washington, D.C. 20021.

JEEPS — $19.30!! — CARS — $13.50!! — 650,000 ITEMS!! — GOVERNMENT SURPLUS!! — Most COMPREHENSIVE DIRECTORY AVAILABLE tells how, where to buy!! — YOUR AREA — $2. — MONEYBACK GUARANTEE!! — "Government Information Services", Department GE-86, Box 99249, San Francisco, California 94109.

PERSONALS

MAKE FRIENDS WORLDWIDE through international correspondence, illustrated brochure free. Hermes-Verlag, Box 110660/Z, D-1000 Berlin 11, W. Germany.

PENFRIENDS — ENGLAND — USA, through correspondence. Send age, interests. Free reply. Harmony, Box 89PE, Brooklyn, New York, 11235.

CORRESPONDENCE FOR FRIENDSHIP IN PHILIPPINES, MALAYSIA. Free information. AACC-(PE), Box 1542, Canoga Park, Calif. 91304.

INSTRUCTION

UNIVERSITY DEGREES BY MAIL! Bachelors, Masters, Ph.D.'s. Free revealing details. Counseling, Box 317-PE06, Tustin, California 92680.

LEARN WHILE ASLEEP! HYPNOTIZE! Astonishing details, strange catalog free! Autosuggestion, Box 24-ZD, Olympia, Washington 98507.

LEARN ELECTRONIC ORGAN SERVICING at home. Completely revised course covers latest models including digital, LSI's, synthesizers, etc. NILES BRYANT SCHOOL, PO Box 20153, Sacramento, CA 95820.

PASS FCC EXAMS

The Original FCC Tests-Answers exam manual that prepares you at home for FCC First and Second Class Radiotelephone licenses. Newly revised multiple choice exams cover all areas tested on the actual FCC exam. Plus "Self-Study Ability Test". Proven! $12.95 postpaid. (Add $2.00 for first class Air Mail.) Moneyback Guarantee.

COMMAND PRODUCTIONS
Radio Engineering Division
P.O. Box 26348-P
San Francisco, CA 94126

TESTS-ANSWERS FOR FCC FIRST AND SECOND CLASS COMMERCIAL LICENSE

MEDICAL ELECTRONICS TECHNOLOGY, home study. Troubleshoot medical instruments. MDC, P.O. Box 124, Pinedale, CA 93650.

LEARN TELEVISION-Complete theory in really simple language. Many illustrations and complete transmitter & receiver circuits. $6.50 post paid in USA. Aptron Laboratories, P.O. Box 323, Bloomington, IN 47402.

COLLEGE DEGREES BY SPECIAL EVALUATION of EXISTING Credentials & Job Experience. Fast, Inexpensive, (614) 863-1791. Guidance, Box 13151-A6, Columbus, Ohio 43213. Be Specific.

YOU CAN NOW EARN A Bachelor, Master, or Doctoral Degree without leaving home. Courses are under faculty guidance. Kensington University, (P.O. Box 2036-M), 512 E. Wilson, Glendale, CA 91209.

ATTENTION
ELECTRONIC TECHNICIANS

Highly Effective Home Study BSEE Degree Program for Experienced Electronic Technicians Our New Advanced Placement Program grants Credit for previous Schooling & Professional Experience. Advance Rapidly! Our 36th Year!

FREE DESCRIPTIVE LITERATURE!

Cook's Institute of Electronics Engineering
DESK 15 , P.O. BOX 20345, JACKSON, MS 39209

COMPUTER PROGRAMMING COURSES taught in private colleges throughout the U.S. Excellent jobs for graduates. Write Computer Careers, P.O. Box 302B, Rapid City, SD 57709.

TECHNICAL REPORTS: Keep pace with technology. Stay current beyond immediate job requirements. Engineers, Technicians, Computer Science Personnel. Free Brochure. ADVANCED TECHNOLOGY EDUCATIONAL SYSTEMS, 4615 North Park Avenue, Suite 1519, Chevy Chase, Maryland 20015.

SPEAKERS in any room. No wiring. Up to 100 watts. For information send $3.95 to D to R Enterprises, 323 N. Brockway, Palatine, IL 60067.

FOR INVENTORS

PATENT AND DEVELOP your invention. Registered Patent Agent and Licensed Professional Engineer, Send for FREE PATENT INFORMATION every inventor should have. Richard L. Miller, P.E., 3612 Woolworth Building, New York, NY 10007. (212) 267-5252.

MANUFACTURER SEEKING Patented, Unpatented Inventions. Generous royalties. Advantek International, 1100 17th NW, Washington, DC 20036.

INVENTORS Patent your invention. Free initial consultation. We are registered by the U.S. Government. VICTOR J. EVANS & CO., 4637 Eastern Ave., N.E., Washington, DC 20018. Since 1898.

INVENTIONS WANTED

FREE CONSULTATION ● NO IDEA TOO SMALL

Disclosure registration. Potential cash or royalties from manufacturers seeking new ideas. For free information on how to register your ideas. Call or write.

AMERICAN INVENTORS CORP.
59 Interstate Dr. Dept PE
West Springfield, MA 01089 (413) 737-5376
A Fee Based Service Company

BUSINESS OPPORTUNITIES

FREE CATALOGS. Repair air conditioning, refrigeration. Tools, supplies, full instructions. Doolin, 2016 Canton, Dallas, Texas 75201.

MECHANICALLY INCLINED individuals desiring ownership of Small Electronics Manufacturing Business — without investment. Write: BUSINESSES, 92-K6 Brighton 11th, Brooklyn, New York 11235.

MECHANICALLY INCLINED INDIVIDUALS

Assemble electronic devices in your home. Knowledge, or experience not necessary. Get started in spare time. Above average profits. $300 - $600/Wk possible. Sales handled by others. No investment — Write for free details.

ELECTRONIC DEVELOPMENT LAB
Box 1560PE, Pinellas Park, FL 33565

ERASE DEBTS with little-known law — create wealth!! Details FREE — Blueprints, No. EE6, LaGrangeville, NY 12540.

BORROW $25,000 "OVERNIGHT." Any purpose. Keep indefinitely! Free Report! Success Research, Box 29070-GF, Indianapolis, IN 46229.

FREE BOOK "2042 Unique Proven Enterprises." Fabulous "unknowns," second inflation income. Haylings-M. Carlsbad, CA 92008.

ATTENTION—T.V. MEN/related fields! HI-PROFIT/LUCRATIVE. YOU can rebuild CRT's for $3 to $10 when you own our patented equipment. Lakeside, 4071 Elston, Chicago, IL 60618. (312) 583-6565.

NEW TAX LOOPHOLES DISCOVERED. Everyone Eligible. Free sample newsletter. Write ULC, Box 179-BA, Clarkston, GA 30021.

BIG MONEY IN BUSINESS PRINTING! 25% COMMISSION PLUS BIGGEST CASH BONUS! Build your own profitable year around business. Show tremendous line of salesbooks, register forms, unit sets, letterheads, envelopes, invoices, statements, business cards and dozens of other printed products. Lowest prices in industry. Something for every business and professional person. Free sales kit includes ad specialties, calendars, signs and ad matches. No experience needed. Our catalogs are easy to understand. We're over 50 but still young and aggressive, so we can show you the road to a very profitable full or part time career. Free sales kit. National Press, Dept. 154, North Chicago, IL 60064.

BORROW $30,000 without interest! All eligible. Repay anytime. Free details. Infohouse, Box 1004, PE6, New York, NY 10003.

WANT YOUR OWN RADIO STATION? Investment/experience unnecessary. Free information. "Broadcasting", Box 130-A6, Paradise, CA 95969.

INTERNATIONAL BUSINESS OPPORTUNITY. Profits worldwide, your own business from home, without capital, experience. Details FREE! Resource Corporation, Box 4667PE, Philadelphia, PA 19127.

SEND $10 for a list of 100 Calif. employers wanting to hire technicians to: MEU, P.O. Box 3509, Santa Rosa, CA 95402.

LEARN HOW TO FORM, Finance, and operate virtually any type business. Send $3.00 to: Information, Box 11215C, Fort Worth, Texas 76110.

MAKE MONEY mailing Science Books for corporations from home! (Apply Now!!) Details — Tribune PE-6c, Box 18553, Wichita, Kansas 67218.

PRINT YOUR BOOKLET 8¢. Booklet Planner - Pricer $1.00. Working goldmine. SPEEDIBOOKS, 23800-C Aurora, Bedford, Ohio 44146.

EMPLOYMENT OPPORTUNITIES

ELECTRONICS/AVIONICS EMPLOYMENT OPPORTUNITIES. Report on jobs now open. Details FREE. Aviation Employment Information Service, Box 240E, Northport, New York 11768.

JOBS OVERSEAS - Big money fast. $20,000 to $50,000 plus per year. Call 716-842-6000, ext. 111C.

SAN FRANCISCO EMPLOYMENT NEWS. Who's hiring in Bay Area, Silicon Valley electronics, computer, telecommunications fields. Free details. ISR-11, Box 3237, Fremont, CA 94538.

REPAIRS & SERVICES

ALL T.V. TUNERS repaired $11.95. Also repair Modules. Fast, quality work. MIKE'S T.V. TUNER SERVICE, Box 187, Bean Station, TN 37708. (615) 581-6393.

REAL ESTATE

BIG . . . FREE SUMMER CATALOG! Over 2,800 top values coast to coast! UNITED FARM AGENCY, 612-EP West 47th, Kansas City, MO 64112.

RUBBER STAMPS

RUBBER STAMPS, BUSINESS CARDS. Many new products. Catalog. Jackson's, E-100, Brownsville Rd., Mt. Vernon, Ill. 62864.

BOOKS AND MAGAZINES

ELECTRONICS BOOKS AVAILABLE. World publishers. Lowest prices. Ask catalogue. Business promotion, Lajpatrai Market, Delhi, India.

ELECTRONIC MUSIC and home recording in Polyphony magazine. Advanced applications, interviews, projects, computer music. Sample $1.50. Subscription (6 issues). $8.00 US/$10.00 foreign. POLYPHONY, Box P20305, Okla. City, OK 73156.

LEARN CHORDS and how to USE them. Add FULL SOUND to your playing. A proven approach. GET LASTING RESULTS from your practice. Beginners or advanced. Two illustrated volumes (385p) on LEARNING and USING CHORDS. No risk - FREE INFORMATION, MLS PUBLISHING, Dept. 11PE, RD3 Box 142, Olean, NY 14760.

THE SUPERMARKET OF ELECTRONICS — thousands of items for sale or trade each month. Free classified ad with subscription. Only $5.00 to Nuts & Volts, POB 1111-P, Placentia, CA 92670.

MUSICAL INSTRUMENTS

MUSICAL INSTRUMENTS' HOT LINE! Incredible prices: Amps, PA gear. All instruments. Huge selection. Sam Ash, established 1924. 800-645-3518. NYS: (212) 347-7757.

RECORDS & TAPES

RECORDS — TAPES! Discounts to 73% All labels; no purchase obligations; newsletter; discount dividend certificates. 100% guarantees. Free details. Discount Music Club, 650 Main St., Dept. 5-0681, New Rochelle, NY 10801.

VIDEO CASSETTE RENTALS AND SALES. ALL ratings. Free details. 20/20 VIDEO, Dept. E, Box 6162, Chicago, IL 60680.

DO-IT-YOURSELF

AVAILABLE SERVICING DATA for Hi-Fi units, Tape Recorders, Auto Radios, CB's, Scanners, TV's, and VCR's. PHOTOFACT® 1981 Index lists data available and source on over 110,000 consumer electronic units. Send $2.50 plus 50 cents shipping to Howard W. Sams Co., Dept. X0113, 4300 W. 62nd St., Indpls., IN 46268.

PRINTED CIRCUIT Boards with running water! Technological breakthrough. Precise reproduction. Ideal for beginners. Free info. COVAL, Dept. PE6, 2706 Kirby, Champaign IL 61820.

WELDING ALUMINUM? It's easy with the LUMIWELD Process. Designed for "Do-It-Yourselfers". Joins Aluminum to Copper. No special skills or expensive equipment. Money-back guarantee. For details: Send S.A.S.E. Dept. PE., ALUMISMITHS Inc., P.O.B. 517, DeLand, FL 32720. Featured in Pop. Sci. March, 1980.

ENGINES & MOTORS

ENGINES TO 19 h.p. for mowers, tillers, hobby. Repair-manuals, parts. Tremendous savings. Fast, dependable, Illustrated price catalog $1.00. Ashland Small Engines, Ashland, MO 65010.

HYPNOTISM

FREE Hypnotism. Self-Hypnosis. Sleep Learning Catalog! Drawer H400, Ruidoso, New Mexico 88345.

MISCELLANEOUS

MPG INCREASED! Bypass Pollution Devices easily. REVERSIBLY!! Free details — Posco GEE6, LaGrangeville, NY 12540.

AUTOMOBILE RE-TUNING FOR MAXIMIZED ECONOMY. Details FREE! Techneering, Box 12191DD, Norfolk, VA 23502.

LARGEST SUPPLY OF MAGIC-TRICKS, books, novelties. Send stamp. Advance Magics, 67 East Main, Price, Utah 84501.

1981 TENNIS DIRECTORY

The new Winter/Spring Edition includes over 700 product listings, over 250 tennis resorts, complete with specs and information.
TO ORDER, send your payment for $3.95 ($2.95* + $1.00 P&H), $5.00 outside USA, with your name and address to: *Tennis Directory*, Dept. 01674, Box 278, Pratt Station, Brooklyn, NY 11205.

*Residents of CA, CO, DC, FL, IL, MA, MI, MO, NY State, UT and VT add applicable sales tax.

Popular Electronics

ADVERTISERS INDEX

RS no.	ADVERTISER	PAGE no.
2	Albia Electronics	36
3	All Electronics Corp.	90
4	Antenna Specialists	87
5	AP Products	45
6	Atari	17
	Bullet Electronics	100
7	Chaney Electronics	106
	Classified Advertising	108, 109, 110, 111
	Cleveland Institute of Electronics, Inc.	8, 9, 10, 11
1	Communications Electronics	35
	Computer Reference Guide	43
8	Computique	42
9	Creative Computing	94
10	DBX	7
11	Digi-Key Corp.	102
12, 13	Discwasher	Cover 4, 2
63	D.J. Systems	77
14	Downlink	6
	Edmund Scientic	42
15	Egbert Co.	72
16	80 Microprocessing	81
17	Electronic Specialists	92
18	Epson	82
19	ETCO	74
21	Firestik	88
20	Fluke	15
	Global	83
22	Godbout Electronics, Bill	106
	Grantham College of Engineering	81
24	Hanley Engineering	97
25	Hardside	22
26, 27	Heath Co.	25, 38
28	Hewlett-Packard	Cover 3
29	Illinois Audio	91
56	Imsai	94
30	Integrated Circuits	101
31	Jameco Electronics	98, 99
32	JDR Microdevices	105
33	J&R Music World	26
34	Kilobaud	93
39	McIntosh Laboratory, Inc.	22
	MICROCOMPUTER MART	107
35	Micro Ace	57
36	Micro Management Systems	86
37	Microsoft	3
38	Mouser Electronics	81
	Nabih's	90
40	National Guard (Air)	19, 20, 21
	Netronics, R & D Ltd.	39, 89
	NRI Schools	28, 29. 30, 31
46	Ohio Scientific	41
42	OK Machine & Tool Co.	52
43	Olympic Sales	88
	Omega Sales Corp.	95
44	PAIA Electronics, Inc.	92
45	Phoenix Systems	80
58	Pioneer	Cover 2 & 1
47, 48	Poly Paks	80, 85
49	Pulsar Components	100
50	Quest Electronics	106
	Radio Shack	5, 75
51	Scientific Systems	91
52	Simutek	79
	Sinclair Electronics	51
53	Sperry, A.W.	16
57	Tams, Inc.	94
54	3-M	13
	Vapor Jet	33
59	Vector Electronic Co.	107
60	Video Wholesalers	47

ELECTRONICS WORLD®

Personal Electronics News

COMMERCIALLY PRACTICAL SOLAR CONCENTRATOR CELLS are the goal of a contract awarded Photowatt International, Inc. (Tempe, AZ) by the Sandia National Laboratories. Using silicon solar cells mated with acrylic Fresnel lenses that concentrate sunlight by a factor of 400, giving efficiencies on the order of 20%, the systems can achieve an overall sunlight-to-electricity conversion efficiency of 14% to 15%. Sandia is also working with Varian Associates (Palo Alto, CA) to develop GaAs cells that produce higher overall system efficiencies (16.4% has been measured) but these are not yet ready for commercialization.

TALKING BACK TO YOUR TV is the most important aspect of cable television now confronting cable companies and government entities responsible for their enfranchisement. Warner Amex, for example, has recently won two large franchises on the strength of QUBE, its two-way cable system. Local governments all over the country are demanding such two-way services as opinion polling, fire protection, and news-wire stories. However, fewer than 1% of the 4,150 cable systems in place now are interactive, and refurbishing older systems to make them so will cost $1000 to $1500 per mile. The problem appears to be to find the two-way services that will justify making the investment. Most people in the industry seem to agree that home-security services may be one answer.

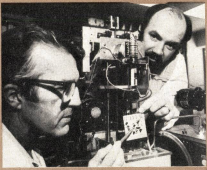

CIRCUIT BOARDS OF PORCELAIN OVER STEEL have been developed by RCA. Said to have improved electrical and heat-resistance characteristics, the new boards offer promise of improved ruggedness and reliability, as well as the capability of accommodating many types of components and circuits. The highly crystallized porcelain can be repeatedly heated to high temperatures without deforming so that many electronic components can be formed directly on the boards.

PRICE DOESN'T TELL ALL—at least not about uhf antenna equipment. That's the conclusion of a study conducted by Georgia Tech and funded by the FCC. The important things to look for are: uhf-only preamps providing approximately 20 dB gain with noise figure of 2 to 5 dB; a match between preamp input and antenna terminal; and RG-6/U coax transmission lines. These requirements should be met with an outlay of about $70 ($10 for antenna, $45 for preamp, and $15 for coax). For the antenna, a 4-bay, bow-tie with screen reflector was found to be the best.

AN ELECTRONICS HALL OF FAME CENTER has been proposed by officials of the National Electronic Service Dealers Association as a tribute to people who have made significant contributions to the electronic industry or its trade associations. Already elected to the Hall of Fame are Dr. Lee de Forest, Thomas A. Edison, Hugo Gernsback, and David Sarnoff. The Hall of Fame Center would include a museum, technical library, and exhibits. Inquiries should be sent to NESDA, Attn: J. W. Williams, 2708 W. Berry St., Fort Worth, TX 76109.

COMPUTING DEVICES MUST HAVE FCC CERTIFICATION if they are manufactured after Jan. 1, 1981 and intended for use in residential areas. If the devices are not certified, they must be labeled as marketed under a temporary waiver of the FCC rules. The required label states that the device can cause objectionable interference to radio and TV reception and, if such interference occurs, the user must take steps to correct the interference. One of the first devices to obtain the FCC certification was Centronics' Models 730 and 737 dot-matrix printers.

The Professional Alternatives: The HP-41C And The NEW HP-41CV.

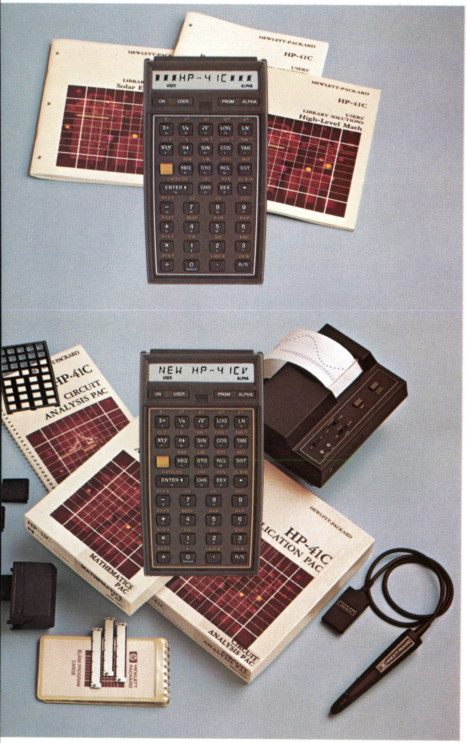

Now Hewlett-Packard offers you a choice in full performance alphanumeric calculators. The new HP-41CV has five times more built-in memory than the HP-41C. Both calculators are powerful yet easy to use. You can communicate with words as well as numbers. For example, label and call up programs by name and receive meaningful prompts while executing programs. Continuous Memory retains programs and data even while the machines are off. Need lots of memory? Choose the HP-41CV. If your needs are more modest, select the HP-41C. The HP-41C can grow with you by adding memory modules.

BOTH OFFER CONTINUAL GROWTH POTENTIAL

By themselves the HP-41C and HP-41CV may be all the calculator you'll ever need. But if you need more capability, you can expand your calculator into a complete computational system. Each calculator has four ports which allow you to plug in a Printer/Plotter, an "Extra Smart" Card Reader or an Optical Wand for reading bar codes. Application Pacs and Solution Books offering complete solutions are also available. And now, HP offers a new service: Custom Modules (ROM's) from your software for high volume, unique problem-solving needs. Costs are reasonable. Call us.

ONLY FROM HEWLETT-PACKARD

Powerful yet easy to use calculators. A full line of peripherals and software. A time-proven logic system-RPN. No equals key. Less keystrokes. Computation is displayed as you proceed. The new HP-41CV and the HP-41C are available now, with new low prices. For details and address of nearest dealer, CALL TOLL-FREE 800-547-3400, Dept. 254A; except Hawaii/ Alaska. In Oregon, 758-1010. Or write Hewlett-Packard, Corvallis, OR 97330, Dept. 254A.

611/07

HP-41C, $250; HP-41CV, $325; Optical Wand, $125; Printer/Plotter, $385; Plug-in Card Reader, $215; Quad Memory Module (brings HP-41C to HP-41CV memory capacity), $95; Memory Module, $30; Application Pacs, most are $30; Solution Books, $12.50.

Prices are suggested retail excluding applicable state and local taxes—Continental U.S.A., Alaska and Hawaii.

HEWLETT PACKARD

CIRCLE NO. 28 ON FREE INFORMATION CARD

The First Discwasher Tape Accessory

discwasher®
PERFECT PATH™
Head Cleaner
● Non-abrasive.
● High technology system; simultaneously cleans heads and removes oxide from tape path.
● No alcohols to damage tape mechanism.

Special non-abrasive cleaning fibers are backed with an exclusive "capture surface" designed to trap tiny particles of tape residue, preventing them from contaminating tape mechanisms.

The Perfect Path Difference:

- "Cleaning contact" is made along the total tape path including guides and heads, normally untouched by wiper cleaners.
- Perfect Path cleans without alcohol or freon. It will not extract and age pinch rollers.
- Perfect Path simultaneously cleans tape heads while removing debris from along the tape path.
- Perfect Path's cleaning fiber grid is non-abrasive. Even after hundreds of passes, it will not scratch heads.
- Perfect Path restores high frequency "air" and transient response of cassette recordings.

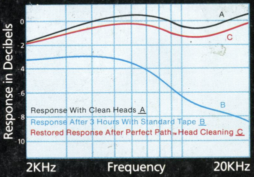

Playback accuracy of a calibrated test tape. Note that after only three hours' play, high frequency response is reduced by as much as 10 dB. One cleaning with the Perfect Path Head Cleaner restores the highs to within 1 dB of the original response.

discwasher®

PERFECT PATH™

Discwasher, Inc., 1407 N. Providence Rd., Columbia, MO 65201

CIRCLE NO. 12 ON FREE INFORMATION CARD